

Analysis and Design of Analog Integrated Circuits
Lecture 12



Feedback

Michael H. Perrott
March 11, 2012



Copyright © 2012 by Michael H. Perrott
All rights reserved.

Open Loop Versus Closed Loop Amplifier Topologies

Open Loop

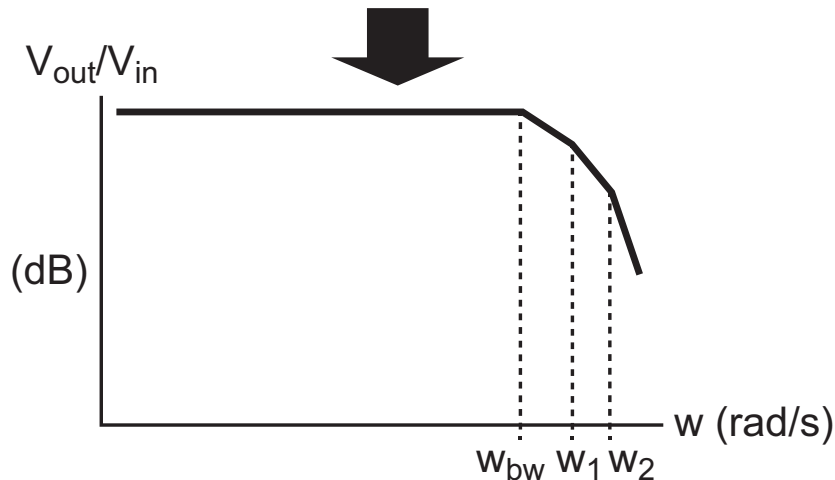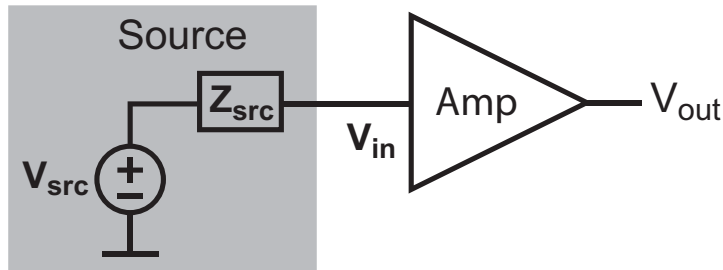


Closed Loop

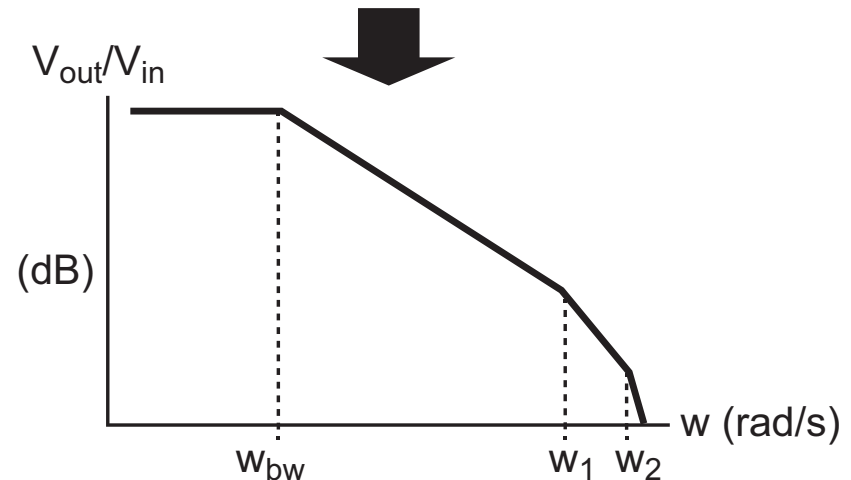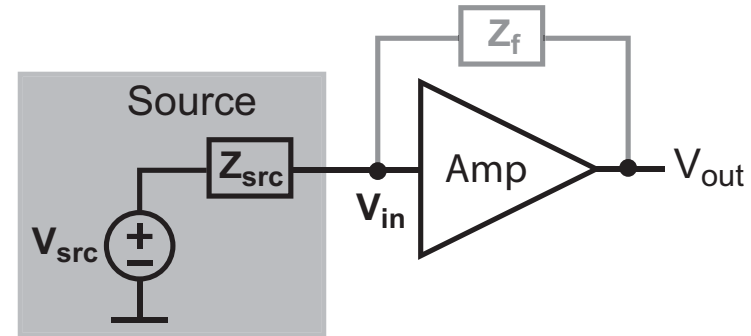


- Open loop – want all bandwidth limiting poles to be as high in frequency as possible
- Closed loop – want one pole to be dominant and all other parasitic poles to be as high in frequency as possible

Consider an Open Loop Integrator

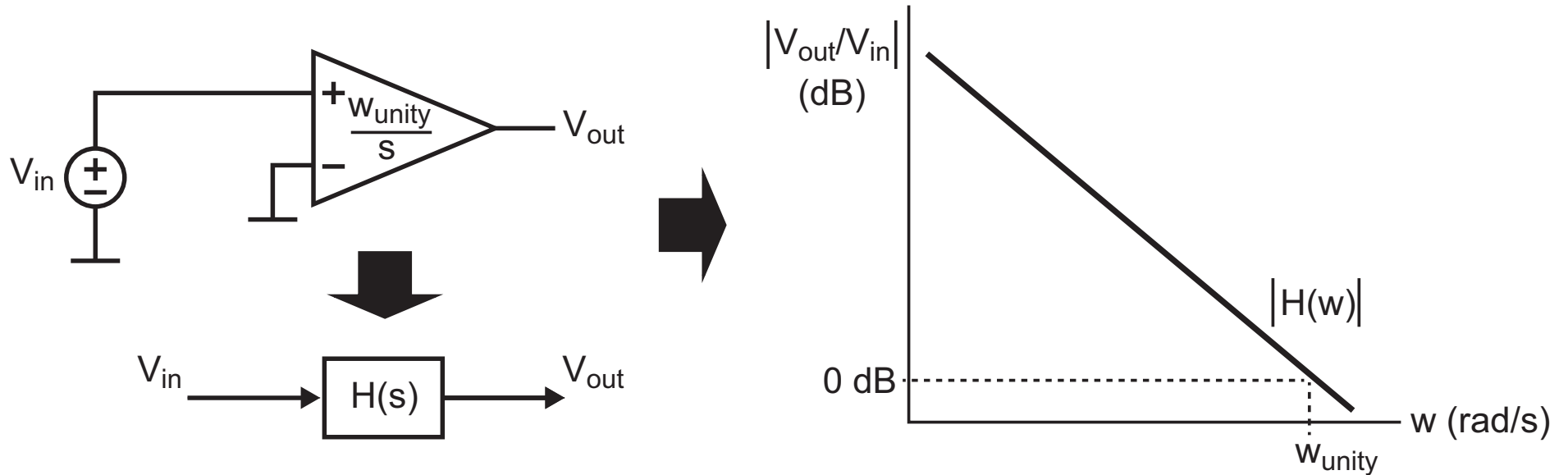

- Parameterize integrator in terms of its unity gain frequency, w_{unity} rad/s
 - Define $H(s) = w_{unity}/s$
 - Note that $|H(w_{unity})| = 1$

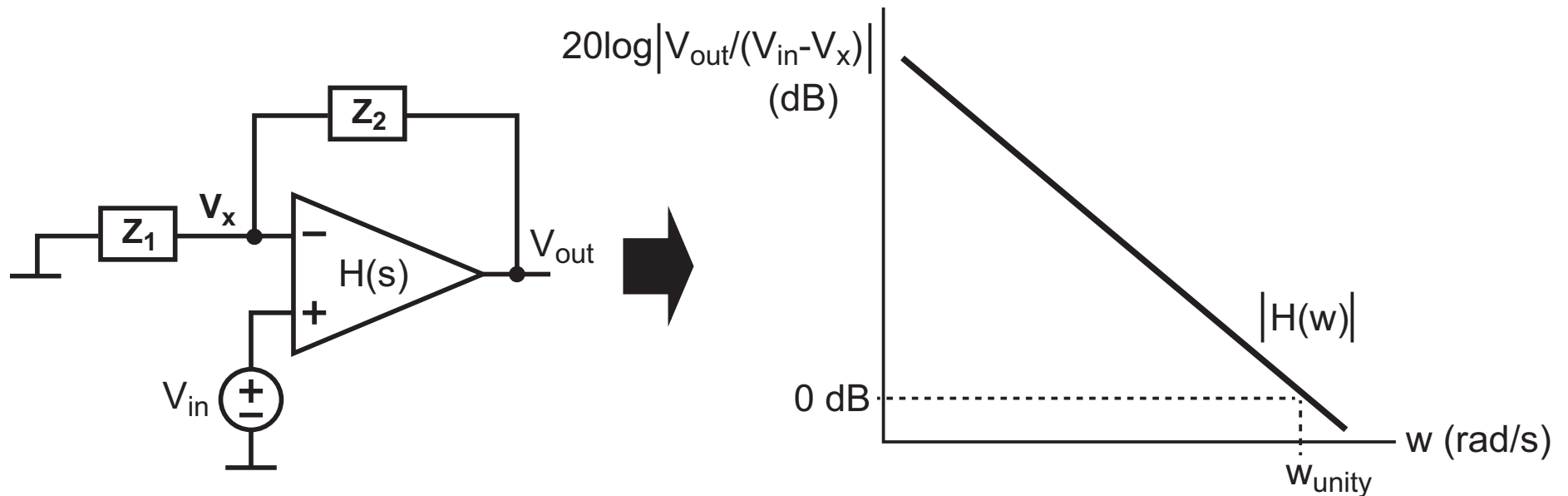Now Surround the Integrator with a Feedback Path




- The *feedforward* path is $H(s) = \omega_{unity}/s$
- The *feedback* path is formed by Z_1 and Z_2
- Derivation of *closed loop* transfer function:

$$\frac{V_{out} - V_x}{Z_2} = \frac{V_x - 0}{Z_1} \quad \text{and} \quad V_{out} = H(s)(V_{in} - V_x)$$

$$\Rightarrow \frac{V_{out}}{V_{in}} = \frac{H(s)}{1 + Z_1/(Z_1 + Z_2)H(s)}$$

Observations of Impact of Feedback

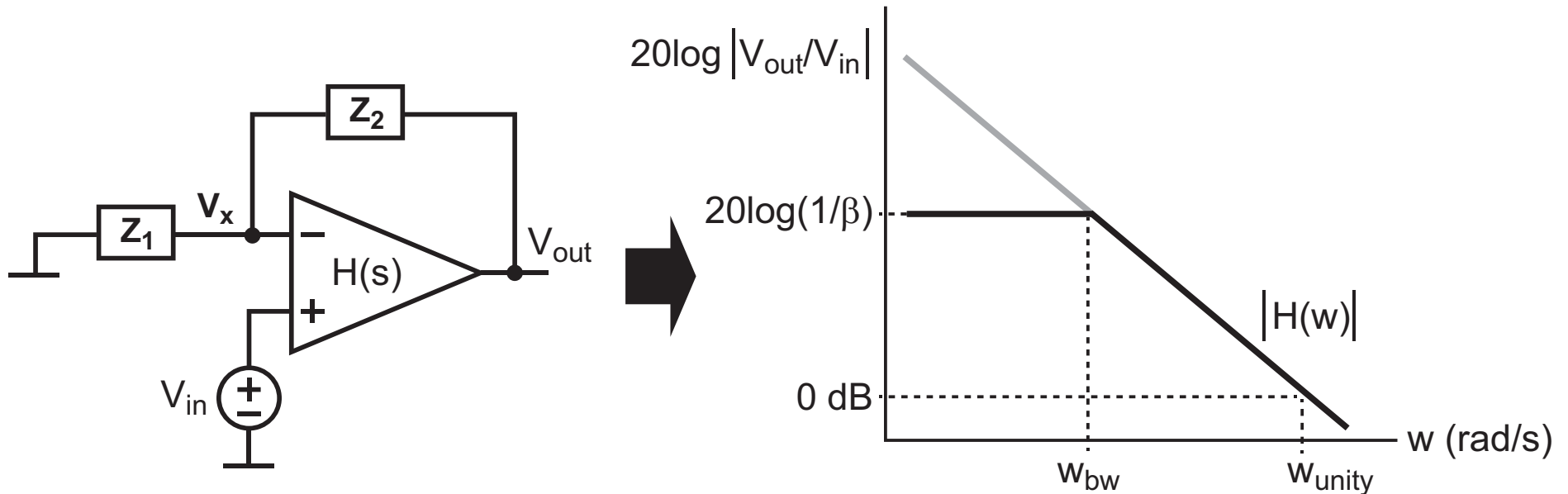

- Define $\beta = Z_1/(Z_1+Z_2)$ and rewrite transfer function as:

$$\frac{V_{out}}{V_{in}} = \frac{H(s)}{1 + Z_1/(Z_1 + Z_2)H(s)} = \frac{H(s)}{1 + \beta \cdot H(s)}$$

- At low frequencies:


$$\left| \frac{V_{out}}{V_{in}} \right|_{s \rightarrow 0} = \frac{\infty}{1 + \beta \cdot \infty} = \frac{1}{\beta}$$

- At high frequencies:

$$\left| \frac{V_{out}}{V_{in}} \right|_{s \rightarrow \infty} = |H(w)|$$

(since $|\beta \cdot H(w)| \ll 1$)

General View of Feedback

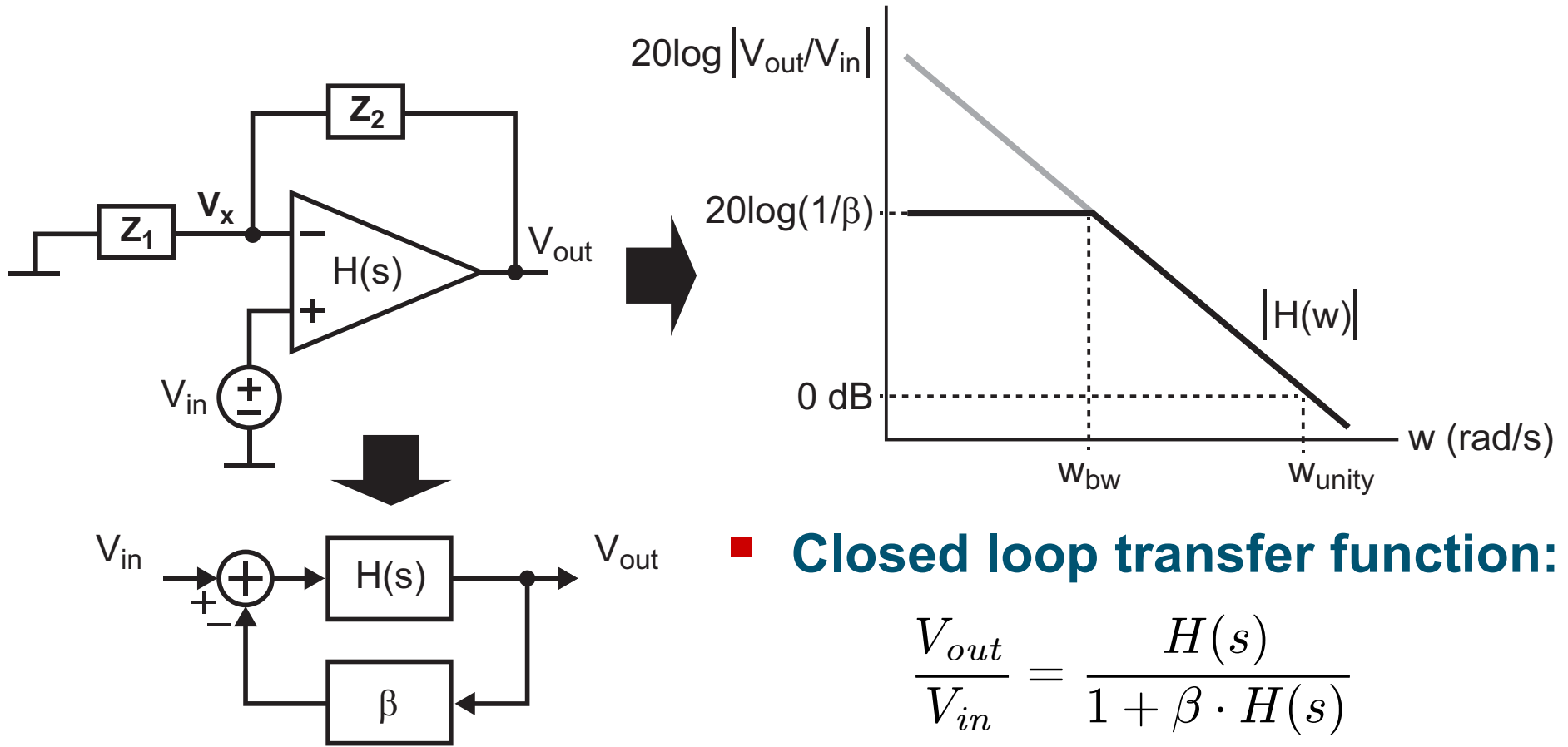

■ **Closed loop transfer function:**

$$\frac{V_{out}}{V_{in}} = \frac{H(s)}{1 + \beta \cdot H(s)}$$

■ **This is called Black's formula**


■ **At low frequencies:**

$$\left| \frac{V_{out}}{V_{in}} \right|_{s \rightarrow 0} = \frac{1}{\beta}$$

At high frequencies:


$$\left| \frac{V_{out}}{V_{in}} \right|_{s \rightarrow \infty} = |H(w)|$$

General Observations of Feedback

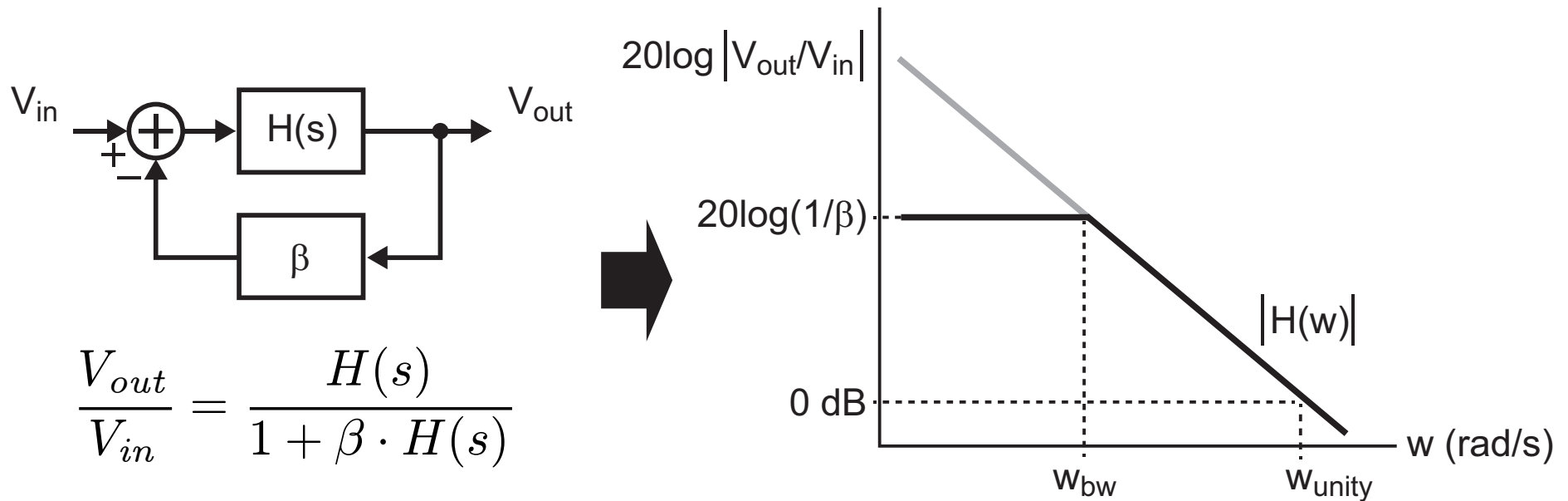

- **The *feedback path* sets the closed loop gain at low frequencies**
 - Assumes the open loop gain is large at low frequencies
 - Implies that accurate *closed loop* gain can be achieved at low frequencies despite variations in *open loop* gain
- **The *feedback path* also influences the closed loop bandwidth**

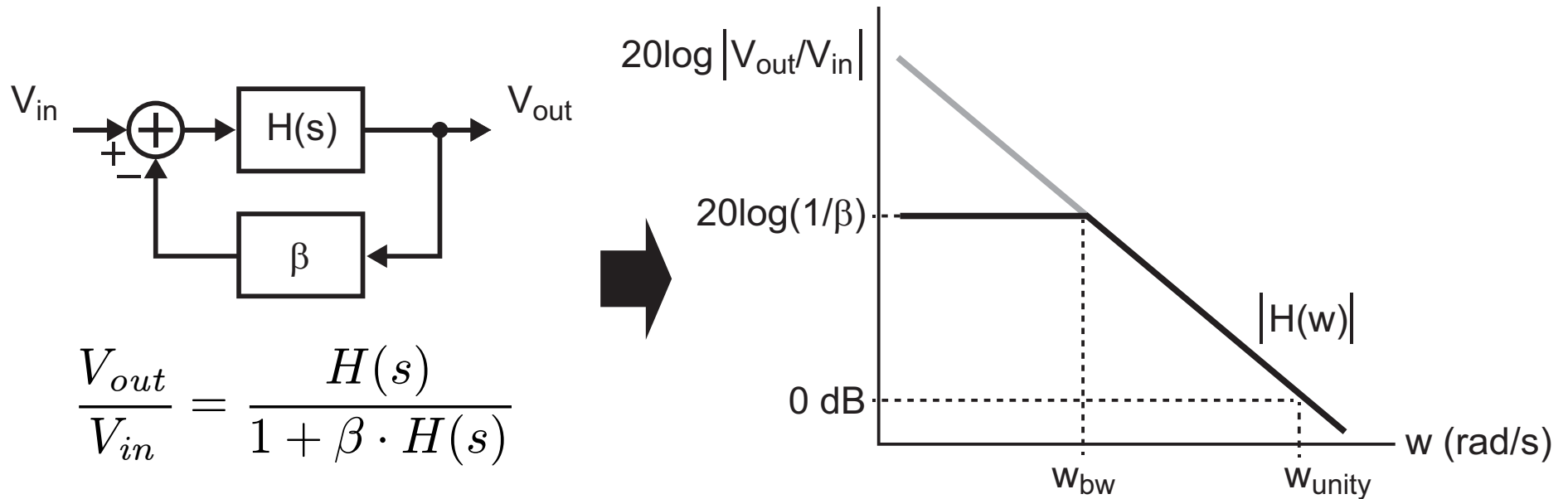Gain Bandwidth Product for Closed Loop Systems




- The low frequency gain is:**

$$\left| \frac{V_{out}}{V_{in}} \right|_{s \rightarrow 0} = \frac{1}{\beta}$$
 - The bandwidth roughly corresponds to:**

$$|H(w_{bw})| \approx \frac{1}{\beta}$$
- For $H(s) = \frac{w_{unity}}{s} \Rightarrow \left| \frac{w_{unity}}{w_{bw}} \right| \approx \frac{1}{\beta} \Rightarrow w_{unity} = \frac{1}{\beta} \cdot w_{bw}$

Closed loop systems exhibit constant gain-bandwidth product set by the unity gain frequency of the open loop amplifier

Example: Unity Gain Amplifier

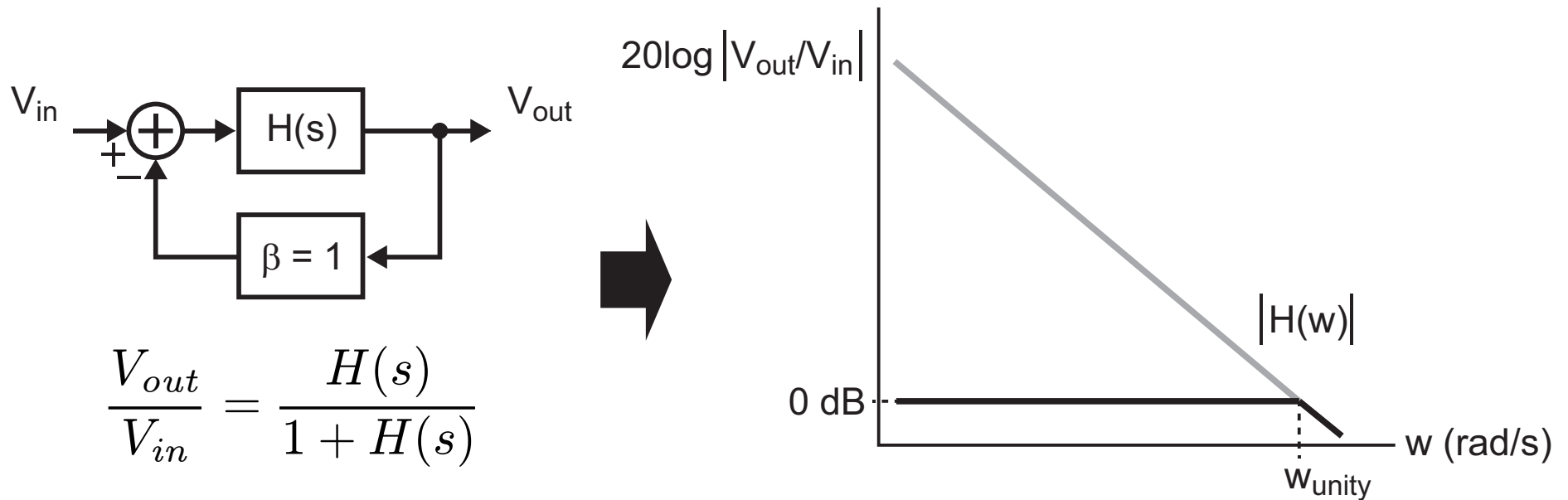


$$\frac{V_{out}}{V_{in}} = \frac{H(s)}{1 + H(s)}$$

- The low frequency gain is: $\left| \frac{V_{out}}{V_{in}} \right|_{s \rightarrow 0} = 1$
- The bandwidth roughly corresponds to: $|H(w_{bw})| \approx w_{unity}$
- Gain bandwidth product is w_{unity} : $1 \cdot w_{unity} = w_{unity}$

Unity gain closed loop amplifiers maximize the closed loop bandwidth assuming closed loop gain ≥ 1

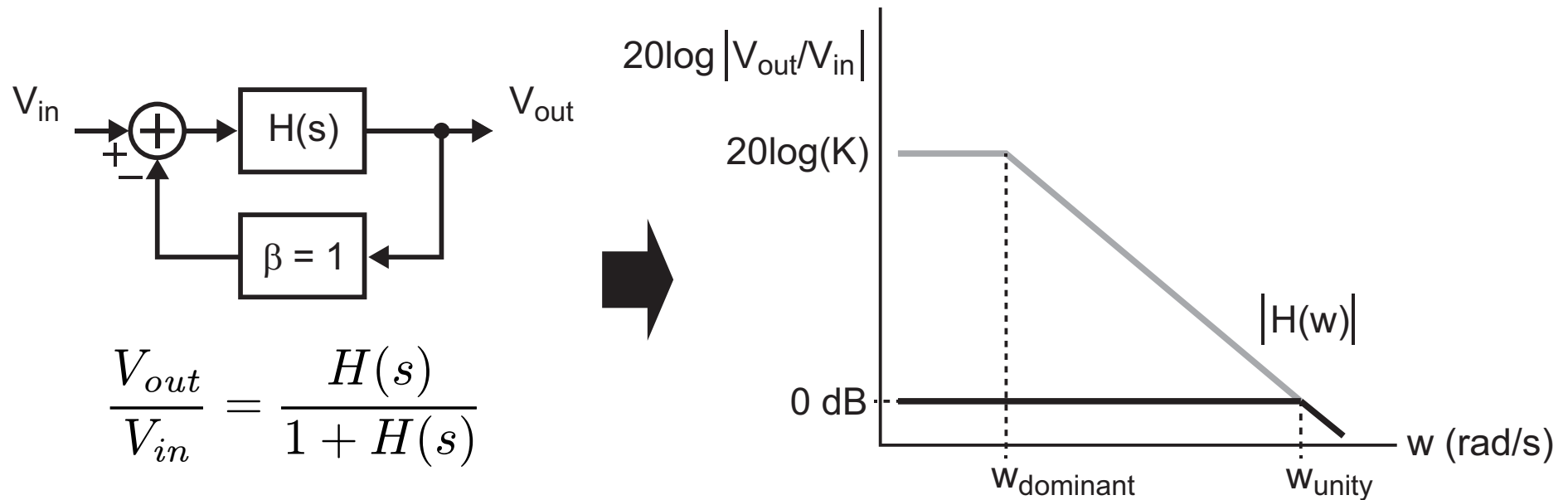Issue: Open Loop Amplifiers have Finite DC Gain




- Let us now model $H(s)$ as:

$$H(s) = \frac{K}{1 + s/w_{dominant}}$$

- To first order, the closed loop bandwidth and gain are relatively unchanged

What is the impact of having finite, open loop, DC gain?

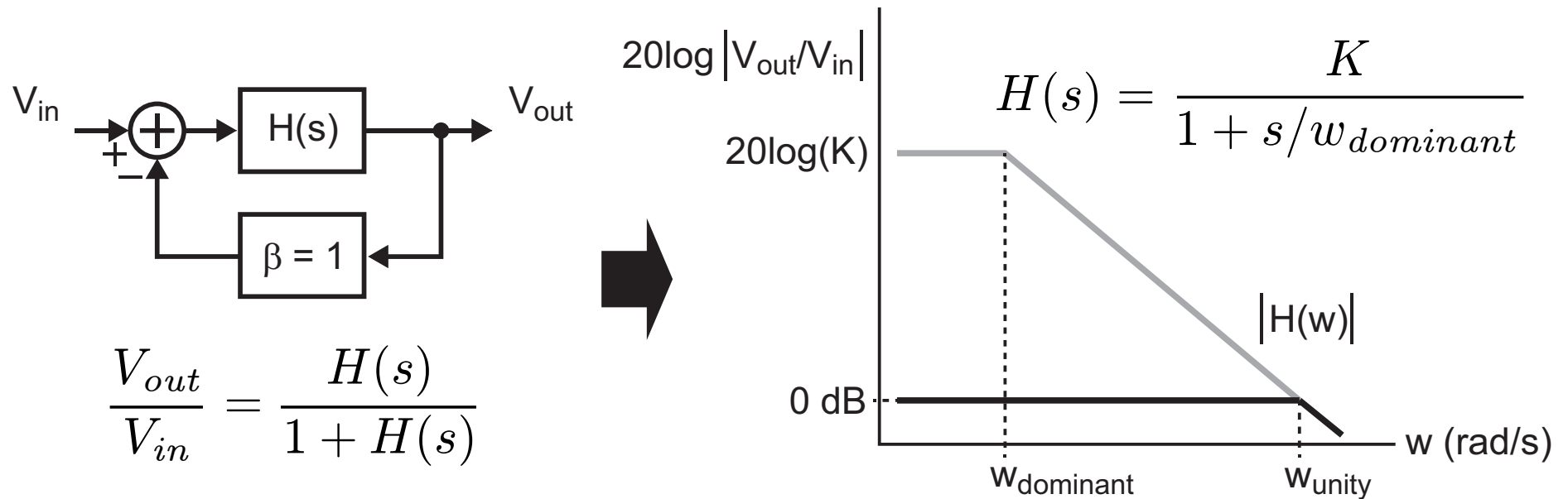Further Examination of Finite, Open Loop, DC Gain




- For unity gain configuration of closed loop amplifier:

$$\left| \frac{V_{out}}{V_{in}} \right|_{s \rightarrow 0} = \left| \frac{H(s)}{1 + H(s)} \right|_{s \rightarrow 0} = \frac{K}{1 + K} = \frac{1}{1 + 1/K}$$

- We see that finite open loop DC gain leads to a slight reduction of the closed loop DC gain
 - We want $K \gg 1$ for the unity gain closed loop amplifier

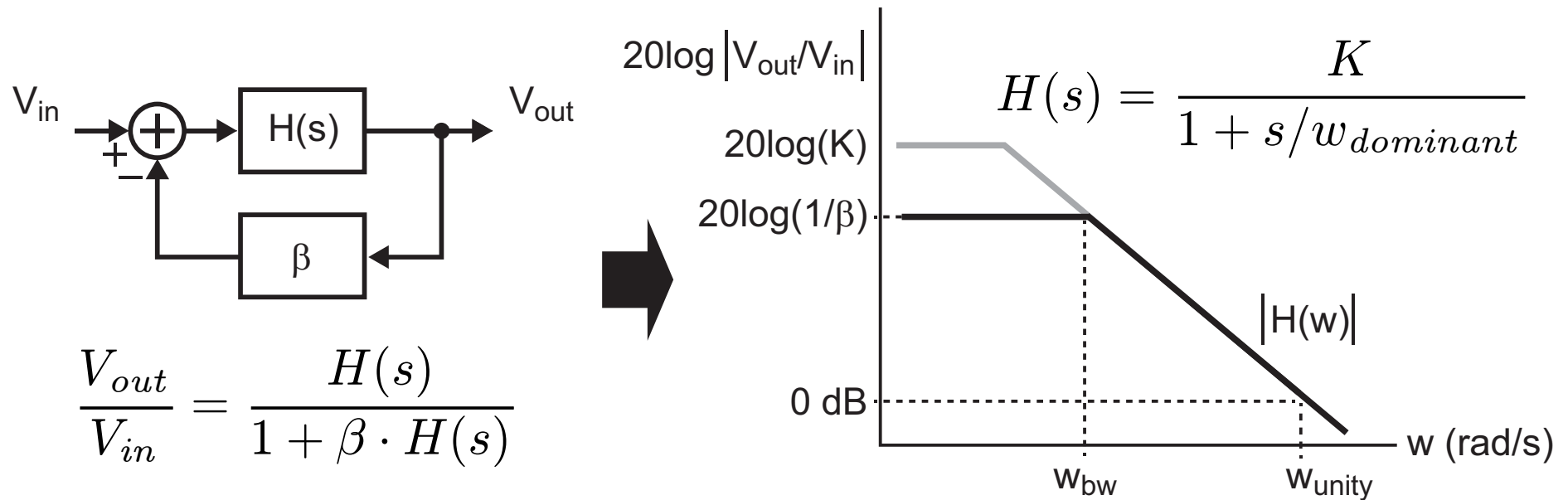More General View of Finite, Open Loop, DC Gain




- For general configuration of closed loop amplifier:

$$\left| \frac{V_{out}}{V_{in}} \right|_{s \rightarrow 0} = \frac{K}{1 + \beta \cdot K} = \left(\frac{1}{\beta} \right) \frac{1}{1 + (1/\beta)/K}$$

- Finite open loop DC gain still leads to reduction of closed loop DC gain
 - We want $K \gg 1/\beta$ in this case
 - We will see implications of this issue later in the class

The Issue of Parasitic Open Loop Poles

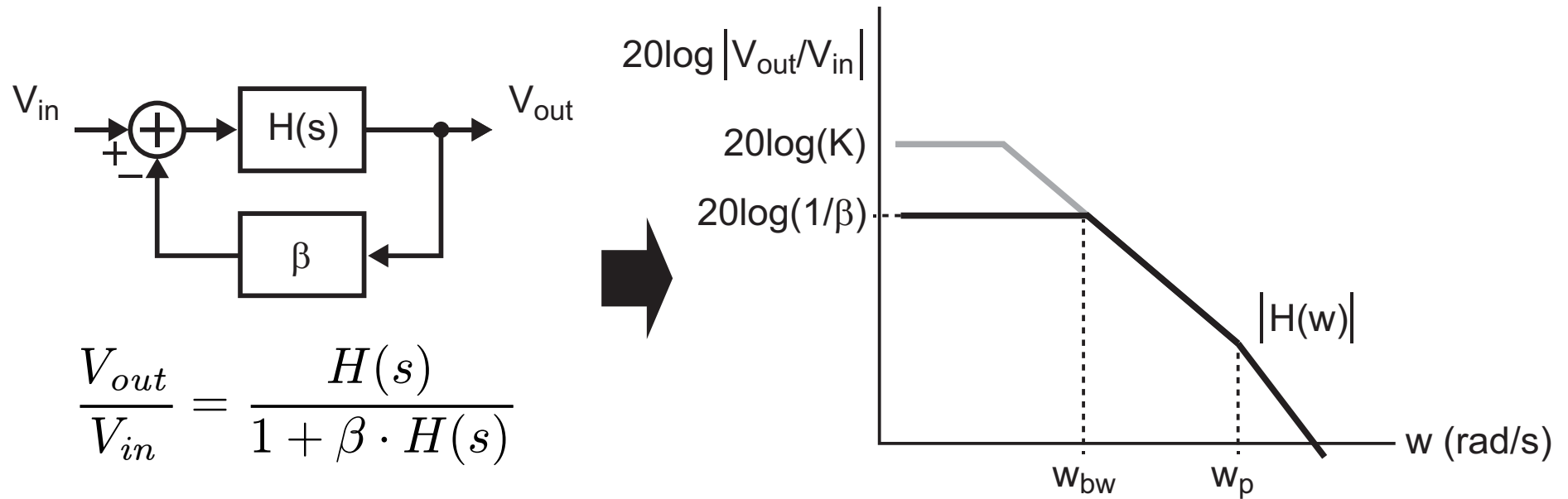


- **Practical amplifiers have non-dominant poles, too:**

$$H(s) = \left(\frac{K}{1 + s/\omega_{dominant}} \right) \left(\frac{1}{1 + s/\omega_p} \right)$$

- **Of course, there can be multiple parasitic poles and also zeros**
- **A key issue of such parasitic poles is their influence on the *stability* of the closed loop amplifier**

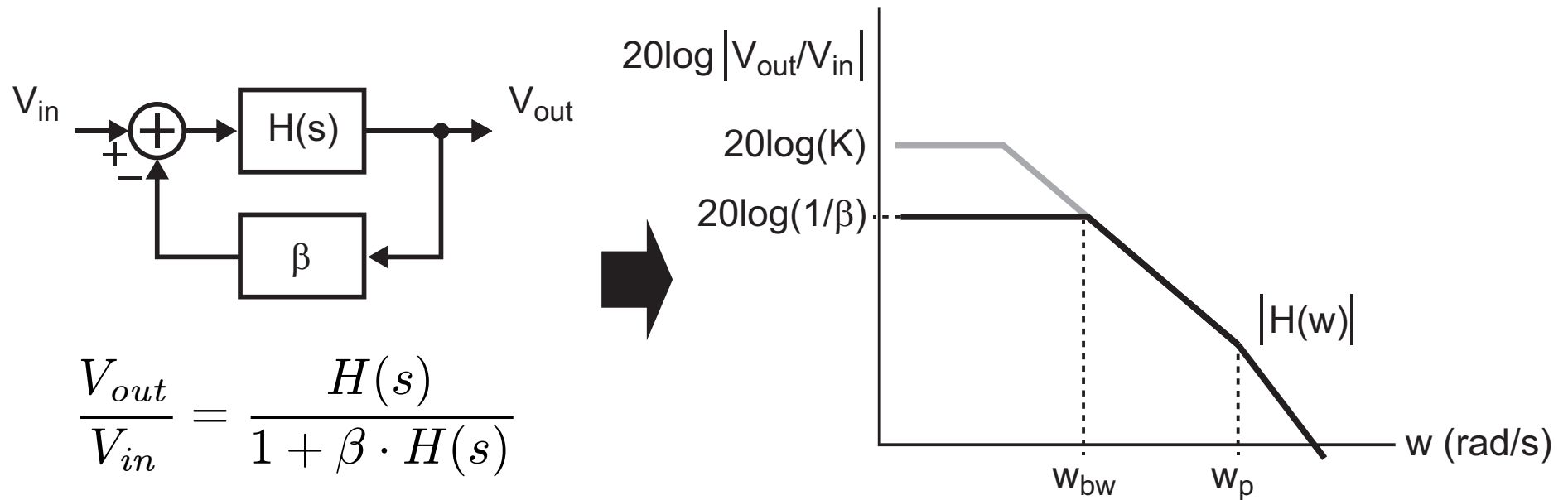Key Tool for Assessing Stability: Open Loop Response



- We define the open loop response, $A(s)$, as:

$$A(s) = \beta \cdot H(s)$$

- Note that the unity gain frequency, ω_0 , of $A(\omega)$ is approximately the same as the closed loop bandwidth, ω_{bw}

$$|A(\omega_0)| = 1 \Rightarrow \beta \cdot |H(\omega_0)| = 1 \Rightarrow |H(\omega_0)| = 1/\beta$$

- Looking at the plot above, we can see that the intersection of $|H(\omega)|$ and $1/\beta$ corresponds to the closed loop bandwidth, ω_{bw}

Stability Analysis Based on Phase Margin of $A(w)$

- **Phase margin** is a key metric when examining the stability of a system
 - Phase margin is defined as $180^\circ + \text{phase}\{A(w_0)\}$
 - w_0 corresponds to the unity gain frequency of the open loop response (i.e., $|A(w_0)| = 1$)
 - w_0 is *approximately* the same as the closed loop bandwidth, w_{bw}
 - Phase margin must be greater than 0 degrees for the closed loop system to be stable
 - Typically want phase margin to be greater than 45°
- **Key skill:** you must be able to plot Bode plots in both magnitude and phase!

Review of Bode Plot Basics

■ Example:

$$A(w) = \frac{1 + jw/w_z}{(1 + jw/w_{p1})(1 + jw/w_{p2})}$$

- **Log of magnitude (dB):** $20 \log |A(w)|$
 $= 20 \log |1 + jw/w_z| - 20 \log |1 + jw/w_{p1}| - 20 \log |1 + jw/w_{p2}|$
 - Taking the log allows the poles and zeros to be plotted separately and then added together
- **Phase:** $\angle A(w)$
 $= \angle(1 + jw/w_z) - \angle(1 + jw/w_{p1}) - \angle(1 + jw/w_{p2})$
 - Phase of poles and zeros can also be plotted separately and then added together


Review: Plotting the Magnitude of Poles

- Plot the magnitude response of pole w_{p1}

$$20 \log |A_{p1}(w)| = 20 \log \left| \frac{1}{1 + jw/w_{p1}} \right| = -20 \log |1 + jw/w_{p1}|$$

- For $w \ll w_{p1}$: $20 \log |A_{p1}(w)| \approx -20 \log |1| = 0$

- For $w \gg w_{p1}$: $20 \log |A_{p1}(w)| \approx -20 \log |w/w_{p1}|$

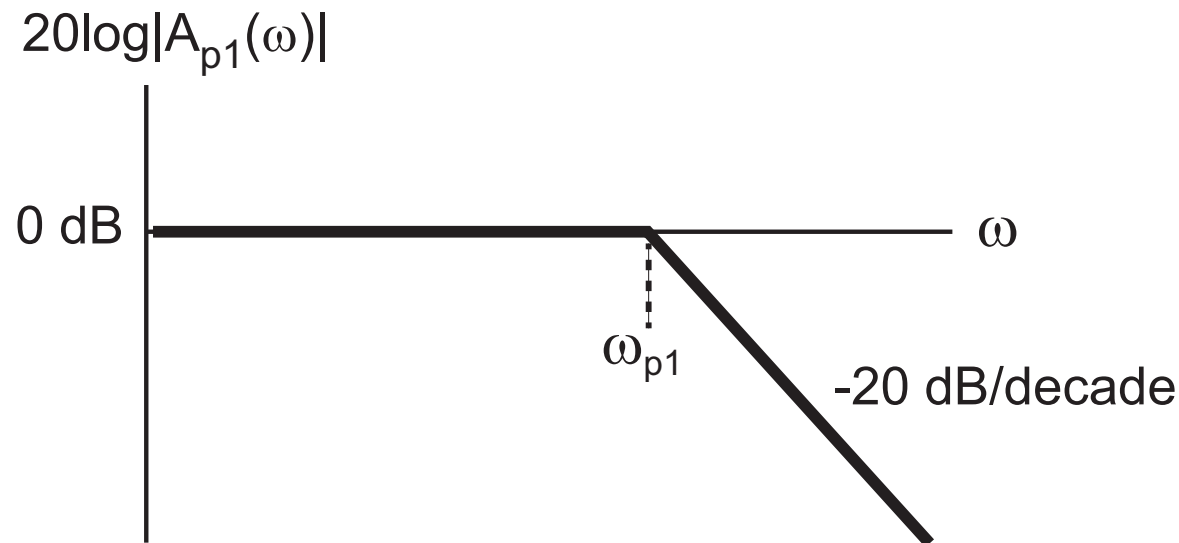


Plotting the Phase of Poles

- Plot the phase response of pole w_{p1}

$$\angle A_{p1}(w) = -\angle(1 + jw/w_{p1}) = -\arctan(w/w_{p1})$$

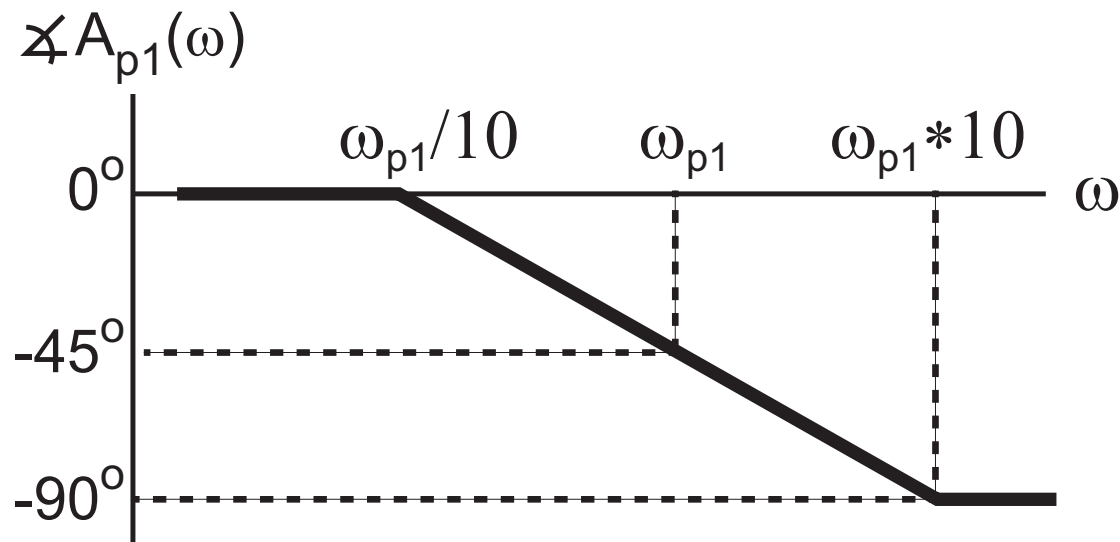- For $w \ll w_{p1}$: $\angle A_{p1}(w) \approx -\arctan(0) = 0^\circ$
- For $w = w_{p1}$: $\angle A_{p1}(w) \approx -\arctan(1) = -45^\circ$
- For $w \gg w_{p1}$: $\angle A_{p1}(w) \approx -\arctan(\infty) = -90^\circ$




Review: Plotting the Magnitude of Zeros

- Plot the magnitude response of zero w_z

$$20 \log |A_z(w)| = 20 \log |1 + jw/w_z|$$

- For $w \ll w_z$: $20 \log |A_z(w)| \approx 20 \log |1| = 0$
- For $w \gg w_z$: $20 \log |A_z(w)| \approx 20 \log |w/w_z|$

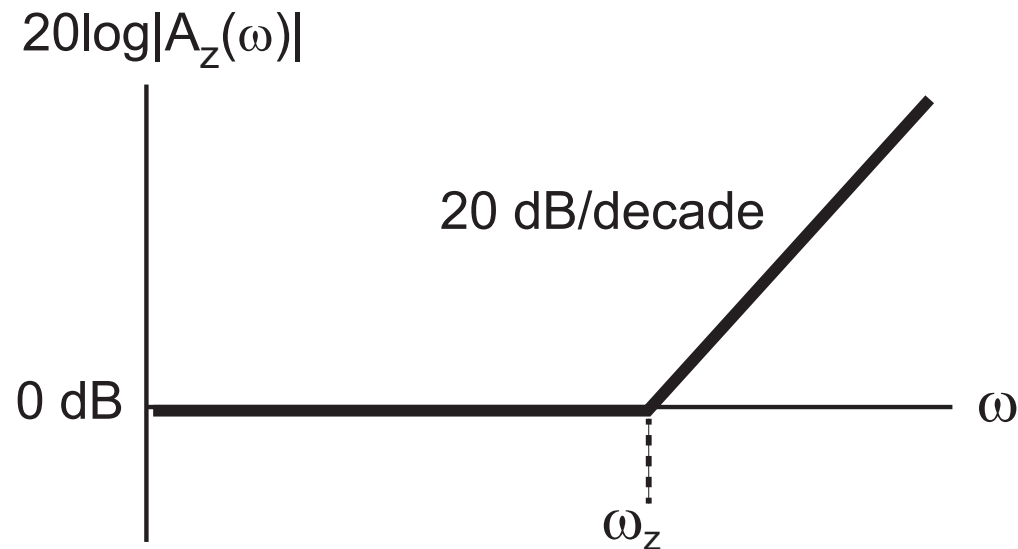


Plotting the Phase of Zeros


- Plot the phase response of zero w_z

$$\angle A_z(w) = \angle(1 + jw/w_z) = \arctan(w/w_z)$$

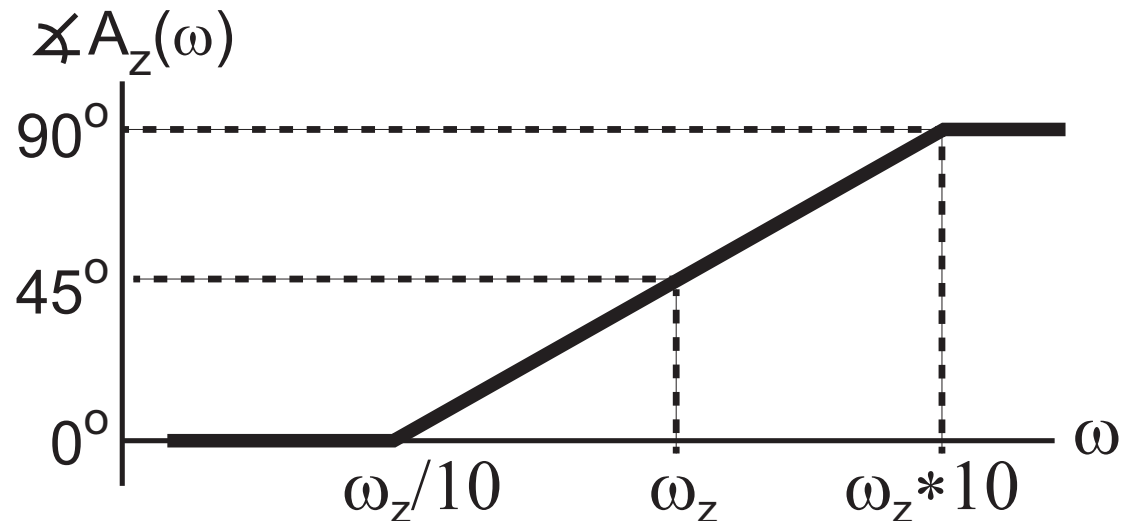- For $w \ll w_z$: $\angle A_z(w) \approx \arctan(0) = 0^\circ$
- For $w = w_z$: $\angle A_z(w) \approx \arctan(1) = 45^\circ$
- For $w \gg w_z$: $\angle A_z(w) \approx \arctan(\infty) = 90^\circ$



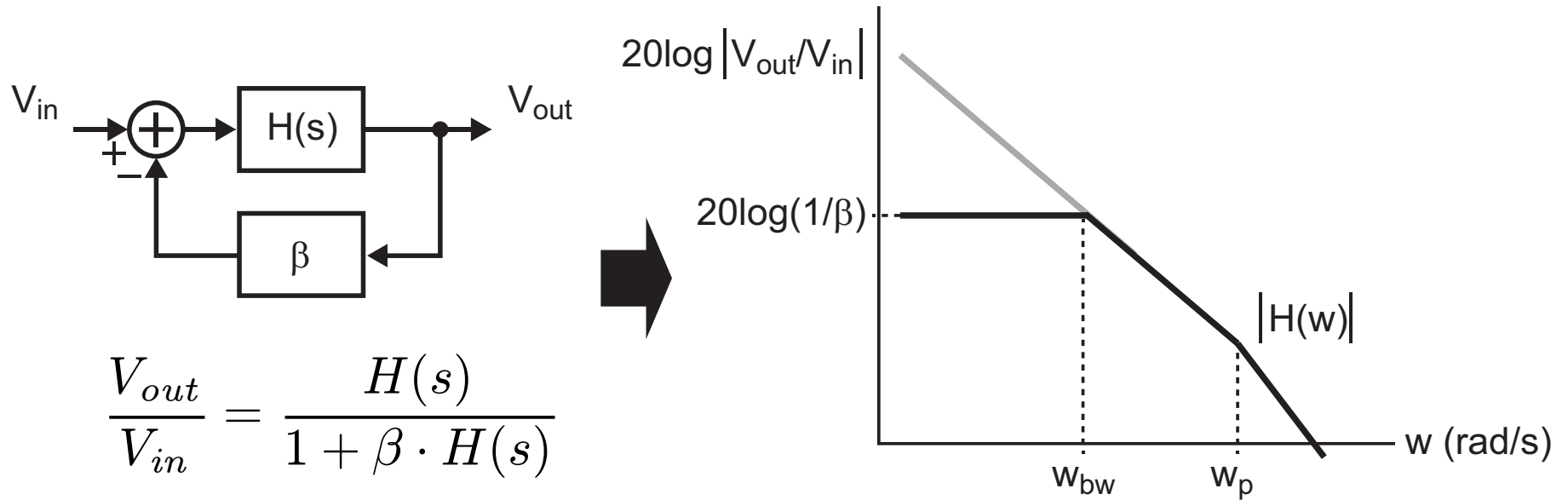Example of Closed Loop Stability Evaluation




- Consider the case where:

$$H(s) = \left(\frac{K}{s} \right) \left(\frac{1}{1 + s/w_p} \right)$$

- This implies that:


$$A(s) = \beta \left(\frac{K}{s} \right) \left(\frac{1}{1 + s/w_p} \right)$$

Phase Margin Versus Open Loop Gain

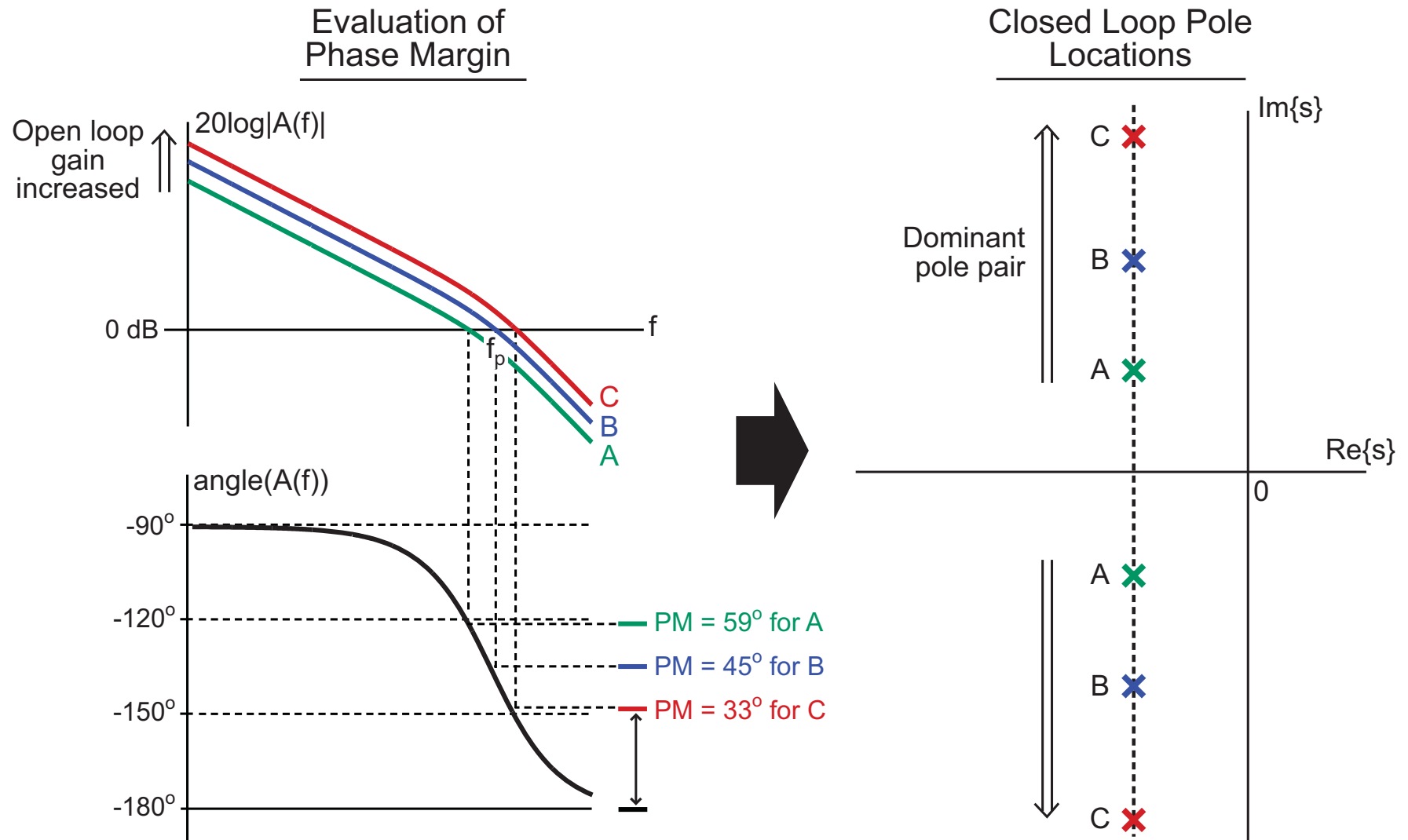


- Note the closed loop pole locations versus open loop gain
 - Is the closed loop system unstable for any case above?

Corresponding Closed Loop Behavior

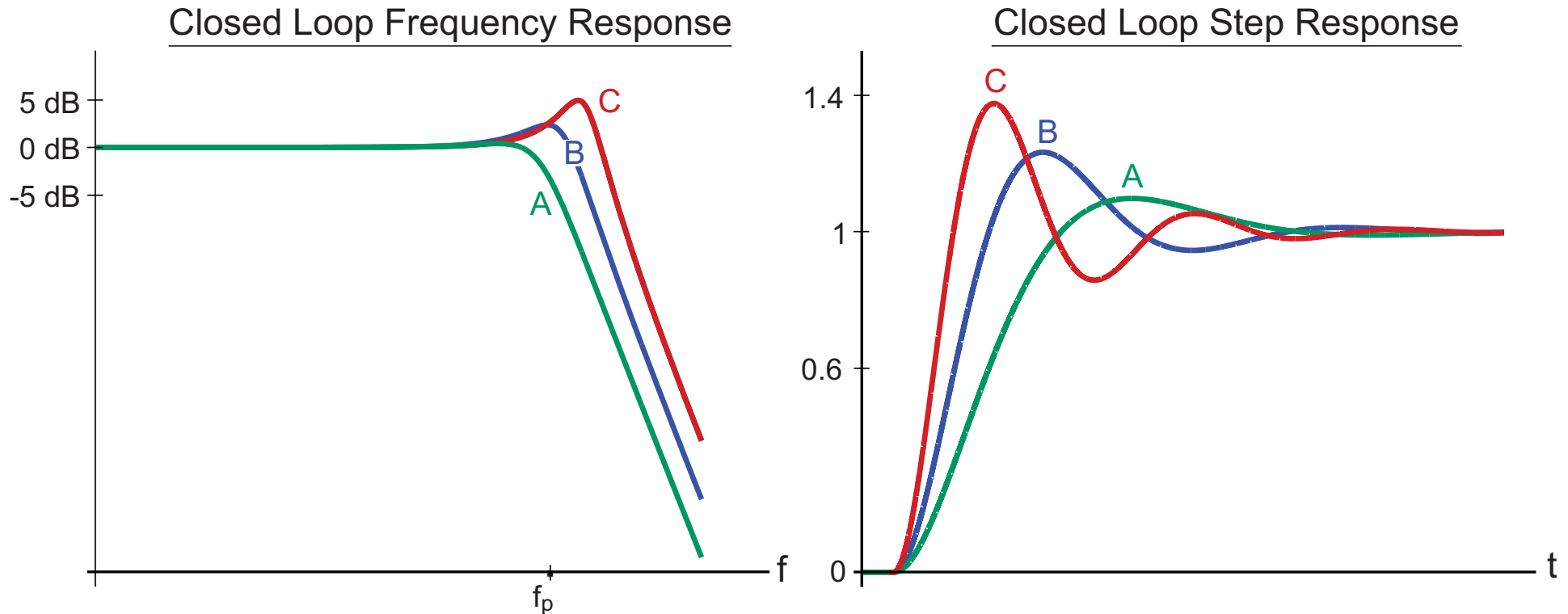


- **Frequency response sees more peaking with higher open loop gain**
 - How does this relate to the movement of the closed loop pole locations?
- **Step response see more ringing with higher open loop gain**
 - How does this relate to the closed loop frequency response?

Some Key Observations

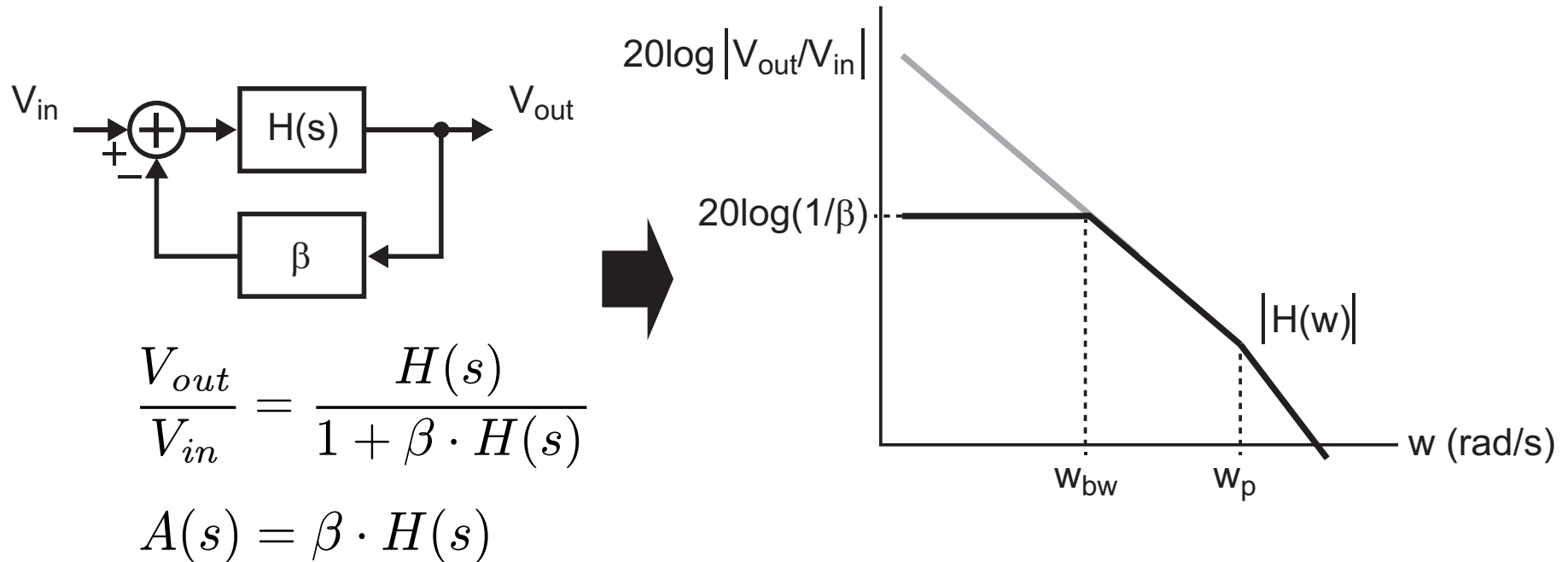

- We have seen that increasing the open loop gain of $A(w)$ leads to *higher* closed loop bandwidth
 - How is this consistent with the statement that increasing closed loop gain leads to *lower* closed loop bandwidth?
- As an exercise, consider the impact of the following:
 - Keep β unchanged and increase the open loop gain of $H(w)$
 - Keep $H(w)$ unchanged and increase β

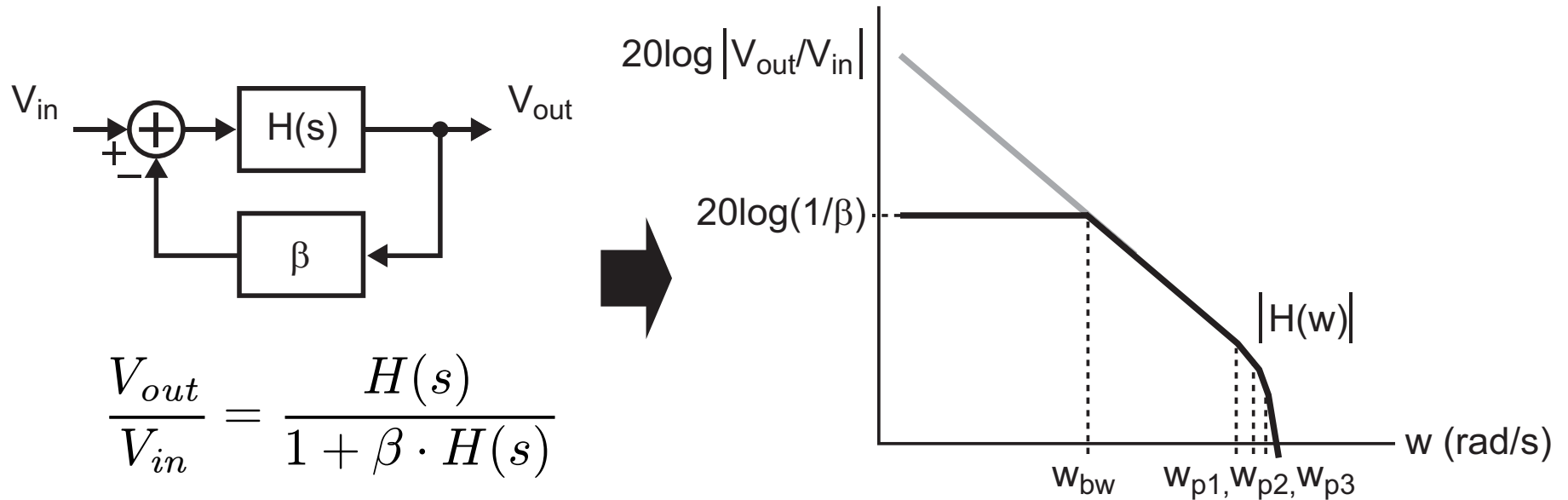Example 2 of Closed Loop Stability Evaluation




- Consider the case where:

$$H(s) = \left(\frac{K}{s} \right) \left(\frac{1}{1 + s/w_{p1}} \frac{1}{1 + s/w_{p2}} \frac{1}{1 + s/w_{p3}} \right)$$

- This implies that:


$$A(s) = \beta \left(\frac{K}{s} \right) \left(\frac{1}{1 + s/w_{p1}} \frac{1}{1 + s/w_{p2}} \frac{1}{1 + s/w_{p3}} \right)$$

Phase Margin Versus Open Loop Gain

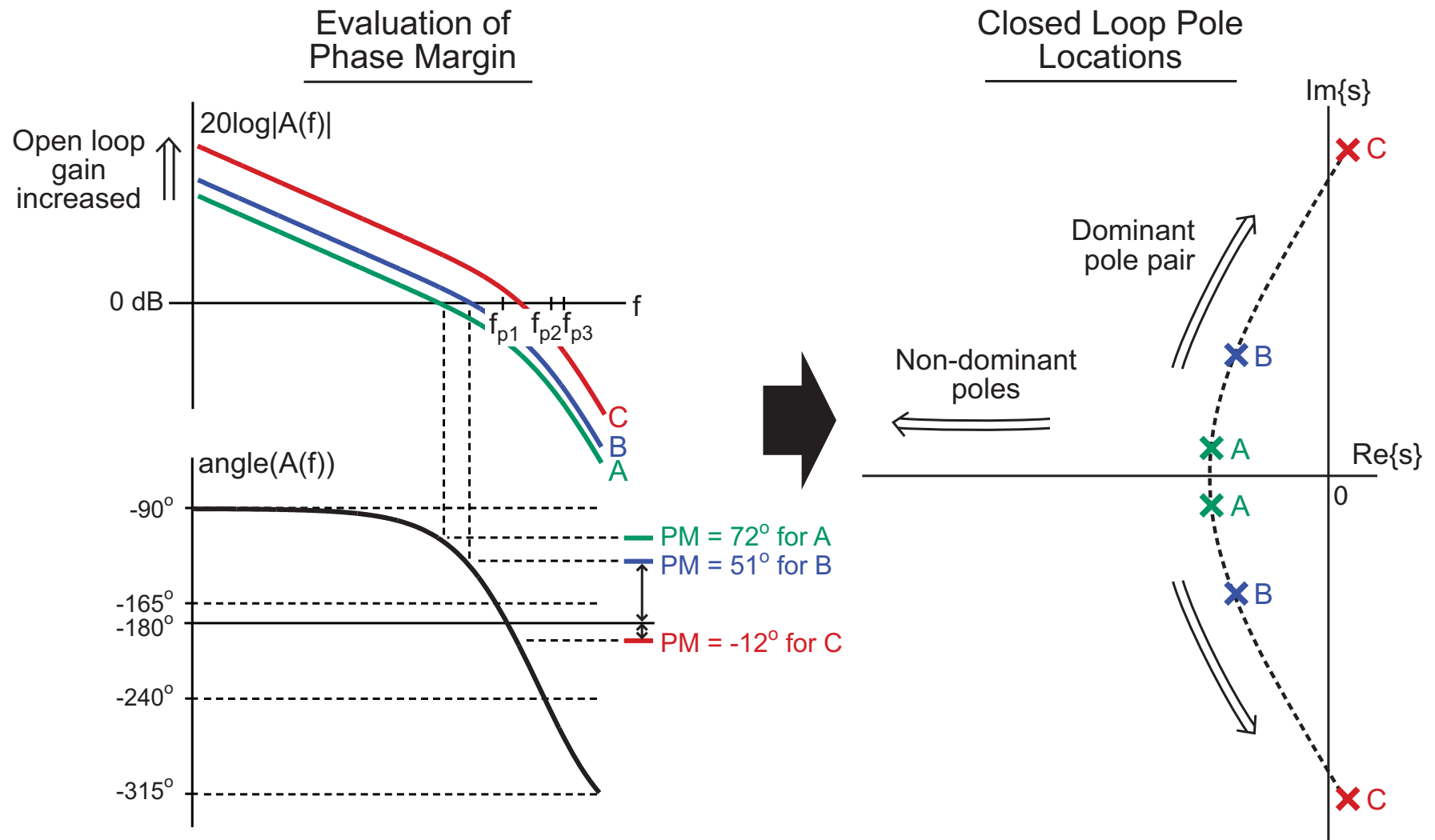

- Note the closed loop pole locations versus open loop gain
 - Is the closed loop system unstable for any case above?



Corresponding Closed Loop Behavior

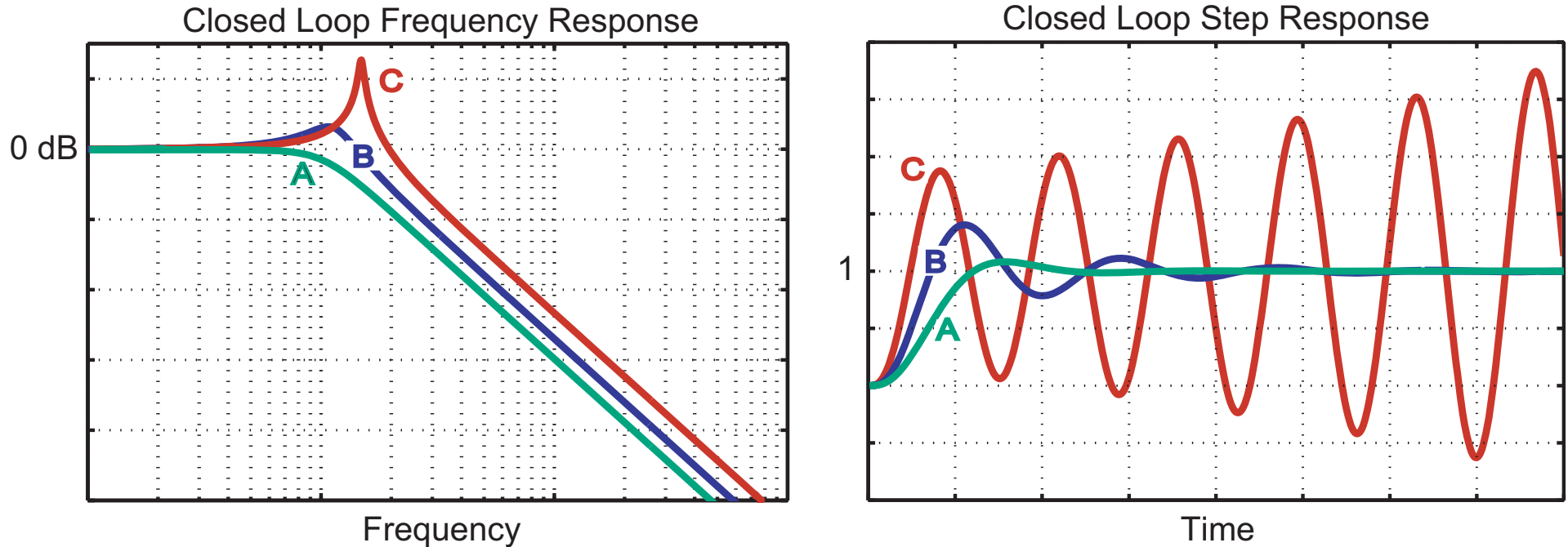



- Frequency response again sees more peaking with higher open loop gain
 - How does this relate to the movement of the closed loop pole locations?
- Step response ringing grows for high open loop gain
 - How does this relate to the closed loop pole locations?

Open Loop Versus Closed Loop Amplifier Topologies

Open Loop

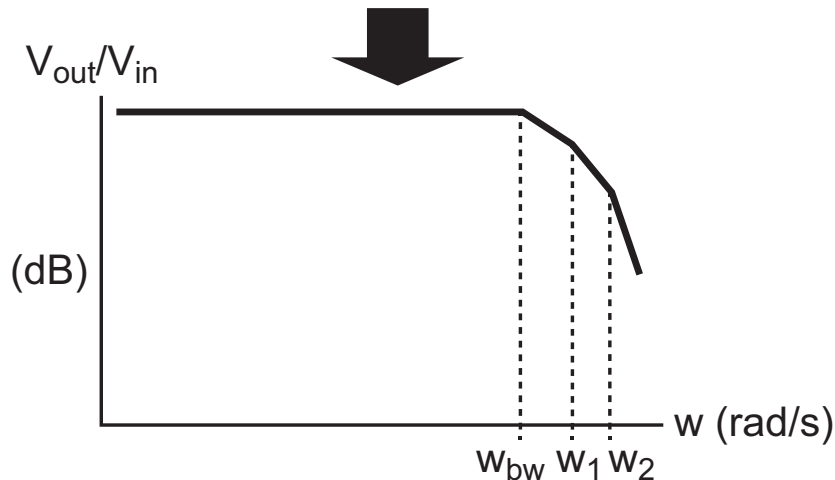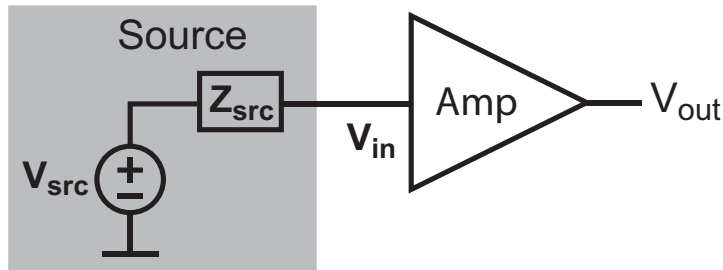

Closed Loop

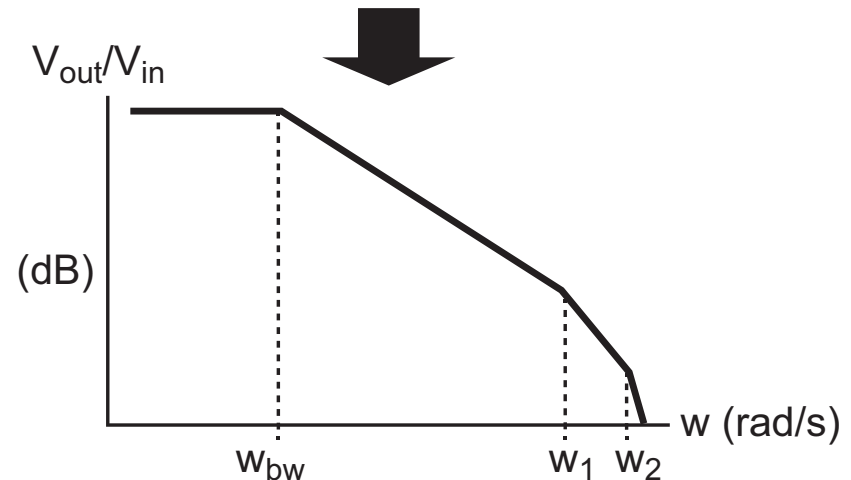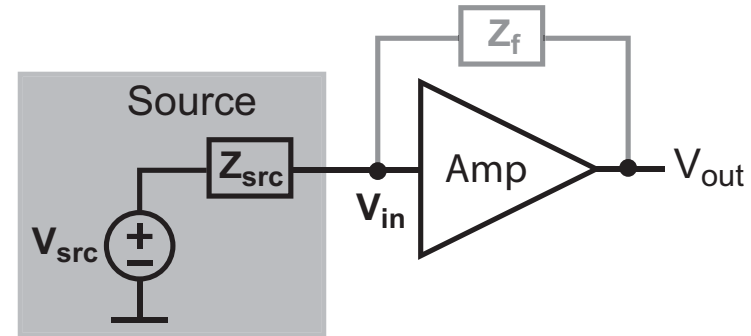

- Now that we understand the phase margin criterion, can you explain why amplifiers designed to be within a closed loop system should have one dominant pole that is much lower in frequency than the parasitic poles?

Summary

- **Feedback systems offer the benefit of accurate gain at low frequencies**
 - Assumes accurate feedback and high open loop DC gain
 - Gain-bandwidth product of the closed loop system equals w_{unity} of the open loop amplifier
- **Accuracy of the closed loop DC gain is reduced with lower open loop DC gain**
 - Want the open loop DC gain to be much higher than the desired closed loop DC gain for reasonable accuracy
- **Stability of the closed loop system is often evaluated using the phase margin criterion**
 - Examines the phase at unity gain frequency of the open loop response, $A(w_o) = \beta \cdot H(w_o)$, where $|A(w_o)| = 1$
 - w_o is approximately the same as the closed loop bandwidth, w_{bw}