

Analysis and Design of Analog Integrated Circuits
Lecture 18

Key Opamp Specifications


Michael H. Perrott

April 8, 2012


Copyright © 2012 by Michael H. Perrott

All rights reserved.

 Recall: Key Specifications of Opamps (Open Loop)




For Open Loop Characterization
 Set $R_{huge} \gg |Z_{out}|$
 and $1/(R_{huge} C_{huge}) \ll \omega_{dom}$

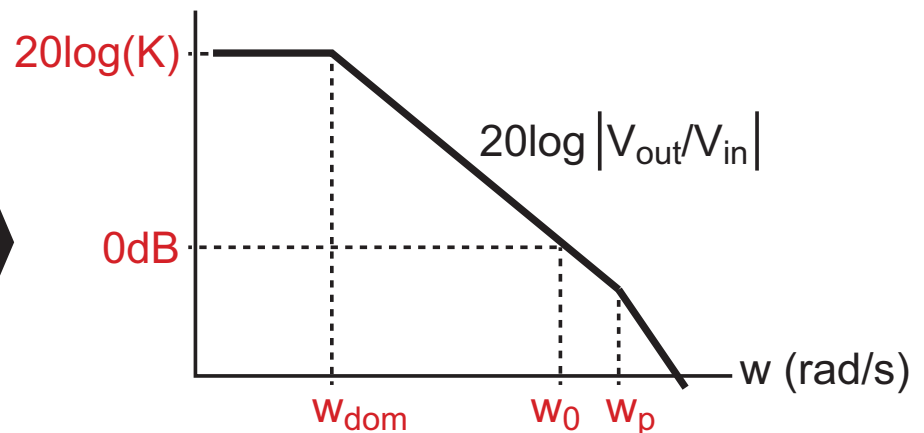

- DC small signal gain: K
- Unity gain frequency: ω_0
- Dominant pole frequency: ω_{dom}
- Parasitic pole frequencies: ω_p (and higher order poles)
- Output swing (max output range for DC gain $> K_{min}$)

 Recall: Key Specifications of Opamps (Closed Loop)




- Offset voltage
- Settling time (closed loop bandwidth)
- Input common mode range
- Equivalent Input-Referred Noise
- Common-Mode Rejection Ratio (**CMRR**)

$$CMRR = \left(\frac{\delta V_{offset}}{\delta V_{in}} \right)^{-1}$$

- Power Supply Rejection Ratio (**PSRR**)

$$PSRR^+ = \left(\frac{\delta V_{offset}}{\delta V_{dd}} \right)^{-1} \quad PSRR^- = \left(\frac{\delta V_{offset}}{\delta V_{ss}} \right)^{-1}$$

Basic Two Stage CMOS Op Amp

 


- This is a common “workhorse” opamp for medium performance applications
- Provides a nice starting point to discuss various CMOS opamp design issues
- Starting assumptions: $W_1/L_1 = W_2/L_2$, $W_3/L_3 = W_4/L_4$


Key Specifications Discussed In This Lecture

- **Systematic offset voltage**
- **CMRR**
- **PSRR⁺ and PSRR⁻**
- **Input-referred voltage noise**
- **Slew rate**

A Closer Look at Offset Voltage

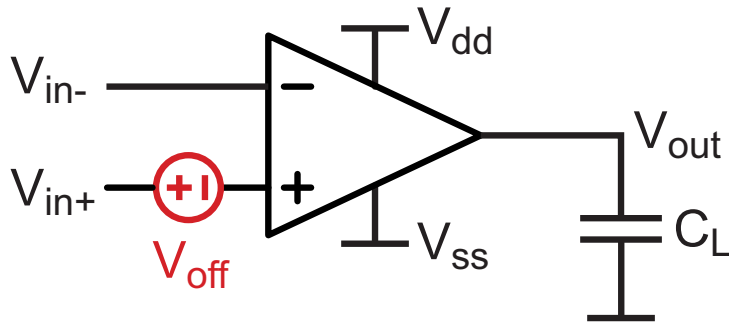
 
$$V_{out} = H(s) (V_{in+} - V_{in-} - V_{off})$$



Assume:


- Input to opamp is a DC signal
- Amplifier is not saturated
- DC gain of amplifier is large

$$V_{out} = K (V_{in+} - V_{in-} - V_{off})$$

$$\Rightarrow V_{in+} - V_{in-} = V_{off} + V_{out}/K \approx V_{off}$$

Two sources of offset: systematic and random


Systematic Offset: First Stage Analysis

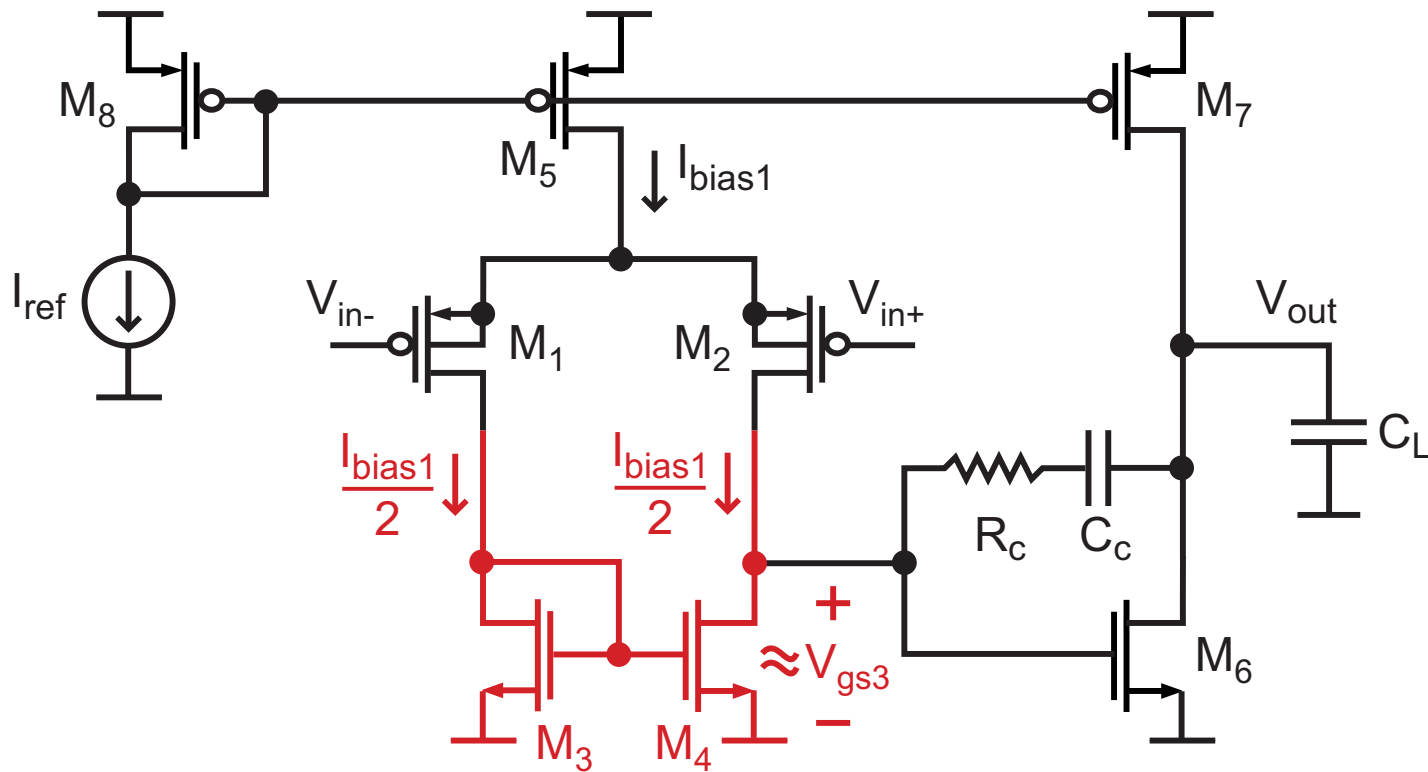

- For zero systematic offset we want V_{out} to be at roughly mid-rail assuming $V_{in+} = V_{in-}$
 - $V_{in+} = V_{in-}$ leads to equal currents in M_3/M_4
 - Equal currents and equal V_{gs} for M_3/M_4 leads to:

$$V_{ds4} = V_{ds3} = V_{gs3}$$

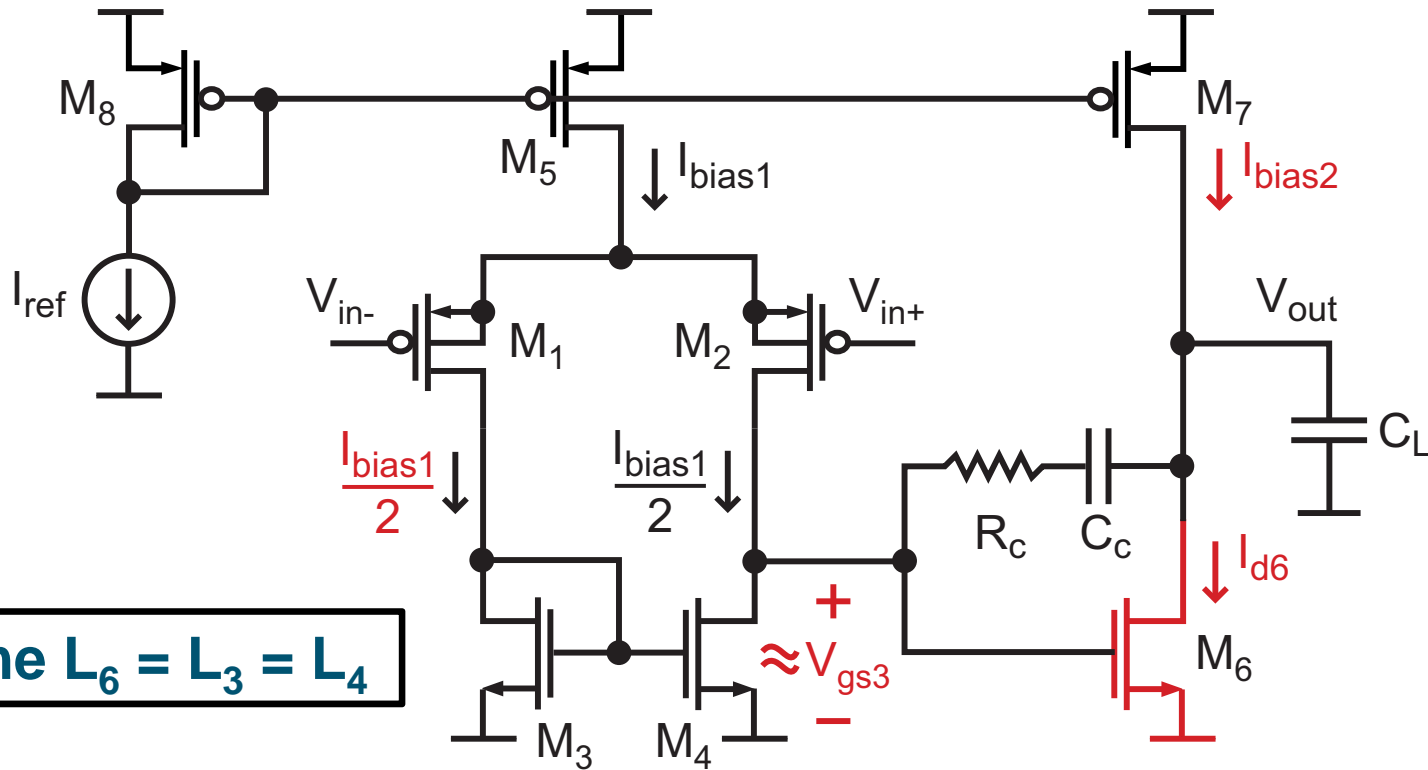Key Constraints To Achieve Zero Systematic Offset




- For mid-rail V_{out} , we need $I_{d6} = I_{bias2}$

$$\Rightarrow I_{d6} = \frac{1}{2} \mu_n C_{ox} \frac{W_6}{L_6} (V_{gs3} - V_{TH})^2 = I_{bias2}$$

Also: $\frac{1}{2} \mu_n C_{ox} \frac{W_3}{L_3} (V_{gs3} - V_{TH})^2 = \frac{I_{bias1}}{2} \Rightarrow \frac{W_6}{2W_3} = \frac{I_{bias2}}{I_{bias1}} = \frac{W_7}{W_5}$

 Key Common-Mode Rejection (CMRR) Observations



- **CMRR defined as a_{vd}/a_{vc} , where**


$$a_{vd} = a_{vd1}a_{vd2}$$

$$a_{vc} = a_{vc1}a_{vc2}$$

- **Inspection of the above reveals that CMRR is determined by the first stage**

$$CMRR = \frac{a_{vd1}a_{vd2}}{a_{vc1}a_{vc2}} = \frac{a_{vd1}}{a_{vc1}} = CMRR_1$$

Common Mode Gain and Resulting CMRR

 

- Differential gain was derived in Lecture 17


$$a_{vd1} = g_{m1} (r_{o2} || r_{o4})$$

- Common-mode gain is calculated from the above as

$$a_{vc1} = \frac{1/g_{m4}}{1/g_{m2} + 2r_{o5}} \approx \frac{1}{2g_{m4}r_{o5}}$$

$$\Rightarrow CMRR = \frac{a_{vd1}}{a_{vc1}} = \boxed{2g_{m1}(r_{o2} || r_{o4})g_{m4}r_{o5}}$$

 Characterizing CMRR with Changes in Offset Voltage




- Consider V_{in} as a common-mode signal which has an *open loop* impact on V_{out} as

$$\Delta V_{out} = a_{vc} \Delta V_{in}$$

- However, the *closed loop* configuration above tries to keep $V_{in+} = V_{in-}$ subject to finite differential gain a_{vd}

$$\begin{aligned} V_{out} &= a_{vd}(V_{in} - V_{out}) = a_{vd}V_{offset} \\ \Rightarrow \Delta V_{offset} &= \frac{1}{a_{vd}} \Delta V_{out} = \frac{a_{vc}}{a_{vd}} \Delta V_{in} \\ \Rightarrow \frac{\Delta V_{offset}}{\Delta V_{in}} &= \frac{a_{vc}}{a_{vd}} = (CMRR)^{-1} \end{aligned}$$

Power Supply Rejection Ratio (PSRR)

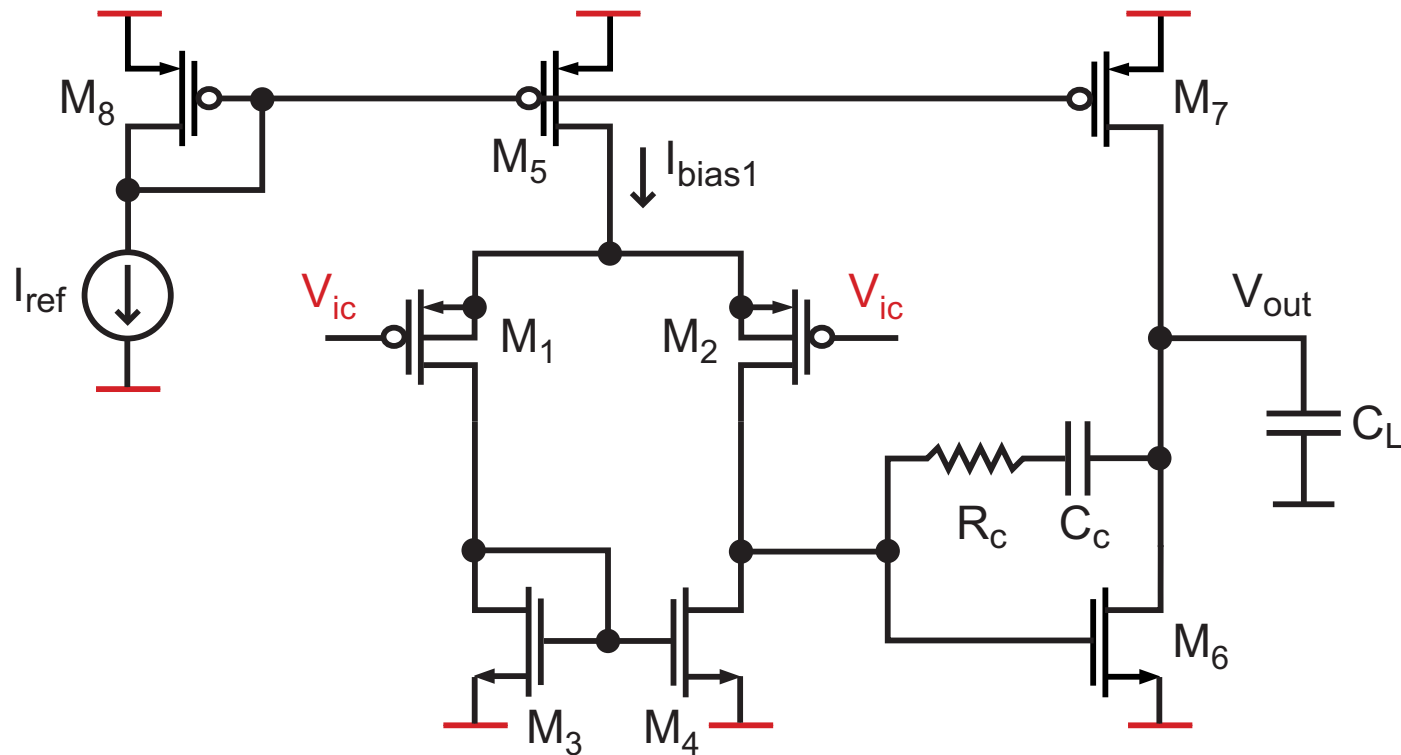


- We now consider the impact of positive and negative supply variation on the output of the amplifier
 - Key assumption: $V_{in+} = V_{in-} = V_{ic}$
- Definitions:

$$PSRR^+ = \frac{a_{vd}}{a^+}$$


$$PSRR^- = \frac{a_{vd}}{a^-}$$

Simplification of Current Mirror

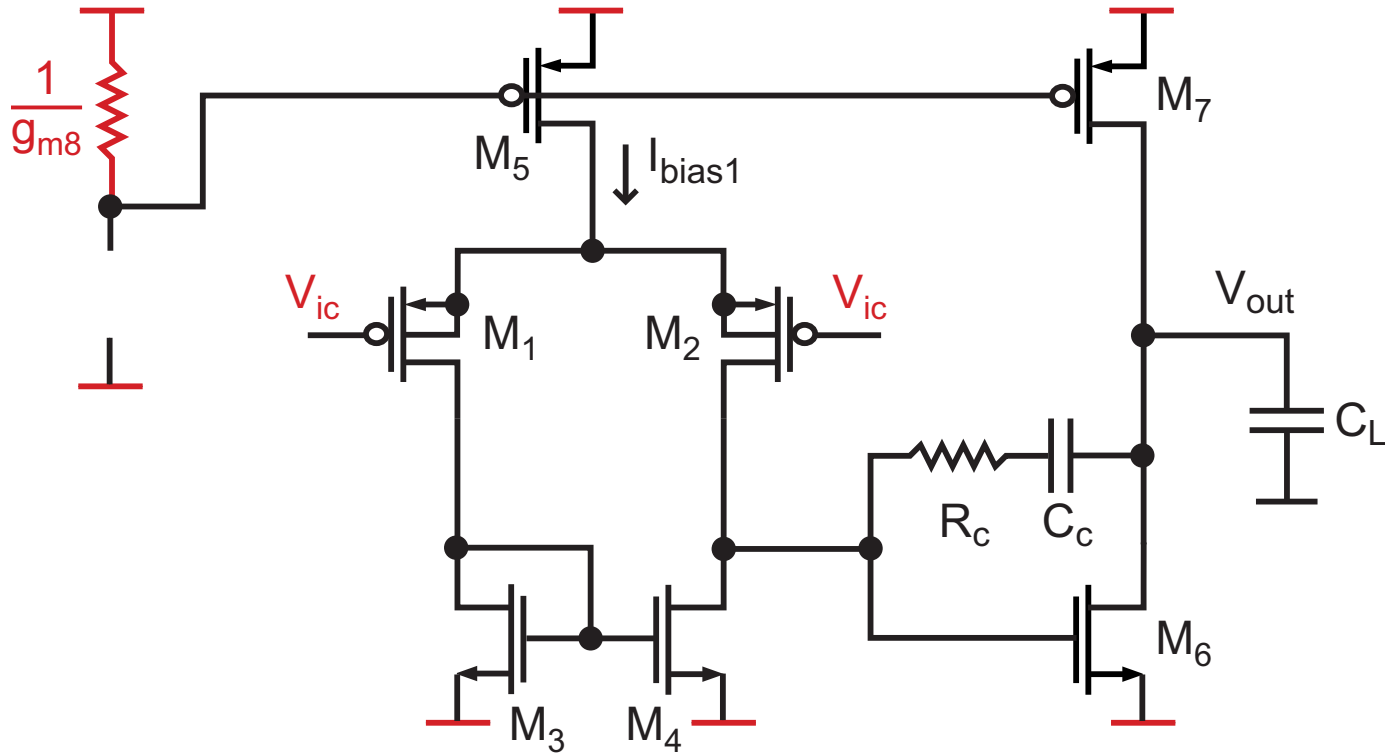


- **Replace current reference and diode connected device M_8 with their small signal models**
 - We see that positive and negative supply variations have no impact on V_{gs} of M_5 and M_7
 - We can ignore M_8 and current reference in our PSRR analysis

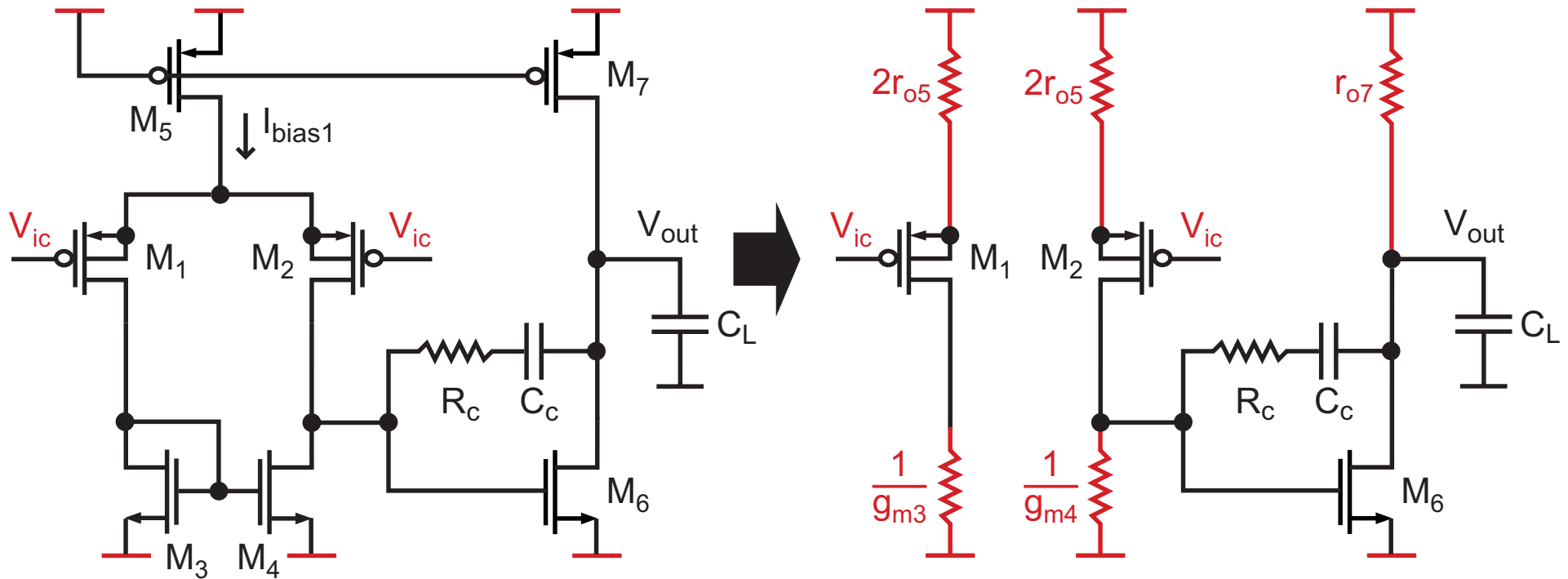Further Simplifications for PSRR Calculations



- Observe that positive and negative supply variations have equal impact on both sides of the differential pair
 - We can use common-mode analysis for the first stage

 Calculation of $PSRR^+$ At Low Frequencies




■ Calculation of impact of V_{s+} on V_{out}

$$V_{out} = \frac{r_{o6}}{r_{o6} + r_{o7}} V_{s+} + g_{m6}(r_{o6} || r_{o7}) \left(\frac{1}{2g_{m4}r_{o5}} \right) V_{s+}$$

$$\Rightarrow a_+ = \frac{V_{out}}{V_{s+}} \approx 1$$

$$\Rightarrow PSRR^+ = \frac{a_{vd}}{a_{v+}} \approx a_{vd} = \boxed{g_{m1}(r_{o2} || r_{o4})g_{m6}(r_{o6} || r_{o7})}$$

Calculation of PSRR At Low Frequencies

 


■ Calculation of impact of V_{s-} on V_{out}

$$V_{out} \approx \frac{r_{o7}}{r_{o6} + r_{o7}} V_{s-} + g_{m6}(r_{o6} || r_{o7}) \left(\frac{1}{g_{m4}(g_{m2}r_{o2})2r_{o5}} \right) V_{s-}$$

$$\Rightarrow a_- = \frac{V_{out}}{V_{s-}} \approx 1$$

$$\Rightarrow PSRR^- = \frac{a_{vd}}{a_{v-}} \approx a_{vd} = \boxed{g_{m1}(r_{o2} || r_{o4})g_{m6}(r_{o6} || r_{o7})}$$

 Characterizing PSRR with Changes in Offset Voltage



- Consider V_{dd} as a common-mode signal which has an *open loop* impact on V_{out} as

$$\Delta V_{out} = a_+ \Delta V_{dd}$$


- However, the *closed loop* configuration above tries to keep $V_{in+} = V_{in-}$ subject to finite differential gain a_{vd}

$$V_{out} = a_{vd}(V_{in} - V_{out}) = a_{vd}V_{offset}$$

$$\Rightarrow \Delta V_{offset} = \frac{1}{a_{vd}} \Delta V_{out} = \frac{a_+}{a_{vd}} \Delta V_{dd}$$


$$\Rightarrow \frac{\Delta V_{offset}}{\Delta V_{dd}} = \frac{a_+}{a_{vd}} = \left(PSRR^+\right)^{-1} \quad \text{(Similar for PSRR-)}$$

Noise Analysis for a Two Stage Opamp

 

- Each opamp stage will contribute noise
 - ▬ Typically the spectral density of the noise will be of the same order at each stage
- Input referral of the noise reveals that the second stage noise will have much less impact than the first stage noise
 - ▬ Input-referred noise calculations of an opamp need only focus on the first stage

Input-Referral of MOS Device Noise

 

■ Transistor drain current noise:

$$\overline{i_{nd}^2} = \underbrace{4kT \frac{\gamma}{\alpha} g_m \Delta f}_{\text{Thermal noise}} + \underbrace{\frac{K_f}{f} \frac{g_m^2}{WLC_{ox}^2} \Delta f}_{\text{1/f noise}}$$

Thermal noise

1/f noise

Note:

$$g_{ds0} = \frac{g_m}{\alpha}$$

■ Input-referred voltage noise:


$$\overline{v_{ni}^2} = \underbrace{4kT \frac{\gamma}{\alpha} \frac{1}{g_m} \Delta f}_{\text{Thermal noise}} + \underbrace{\frac{K_f}{f} \frac{1}{WLC_{ox}^2} \Delta f}_{\text{1/f noise}}$$

Thermal noise

1/f noise

Impact of thermal versus 1/f noise depends on g_m

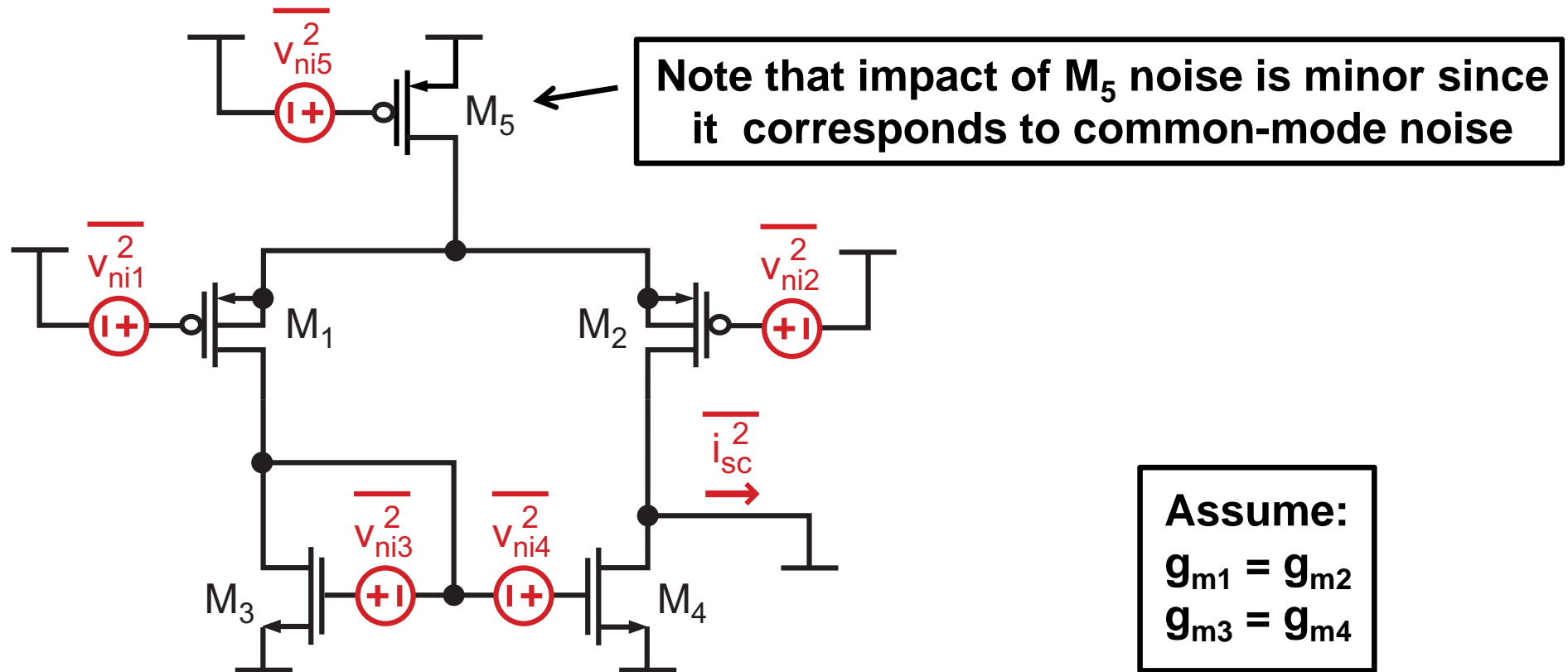
Analysis of Op Amp Output Noise (First Stage)



$$\overline{i_{sc}^2} = g_{m1}^2 \left(\overline{v_{ni1}^2} + \overline{v_{ni2}^2} \right) + g_{m3}^2 \left(\overline{v_{ni3}^2} + \overline{v_{ni4}^2} \right)$$

$$\Rightarrow \overline{i_{sc}^2} = 2g_{m1}^2 \overline{v_{ni1}^2} + 2g_{m3}^2 \overline{v_{ni3}^2}$$

Determining Input-Referred Noise

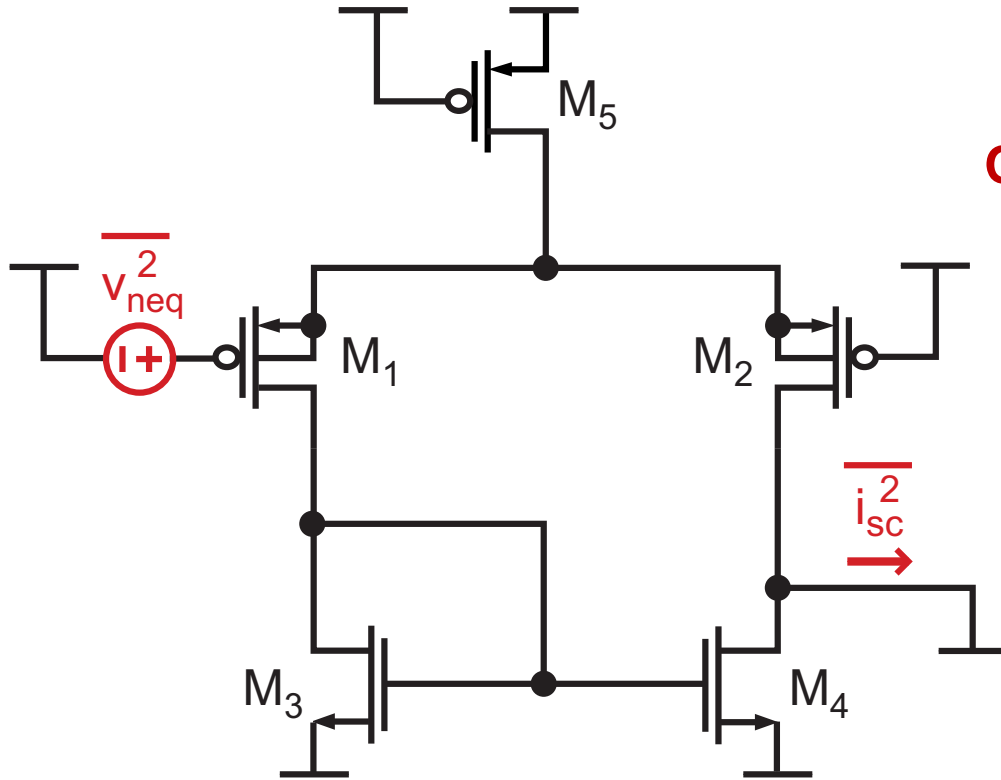

Output noise due to equivalent input-referred noise:

$$\overline{i_{sc}^2} = g_{m1}^2 \overline{v_{neq}^2}$$

Assume:


$$g_{m1} = g_{m2}$$

$$g_{m3} = g_{m4}$$

- Output noise due to individual devices (Slide 20):


$$\overline{i_{sc}^2} = 2g_{m1}^2 \overline{v_{ni1}^2} + 2g_{m3}^2 \overline{v_{ni3}^2} = g_{m1}^2 \overline{v_{neq}^2}$$
 
$$\overline{v_{neq}^2} = 2\overline{v_{ni1}^2} + 2 \left(\frac{g_{m3}}{g_{m1}} \right)^2 \overline{v_{ni3}^2}$$




Want $g_{m1} > g_{m3}$
for low noise

Characterizing Input-Referred Noise

 



- **Placing the amplifier within unity gain feedback configuration causes the overall output noise of the amplifier to become referred to the input**
 - We can now examine the low frequency content of the input-referred noise by simply probing the noise of V_{out}

Recall: Slew Rate Issues for Opamps

 

- **Output currents of practical opamps have max limits**
 - Impacts maximum rate of charging or discharging load capacitance, C_L
 - For large step response, this leads to the output lagging behind the ideal response based on linear modeling
 - We refer to this condition as being slew-rate limited
- **Where slew-rate is of concern, the output stage of the opamp can be designed to help mitigate this issue**
 - Will lead to extra complexity and perhaps other issues

  
Key Observations for Slew Rate Calculations



Current Limits

- **First stage**
 - Max $I_1 = I_{\text{bias1}}$
 - Min $I_1 = -I_{\text{bias1}}$
- **Second stage**
 - Max $I_2 = I_{\text{bias2}}$
 - Min $I_2 = \text{Large}$

Slew Rate Analysis (First Stage Limits)

 


- Slew rate refers to maximum voltage slope at output
 - Impact of current limits in first stage:

$$V_{out} = -\frac{1}{C_c} \int I_1 dt \Rightarrow \left. \frac{dV_{out}}{dt} \right|_{max} = -\left. \frac{I_1}{C_c} \right|_{max} = \frac{I_{bias1}}{C_c}$$

$$\left. \frac{dV_{out}}{dt} \right|_{min} = -\left. \frac{I_1}{C_c} \right|_{min} = -\frac{I_{bias1}}{C_c}$$

Slew Rate Analysis (Second Stage Limits)

 

■ Impact of current limits in second stage


- Maximum slope at the output:

$$\left. \frac{dV_{out}}{dt} \right|_{max} = \frac{I_{bias2}}{C_c + C_L}$$

- Minimum slope at the output:

$$\left. \frac{dV_{out}}{dt} \right|_{min} = \text{Large}$$

Slew Rate Analysis (Overall)

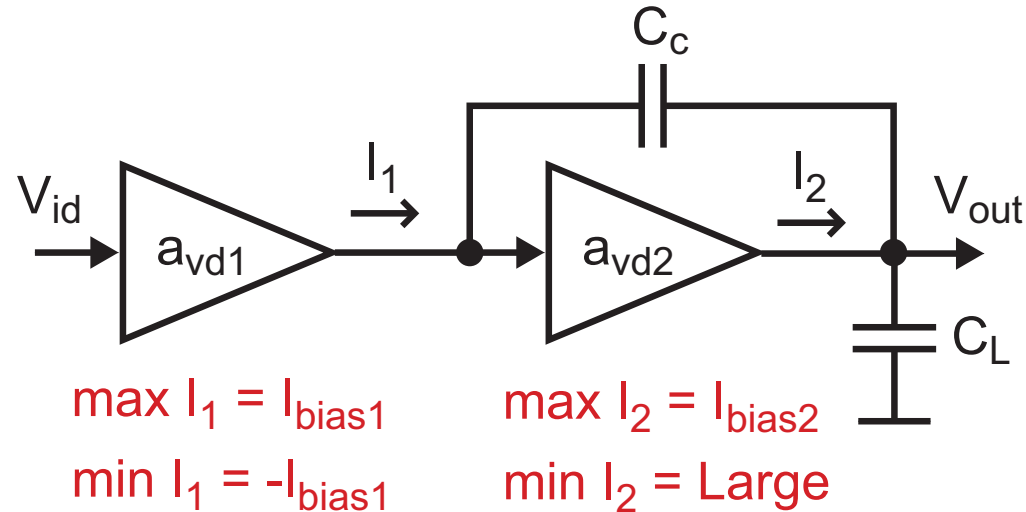


- **Maximum slope at the output:**

$$\left. \frac{dV_{out}}{dt} \right|_{max} = \min \left(\frac{I_{bias1}}{C_c}, \frac{I_{bias2}}{C_c + C_L} \right)$$

- **Minimum slope at the output:**

$$\left. \frac{dV_{out}}{dt} \right|_{min} = \frac{-I_{bias1}}{C_c}$$

Impact of Slew Rate

 

- Consider the closed loop, unity gain configuration above with a sine wave input

$$V_{in} = A \sin(\omega t)$$

- Note: the max slope of the input depends on A and ω

$$\frac{dV_{in}}{dt} = A\omega \cos(\omega t) \quad \Rightarrow \quad \left. \frac{dV_{out}}{dt} \right|_{max} = A\omega$$

Slew rate limits the maximum frequency that the amplifier can track

Summary

- Opamp design must take into consideration many different specifications
- Today we covered
 - Systematic offset voltage
 - CMRR
 - PSRR⁺ and PSRR⁻
 - Input-referred voltage noise
 - Slew rate