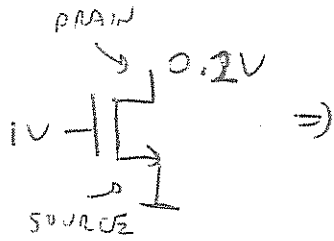


LECTURE 3


SLIDE 19)



$$DV = 1 - V_{THn} = 0.5V$$

SINCE $V_{DS} < DV$

\Rightarrow DEVICE IS IN TRIODE REGION

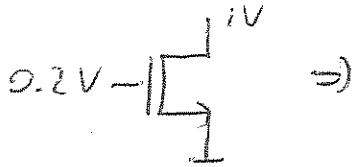

$$DV = 0.2 - V_{THn} < 0$$

\Rightarrow DV IS NOT VALID


\Rightarrow DEVICE IS IN SUBTHRESHOLD REGION



$$DV = 1 - V_{THn} = 0.5V$$

SINCE $V_{DS} = 0.7V > DV$

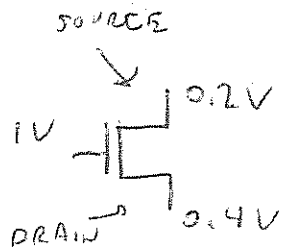\Rightarrow DEVICE IS IN SATURATION REGION




SOURCE CORRESPONDS TO ~~THE~~ NON-GATE TERMINAL AT THE LOWEST POTENTIAL

$$\Rightarrow DV = 1V - 0.2 - V_{THn} = 0.3V$$

SINCE $V_{DS} = 0.4 - 0.2 = 0.2V$

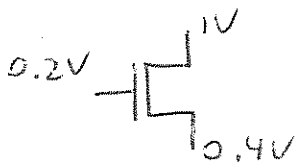$V_{DS} < DV \Rightarrow$ DEVICE IS IN TRIODE REGION




$$\Rightarrow DV = 0.2V - 0.4V - V_{THn} < 0$$

\Rightarrow DV IS NOT VALID

\Rightarrow DEVICE IS IN SUBTHRESHOLD REGION

FOR THIS LOW OF A GATE BIAS (I.E. $V_{GS} \leq 0$) WE WOULD OFFER SAY THE ~~DEV~~ DEVICE IS IN ITS CUTOFF REGION

SLIDE 19)
(CONT.)

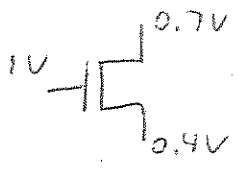


$$OV = 1V - 0.4V - |V_{thn}| = 0.1V$$

SINCE $V_{GS} = 0.3V > OV$

⇒ DEVICE IS IN SATURATION

SLIDE 20)

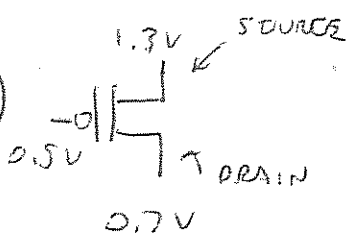


$$OV = 1.3 - 0.5 - |V_{thp}| = 0.3V$$

$$V_{SD} = 1.3 - 0.7 = 0.5V$$

SINCE $V_{SD} > OV$


⇒ DEVICE IS IN SATURATION

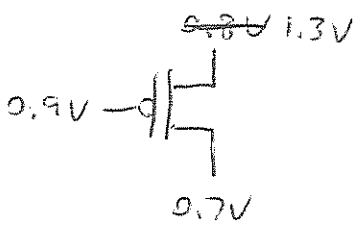

$$OV = 1.3 - 0.9 - |V_{thp}| < 0$$

⇒ OV IS NOT VALID

⇒ DEVICE IS IN SUBTHRESHOLD REGION

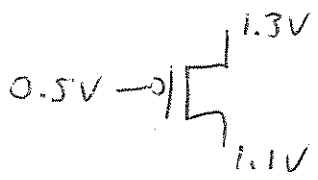


$$OV = 1.3V - 0.5V - |V_{thp}| = 0.3V$$

$$V_{SD} = 1.3 - 1.1 = 0.2V$$

SINCE $V_{SD} < OV$

⇒ DEVICE IS IN TRIODE REGION

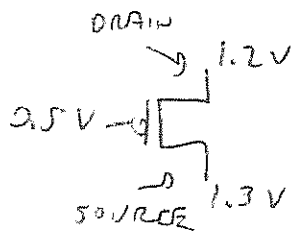


SOURCE CORRESPONDS TO NON-GATE TERMINAL AT THE HIGHEST POTENTIAL

$$OV = 1.3 - 0.5 - |V_{thp}| = 0.3V$$

$$V_{SD} = 1.3 - 1.2 = 0.1V$$

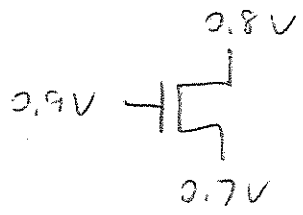SINCE $V_{SD} < OV$ ⇒ DEVICE IS IN TRIODE REGION




$$OV = 0.8 - 0.9 - |V_{thp}| < 0$$

⇒ OV IS NOT VALID

⇒ DEVICE IS IN SUBTHRESHOLD REGION

FOR THIS LAW OF A GATE BIAS (I.E., $V_{SG} \leq 0$) WE WOULD OFTEN SAY THE DEVICE IS IN ITS CUTOFF REGION

SLIDE 20)
(CONT.)

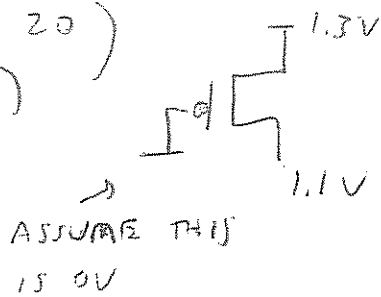


$$OV = 1.3V - 0V - |V_{THp}| = 0.8V$$

$$V_{SD} = 1.3 - 1.1 = 0.2V$$

SINCE $V_{SD} < OV \Rightarrow$ DEVICE IS IN TRIODE REGION

SLIDE 21)

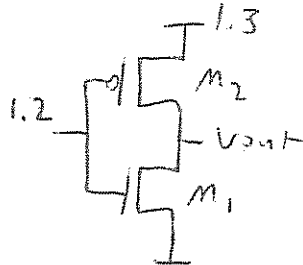

$$M_2 : OV = 1.3 - 1.2 - |V_{THn}| < 0$$


\Rightarrow M₂ IS IN SUBTHRESHOLD REGION

$$M_1 : OV = 1.2 - V_{THn} = 0.7V$$

\Rightarrow M₁ IS IN SATURATION OR TRIODE

SINCE M₁ AND M₂ HAVE THE SAME SIZE,
M₁ WILL SUPPORT MUCH MORE CURRENT FLOW
THAN M₂ UNDER THE GIVEN BIAS CONDITIONS
 \Rightarrow V_{out} WILL TEND TOWARD 0V IF V_{out} $\approx \frac{1.3}{2}$

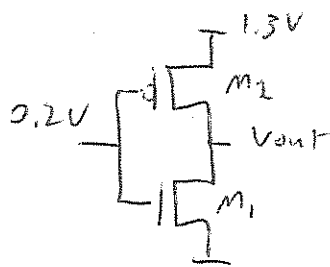\Rightarrow M₁ WILL BE IN THE TRIODE REGION



$$M_2 : OV = 1.3 - 0.2 - |V_{THn}| = 0.6V$$

\Rightarrow M₂ IS IN SATURATION OR TRIODE

$$M_1 : OV = 0.2 - V_{THn} < 0$$


\Rightarrow M₁ IS IN SUBTHRESHOLD REGION

SINCE M₁ AND M₂ HAVE THE SAME SIZE,
M₂ WILL ~~SUPPORT~~ SUPPORT MUCH MORE CURRENT FLOW
THAN M₁ UNDER THE GIVEN BIAS ~~COND~~ CONDITIONS
IF V_{out} $\approx \frac{1.3}{2}$

\Rightarrow V_{out} WILL TEND TOWARD 1.3V

\Rightarrow M₂ WILL BE IN TRIODE REGION

SLIDE 20
(CONT.)

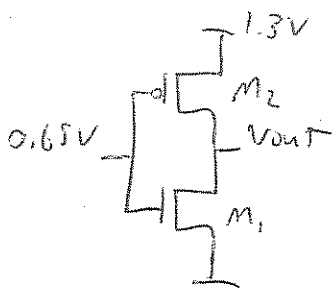

$M_2: DV = 1.3 - 0.65 - |V_{THP}| = 0.15V$
 $\Rightarrow M_2$ IS IN SATURATION OR TRIODE

$M_1: DV = 0.65 - V_{THN} = 0.15V$
 $\Rightarrow M_1$ IS IN SATURATION OR TRIODE

CONSIDER $V_{OUT} = \frac{1.3}{2} = 0.65V$


~~WHILE M_1 AND M_2~~ SINCE M_1 AND M_2 ARE THE SAME SIZE AND BOTH HAVE ^{SAME} $DV > 0$, THEIR CURRENT CARRYING CAPABILITY WILL BE DETERMINED BY $m_n C_{ox}$ ~~AND~~ VERSUS $m_p C_{ox}$.

\Rightarrow SINCE $m_n C_{ox} > m_p C_{ox}$, M_1 WILL ~~NOT~~ HAVE GREATER CURRENT CARRYING CAPABILITY

$\Rightarrow V_{OUT}$ WILL TEND TOWARDS ZERO

$\Rightarrow M_1$ WILL BE IN TRIODE, M_2 WILL BE IN SATURATION

SLIDE 22)

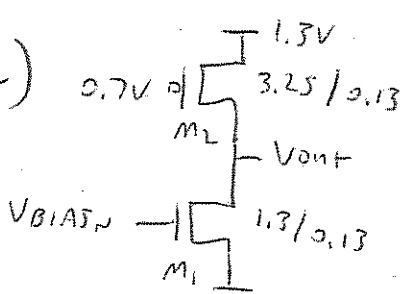

DETERMINE CURRENT FROM M_2 ~~ASSUMING~~ ASSUMING $V_{out} = 0.5V$

$M_2: DV = 1.3 - 0.7 - |V_{THP}| = 0.1V$

$V_{SD} = 1.3 - V_{out} = 0.8V$

$\Rightarrow M_2$ WILL BE IN SATURATION

$$M_2: I_D = \frac{1}{2} m_p C_{ox} \frac{W}{L} (V_{SD} - (-V_{THP}))^2 (1 + \lambda V_{SD})$$

$$= \frac{1}{2} (20 \times 10^{-6}) \frac{3.25}{0.13} (0.1)^2 = 2.5 \mu A$$

M_1 : WE ARE NOT SURE IF M_1 WILL BE IN TRIODE OR SATURATION (SUBTHRESHOLD IS VERY UNLIKELY SINCE DEVICE SIZE OF M_1 WOULD NEED TO BE MUCH LARGER THAN M_2 IN ORDER TO SUPPORT SIMILAR CURRENT WHILE IN SUBTHRESHOLD REGION)

SLIDE 22
(CONT.)

WE FIRST GUESS THAT M_1 IS IN SATURATION

$$\Rightarrow I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{THN})^2 (1 + \lambda V_{DS})$$

$$2.5 \times 10^{-6} = \frac{1}{2} (50 \times 10^{-6}) \left(\frac{1.3}{0.13} \right) (DV)^2$$

$$\Rightarrow (DV)^2 = 0.01 \Rightarrow DV = 0.1V$$

SINCE THE ABOVE WORKED OUT, (I.E. $DV > 0$
OUR GUESS WAS CORRECT (AND $V_{DS} = 0.5 > DV$)

$$\Rightarrow V_{BIASN} = V_{THN} + DV = 0.5 + 0.1 = 0.6V$$

M_1 AND M_2 ARE BOTH IN SATURATION

NOTE: ONE COULD HAVE ALSO STARTED WITH THE
GUESS THAT M_1 WAS IN TRIODE REGION

$$\Rightarrow I_D = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{THN} - V_{DS}/2) V_{DS}$$

SINCE V_{OUT} IS ASSUMED TO BE 0.5V:

$$2.5 \mu A = (50 \times 10^{-6}) \left(\frac{1.3}{.13} \right) (V_{GS} - 0.5 - 0.25) 0.5$$

$$\Rightarrow 5 \times 10^{-3} = (V_{GS} - 0.75) 0.5$$

$$\Rightarrow 10 \times 10^{-3} = V_{GS} - 0.75 \Rightarrow V_{GS} = 0.76$$

$$\Rightarrow DV = V_{GS} - V_{THN} = 0.76 - 0.5 = 0.26$$

BUT $V_{DS} = 0.5$ ASSUMING $V_{OUT} = 0.5V$

\Rightarrow SINCE $V_{DS} > DV$ IN THIS CALCULATION,
THE TRIODE REGION ASSUMPTION IS INCORRECT!