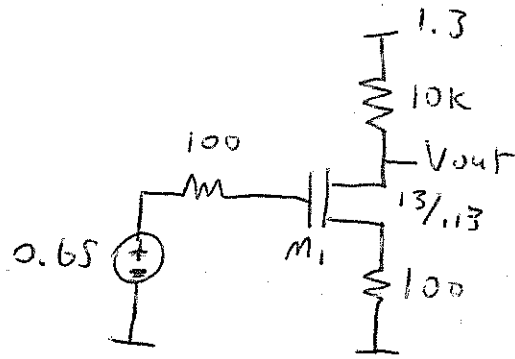
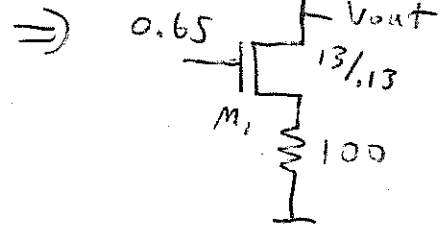


LECTURE 4

SLIDE 16)

GATE
RESISTANCE
HAS ZERO
CURRENT

TO SOLVE FOR OPERATING POINT (I.E., LARGE SIGNAL),
FIRST TRY ASSUMING THAT M_1 IS IN SATURATION

NOTE THAT $V_{GS} = 0.65 - I_D \cdot 100$, IGNORE \Rightarrow FOR NOW

$$\begin{aligned} \Rightarrow I_D &= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2 \\ &= \frac{1}{2} 50 \times 10^{-6} (100) (0.65 - I_D \cdot 100 - 0.5)^2 \\ &= 2.5 \times 10^{-3} (0.15 - I_D \cdot 100)^2 \end{aligned}$$

$$\Rightarrow \frac{I_D}{2.5 \times 10^{-3}} = (0.15)^2 - 2(0.15)(100)I_D + 100^2 I_D^2$$

$$\Rightarrow 0 = (0.15)^2 - 430 I_D + 10 \times 10^3 I_D^2$$

$$\Rightarrow I_D = \frac{430 \pm \sqrt{430^2 - 4 \cdot 10 \times 10^3 \cdot (0.15)^2}}{2 \cdot 10 \times 10^3}$$

$$= 21.5 \times 10^{-3} \pm 21.4476 \times 10^{-3}$$

$$= 42.9476 \times 10^{-3} \text{ OR } 52.39 \times 10^{-6}$$

BUT 42 mA IS NOT POSSIBLE SINCE THAT WOULD
IMPLY A VOLTAGE DROP ACROSS THE 100Ω
RESISTOR OF 4.2 V $\Rightarrow V_{GS} = 0.65 - 4.2 < 0$!

THEREFORE $I_D = 52.39 \mu\text{A}$ $\left(V_S = 52.39 \mu\text{A} \cdot 100 \right)$
 $= 5.239 \text{ mV}$

SINCE V_S IS ONLY 5.2 mV, THE IMPACT ON V_{TH} IS QUITE SMALL AND CAN BE IGNORED

$$I_D = 52.39 \mu A \Rightarrow V_{out} = 1.3 - 10k \cdot 52.39 \mu A \\ = 0.776 V$$

$$\Rightarrow V_{OS} = 0.776 - 0.0052 \approx 0.77 V$$

$$DV = 0.68 - 0.0052 - V_{THN} \approx 0.145 V$$

SINCE $V_{OS} > DV$, DEVICE IS INDEED IN SATURATION

NOW WE CAN CALCULATE SMALL SIGNAL ~~PARAM~~ PARAMETERS

$$g_m \approx \sqrt{2 \mu_n C_{ox} \frac{W}{L} I_D} = \sqrt{2 (50 \times 10^{-6}) \cdot 100 \cdot 52.4 \mu A} \\ = \boxed{723.9 \times 10^{-6} = g_m}$$

$$g_{mb} = 0 \text{ SINCE } \gamma = 0$$

$$r_o = \frac{1}{\lambda I_D} = \frac{1}{\frac{1}{10} \cdot 52.4 \mu A} = 191 k\Omega$$

NOW WE CAN PLUG IN THE THEVENIN MODEL, BUT FIRST CALCULATE ITS PARAMETERS:


$$R_{THG} = \boxed{\infty}$$

$$R_{THO} = r_o (1 + (g_m + g_{mb}) R_S) + R_S \\ = 191 k (1 + (723.9 \times 10^{-6} + 0) 100) + 100 \\ = \boxed{205 k\Omega}$$

$$R_{THS} = \left(1 + \frac{R_D}{r_o}\right) \left(r_o \parallel \frac{1}{g_m + g_{mb}}\right) \\ = \left(1 + \frac{10k}{191k}\right) \left(191k \parallel \frac{1}{723.9 \times 10^{-6}}\right) \approx \boxed{1.4 k\Omega}$$


$$A_v = g_m r_{o1} \parallel \frac{g_m}{g_m + g_{mb}} = 723.9 \times 10^{-6} \cdot 1.91 \times 10^3 \parallel 1$$

$$\approx 0.993$$

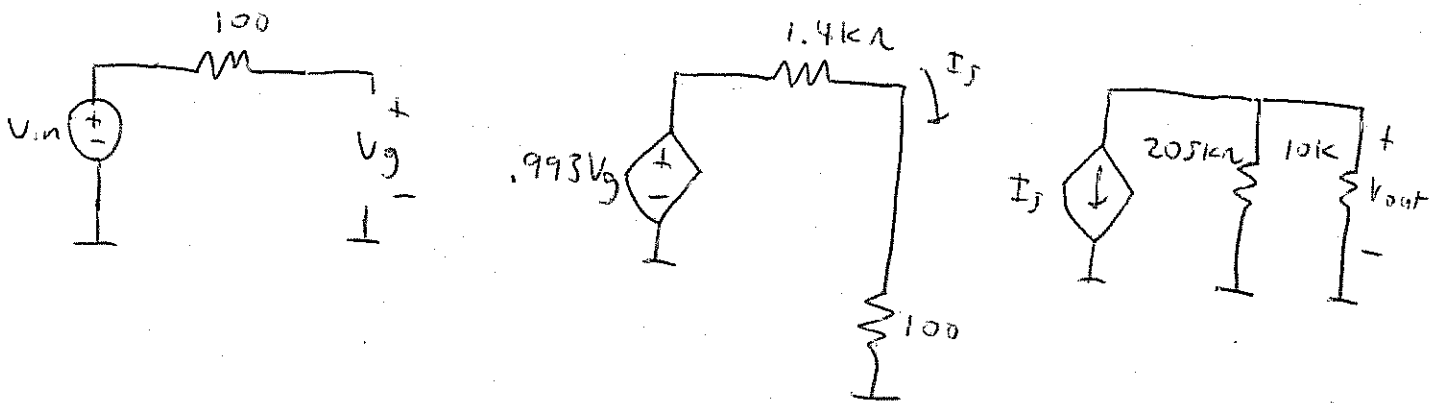

$$\Rightarrow I_J = \frac{0.993 V_g}{1.4k + 100} = 662 \times 10^{-6} V_g$$
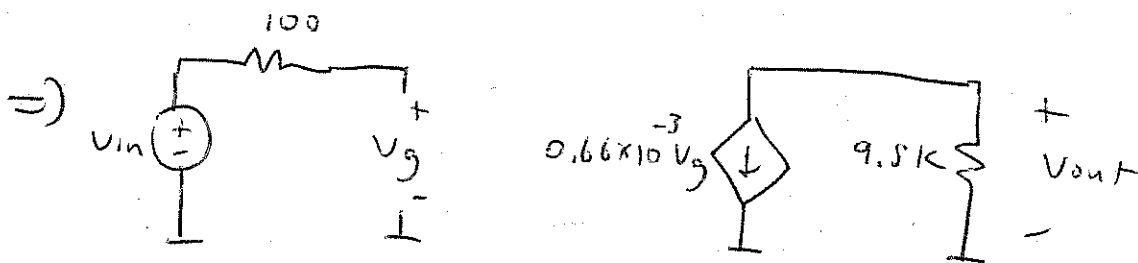
$$\text{Also: } 10k \parallel 205k \approx 9.5k\Omega$$



$$\text{THEREFORE, DC GAIN} = \frac{V_{out}}{V_{in}} = 0.66 \times 10^{-3} \cdot 9.5k$$

$$= \boxed{6.27}$$