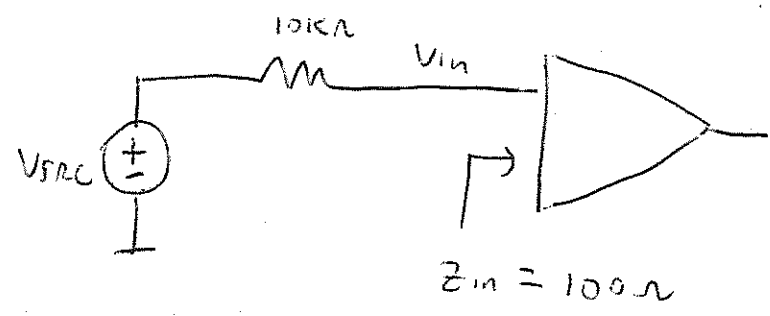


LECTURE 5

SLIDE 6)




$$V_{in} = \frac{100}{10k + 100} V_{src} \approx \frac{100}{10k} V_{src} = \frac{1}{100} V_{src}$$

$\Rightarrow \text{GAIN} = \frac{1}{100}$


$\Rightarrow$  IMPACT OF LOW  $Z_{in}$  AND HIGH  $Z_{src}$  IS  
HIGH ATTENUATION OF THE SOURCE SIGNAL


SLIDE 7)

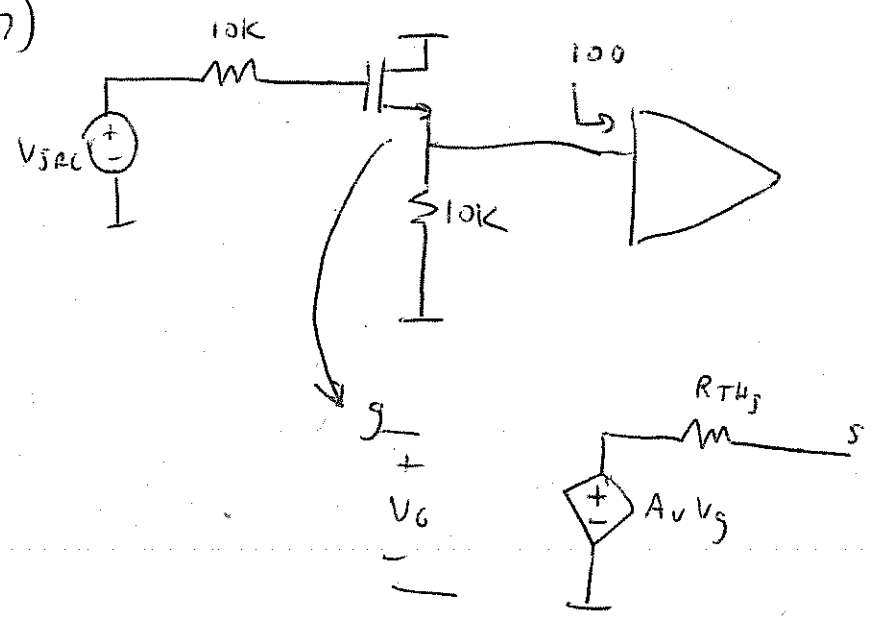

$$A_v = g_m r_{o1} \frac{g_m}{g_m + g_{mb}} = \frac{1}{100} 100k \parallel \frac{g_m}{g_m + 0} \approx 1$$
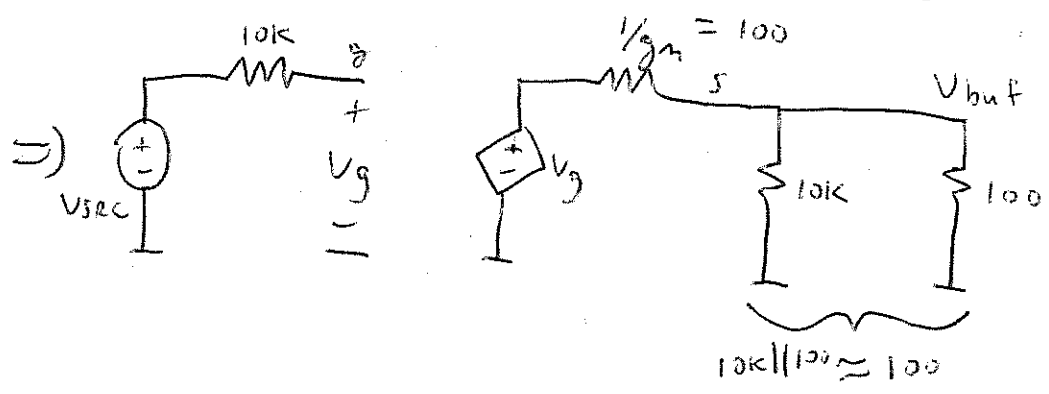
$$R_{thj} = \left(1 + \frac{R_o}{r_o}\right) \left(r_{o1} \parallel \frac{1}{g_m + g_{mb}}\right) \approx \frac{1}{g_m}$$




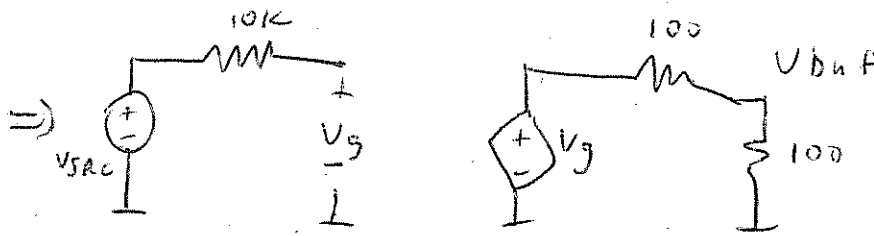

$$\Rightarrow V_{buf} \approx \frac{100}{100+100} V_g = \frac{1}{2} V_{src} \Rightarrow \boxed{\text{GAIN} \approx \frac{1}{2}}$$

THE SOURCE FOLLOWER DRAMATICALLY REDUCED THE ATTENUATION CAUSED BY THE LOW INPUT IMPEDANCE BY PROVIDING A HIGH IMPEDANCE TO THE SOURCE AND A LOW OUTPUT IMPEDANCE TO DRIVE THE  $Z_{in}$  LOAD

SLIDE 8)

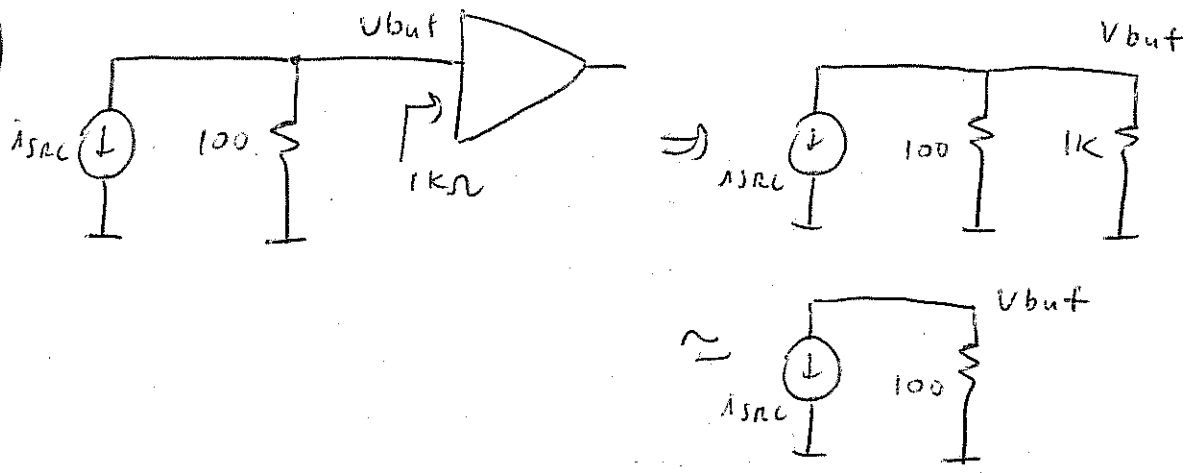

$$\Rightarrow V_{buf} \approx -100 \cdot I_{src}$$


$$\Rightarrow \text{GAIN (TRANSIMPEDANCE)} = \boxed{-100 \Omega}$$

IN THIS CASE, ~~low~~ LOW SOURCE IMPEDANCE RESULTS IN LOW TRANSIMPEDANCE GAIN.

IN THIS CASE, USING A SOURCE FOLLOWER WILL NOT HELP SINCE THE SOURCE IMPEDANCE WILL STILL LIMIT THE TRANSIMPEDANCE GAIN.

SLIDE 9)


3

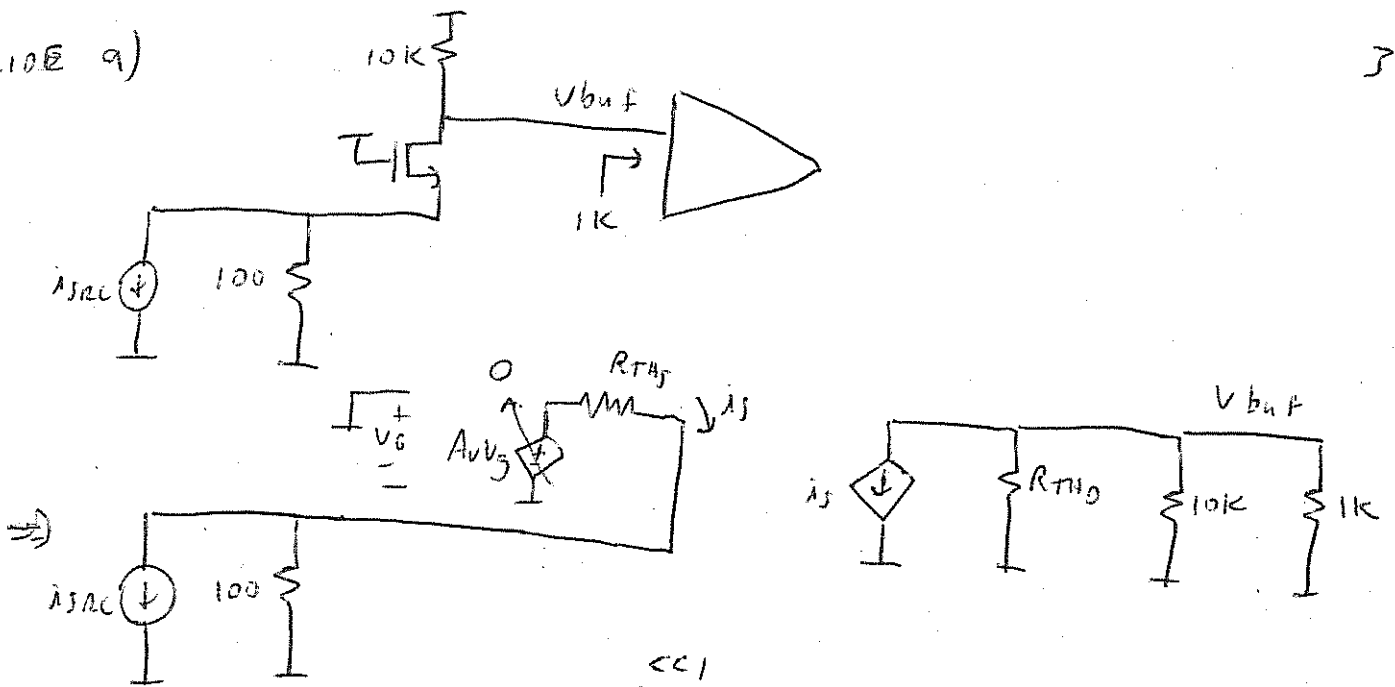

$$R_{TH_S} = \left(1 + \frac{R_D}{r_o}\right) \left(r_o \parallel \frac{1}{g_m + g_{\pi b}}\right) \approx \frac{1}{g_m} = 100$$

$$R_{TH_D} = r_o \left(1 + (g_m + g_{\pi b}) R_S\right) + R_S$$
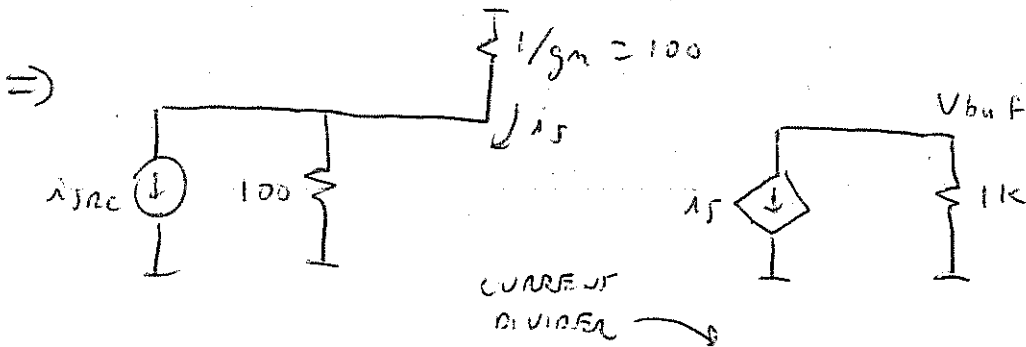
$$\approx \boxed{r_o(1 + 1/100 \cdot 100) = 2 \cdot r_o = 200 \text{ kOhms}}$$




$$V_{buf} \approx -\lambda_S 1k = -\lambda_{Src} \frac{100}{100+100} 1k = -\lambda_{Src} 500$$




⇒ TRANSIMPEDANCE GAIN IS INCREASED TO

-500 (NOTE THAT THE SIGN OF THE GAIN HAS ~~CHANGED~~ BUT IT STAYED THE SAME)

SLIDE 10)

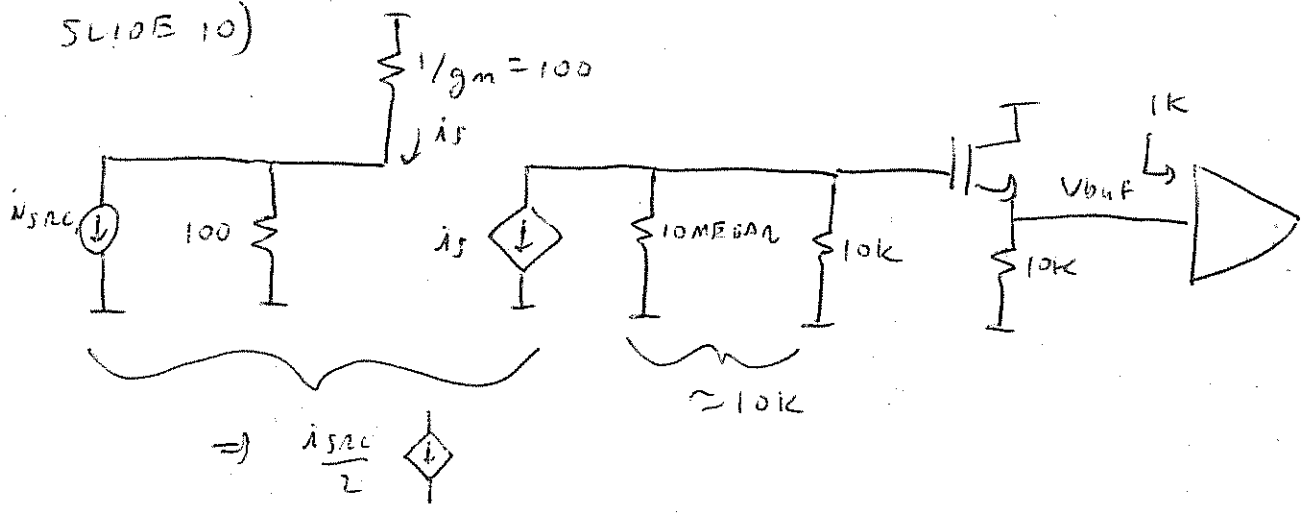

$\Rightarrow \frac{i_{src}}{2}$

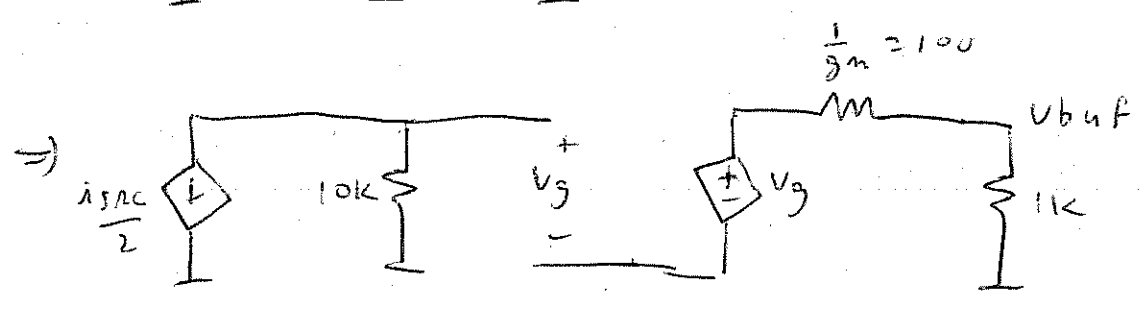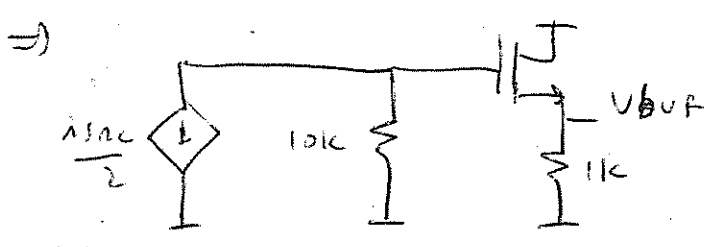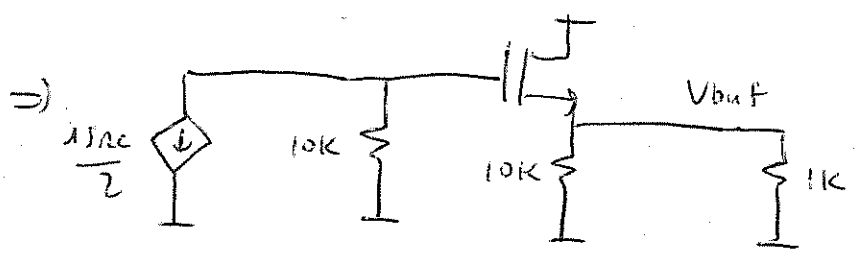


$\Rightarrow V_{buf} \approx \frac{1\text{k}}{1\text{k} + 100} V_0 \approx V_G = -\frac{i_{src}}{2} 10\text{k} = -5000 i_{src}$

$\Rightarrow$  TRANSIMPEDANCE GAIN IS NOW INCREASED TO -5000



$\Rightarrow$  THE SOURCE FOLLOWER PROVIDED AN EFFECTIVE INCREASE IN TRANSIMPEDANCE GAIN BY LOWERING ATTENUATION DUE TO LOW  $Z_{in}$

SLIDE 11)




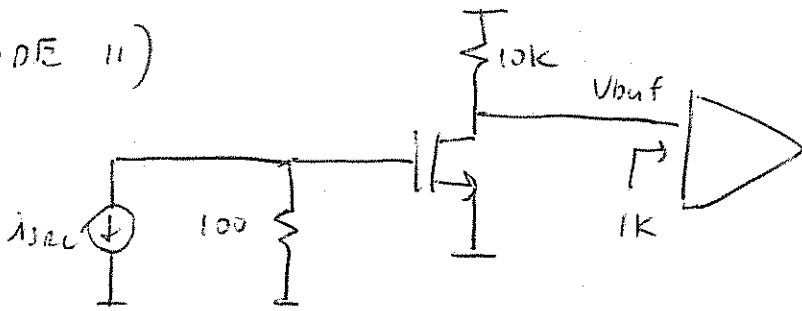


NOTE :  $1K \parallel 10K \approx 1K$

5

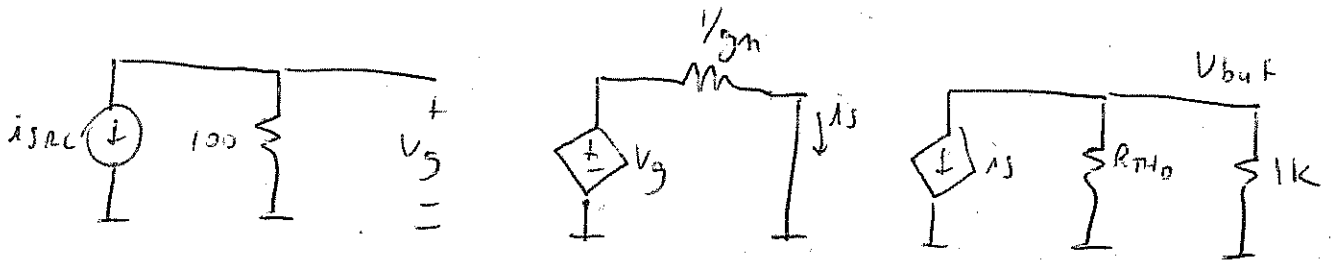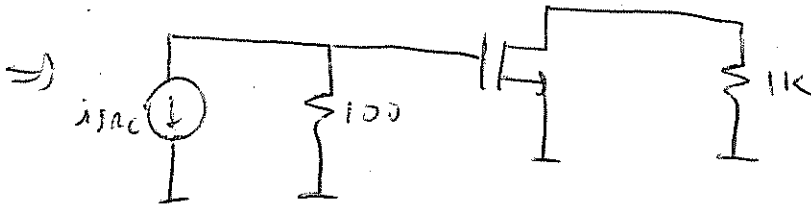
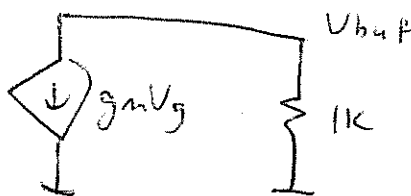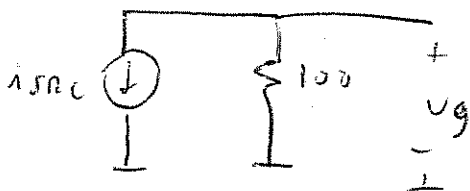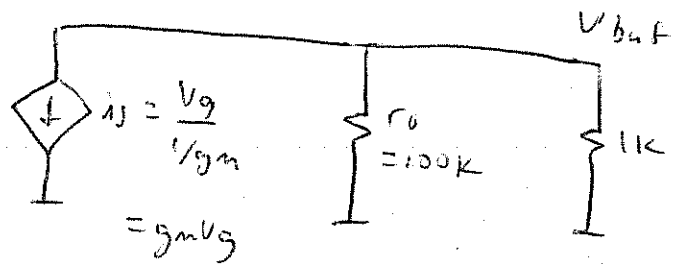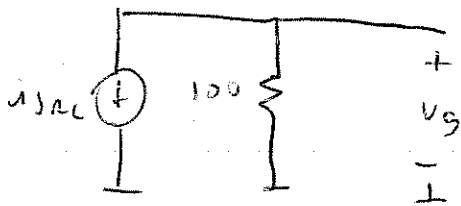
$$R_{TH} = r_o (1 + (g_m + g_{ds}) R_D) + R_D = r_o = 100K$$



$$\Rightarrow V_{buf} \approx -1K g_m V_g = -1K g_m (-i_{SRC} 100)$$

$$= 1K i_{SRC}$$

$\Rightarrow$  TRANSIMPEDANCE

GAIN  $\approx 1K$

(NOTE THAT THE SIGN OF THE GAIN IS FLIPPED COMPARED TO COMMON GATE)

6  
1) COMMON GATE + SOURCE FOLLOWER OFFER

BETTER GAIN THAN SINGLE COMMON SOURCE AMPLIFIER

2) TWO STAGE COMMON SOURCE AMPLIFIER COULD YIELD  
MUCH HIGHER GAIN THAN COMMON GATE + COMMON SOURCE

HOWEVER, THERE ARE MANY OTHER ISSUES IN DESIGNING  
THE AMPLIFIER ~~ON~~ BEYOND JUST GAIN, INCLUDING:

1) BANDWIDTH

2) NOISE

WE WILL DISCUSS THESE TWO ~~ISSUES~~ TOPICS (AND MORE)  
IN FUTURE LECTURES.