


Analysis and Design of Analog Integrated Circuits
Lecture 8

Cascode Techniques

Michael H. Perrott
February 15, 2012

Copyright © 2012 by Michael H. Perrott
All rights reserved.

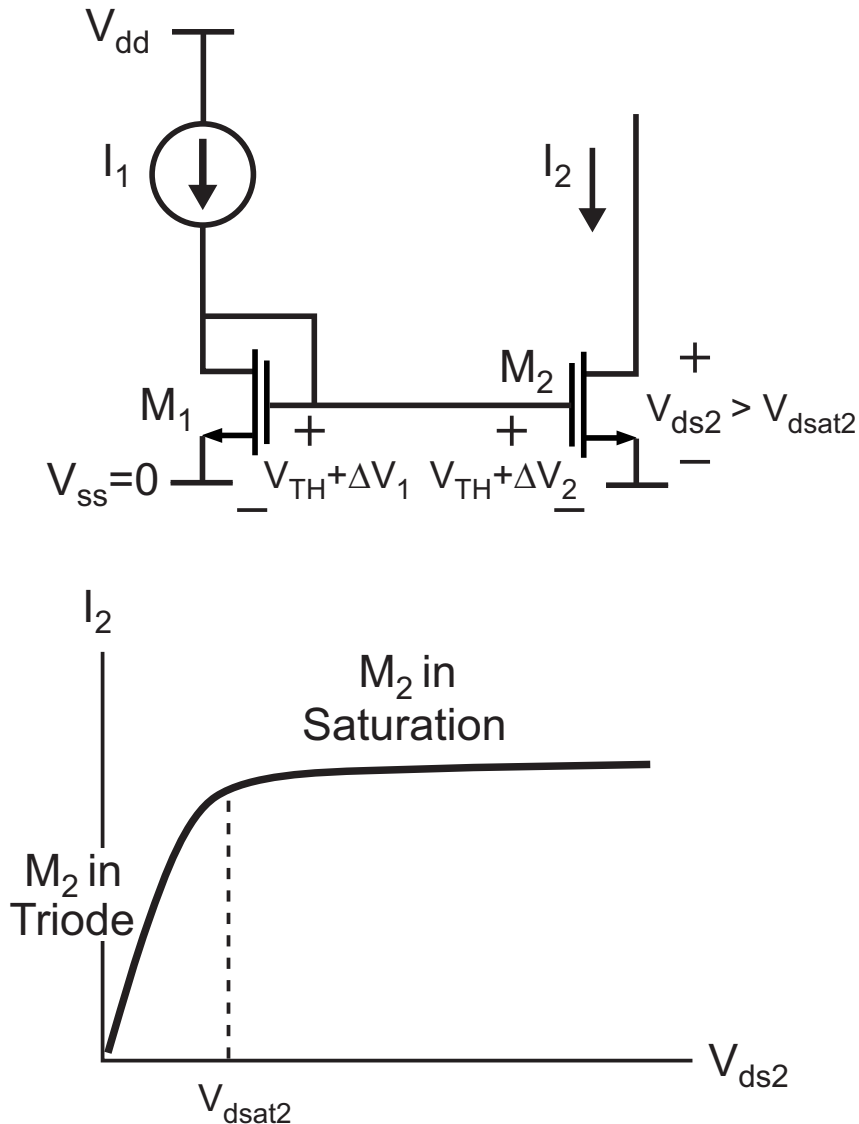Review of Large Signal Analysis of Current Mirrors




$$\frac{I_2}{I_1} = \frac{\frac{1}{2} \mu_n C_{ox} \frac{W_2}{L_2} \overbrace{(V_{GS2} - V_{TH})^2}^{\Delta V_2} (1 + \lambda_2 V_{ds2})}{\frac{1}{2} \mu_n C_{ox} \frac{W_1}{L_1} \underbrace{(V_{GS1} - V_{TH})^2}_{\Delta V_1} (1 + \lambda_1 V_{ds1})}$$

But, $V_{TH} + \Delta V_1 = V_{TH} + \Delta V_2 \Rightarrow \Delta V_1 = \Delta V_2$

$$\Rightarrow \frac{I_2}{I_1} = \underbrace{\frac{W_2}{W_1}}_{\text{Current setting based on geometry}} \underbrace{\frac{L_1}{L_2}}_{\text{Mismatch due to } V_{ds} \text{ difference}}$$

Note: for accurate ratio, set $L_1 = L_2$

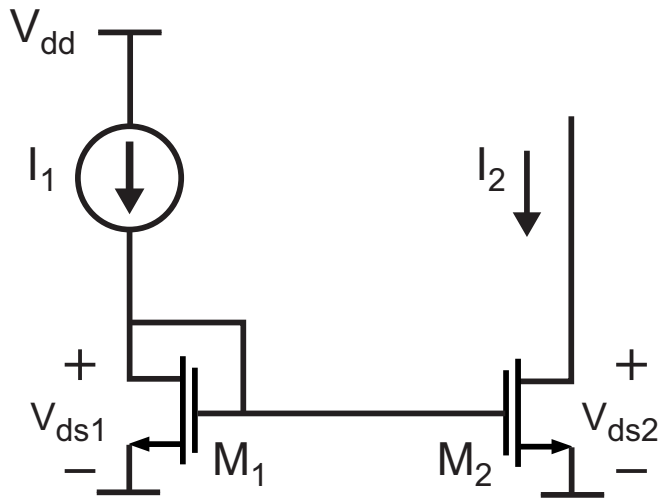The Issue of V_{ds} Mismatch in Current Mirrors




$$\frac{I_2}{I_1} = \frac{W_2}{W_1} \frac{(1 + \lambda_2 V_{ds2})}{(1 + \lambda_1 V_{ds1})}$$

Current setting based on geometry Mismatch due to V_{ds} difference

Note: we are assuming $L_1 = L_2$

- **Issue: Current I_2 can vary significantly as a function of the drain voltage of M_2**
 - We often want a tightly controlled current set only by I_1 and transistor sizes
- **How do we improve the current mirror matching performance?**

Cascode Current Source

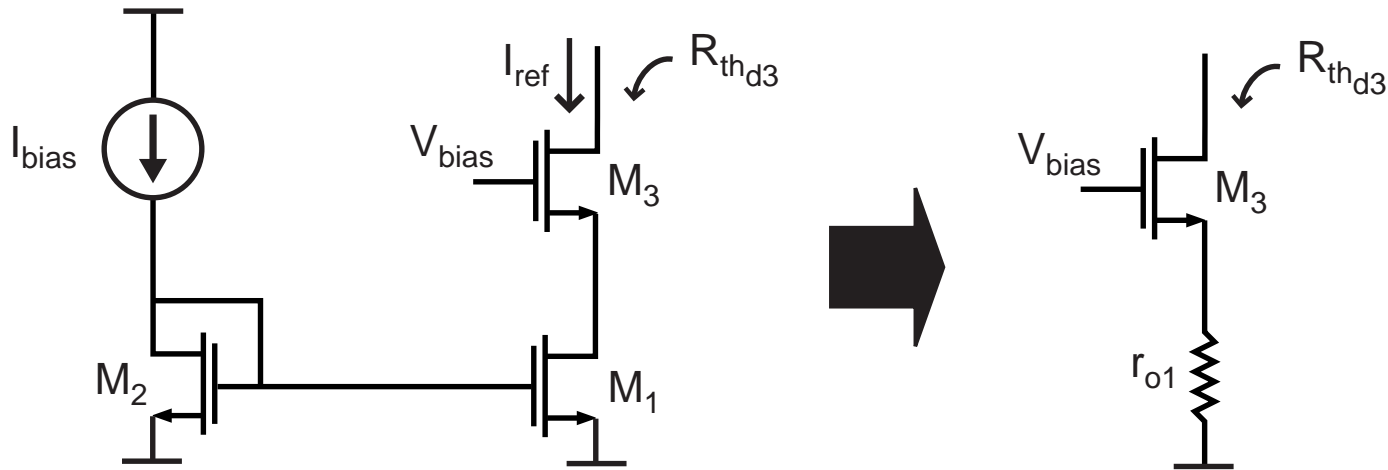


- Offers increased output resistance

- Reduces *small signal* dependence of output current on the output voltage of the current source
- From Lecture 6, we derived:

$$R_{thd3} \approx r_{o3}(1 + g_{m3}R_{thd1}) = r_{o3}(1 + g_{m3}r_{o1}) \approx (g_{m3}r_{o3})r_{o1}$$


- Output resistance boosted by intrinsic gain of M_3 , $g_{m3}r_{o3}$
- But how do we reduce the influence of *large signal* V_{ds} mismatch between M_1 and M_2 ?

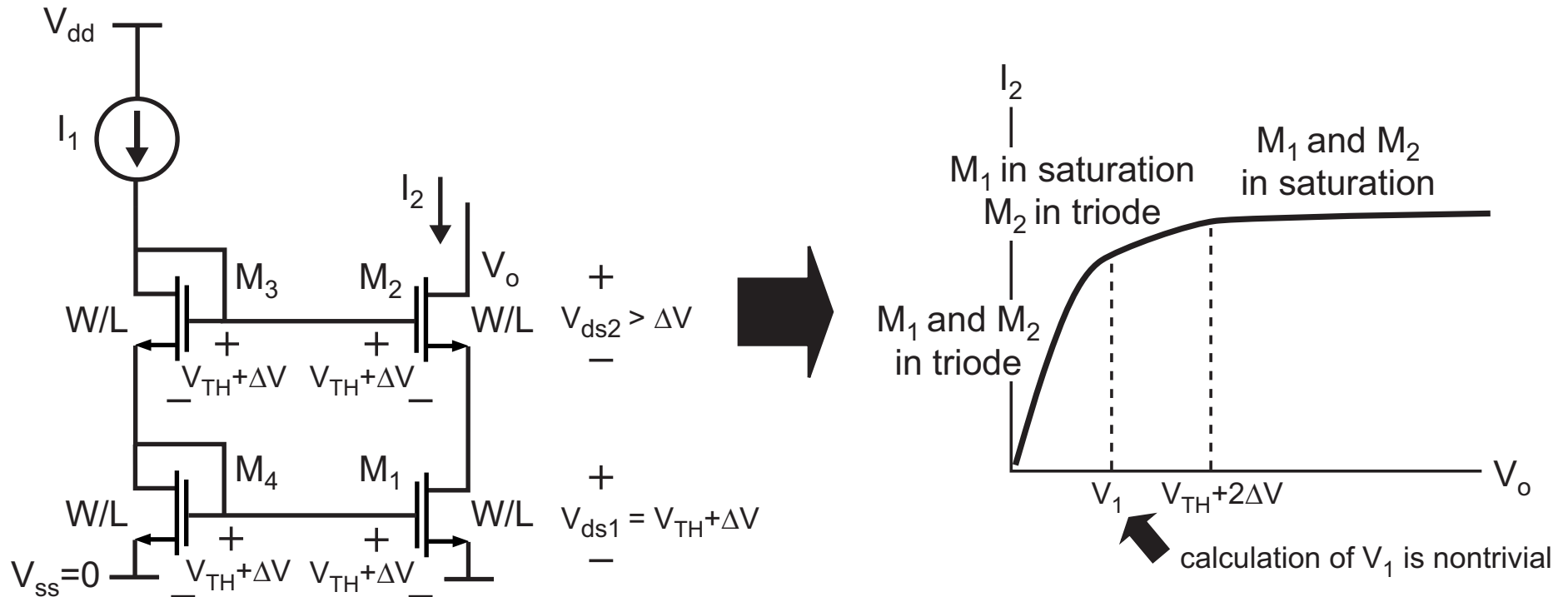The Drawback of Basic Cascode Bias Approach



- **Output voltage range is reduced**
 - Now V_o must be $> V_{TH} + 2\Delta V$
 - What will happen to the output impedance of the current source if the output voltage is too low?
 - Can we improve the voltage range?


Improved Swing Cascode

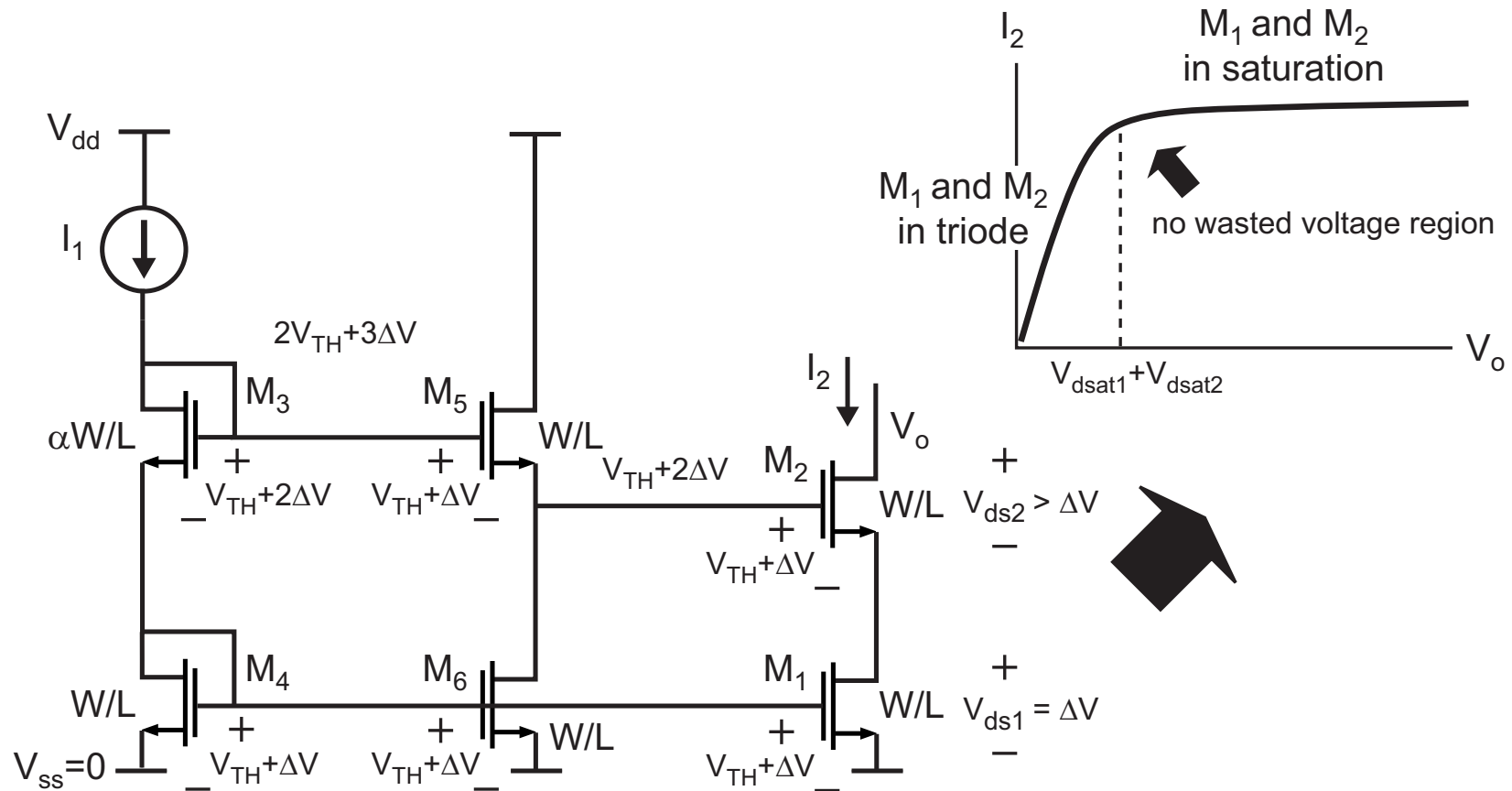

- **Key idea: set size of M_3 such that $V_{ds1} = \Delta V$**
 - Assuming strong inversion for M_1 and M_3 :


$$\Delta V = \sqrt{\frac{2I_d L}{\mu_n C_{ox} W}} \Rightarrow \alpha = \frac{1}{4}$$

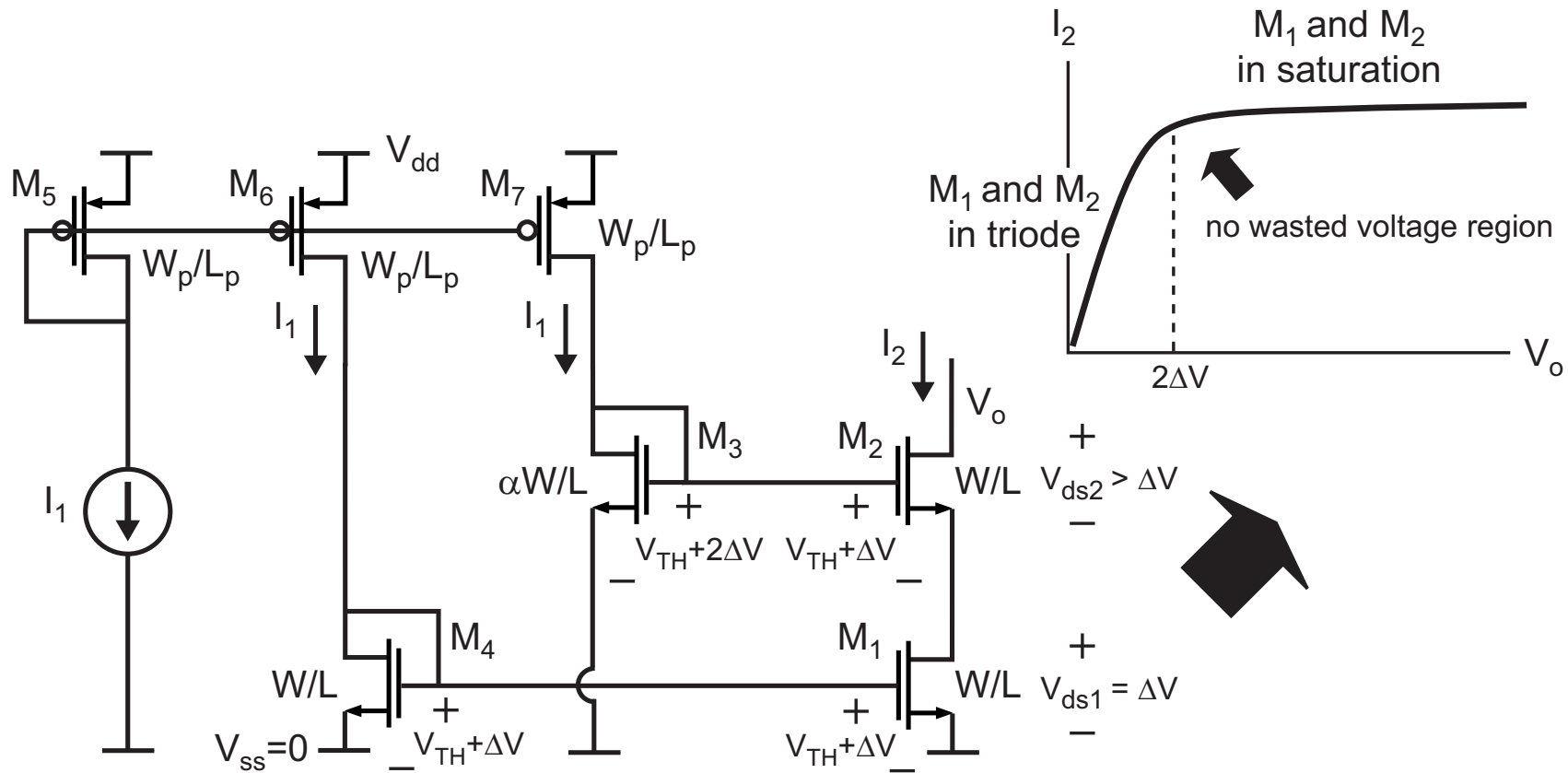Alternative Implementation of Improved Swing Cascode




- Set α as on previous slide
- Note: both implementations share a common problem

The Issue of Current Mismatch

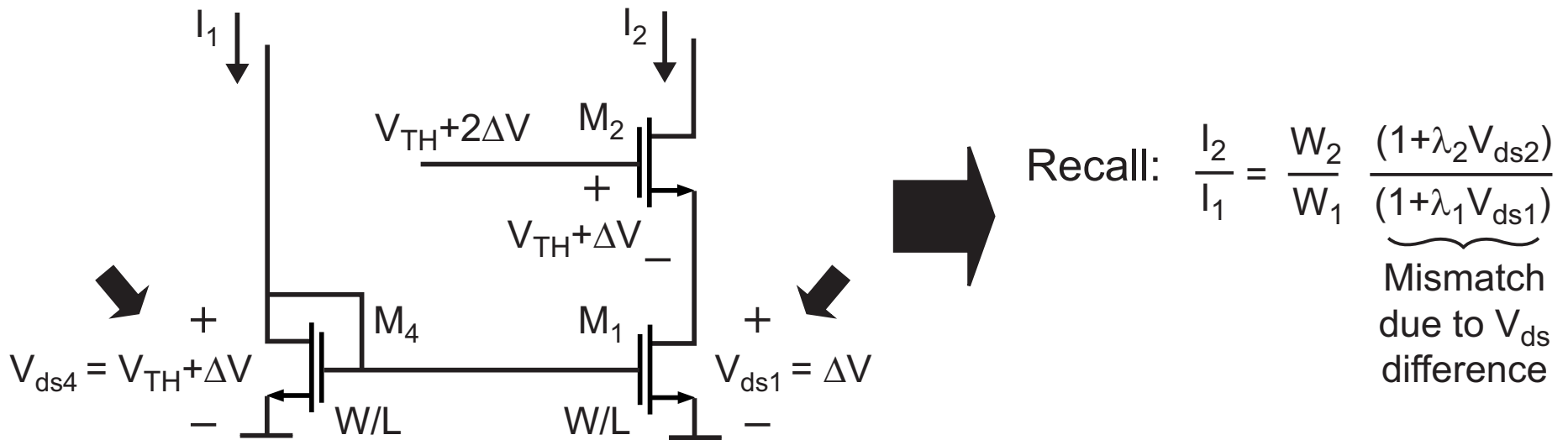


- The improved swing approach causes a systematic mismatch between I_2 and I_1
 - Key issue: $V_{ds1} \neq V_{ds4}$
- Can we fix this problem?

Techniques to Reduce Current Mismatch

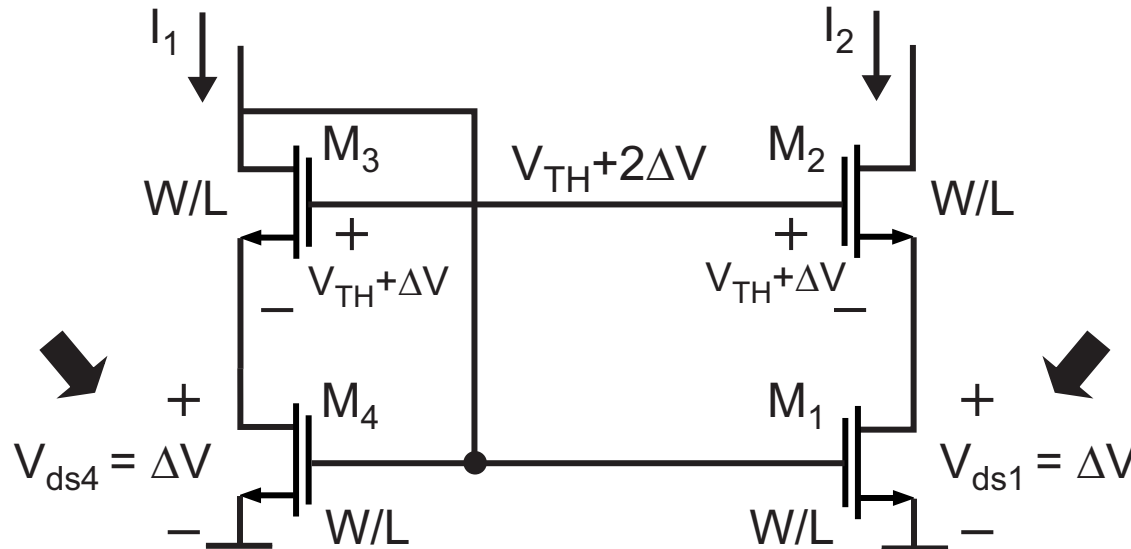


- **Systematic mismatch between I_1 and I_2 is greatly reduced by using the above circuit (now $V_{ds1} \approx V_{ds4}$)**
 - Note that gate bias on M_2 and M_3 may be provided by previously discussed circuits
- **Additional techniques for accurately matching I_1 and I_2**
 - Set $L_1 = L_4 \gg L_{min}$
 - Note: set $L_2 = L_3 \approx L_{min}$ for lower area and capacitance
 - Set $W_2/W_3 = I_2/I_1$ so that $\Delta V_2 = \Delta V_3$

Another Common Cascode Bias Topology

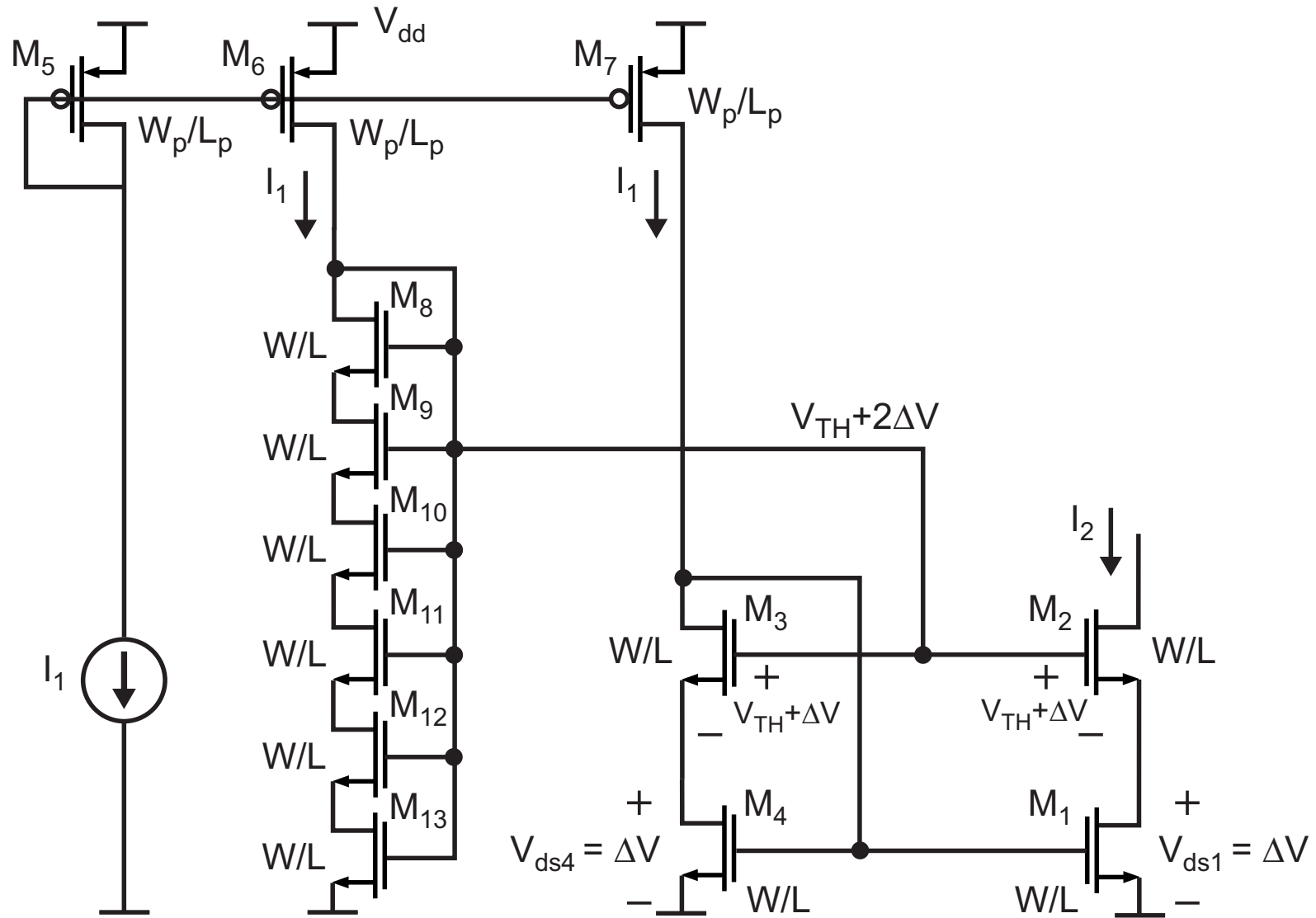

- Key issue: needs two bias current branches

Wilson Current Mirror

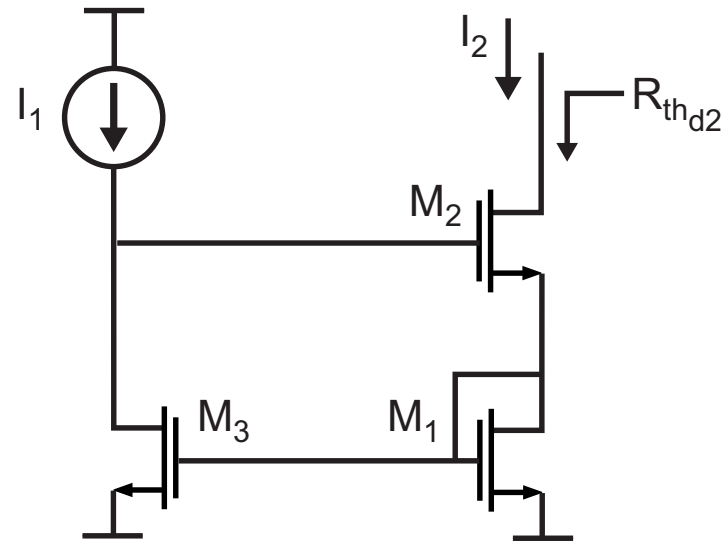


- Relies on feedback in its operation
- Using Hybrid- π analysis

$$R_{thd2} \approx \frac{1}{g_{m1}} (g_{m2} r_{o2}) (g_{m3} r_{o3})$$

- Output resistance comparable to cascode current source
- This circuit is rarely used these days


Enhanced Cascode Current Source

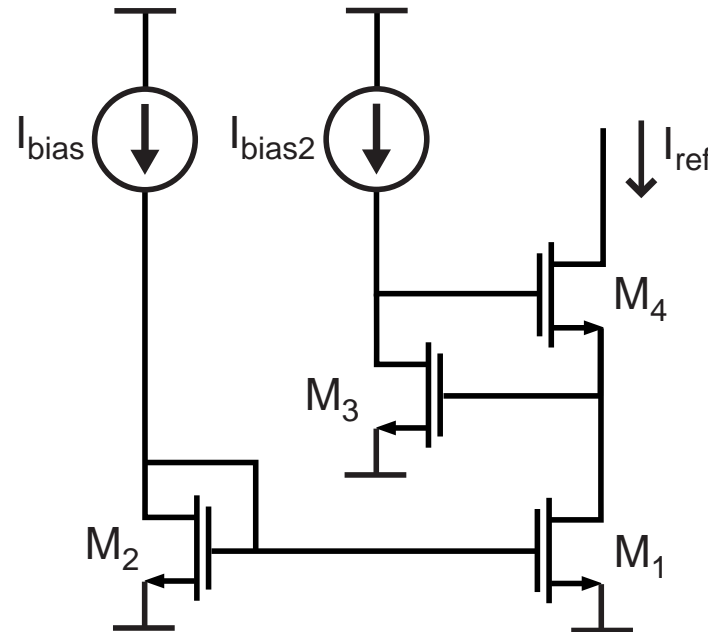

- Offers output resistance comparable to double cascode current source
- As with Wilson mirror, analysis is tricky due to source/gate coupling
 - Using results shown in the following slide:

$$R_{th_{d4}} \approx (g_{m4}r_{o4})(g_{m3}r_{o3})r_{o1}$$

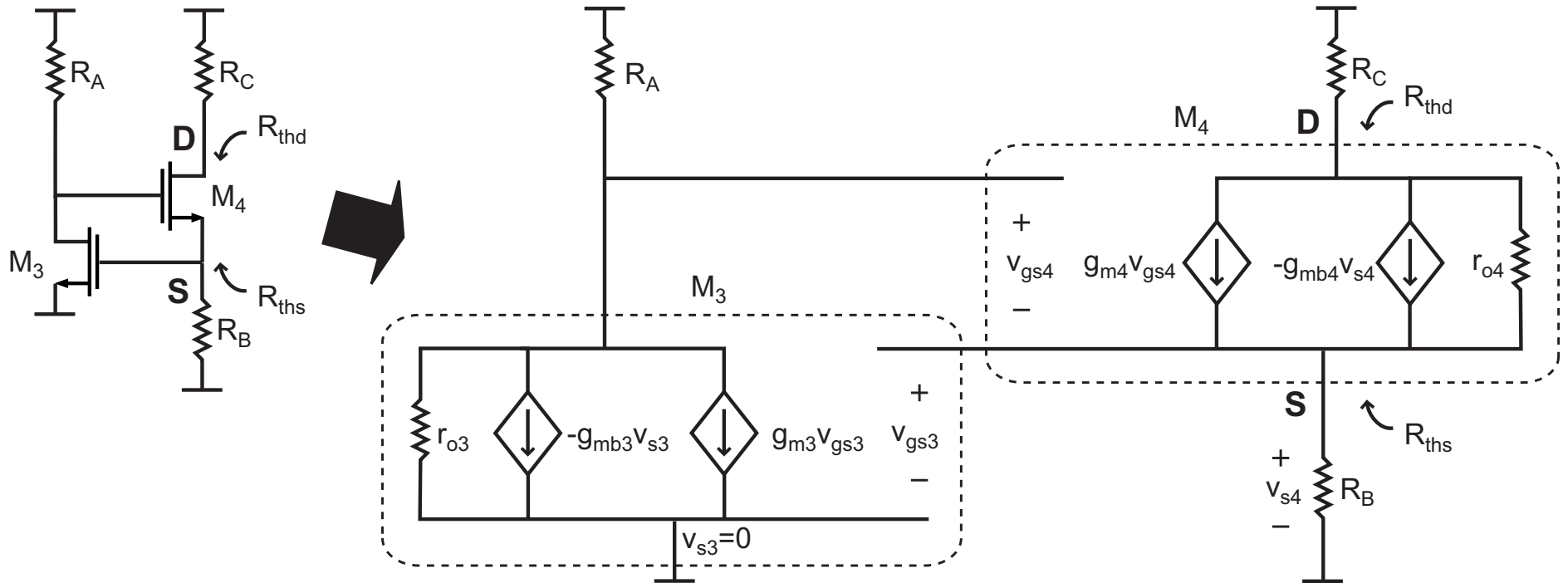Thevenin Resistances for CMOS Transistor Feedback Pair




$$R_{thd} = r_{o4}(1 + (g_{m4}(1 + g_{m3}(R_A || r_{o3})) + 1/r_{o4} + g_{mb4})R_B)$$

$$\approx (g_{m4}r_{o4})(g_{m3}(r_{o3} || R_A))R_B$$

$$R_{ths} = \left(1 + \frac{R_C}{r_{o4}}\right) \left(\frac{1}{g_{mb4}} || r_{o4} || \frac{1}{g_{m4}(1 + g_{m3}(r_{o3} || R_A))}\right)$$


$$\approx \left(1 + \frac{R_C}{r_{o4}}\right) \frac{1}{g_{m4}(g_{m3}(r_{o3} || R_A))}$$

Basic Cascode Amplifier

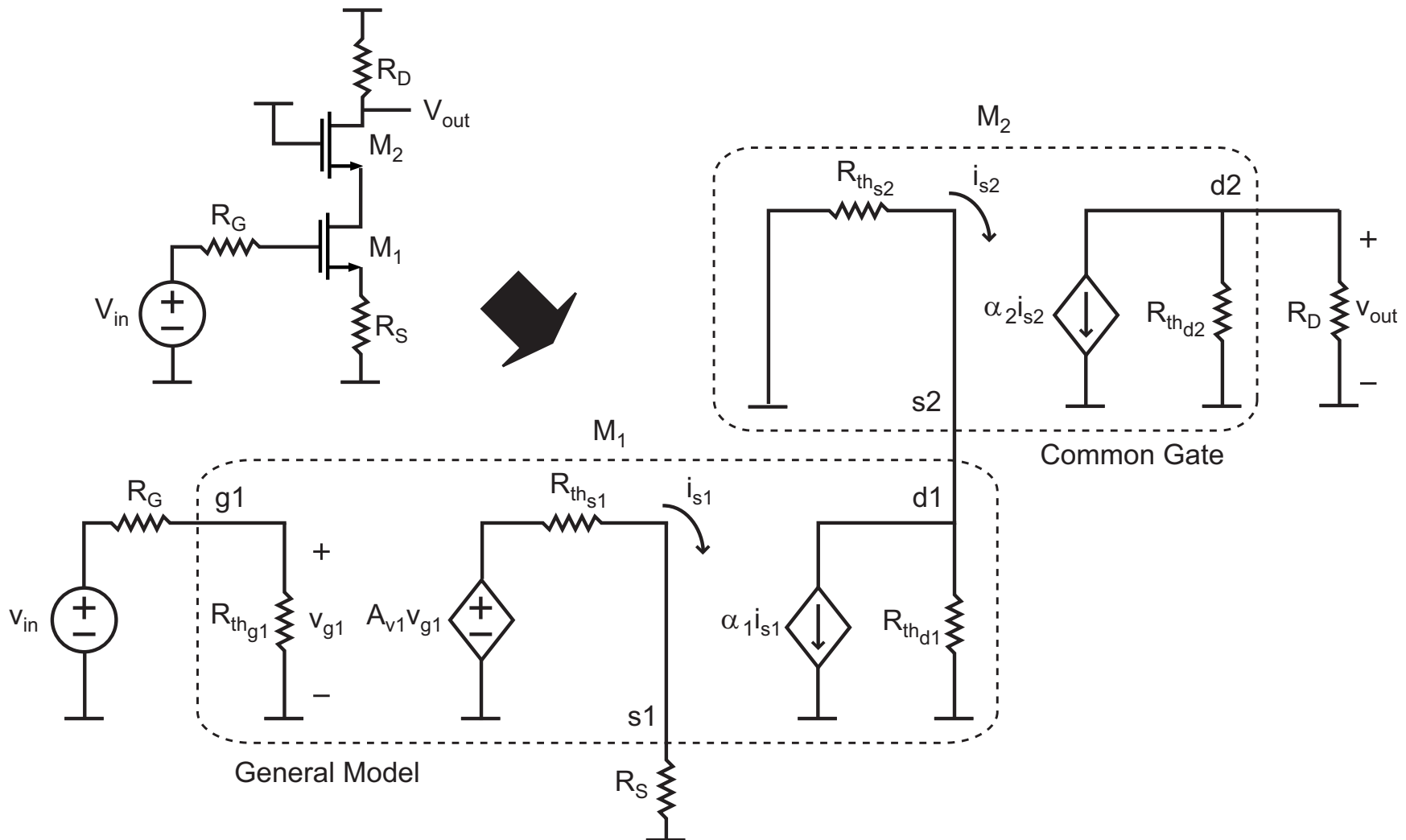

- Allows improved frequency response (discussed later)
- Reduction to two-port will be done in several steps


Eliminate Middle Sections

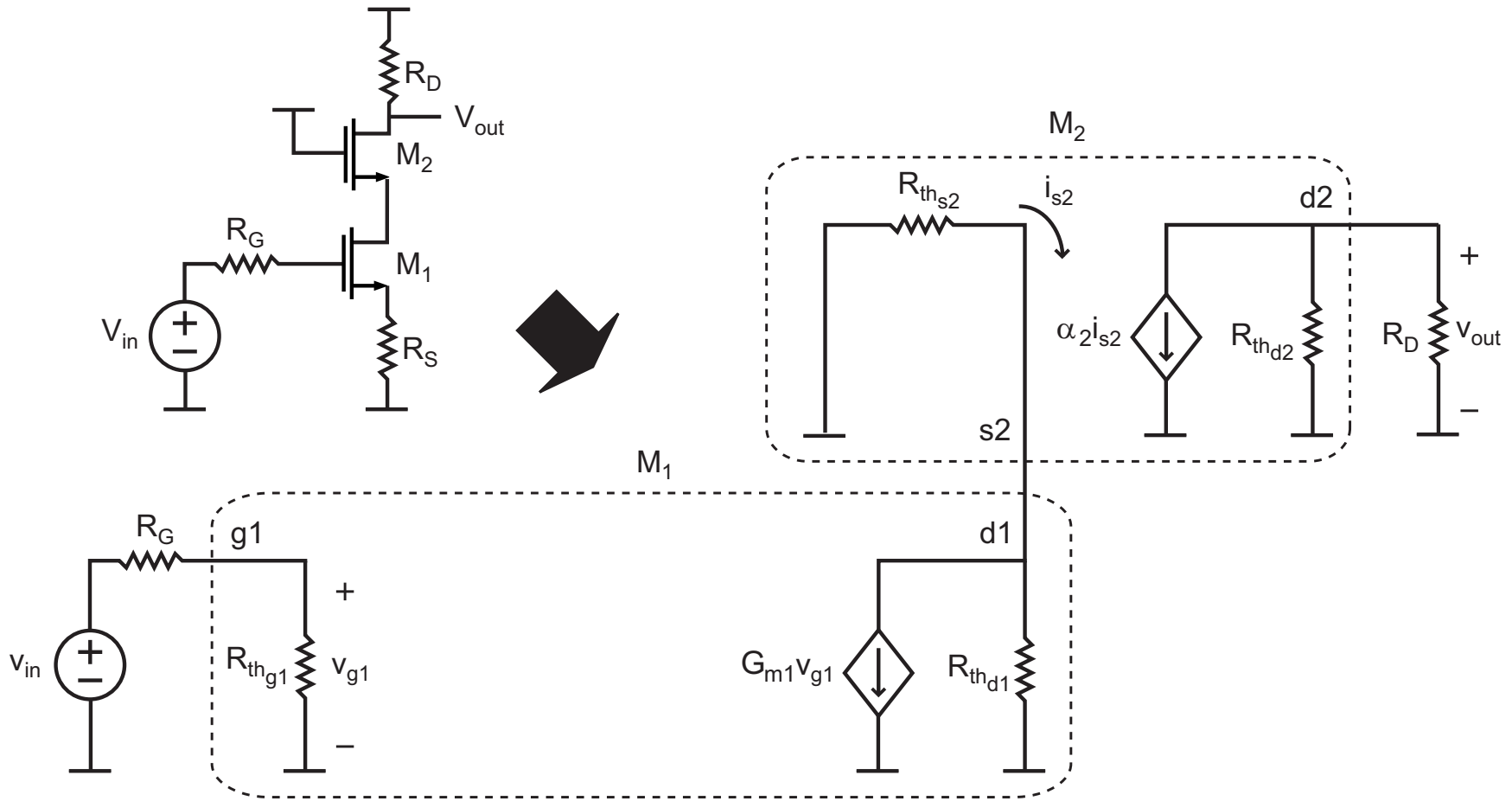

- Calculation of G_{m1} same as for common source amp
- To reduce further, note that

$$R_{thd1} \gg R_{ths2} \Rightarrow \alpha_2 i_{s2} = i_{s2} \approx G_{m1} v_{g1}$$

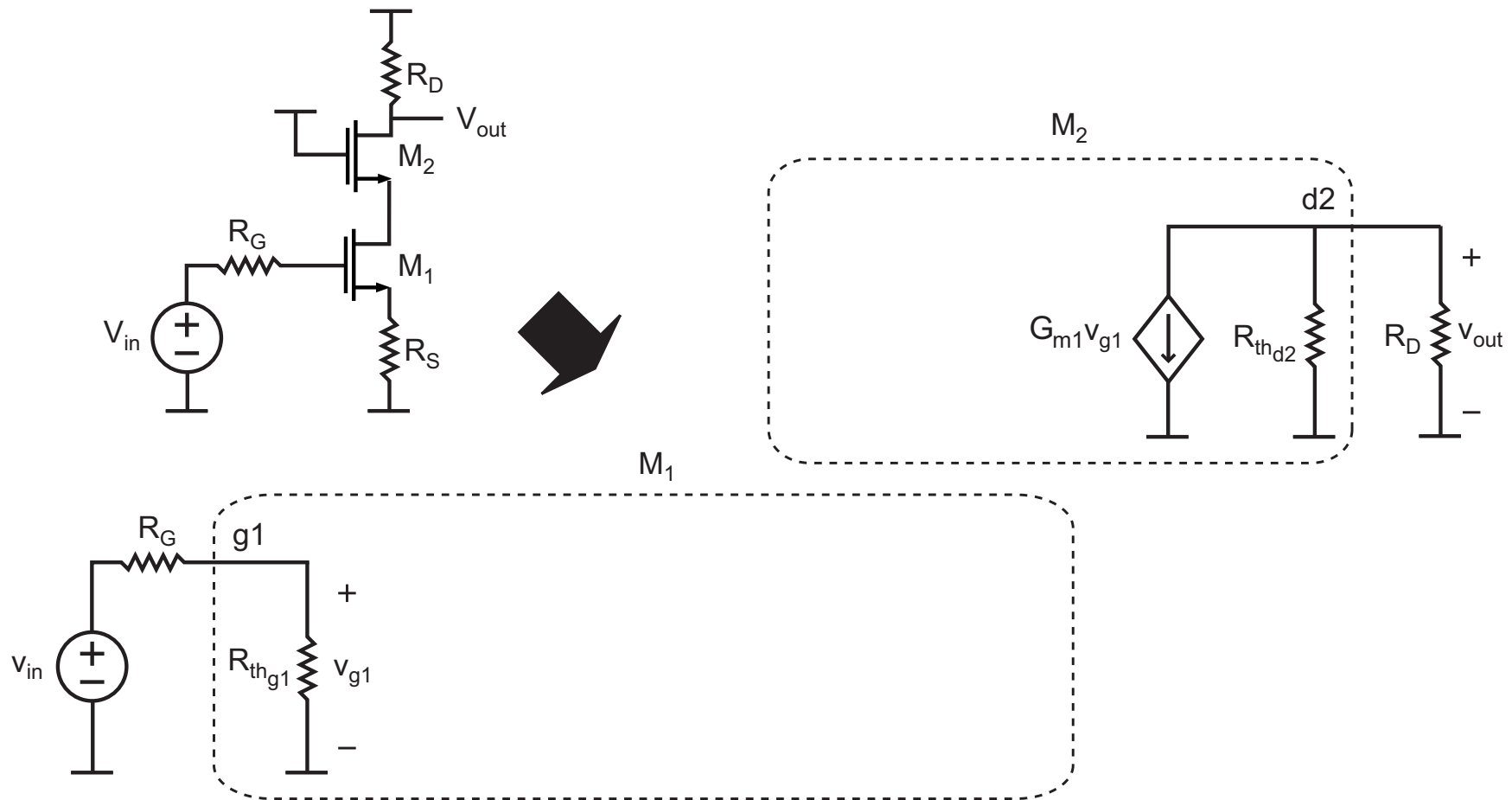Resulting Two-Port Similar to Common Source Amp




- **Key difference: drain impedance much larger**

$$R_{thd2} \approx r_{o2}(1 + g_{m2}R_{thd1}) \approx r_{o2}(1 + g_{m2}r_{o1}(1 + g_{m1}R_S))$$

$$\approx (g_{m2}r_{o2})(g_{m1}r_{o1})R_S$$

Constraints on V_{bias} and Output Range

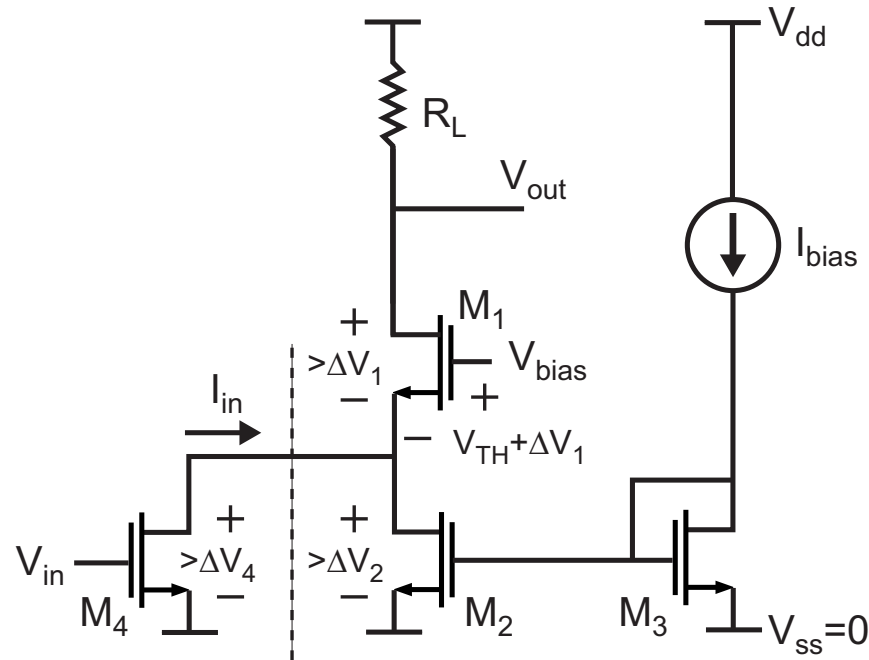

- To keep M_2 and M_4 in saturation

$$V_{bias} - (V_{TH} + \Delta V_1) > \max(\Delta V_2, \Delta V_4)$$


$$\Rightarrow V_{bias} > V_{TH} + \Delta V_1 + \max(\Delta V_2, \Delta V_4)$$

- To keep M_1 in saturation

$$V_{out} - (V_{bias} - (V_{TH} + \Delta V_1)) > \Delta V_1$$

$$\Rightarrow V_{out} > V_{bias} - V_{TH}$$

Calculation of Maximum Output Range

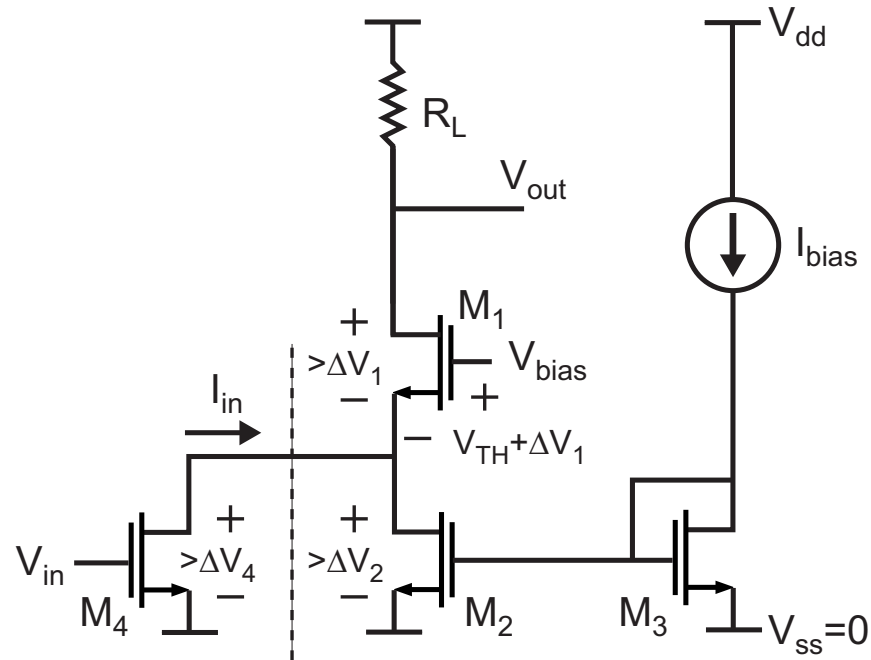

- Minimum V_{bias} allows the maximum output range


$$\Rightarrow V_{bias} = V_{TH} + \Delta V_1 + \max(\Delta V_2, \Delta V_4)$$

- Resulting output range

$$V_{bias} - V_{TH} < V_{out} < V_{dd}$$


$$\Delta V_1 + \max(\Delta V_2, \Delta V_4) < V_{out} < V_{dd}$$

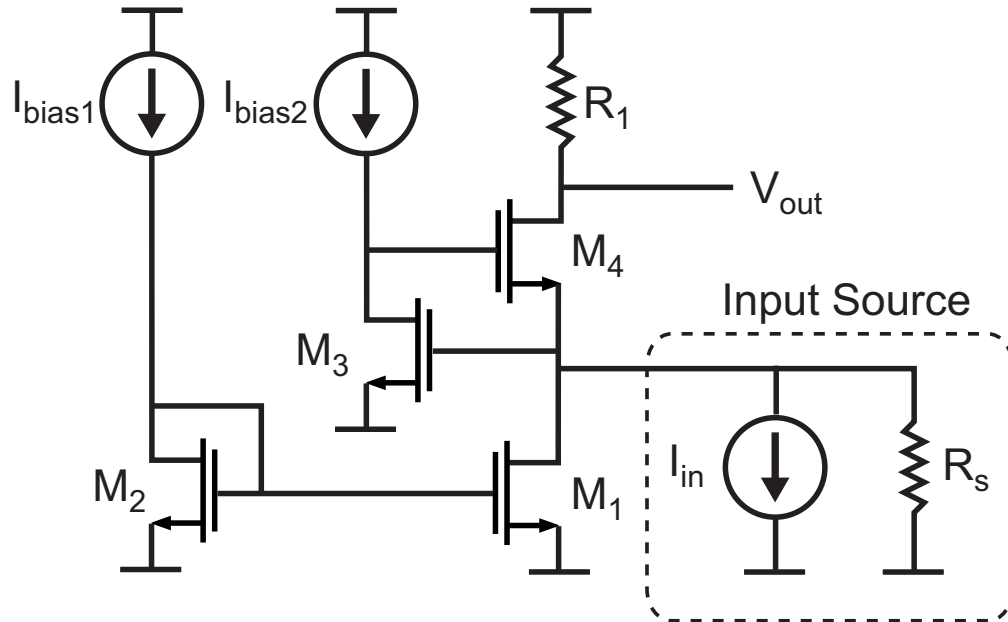Variation on a Theme: Enhanced Cascode Amplifiers



- We can turn the enhanced cascode current source into an amplifier
 - Inject a current input at the source of M_4
- Key aspects of small signal analysis can be done using Thevenin method
 - Simply leverage Thevenin resistance formulas shown on Slide 16

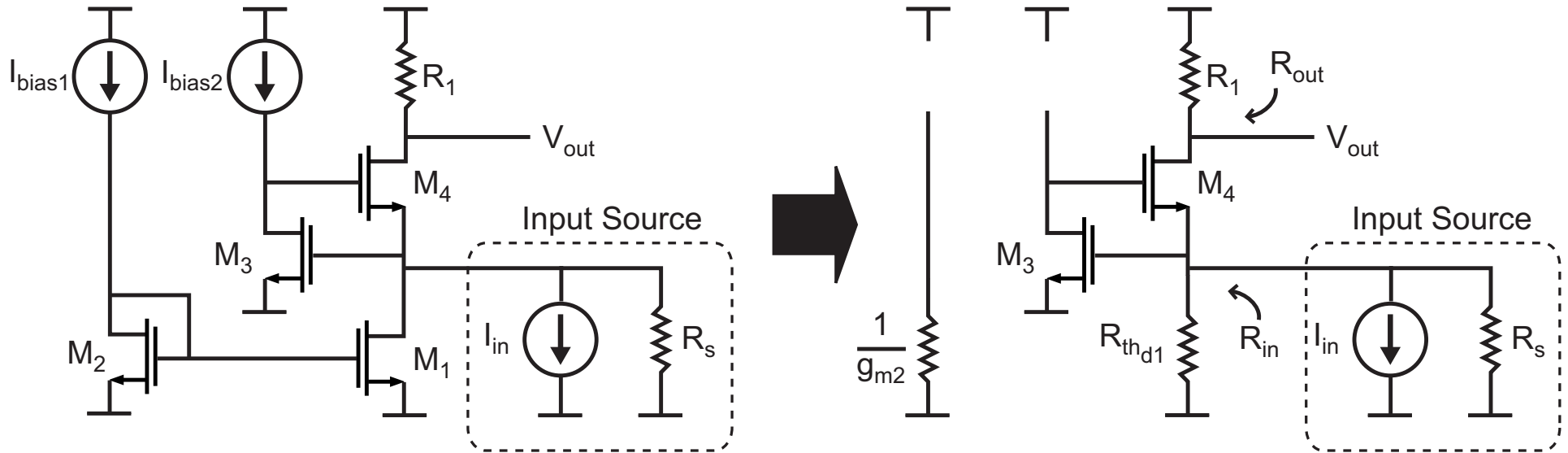Small-Signal Analysis of Enhanced Cascode Amp



- From Thevenin resistance calculations on Slide 16:

- Input impedance is quite low

$$R_{in} \approx R_{thd1} \parallel \left(1 + \frac{R_1}{r_{o4}} \right) \frac{1}{g_{m4}(g_{m3}r_{o3})} \approx \frac{1}{g_{m4}(g_{m3}r_{o3})}$$

- Output impedance is probably determined by R_1

$$R_{out} \approx R_1 \parallel (g_{m4}r_{o4})(g_{m3}r_{o3})(R_{thd1} \parallel R_s) \approx R_1$$

- This amplifier is useful for extracting a current signal while keeping the source voltage nearly constant