

***Fast and Accurate System Level
Simulation of Time-Based Circuits
Using CppSim and VppSim***


Michael H. Perrott

March 12, 2016

Copyright © 2016 by Michael H. Perrott

All rights reserved.

Modern Mixed Signal Circuit Design

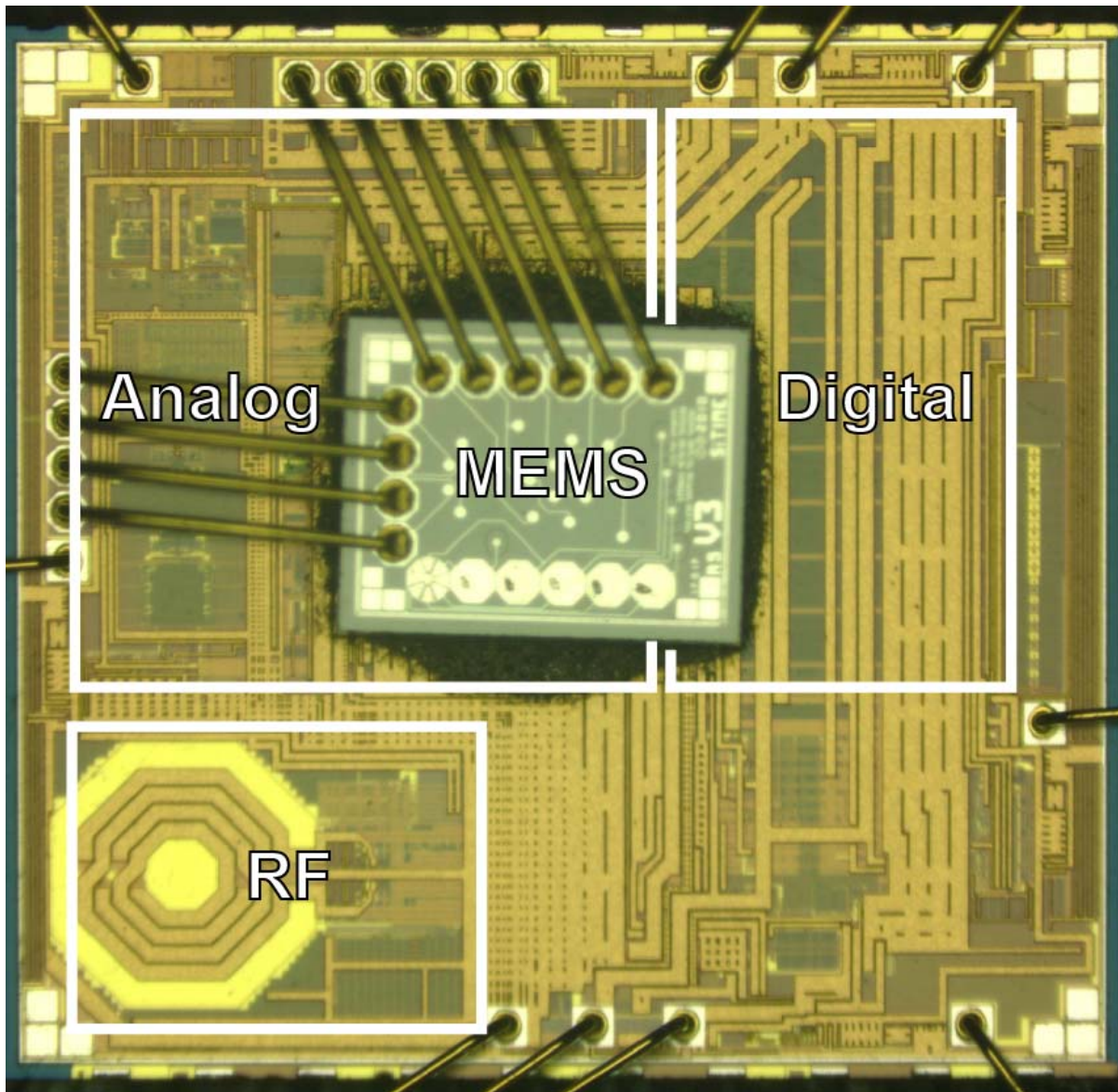


A Programmable MEMS Oscillator


- *Analog*
Temperature sensor, ADC, oscillator sustaining circuit
- *Digital*
signal processing
- *RF*
clocking (2.5 GHz)
- *MEMS*
high Q resonator

System level design is critical

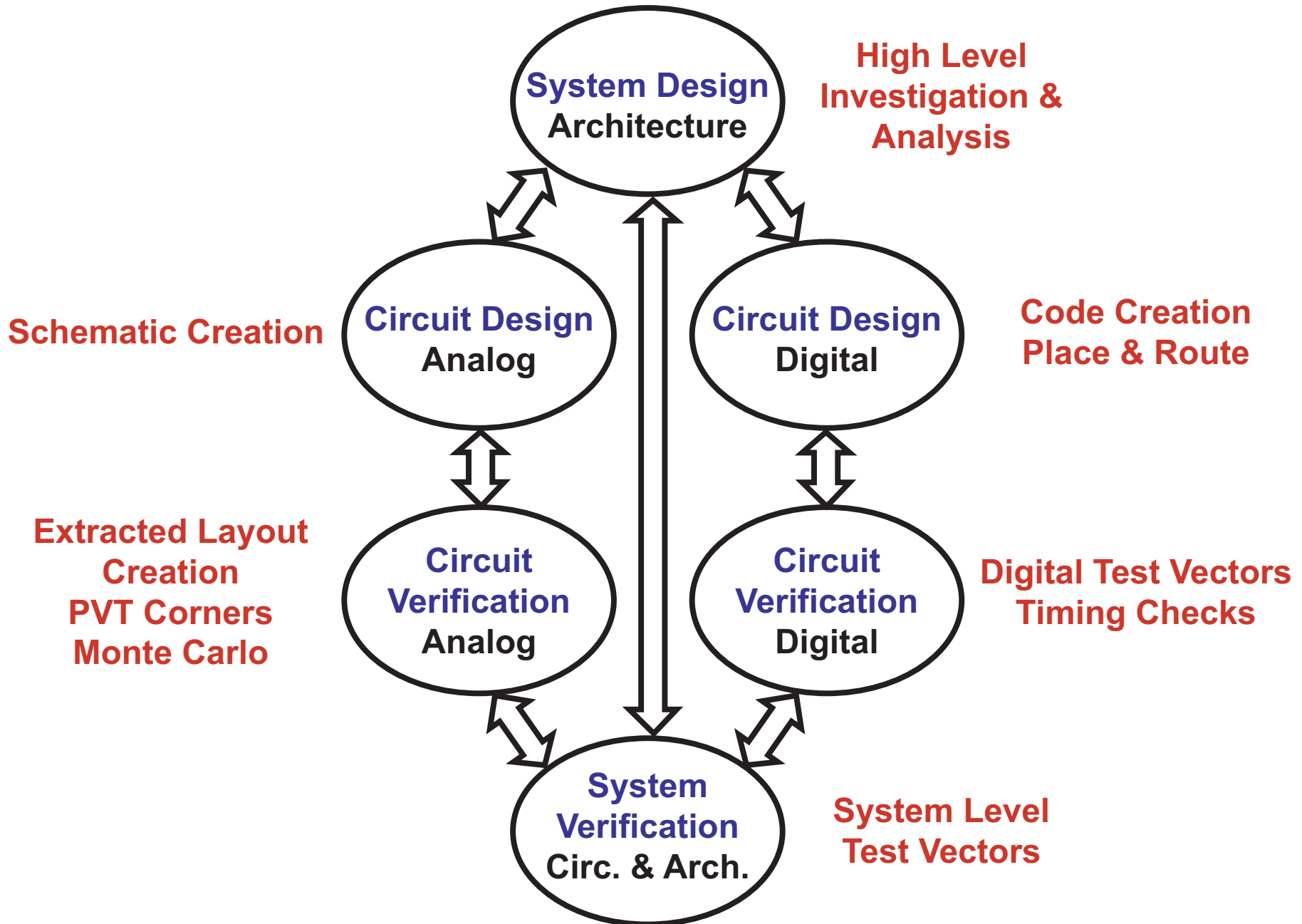Consider a Top Down, Mixed-Signal Design Flow




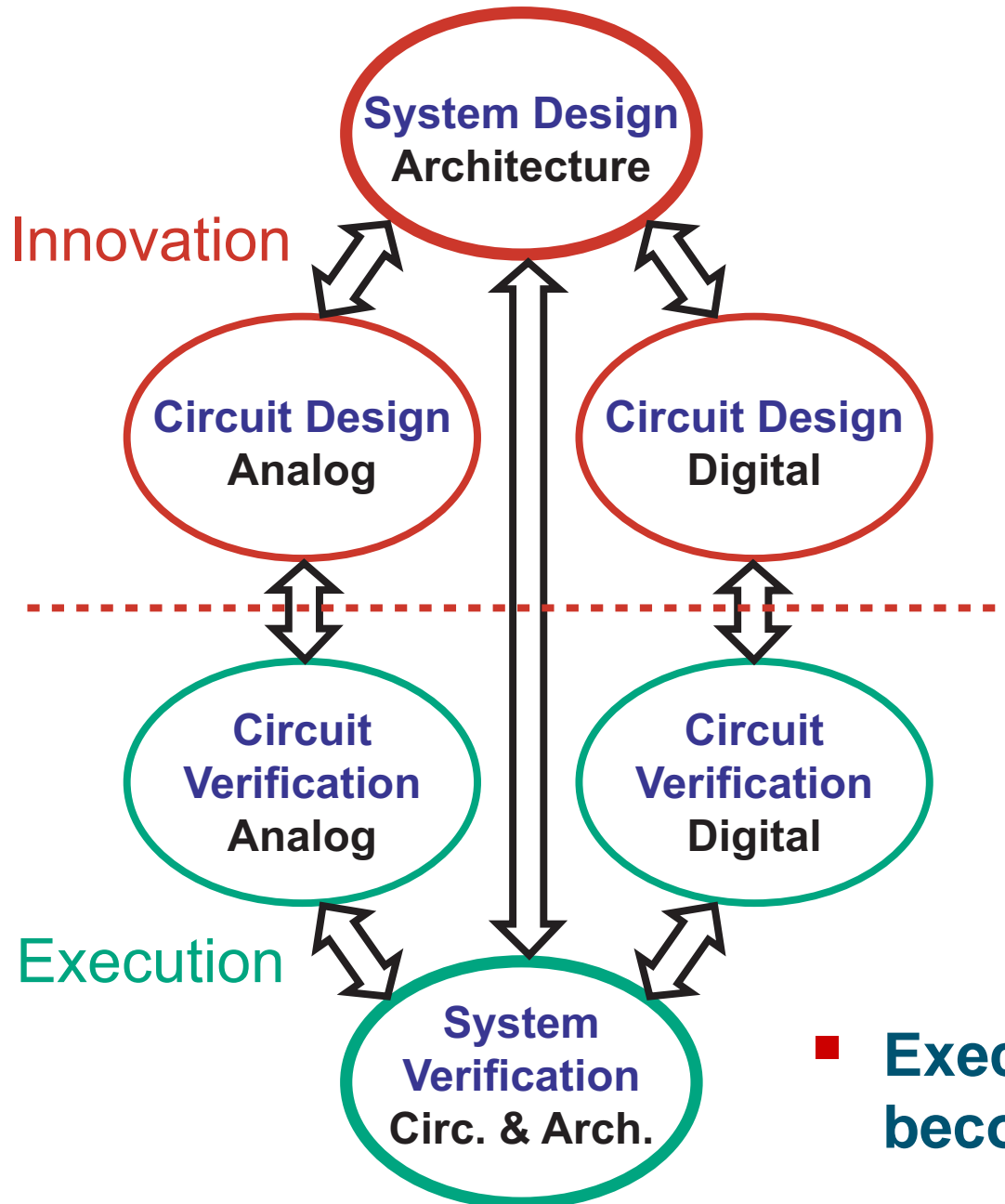
Good Execution Is Certainly A Key to Success



- Execution often becomes key focus

New Circuit Architectures Require Innovation


CppSim

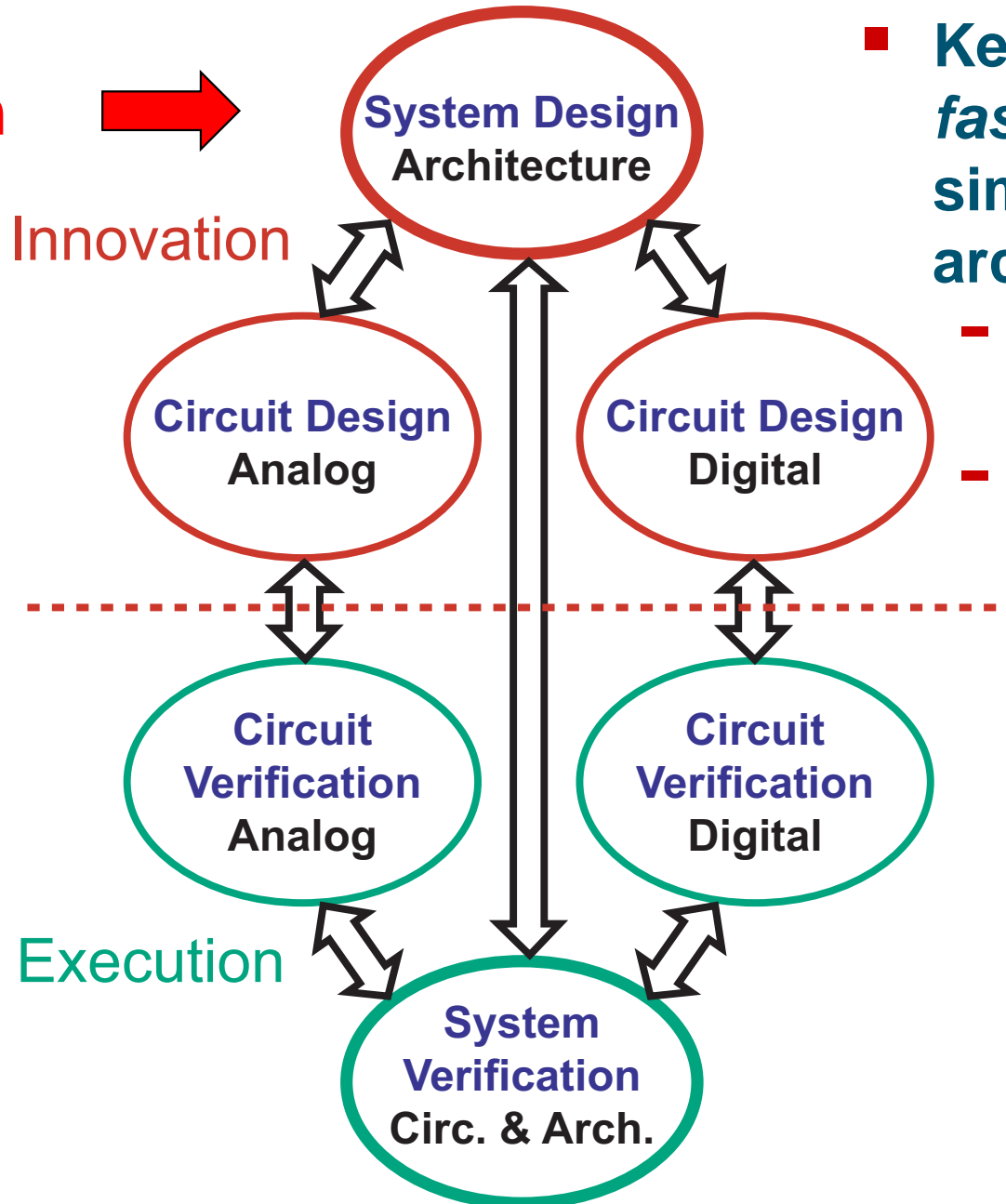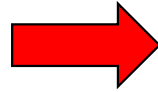

■ Key to innovation is *fast and detailed* simulation of new architectures

- Allows evaluation of *many* new ideas
- Pinpoints key problem areas

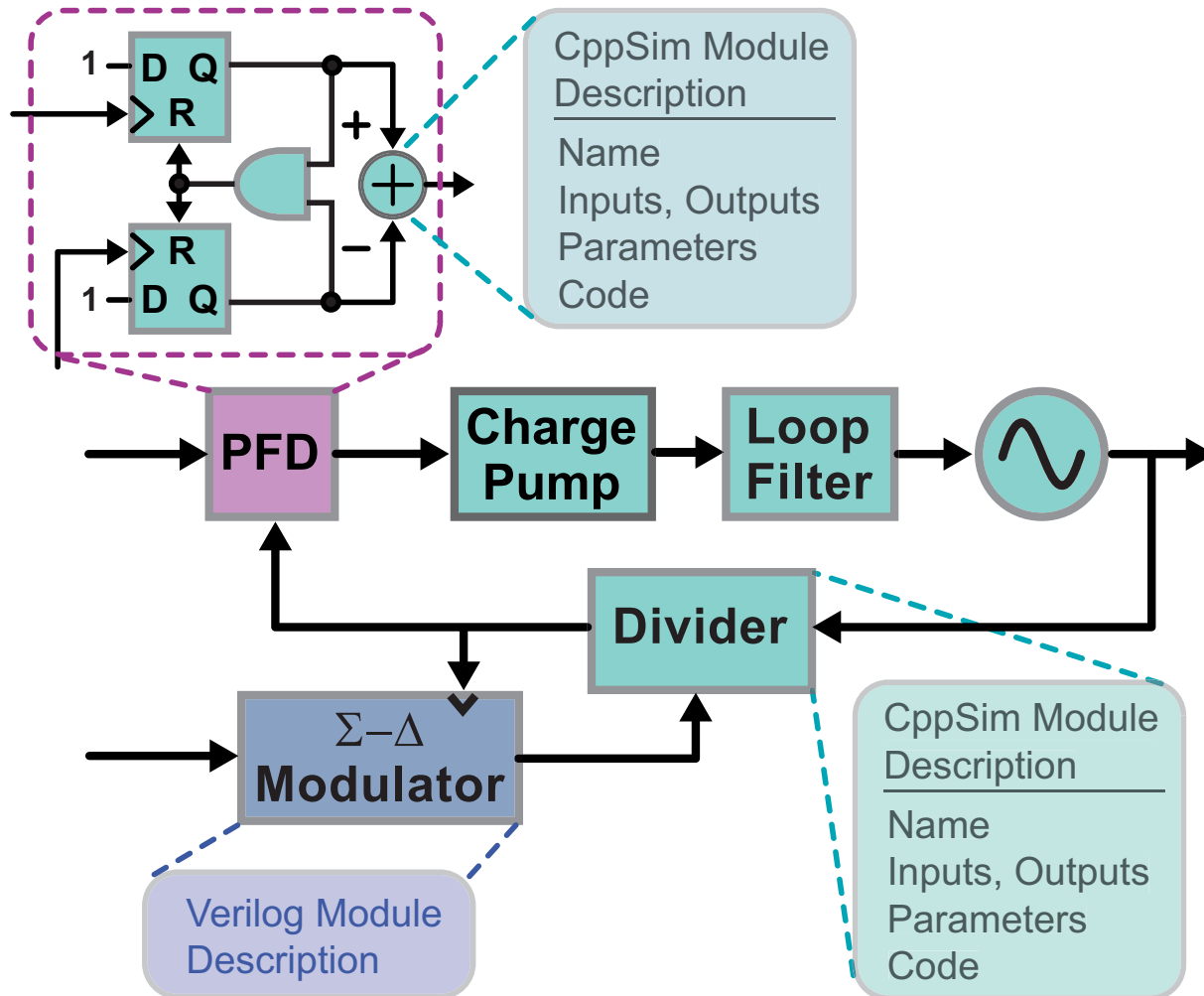
Schematic Based Simulation using CppSim/VppSim




- **Schematic**
 - Provides hierarchical description of system topology
- **Code blocks**
 - Specify module behavior using templated C++ code or Verilog code

- **Designers graphically develop system based on a library of C++/Verilog symbols and code**
 - Easy to create new symbols with accompanying code

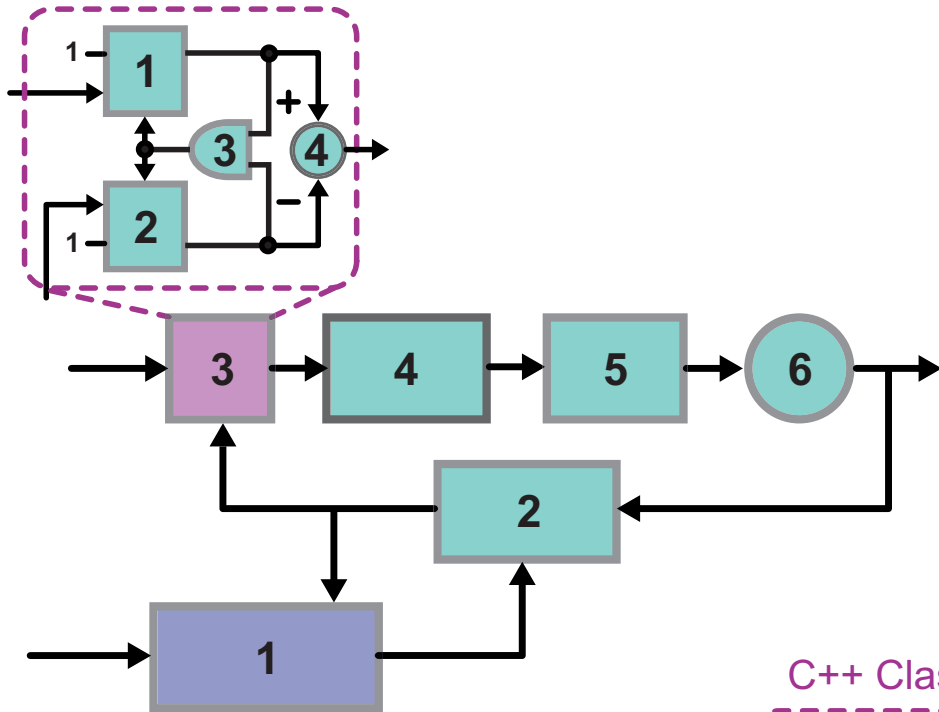CppSim Assembles C++ Classes into Overall Sim Code







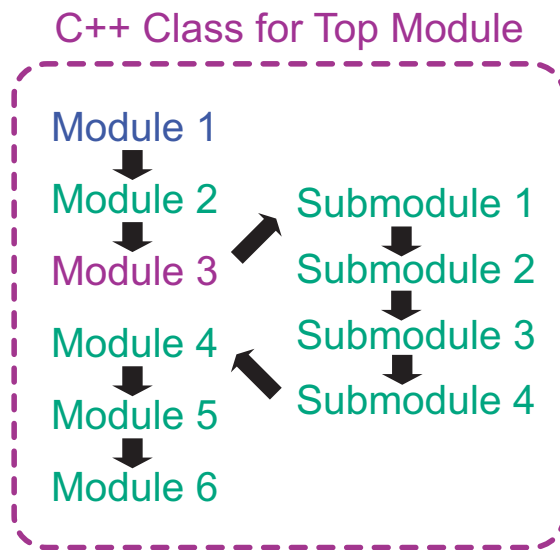- **Block-by-block execution of each module at each time step**
- **Hierarchical description is retained**




- C++ Class for Module 1
- C++ Class for Module 2
- C++ Class for Module 3
- C++ Class for Submodule 1
- C++ Class for Submodule 2
- C++ Class for Submodule 3
- C++ Class for Submodule 4
- C++ Class for Module 4
- C++ Class for Module 5
- C++ Class for Module 6

Time As A Signal

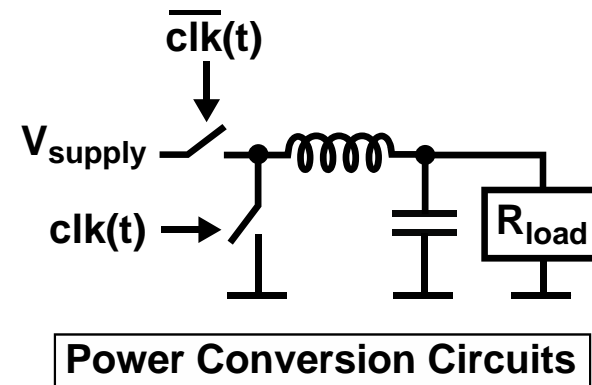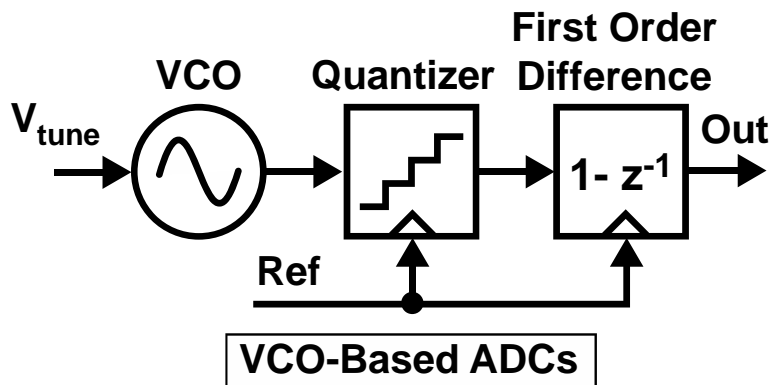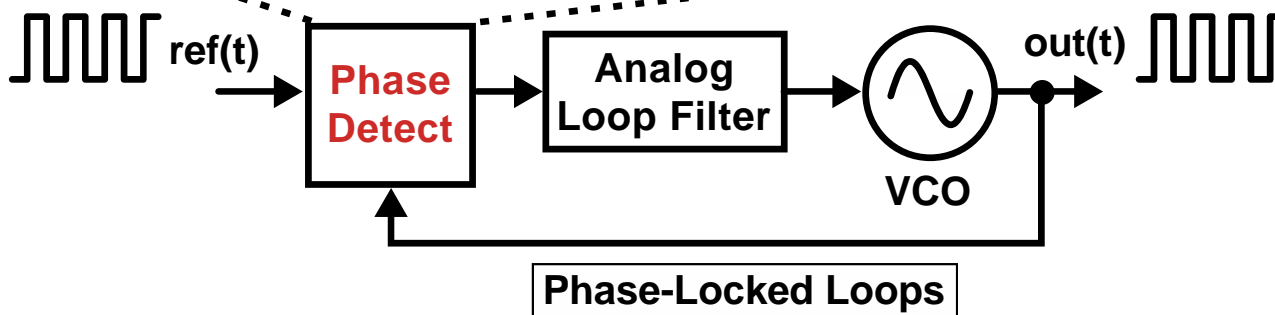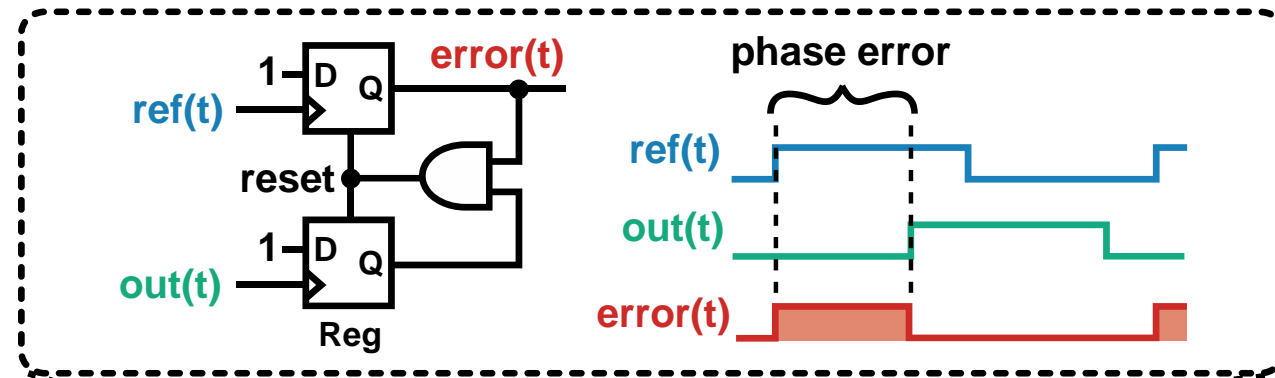


■ CppSim developed to accurately model time in circuits

System-Level Modeling: A Basic Example

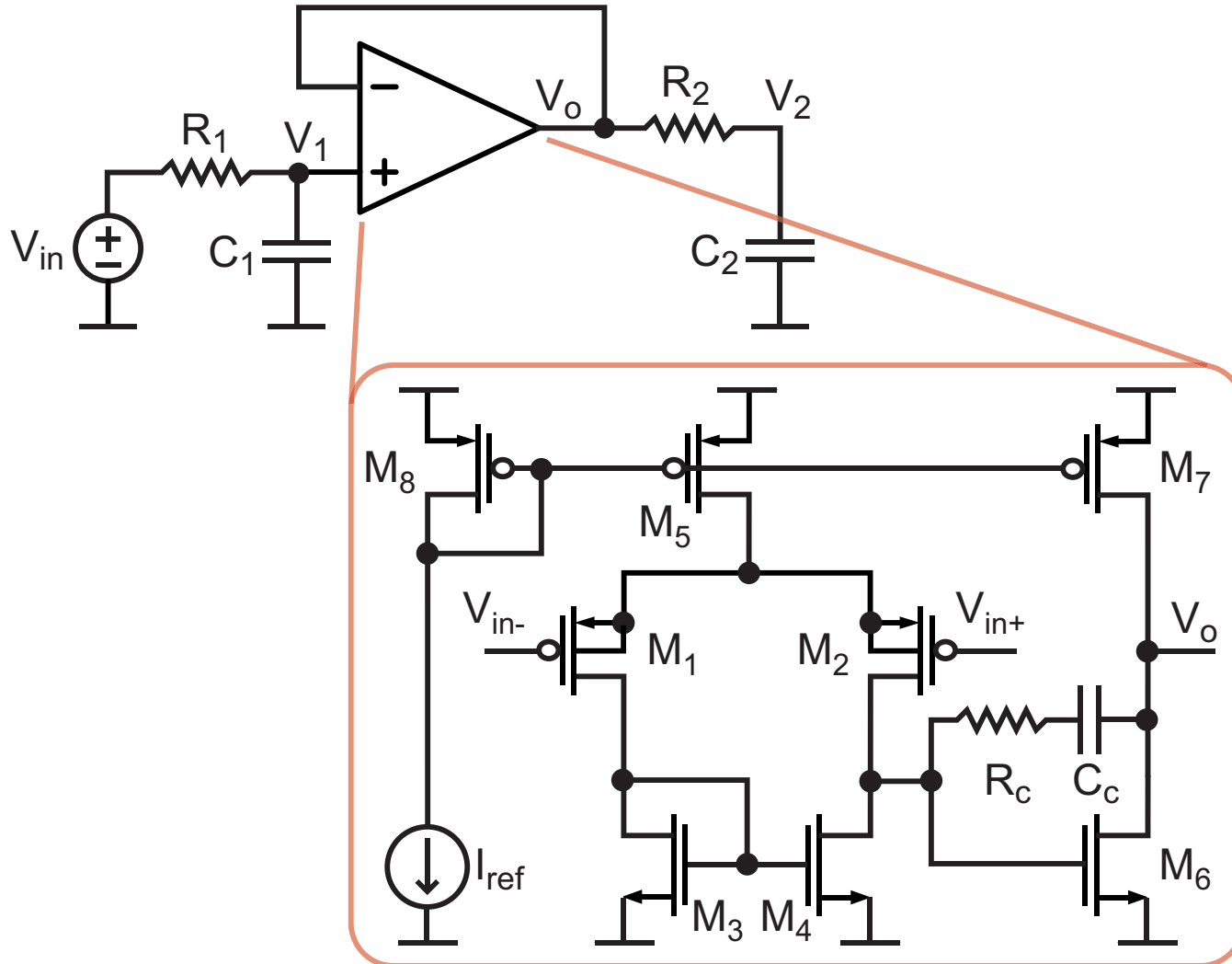


- **Opamp is a nonlinear, transistor-level circuit**
 - **Device level representation mandates SPICE-level simulation**

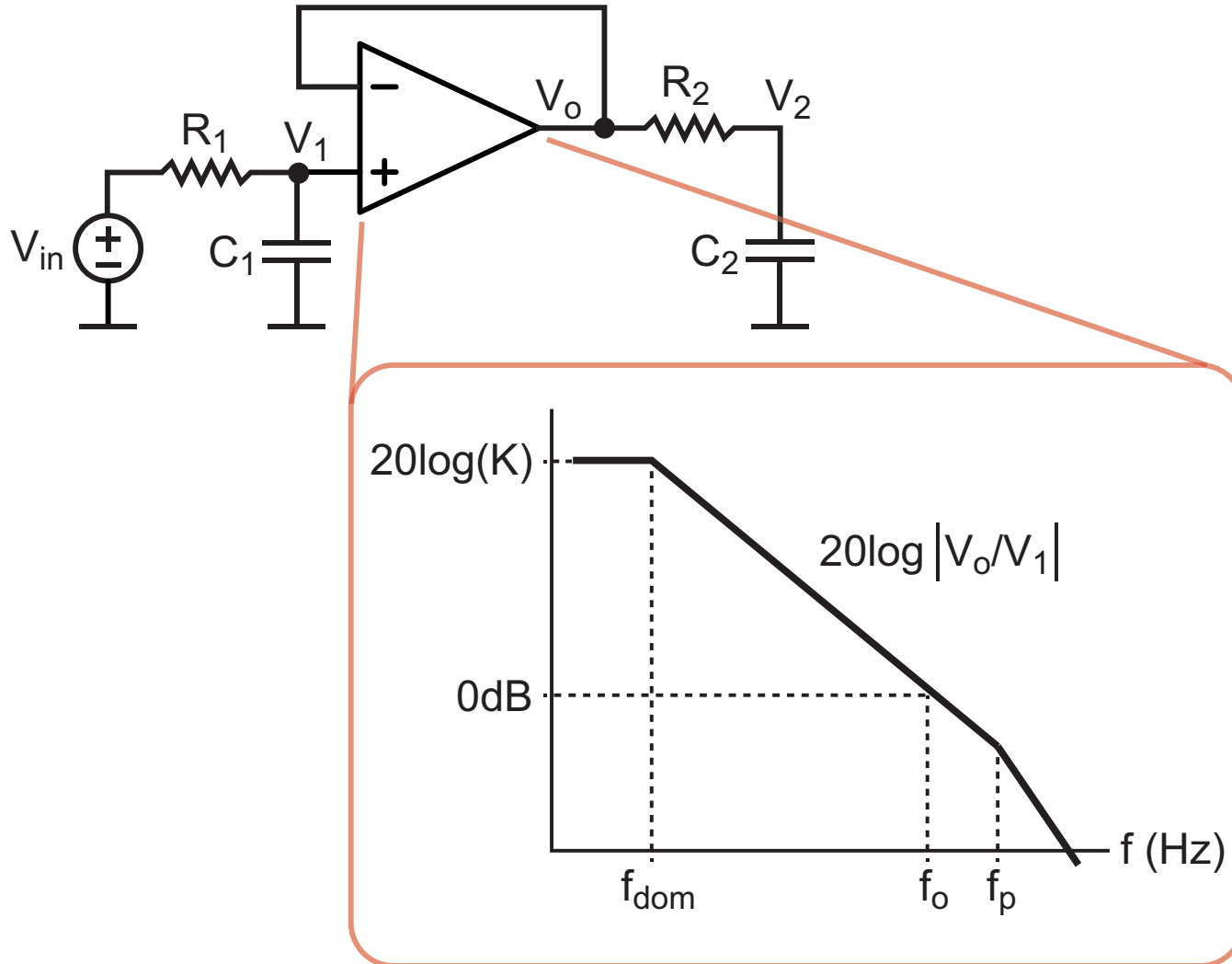Opamps Often Modeled at Transfer Function Level




- Works well for small perturbations about steady-state
 - Key parameters are gain and bandwidth

A Simple Block Diagram Model of Opamp

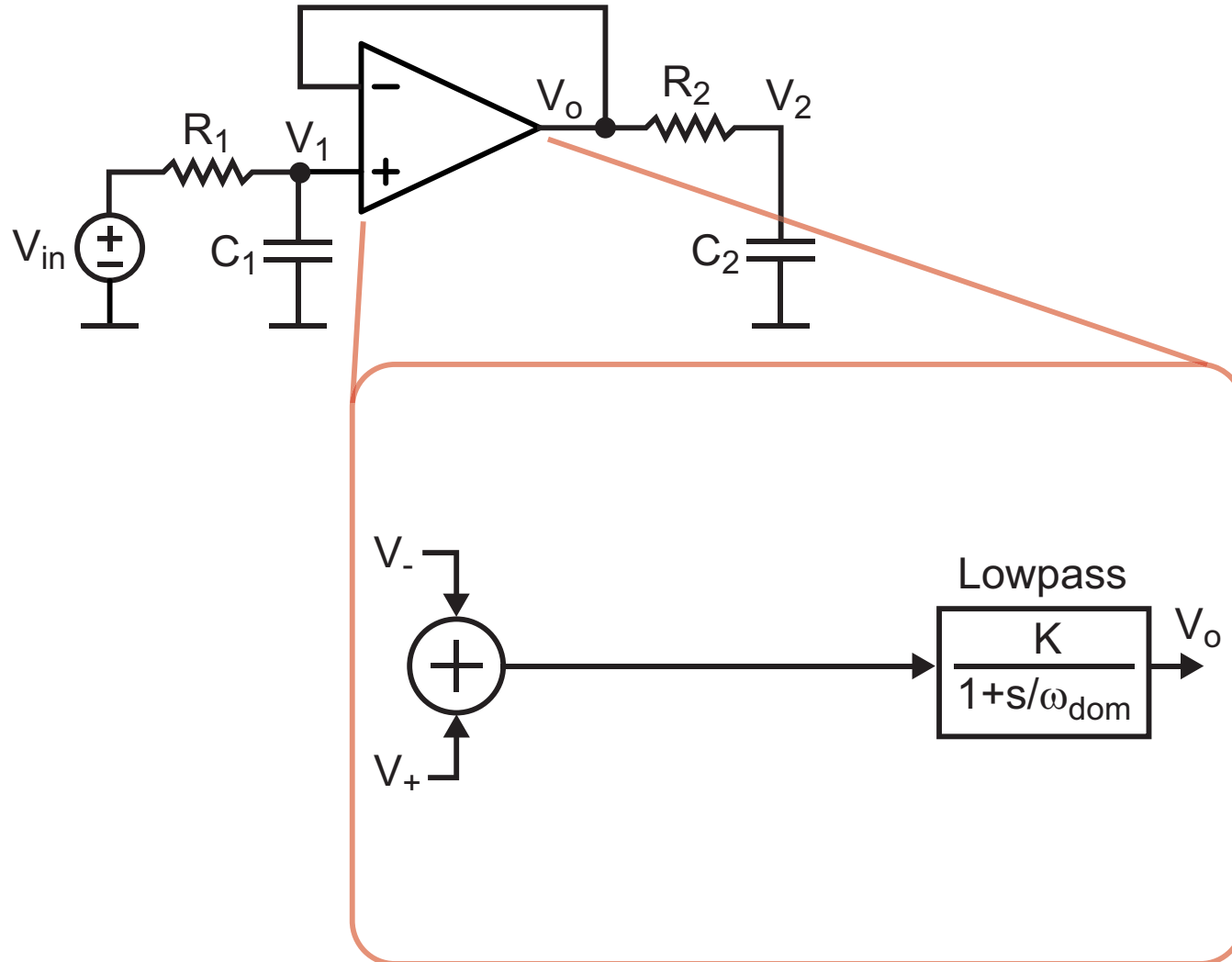


- Approximates first order behavior of opamp

Inclusion of Second Order Effects

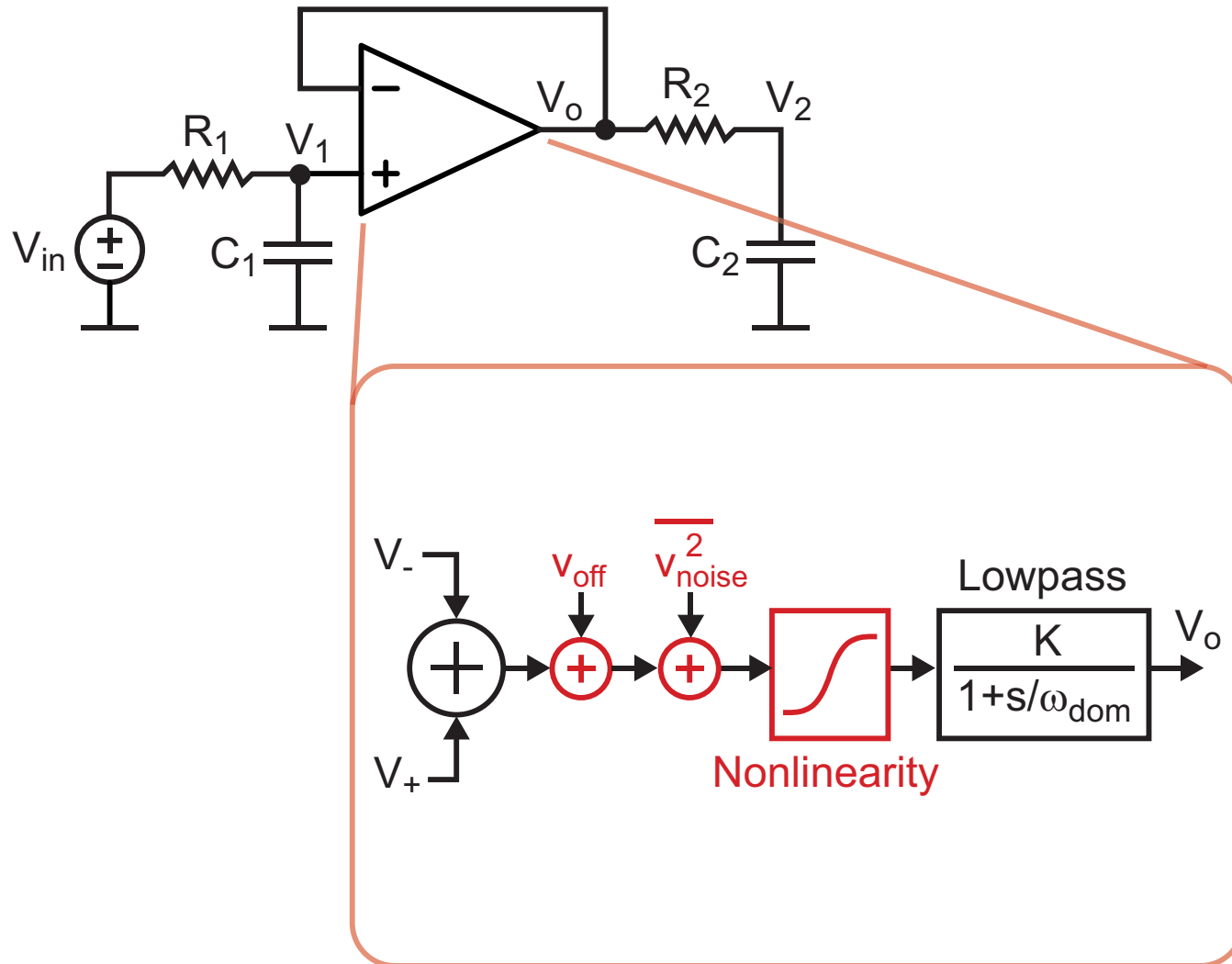


- **Offset, noise, and nonlinearity of front end-differential pair**
 - Parasitic poles are also easy to add as additional blocks

Overall Block Diagram Model

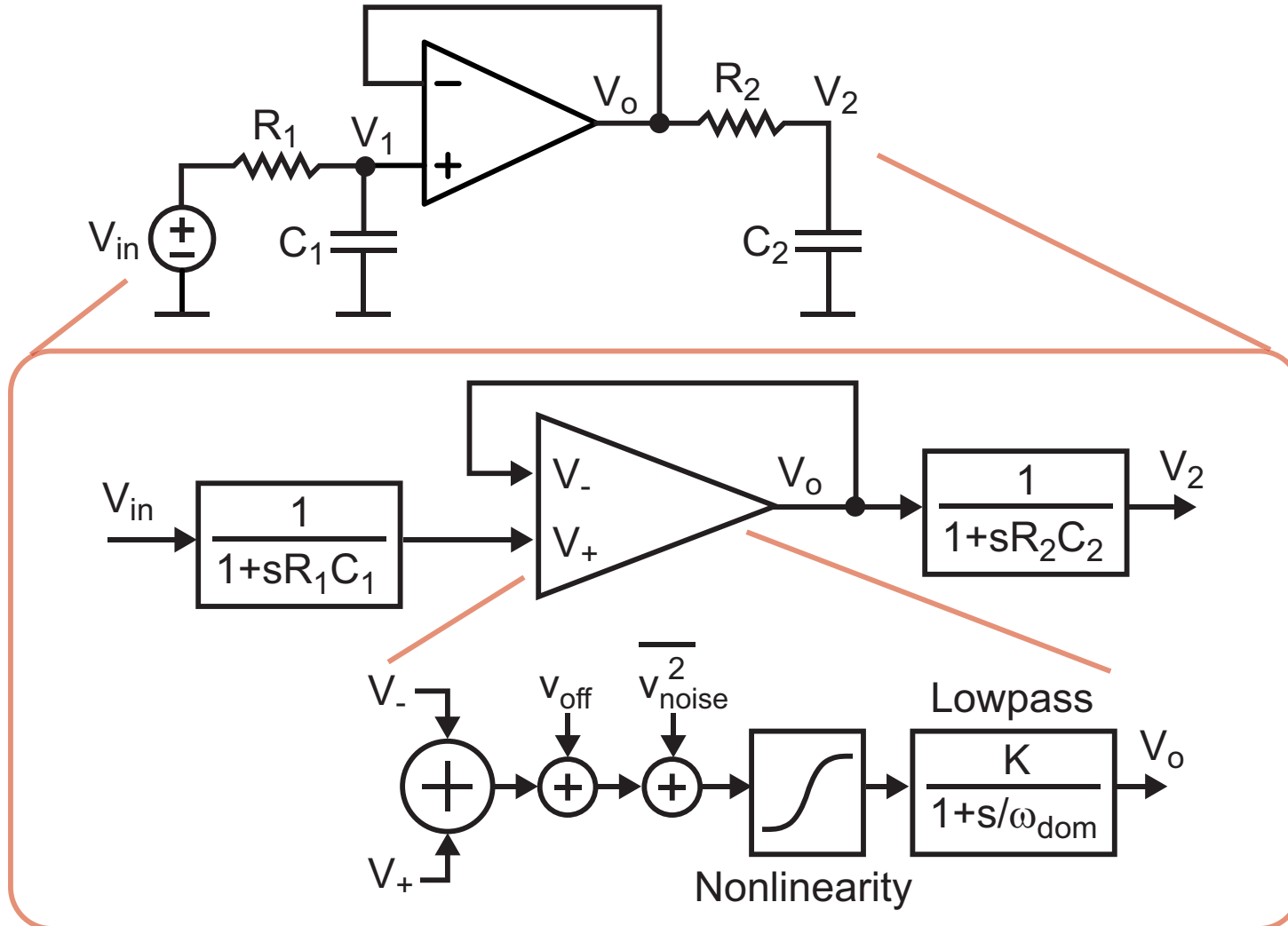


- **Unilateral flow through blocks allows fast simulation**
 - **Compute block outputs one at a time for each time step**

Advantages of Block-by-Block Computation

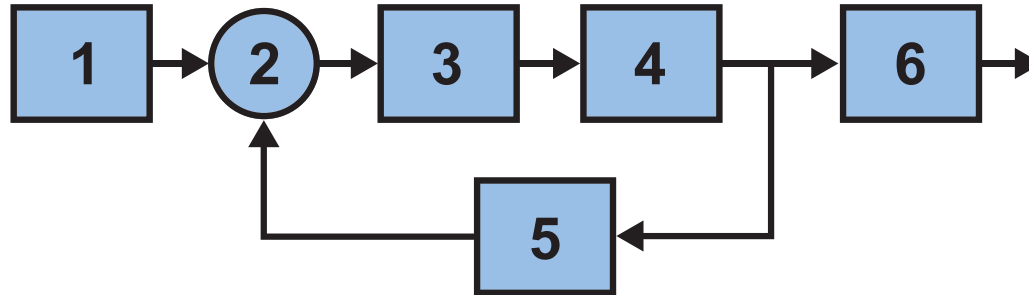

- **Simple, fast computational structure**
 - Simply perform computation for each block one at a time for each time step
 - Extends to hierarchical design quite easily
- **High level of system complexity can be handled**
 - Overall computational load is simply the sum of the computation required for each block
 - Contrast with SPICE whose computational load grows exponentially with the number of elements

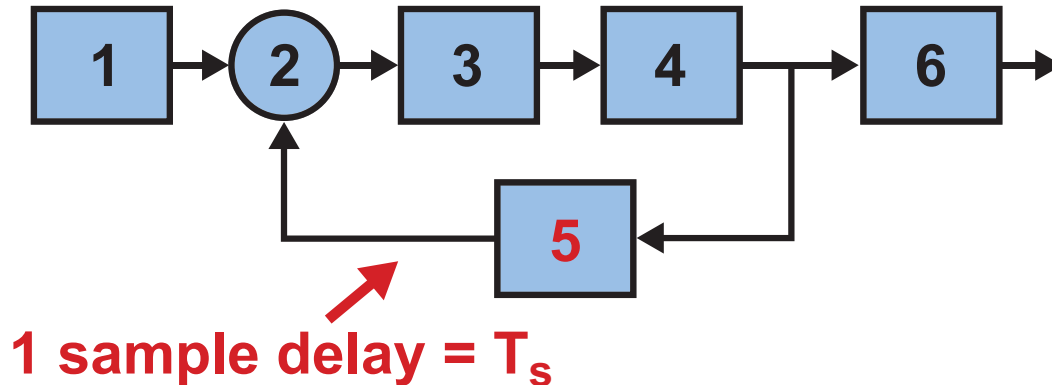
The Issue of Delay with Block-by-Block Computation



- Minimum possible delay within a feedback loop is one sample period
 - Example: Block 2 will not receive updated value from Block 5 until next time sample
 - For unity gain crossover frequency f_o and delay T_s :
 - Phase margin reduced by $f_o \cdot T_s \cdot 360^\circ$

Time step of simulation must be small compared to bandwidth of feedback loops being simulated

The Issue of Block Order

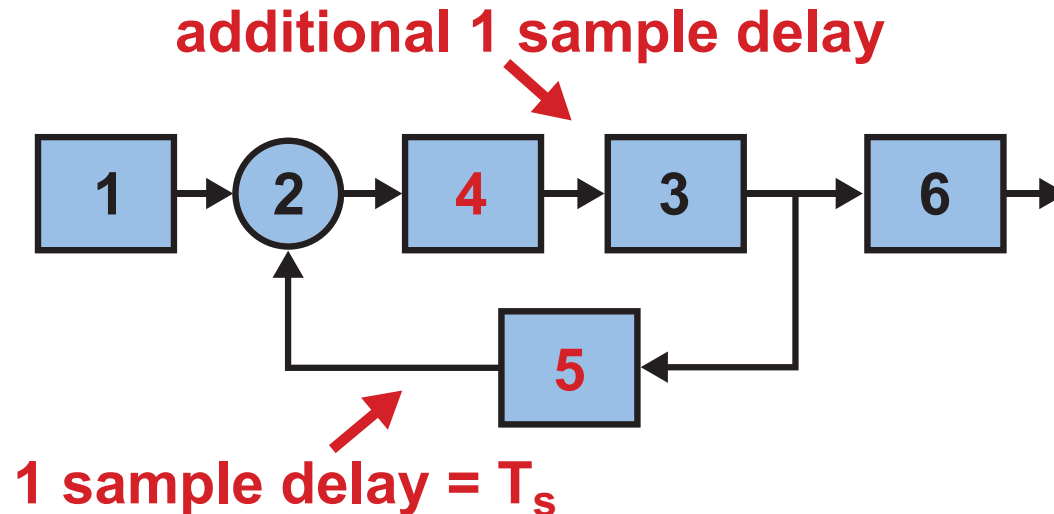


- Poor ordering of blocks leads to additional delay within feedback loops
 - Issue is made worse if blocks computed concurrently
 - Leads to one sample delay *per block*
- Block-by-block computation requires additional algorithm to achieve minimum delay ordering


CppSim provides automatic minimum delay ordering and allows user specified ordering

Time-Based Circuits

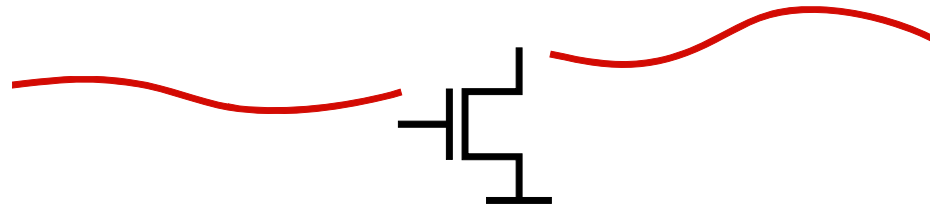- Traditional analog circuits utilize voltage and current with bandwidth constrained signaling



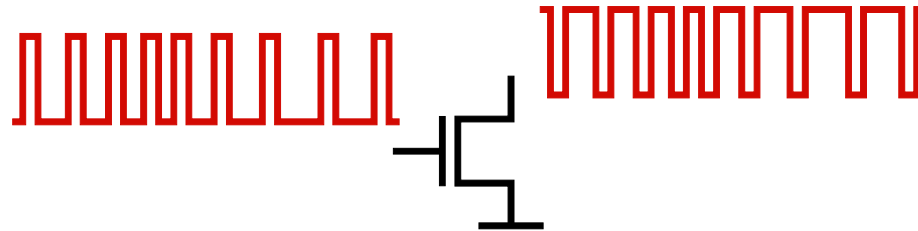
- Time-based circuits utilize the timing of edges produced by “digital” circuits



- Modern CMOS processes are offering faster edge rates and lower delay through digital circuits

High bandwidth of time-based circuits creates challenges for high speed simulation


A Common Time-Based Circuit

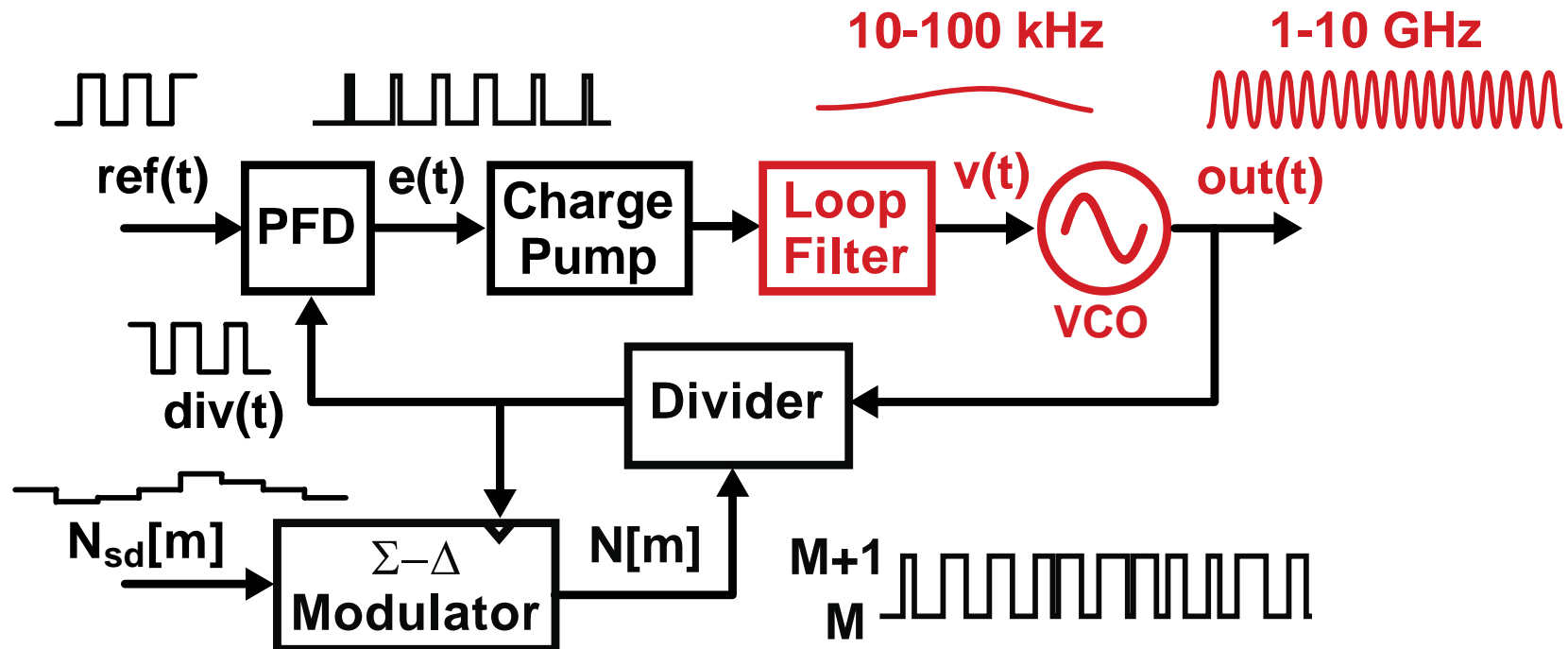

- Consider a fractional-N synthesizer as a prototypical time-based circuit
 - High output frequency \Rightarrow High sample rate
 - Long time constants \Rightarrow Long time span for transients


Large number of simulation time steps required

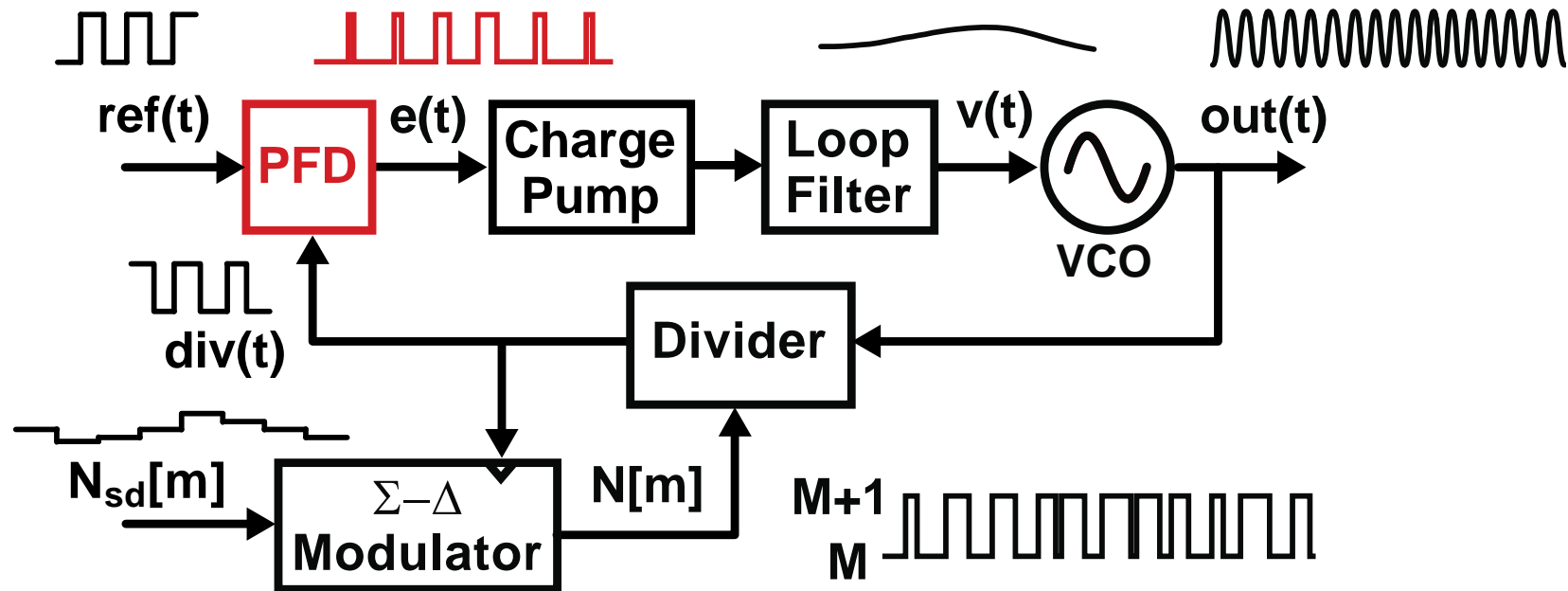Continuously Varying Edges Lead to Accuracy Issues




- PFD output has very high bandwidth
 - Difficult to achieve high accuracy within a conventional discrete-time or SPICE level simulator
- Non-periodic dithering of divider complicates matters
 - Periodic, steady-state methods do not apply

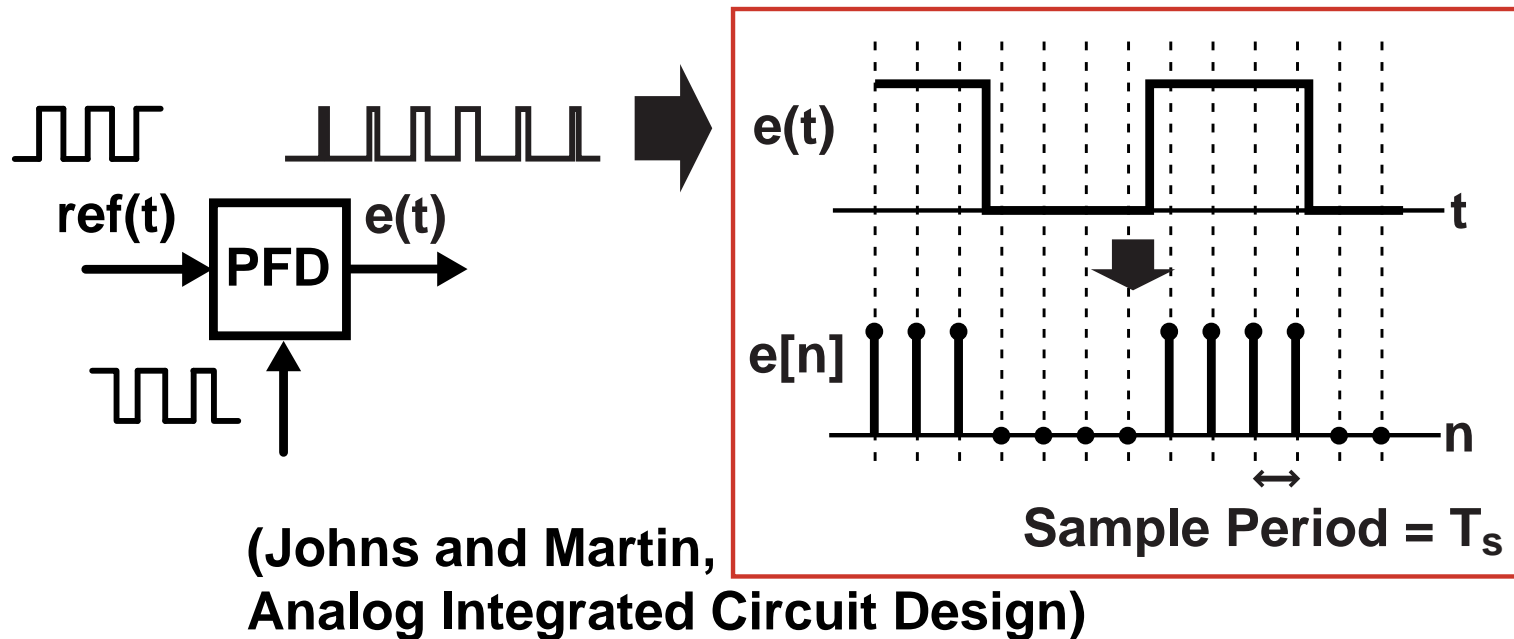Consider A Classical Constant-Time Step Method




- Directly sample the PFD output according to the simulation sample period
 - Simple, fast, readily implemented in Matlab, Verilog, C++
- Issue – quantization noise is introduced
 - This noise can overwhelm the PLL noise sources we are trying to simulate

Alternative: Event Driven Simulation

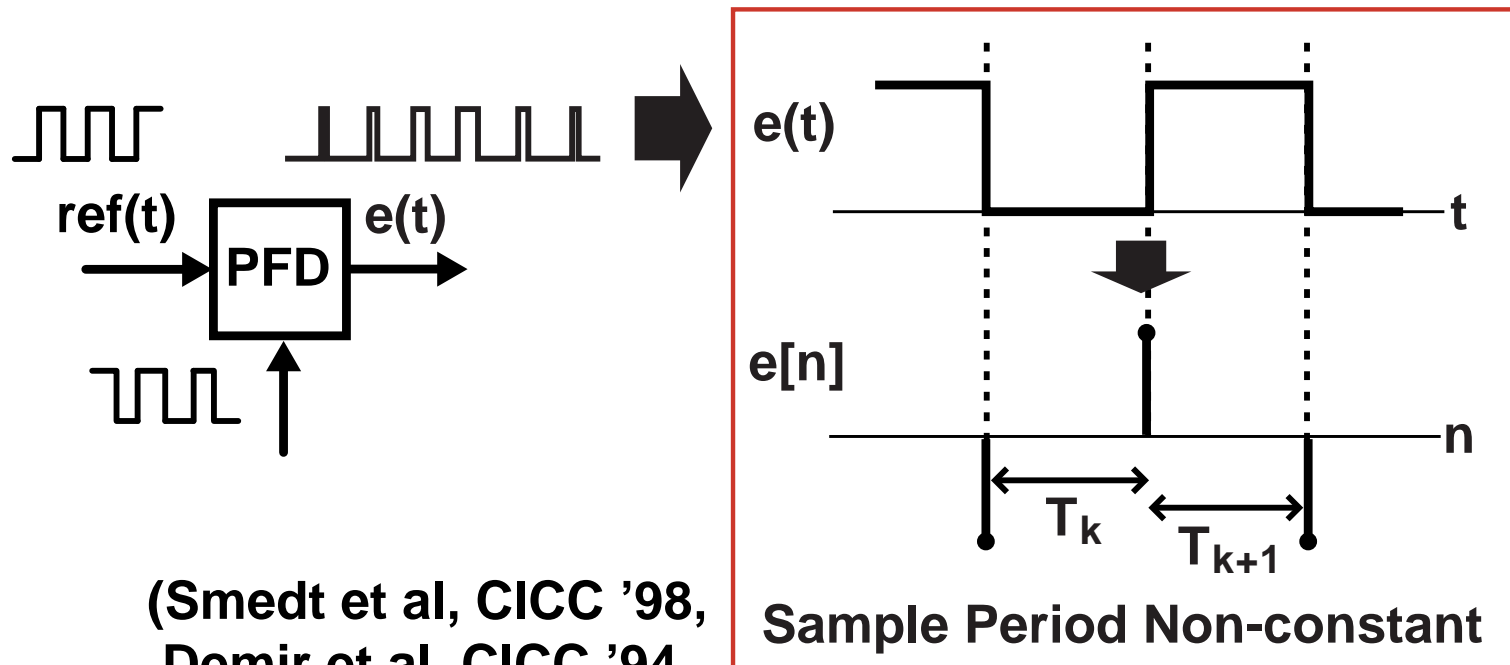

- Set simulation time samples at PFD edges
 - Sample rate can be lowered to edge rate!

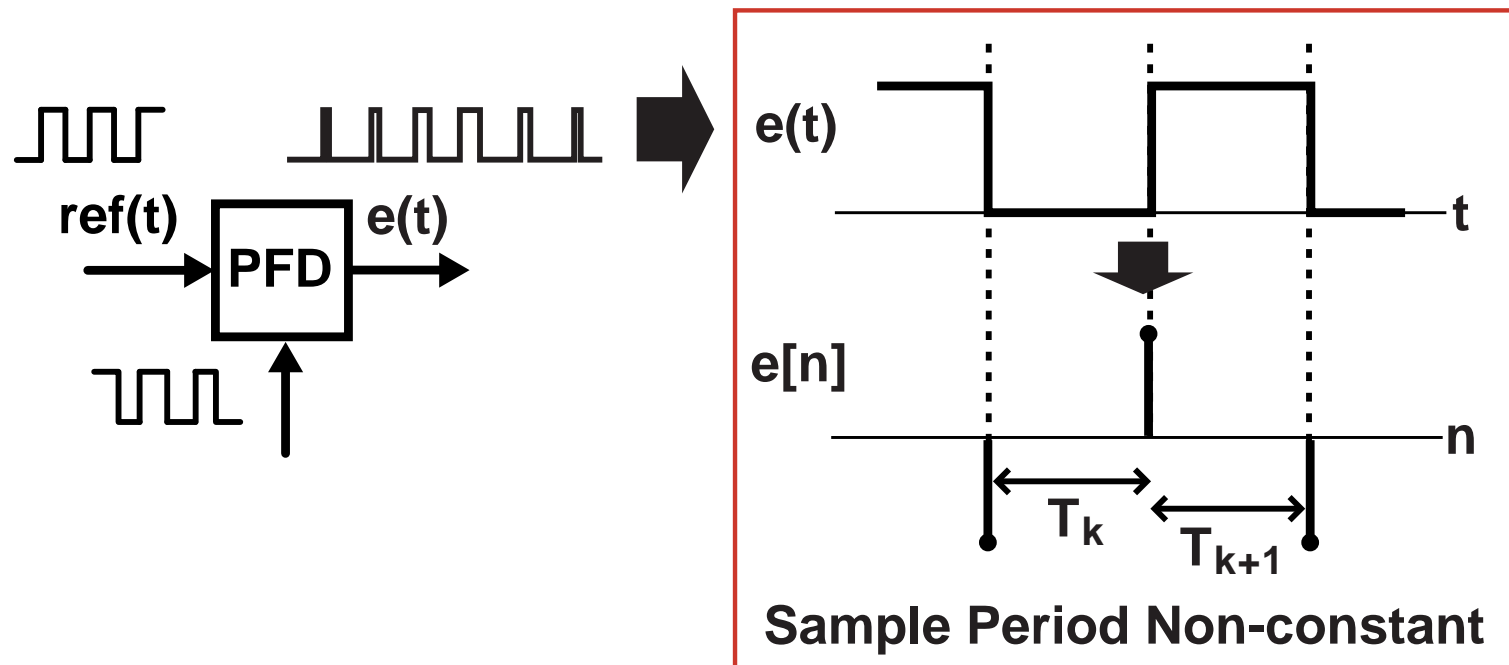
Issue: Non-Constant Time Step Brings Complications



- Filters and noise sources must account for varying time step in their code implementations
- Spectra derived from mixing and other operations can display false simulation artifacts
- Setting of time step becomes progressively complicated if multiple time-based circuits simulated at once




Is there a better way?

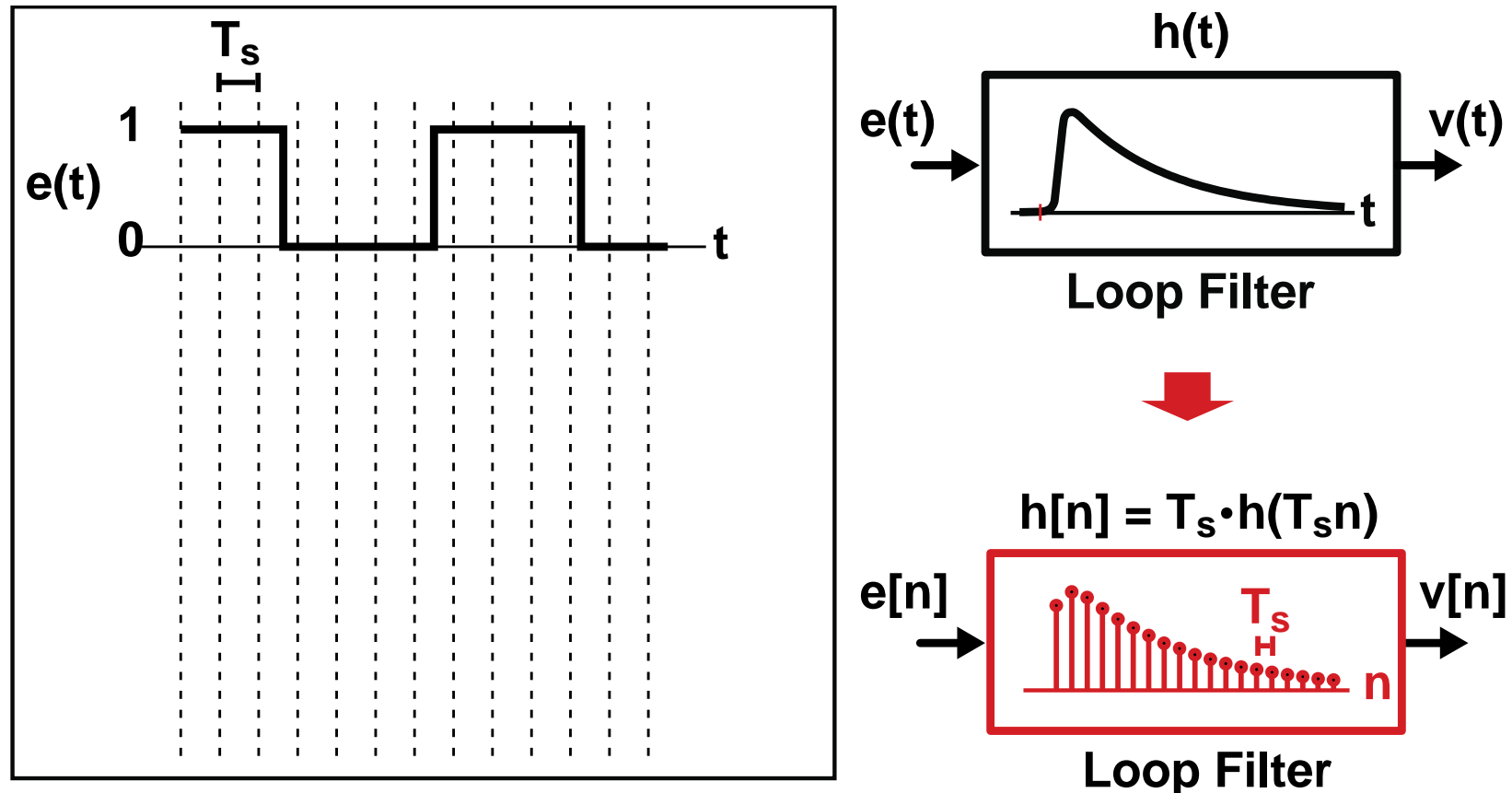Proposed Approach: Use Constant Time Step





- **Straightforward CT to DT transformation of filter blocks**
 - Use bilinear transform or impulse invariance methods
- **Overall computation framework is fast and simple**
 - Simulator can be based on Verilog, Matlab, C++

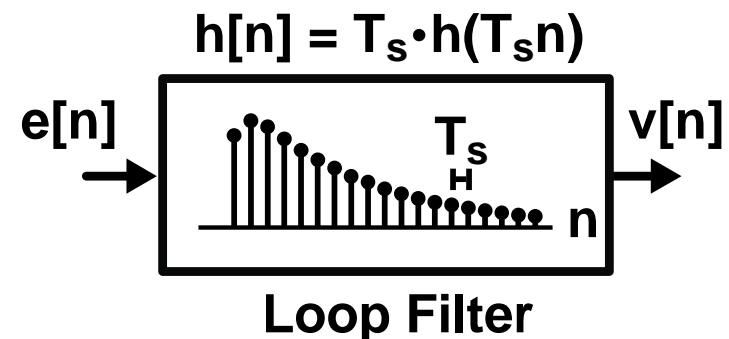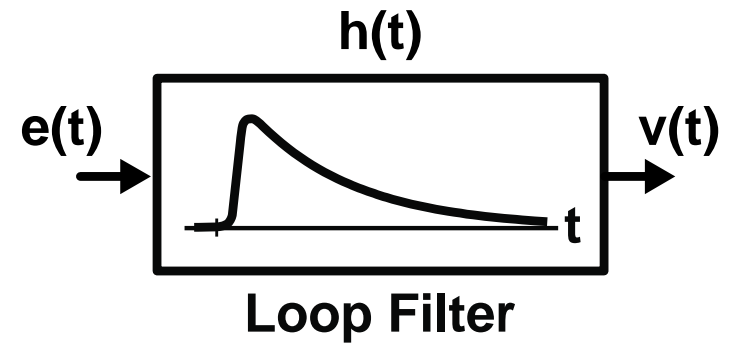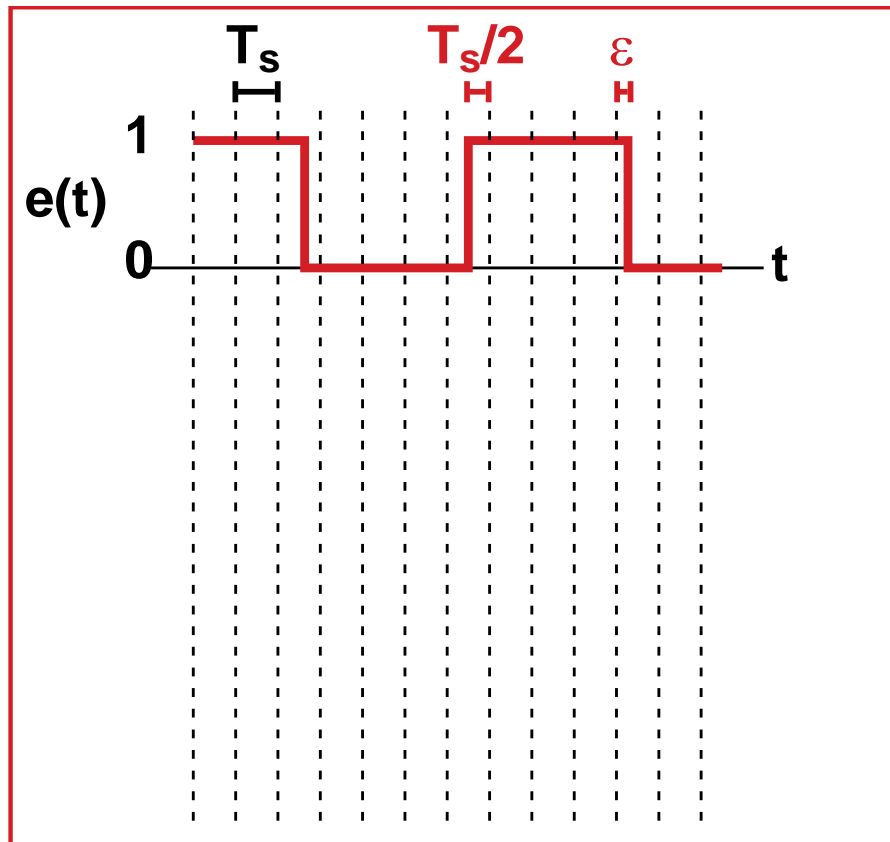Problem: Quantization Noise at PFD Output





- Edge locations of PFD output are quantized
 - Resolution set by time step: T_s
- Reduction of T_s leads to long simulation times

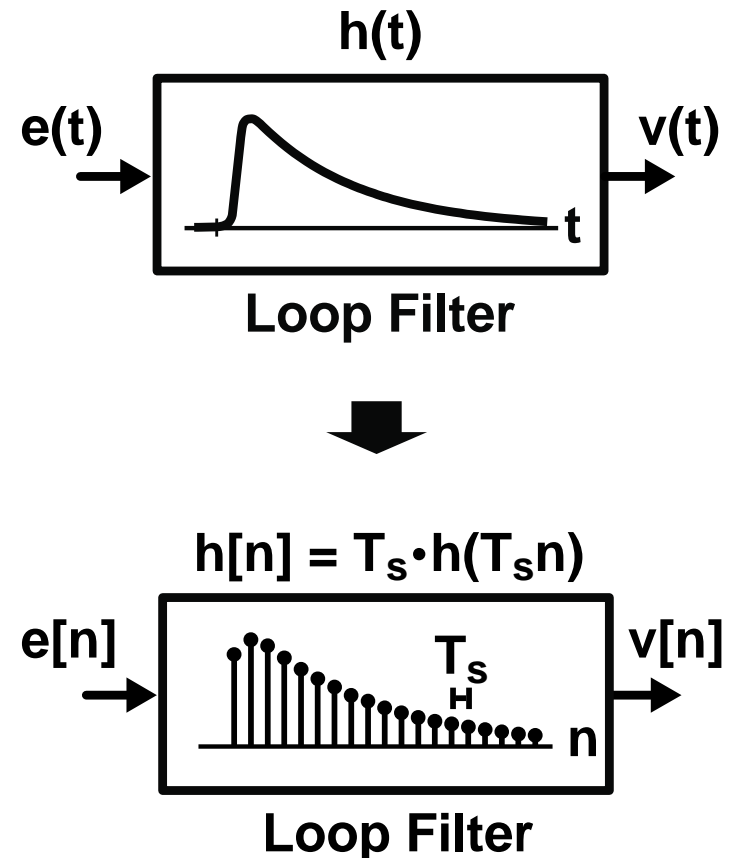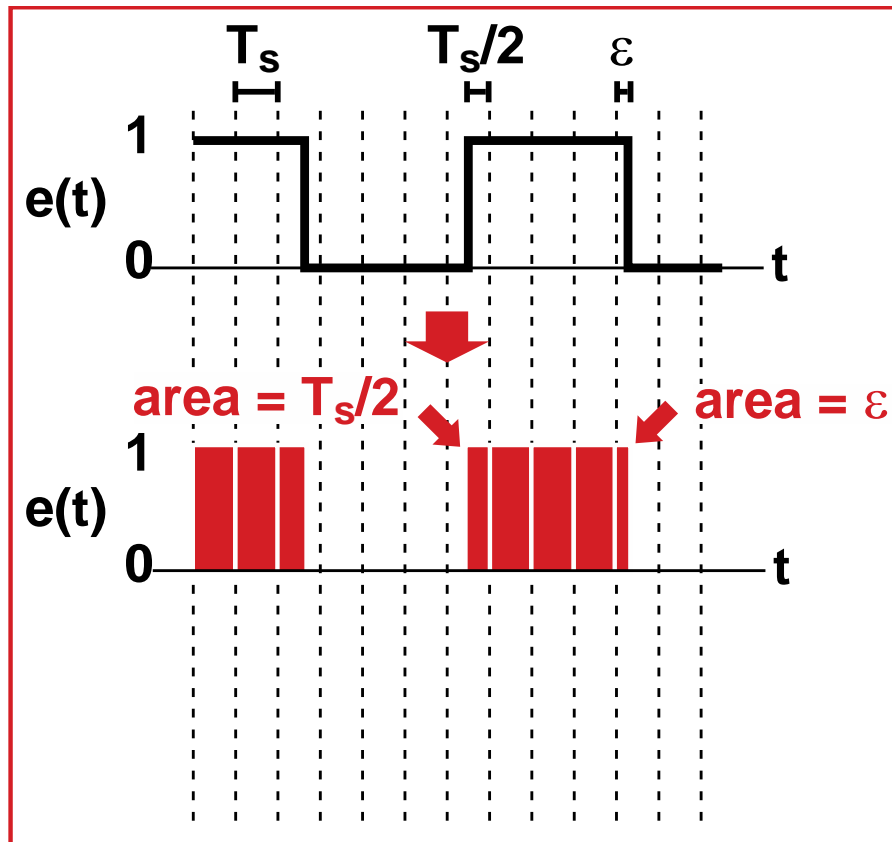Proposed Approach: View as Series of Pulses




- Area of each pulse set by edge locations
- Key observations:
 - Pulses look like impulses to loop filter
 - Impulses are parameterized by their area and time offset

Proposed Area Conservation Method

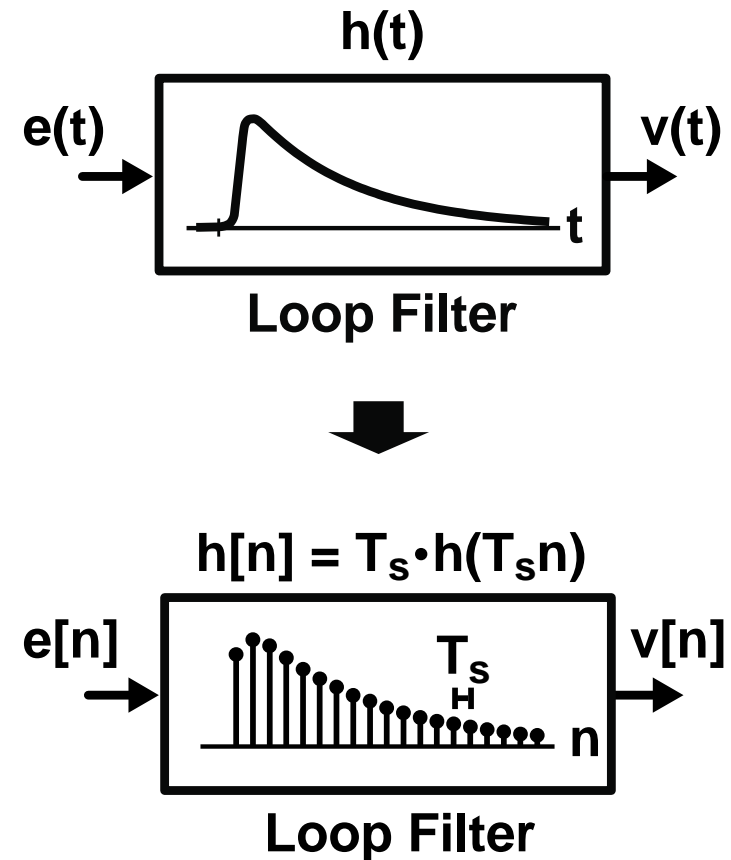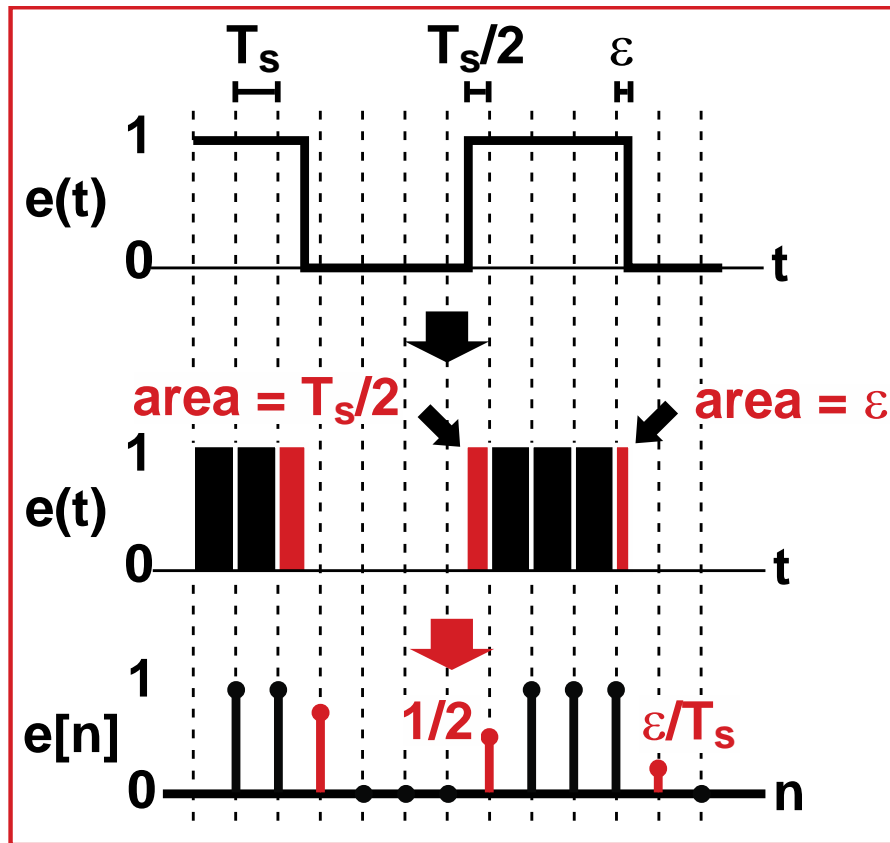


- **Set $e[n]$ samples according to pulse areas**
 - Leads to very accurate results
 - Fast computation

Double_Interp Protocol

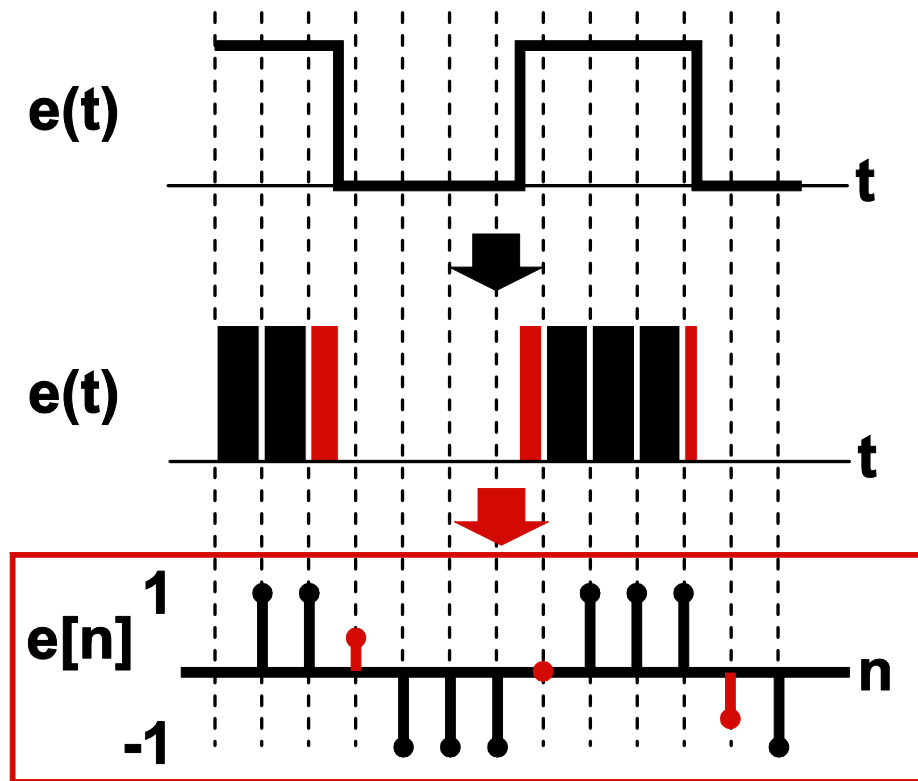



- **Protocol sets signal samples to -1 or 1 except for transitions**
 - Transition values between -1 and 1 are directly related to the edge time location
 - Can be implemented in C++, Verilog, and Matlab/Simulink

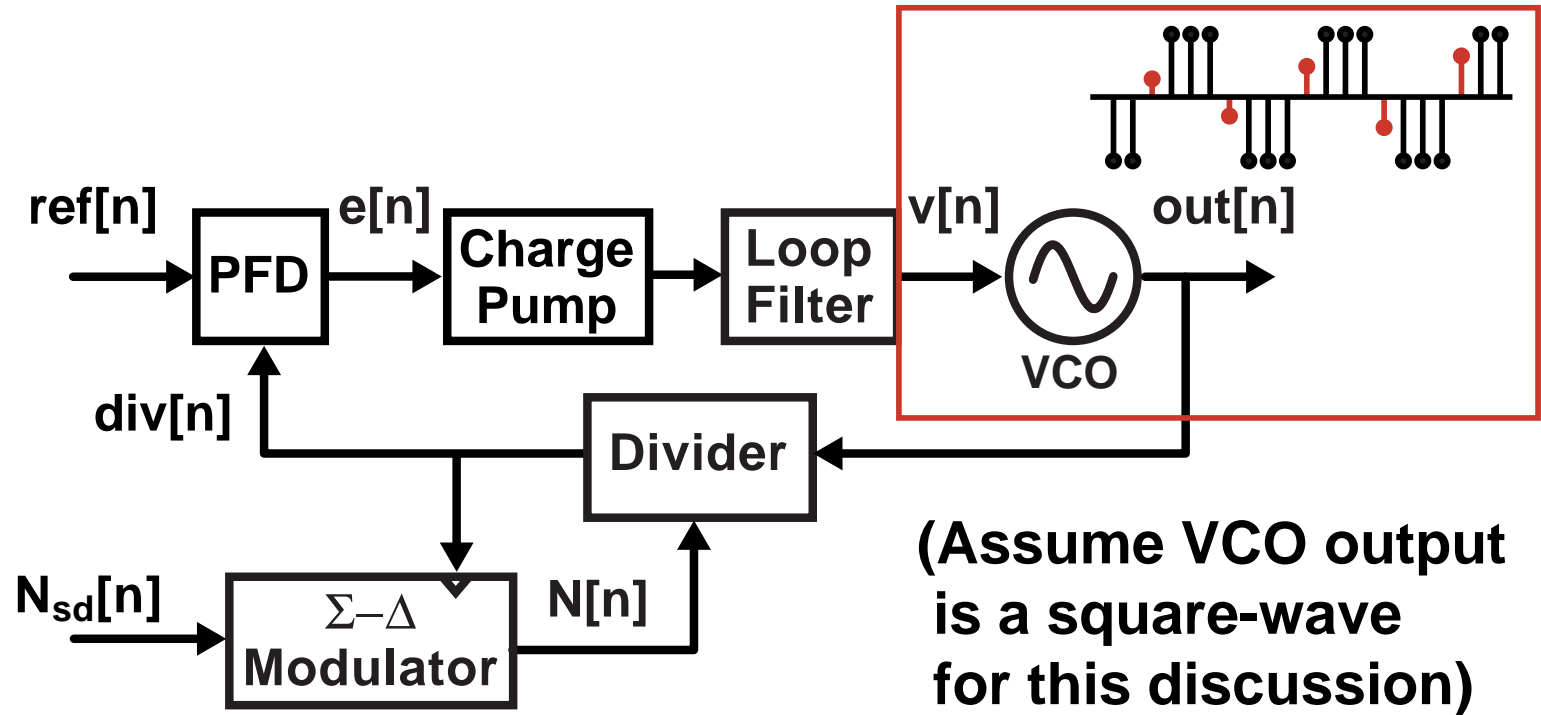VCO is a Key Block for Double_Interp Encoding




- The VCO block is the key translator from a bandlimited analog input to an edge-based waveform
 - We can create routines in the VCO that calculate the edge times of the output and encode their values using the double_interp protocol

Calculation of Transition Time Values

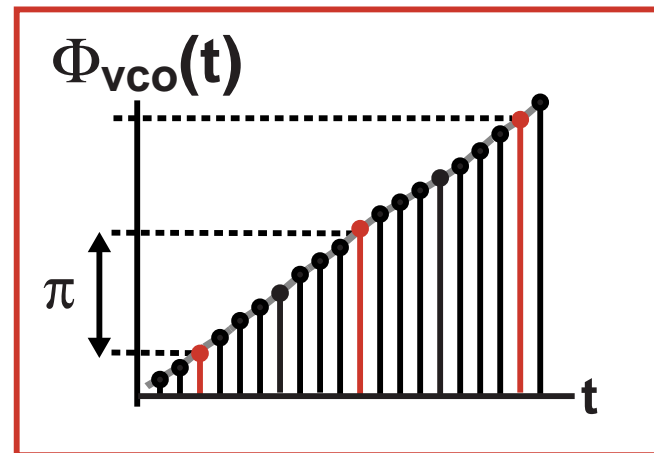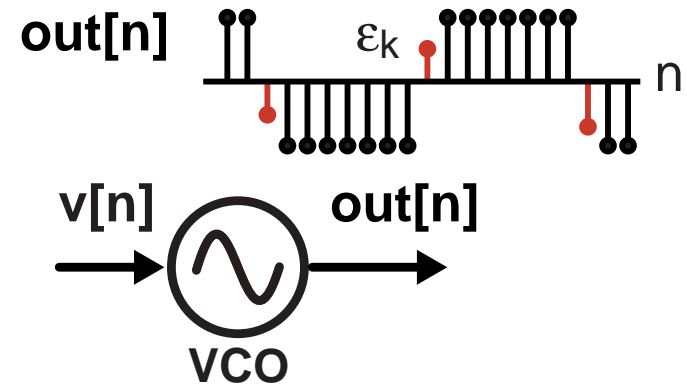


- Model VCO based on its phase

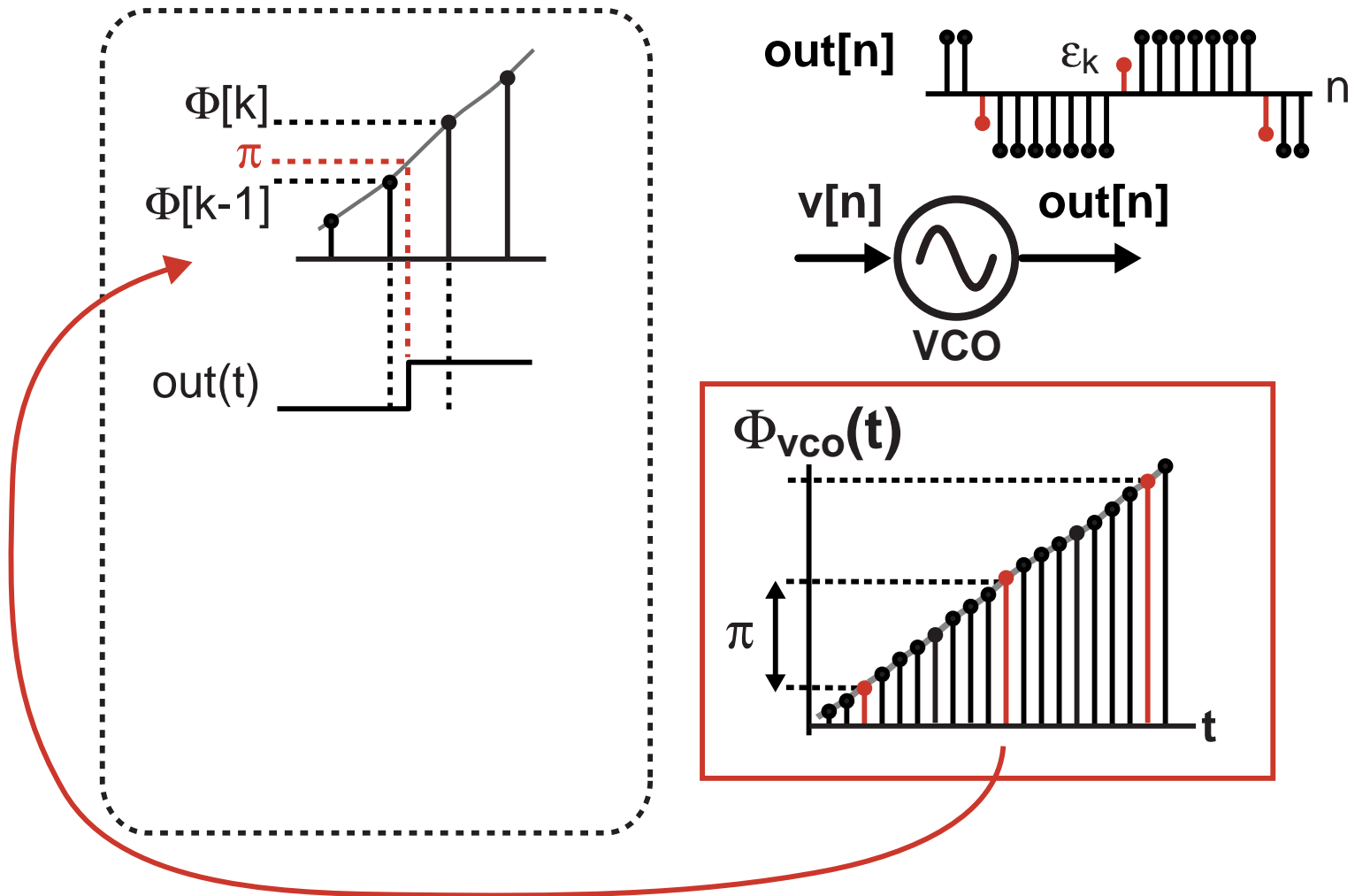Calculation of Transition Time Values (cont.)




- Determine output transition time according to phase

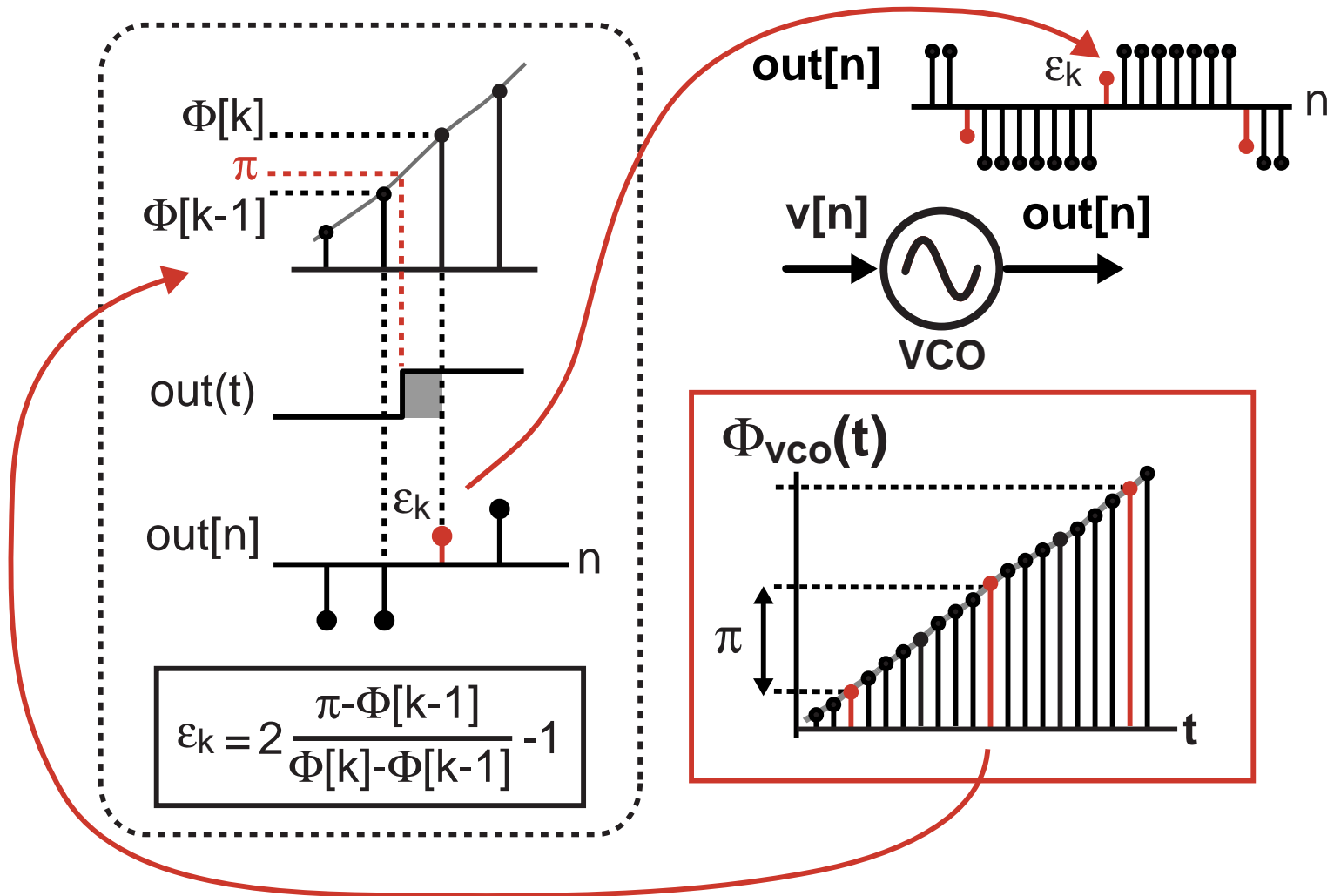Calculation of Transition Time Values (cont.)




- Use first order interpolation to determine transition value

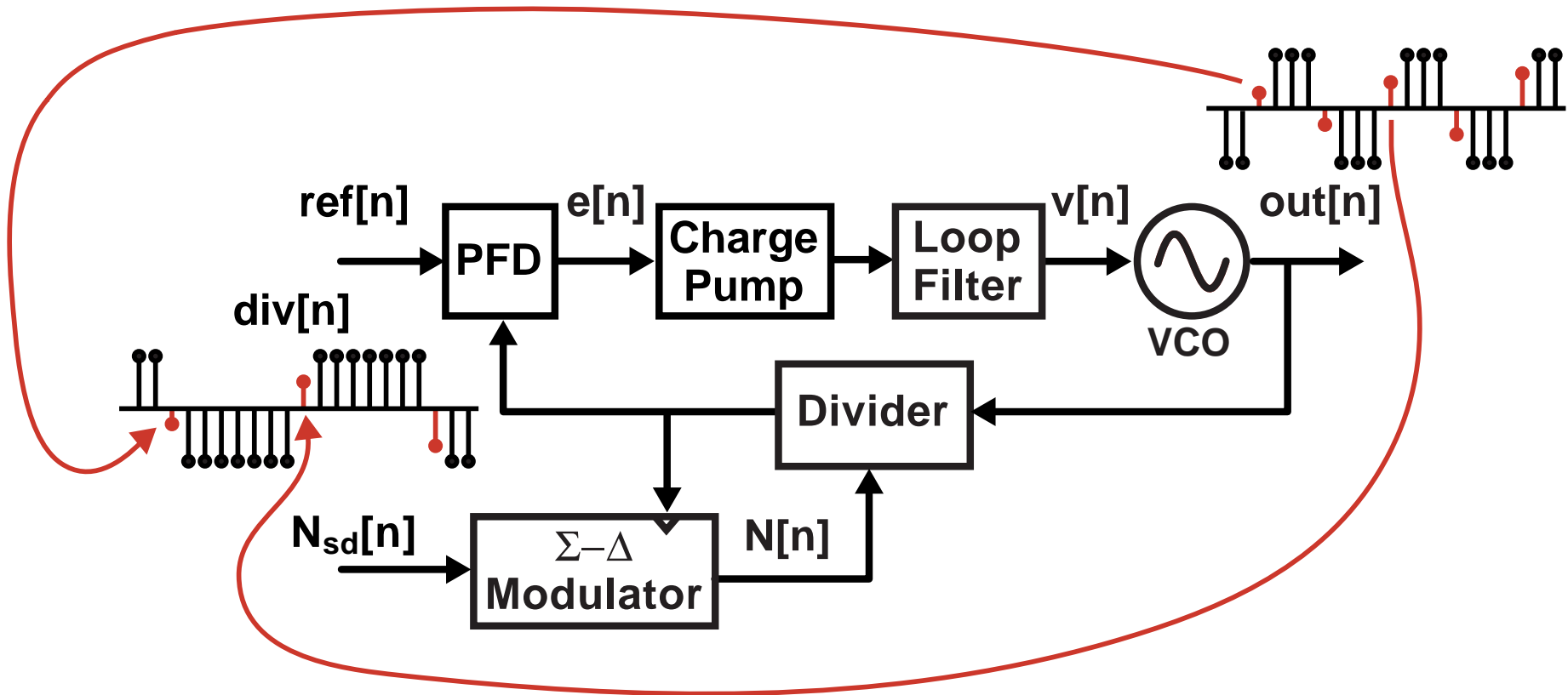Processing of Edges using Double_Interp Protocol




- Frequency divider block simply passes a sub-sampling of edges based on the VCO output and divide value

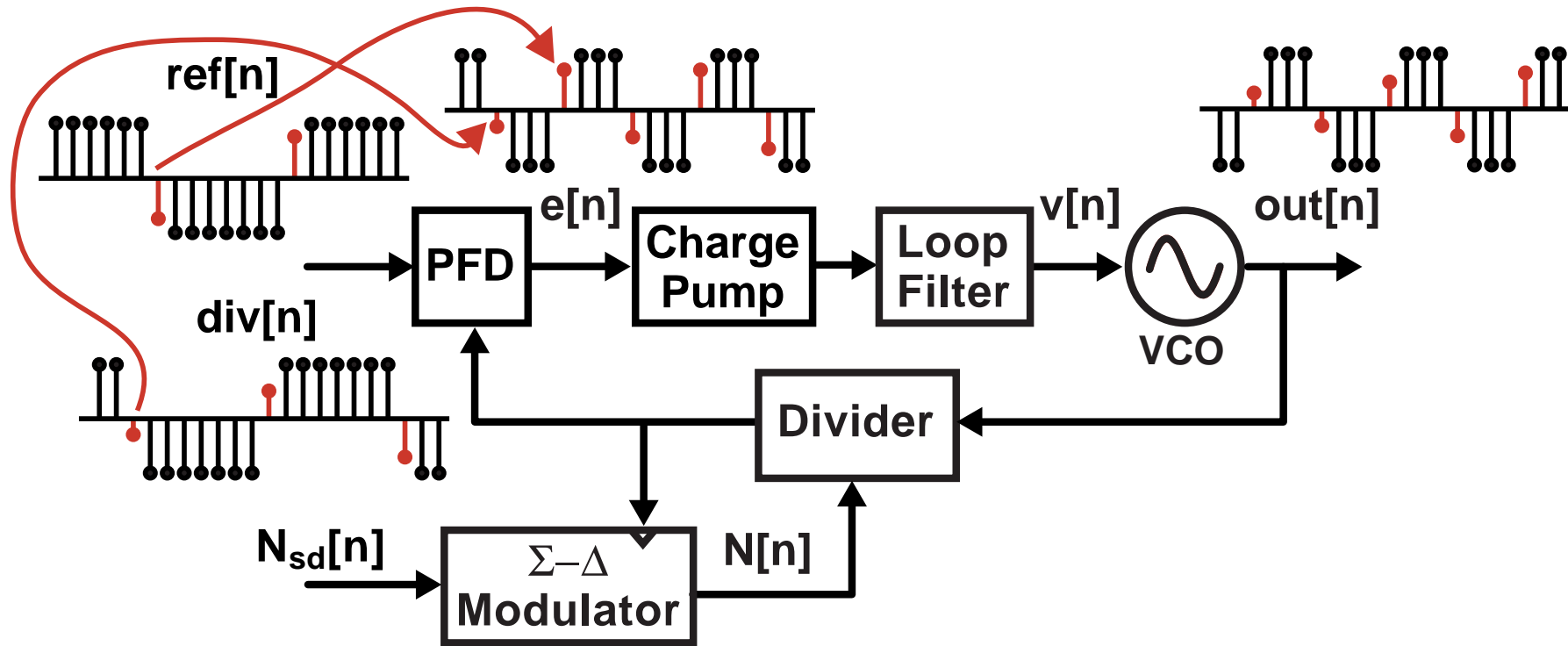Processing of Edges using Double_Interp Protocol




- Phase Detector compares edges times between reference and divided output and then outputs pulses that preserve the time differences

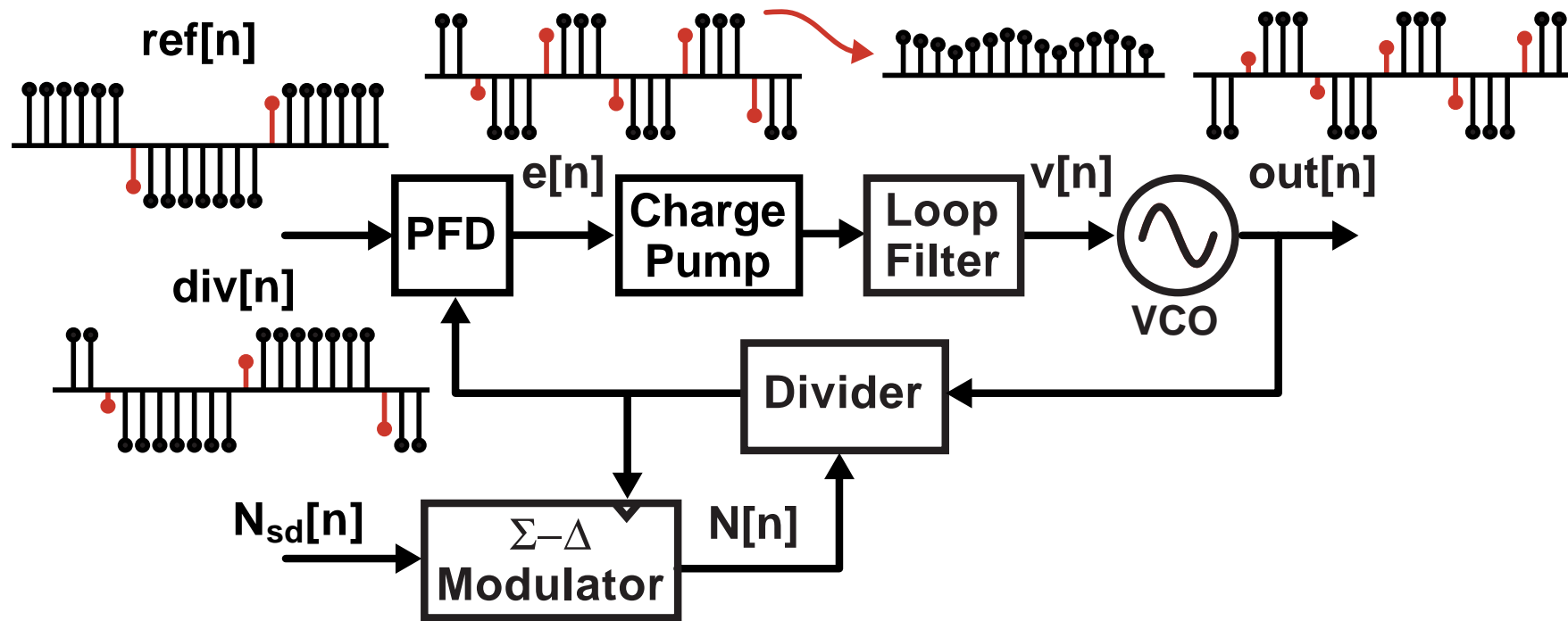Processing of Edges using Double_Interp Protocol




- Charge Pump and Loop filter operation is straightforward to model
 - Simply filter pulses from phase detector as discussed earlier

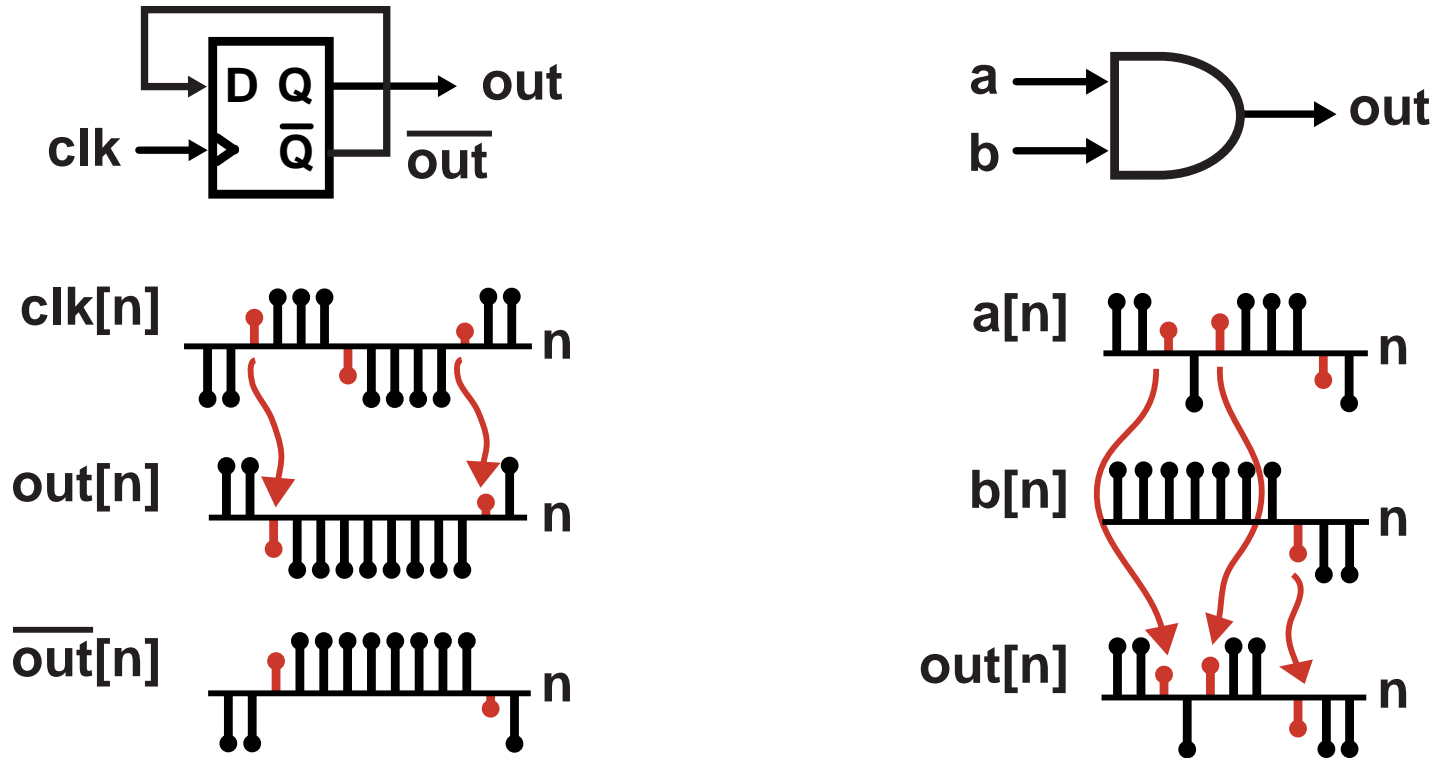Using the Double_Interp Protocol with Digital Gates





- Relevant timing information contained in the input that causes the output to transition
 - Determine which input causes the transition, then pass its transition value to the output

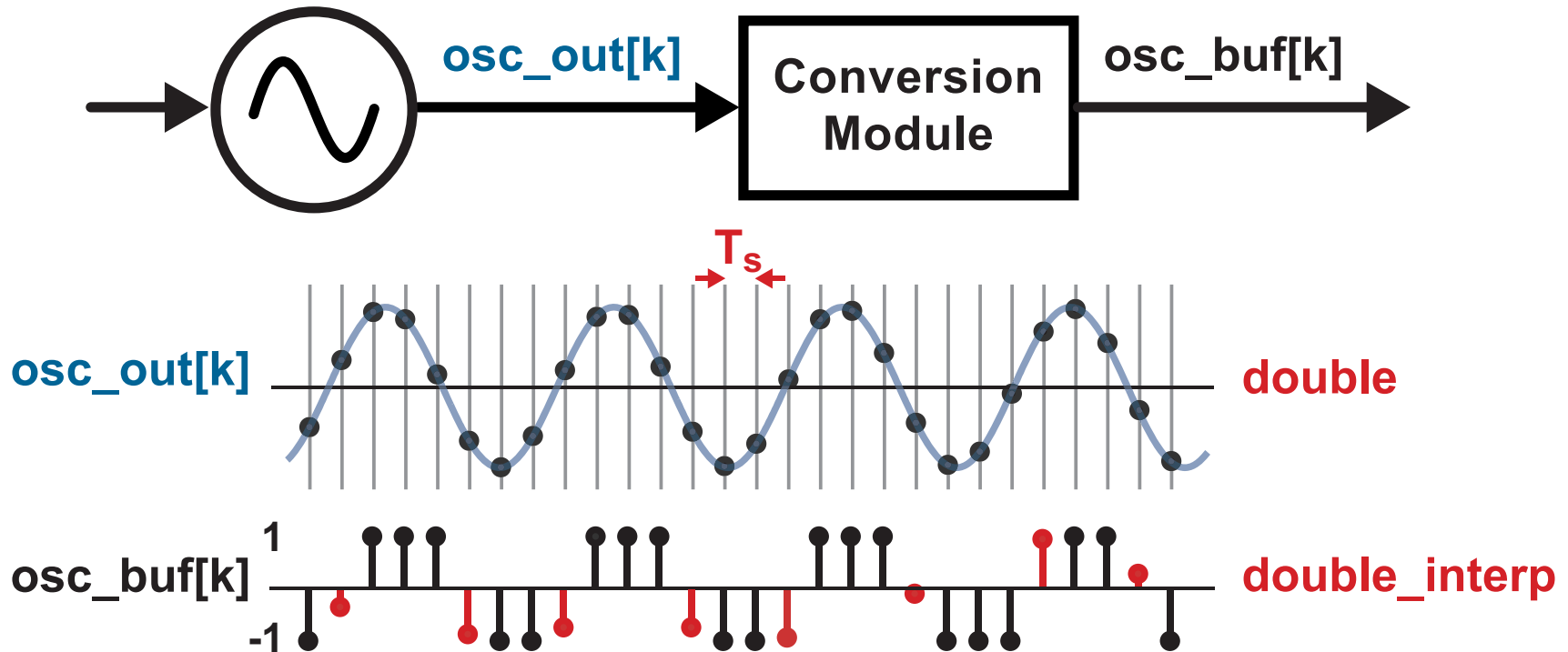Using the Double_Interp Protocol with Sine Waves



- In some systems we must deal directly with sine waves
 - An explicit conversion module should be utilized
 - We can convert to `double_interp` protocol using a similar interpolation technique as described earlier
 - See **`gmsk_limitamp`** module within **GMSK_Example** library
 - Used in module **`gmsk_pll_transmitter`** in the same library

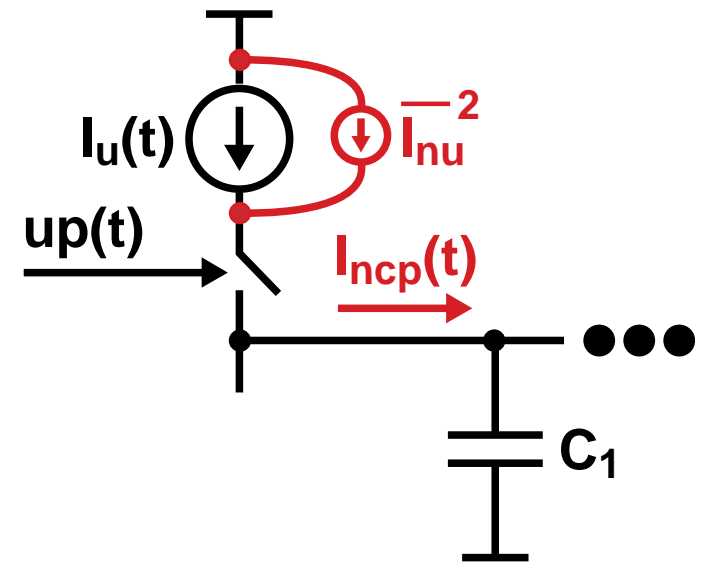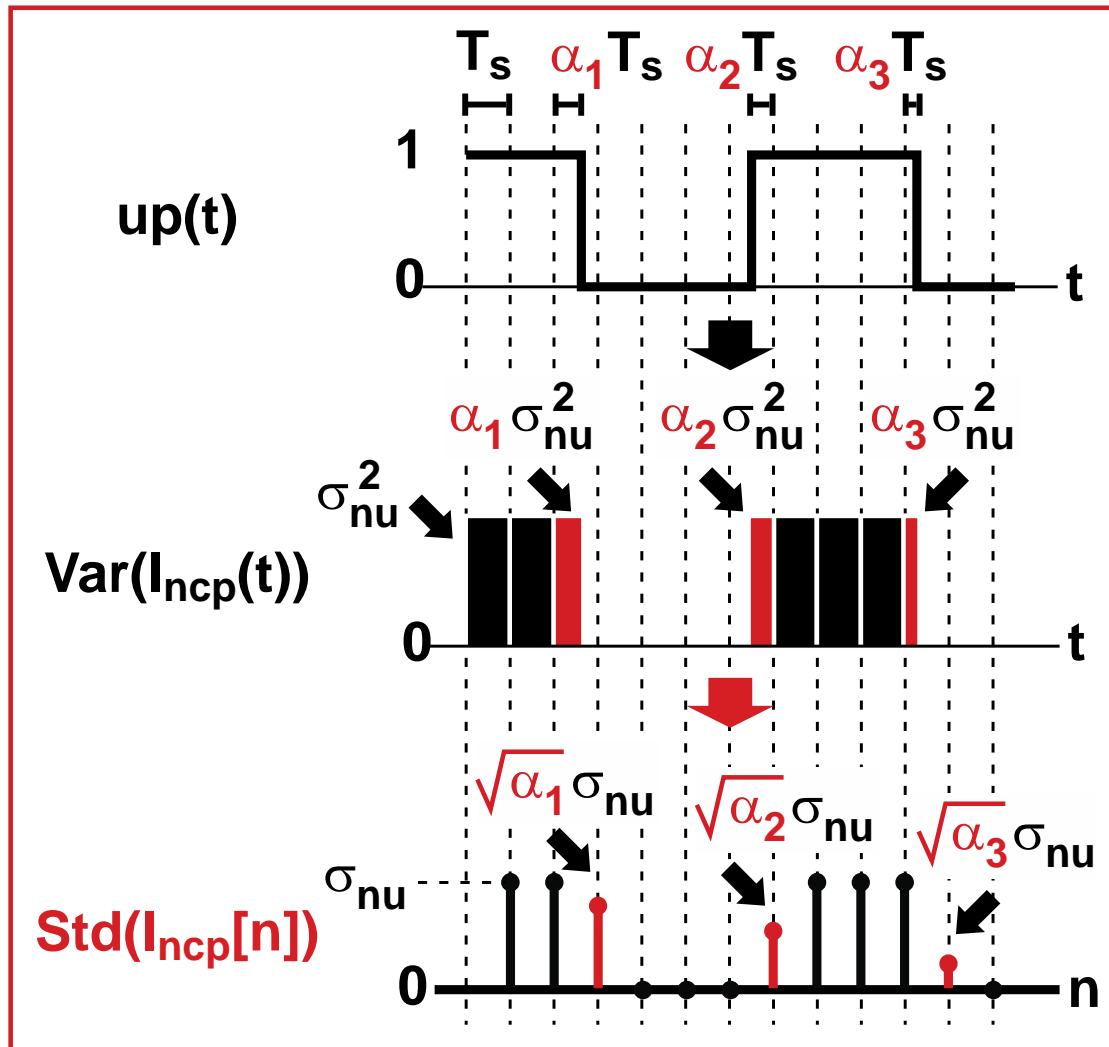Using the Double_Interp Protocol with Noise




$$\sigma_{nu}^2 = T_s \bar{I}_{nu}^{-2}$$

$$\sigma_{nu} = \sqrt{T_s \bar{I}_{nu}^{-2}}$$


- Standard deviation of noise samples impacted by edges
 - Standard deviation scaled by sqrt of “ α ” value for edge time
 - “ α ” value determined using double_interp protocol value

Example: Charge Pump Noise for XOR PD

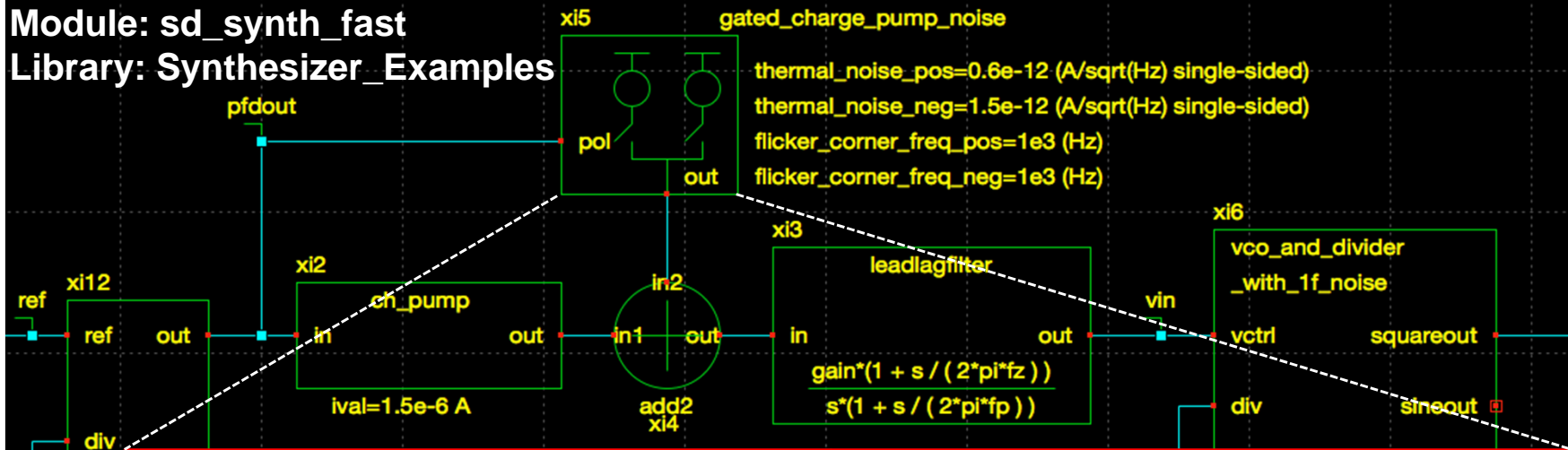


```
pos_noise_val = pos_noise_scale*pos_noise.inp();  
neg_noise_val = neg_noise_scale*neg_noise.inp();  
  
if (pol == 1.0)  
    out = pos_noise_val;  
else if (pol == -1.0)  
    out = neg_noise_val;  
else if (pol >= -1.0 && pol <= 1.0)  
{  
    interp_val = (1.0 + pol)/2.0;  
    out = sqrt(interp_val)*pos_noise_val + sqrt(1.0 - interp_val)*neg_noise_val;  
}  
else  
    out = 0.0;
```

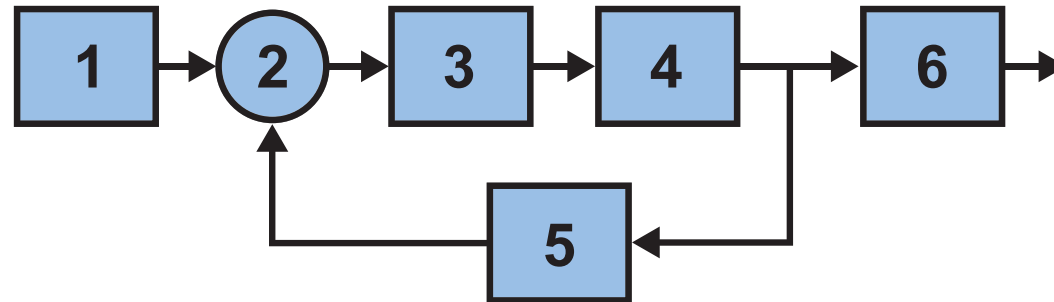Summary of Block-by-Block Computation Method



- Requires unilateral flow through blocks
- Impacts phase margin of feedback loops
 - Need $1/T_s \gg$ bandwidth of feedback loop
 - Need proper ordering of blocks (automatic in CppSim)
- Constant time step simplifies simulation
 - Easier block descriptions
 - Frequency domain analysis become straightforward
 - Time-based signals handled with **double_interp** protocol

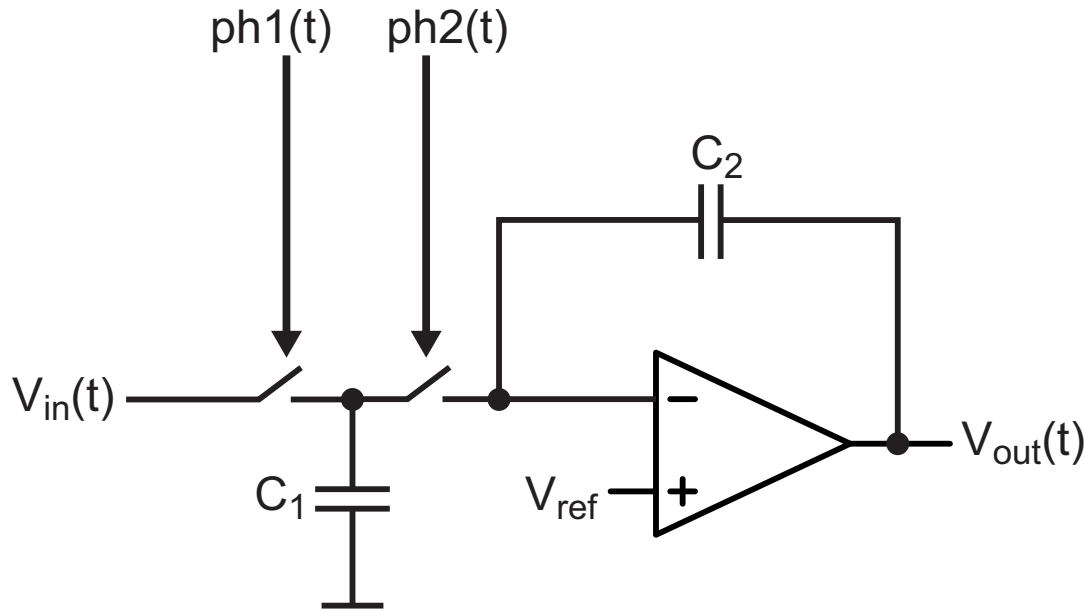
Simulation of Switched Capacitor Circuits



- **Capacitor network with switches can be modeled with unilateral flow blocks, but many practical issues:**
 - Very challenging for beginners, tedious for experts
 - Difficult to check correctness of model
 - Difficult to investigate alternative architectures


We need a way to automate the modeling process...

Automatic Unilateral Model Generation

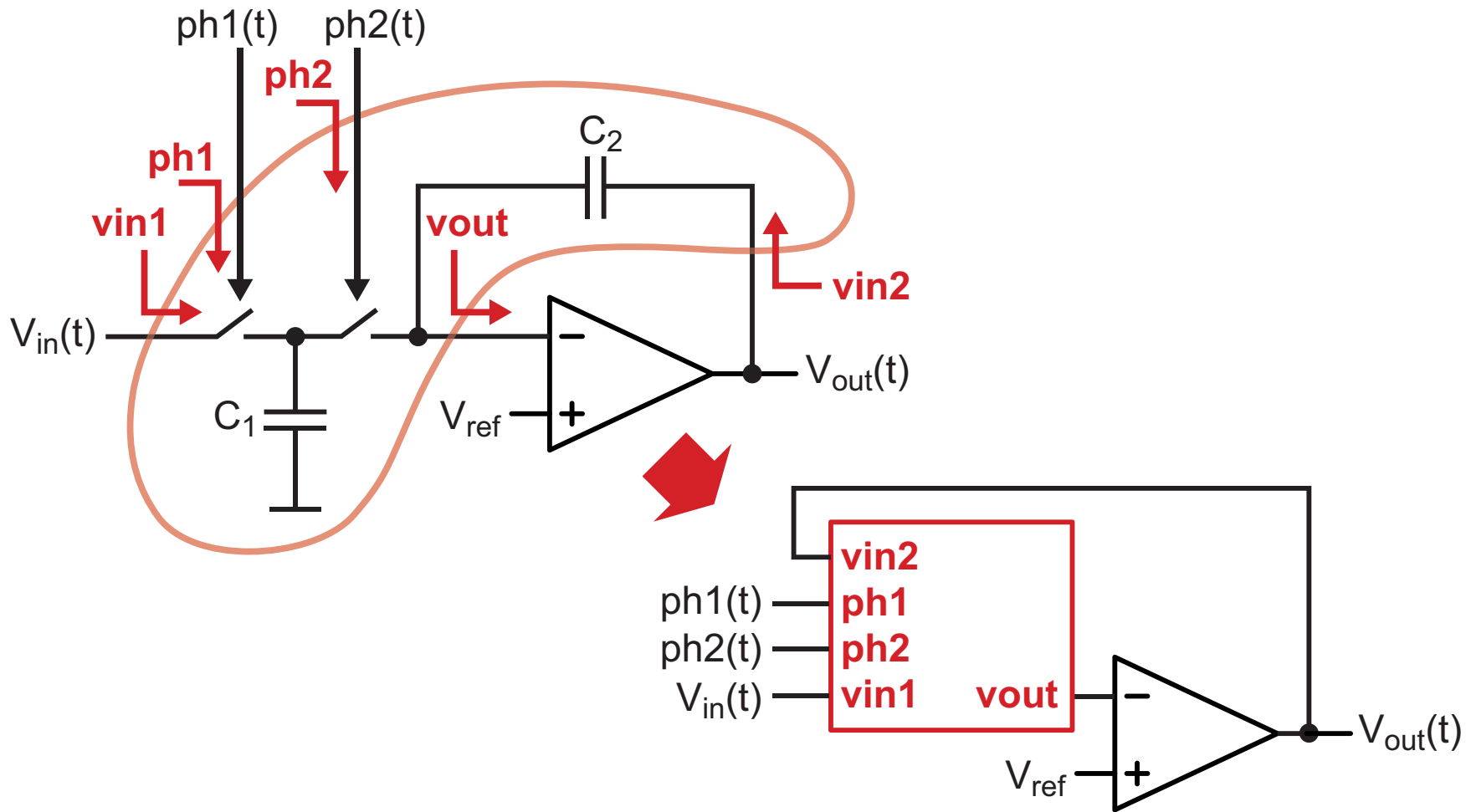


- A linear network with switches can be represented as a state-space model with switch dependent matrices
 - An equivalent unilateral flow block is created

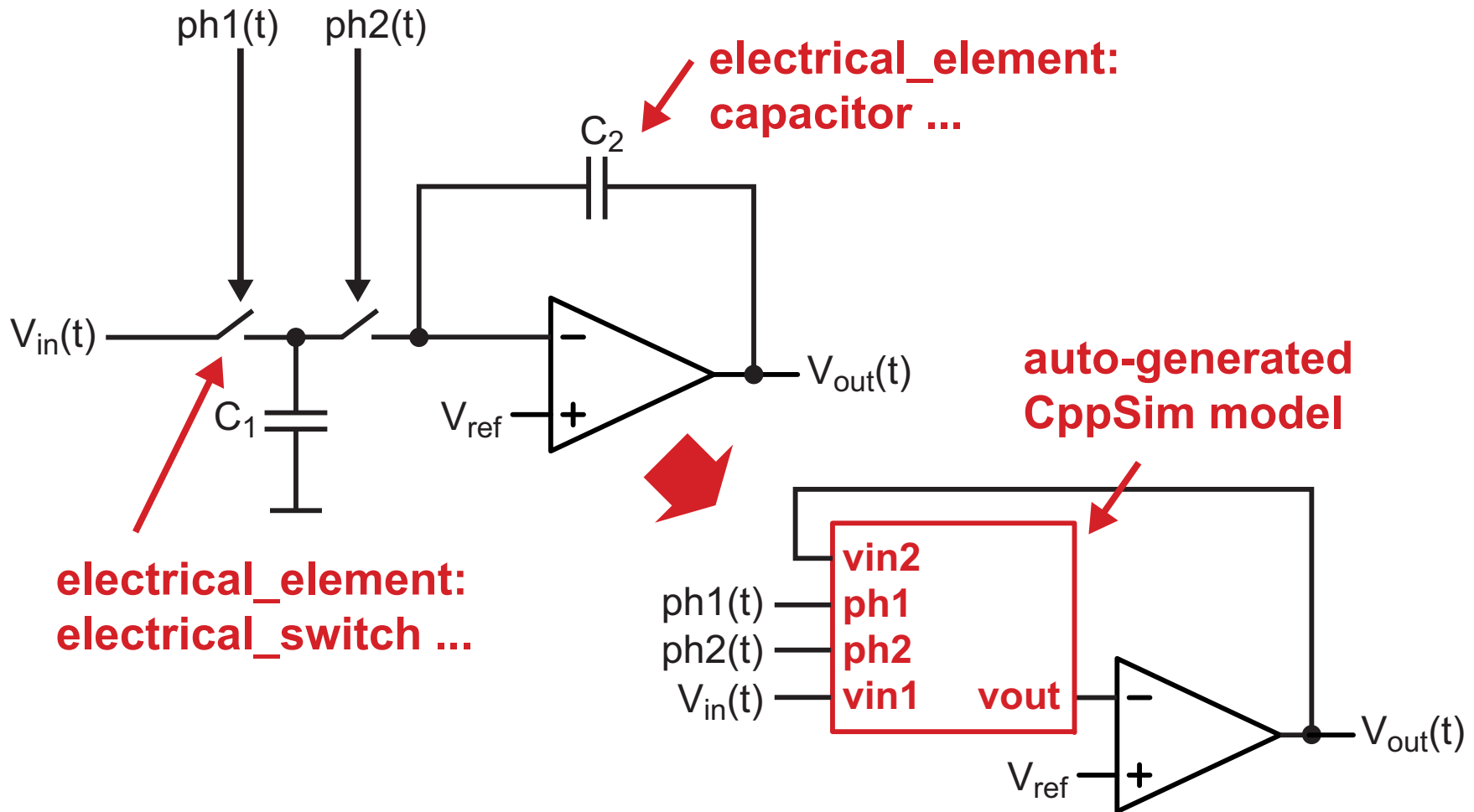CppSim Approach to Linear Networks with Switches




- User specifies the CppSim model for linear elements, switches, and diodes using **electrical_element:** command
 - ▀ Draw the schematic and CppSim takes care of the rest!

Transient Noise Analysis is Supported

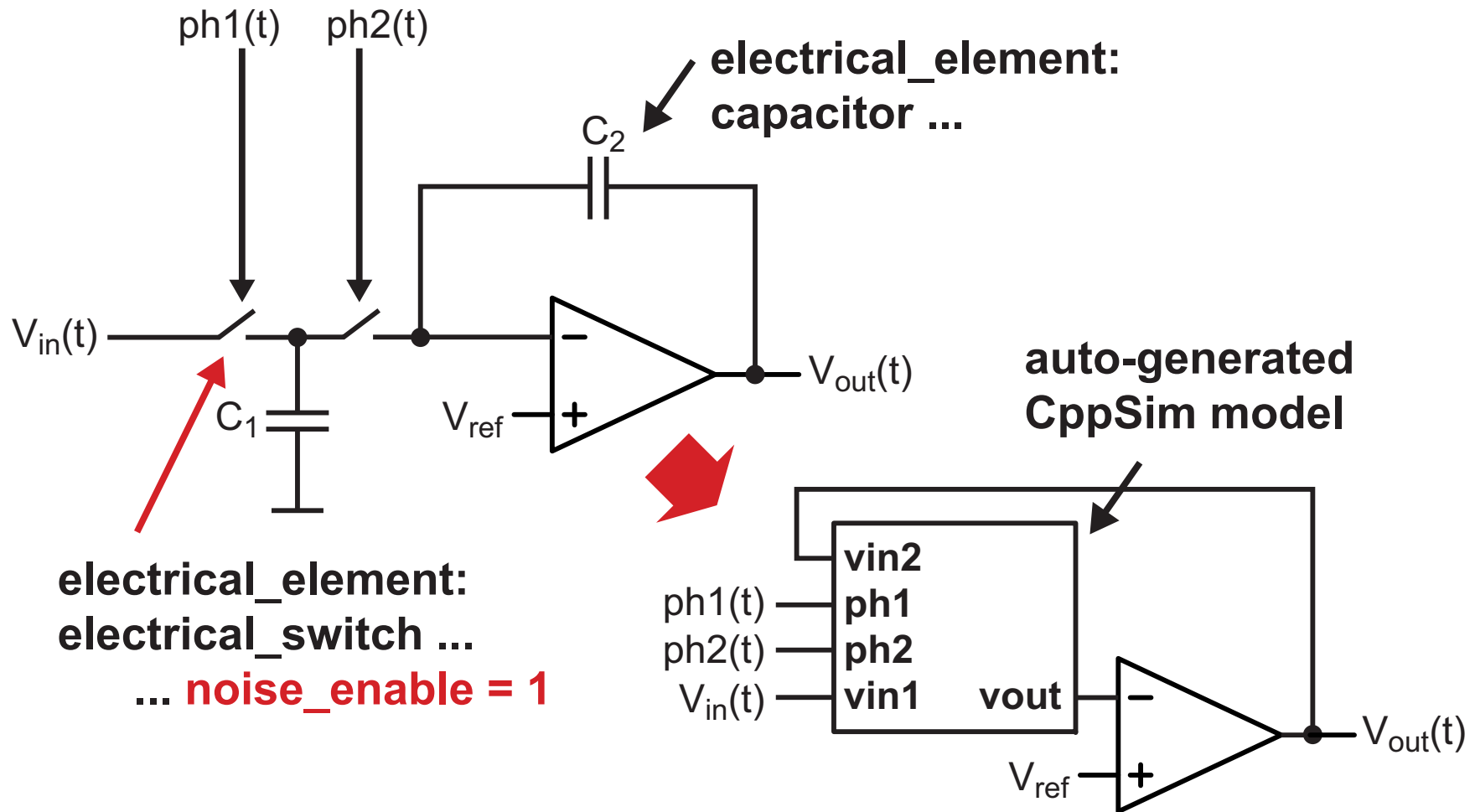


- Resistors, switches, voltage/current thermal + 1/f noise
- For kT/C noise, need adequately small time step, T_s
 - Accuracy requires $1/T_s > 20 \cdot \text{bandwidth of switch settling time}$

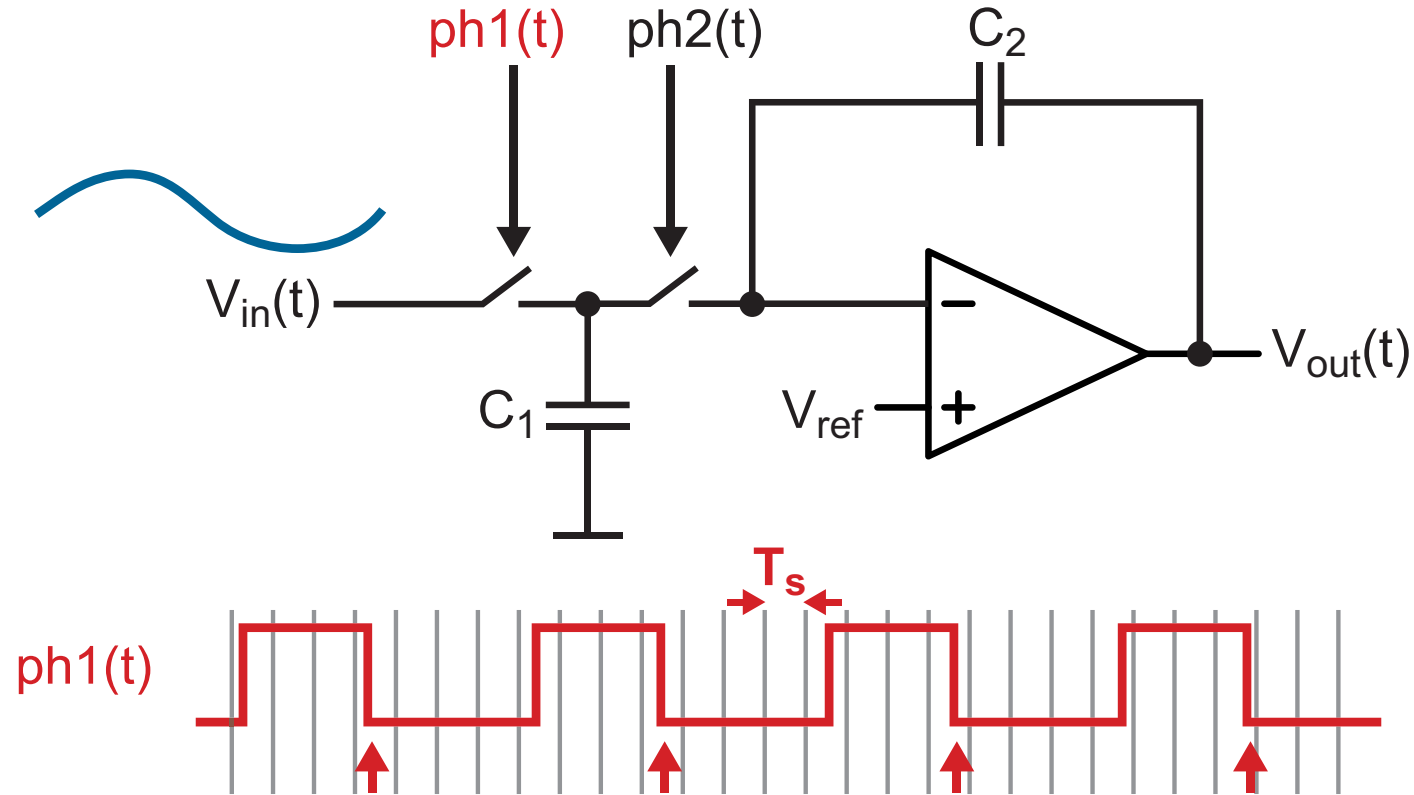Time Based Signals with Electrical Elements




- **Constant time step of CppSim could lead to quantization effects on sample times of clock edges**
 - **Would result in sampling errors of input waveform**

Leverage Double_Interp Protocol

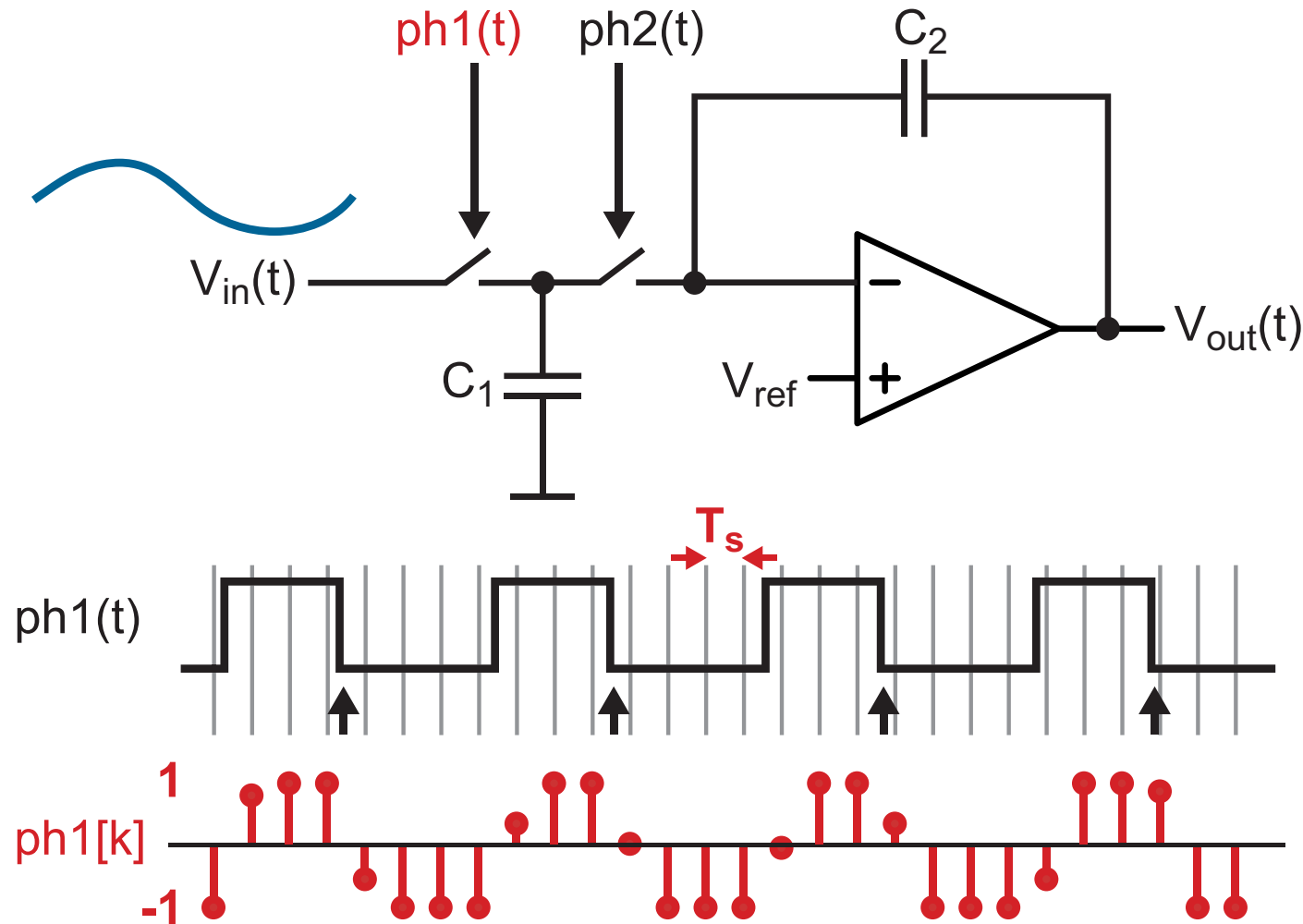


- Electrical switches within CppSim require **double_interp** signals for the control nodes
 - Good timing accuracy achieved despite constant time step

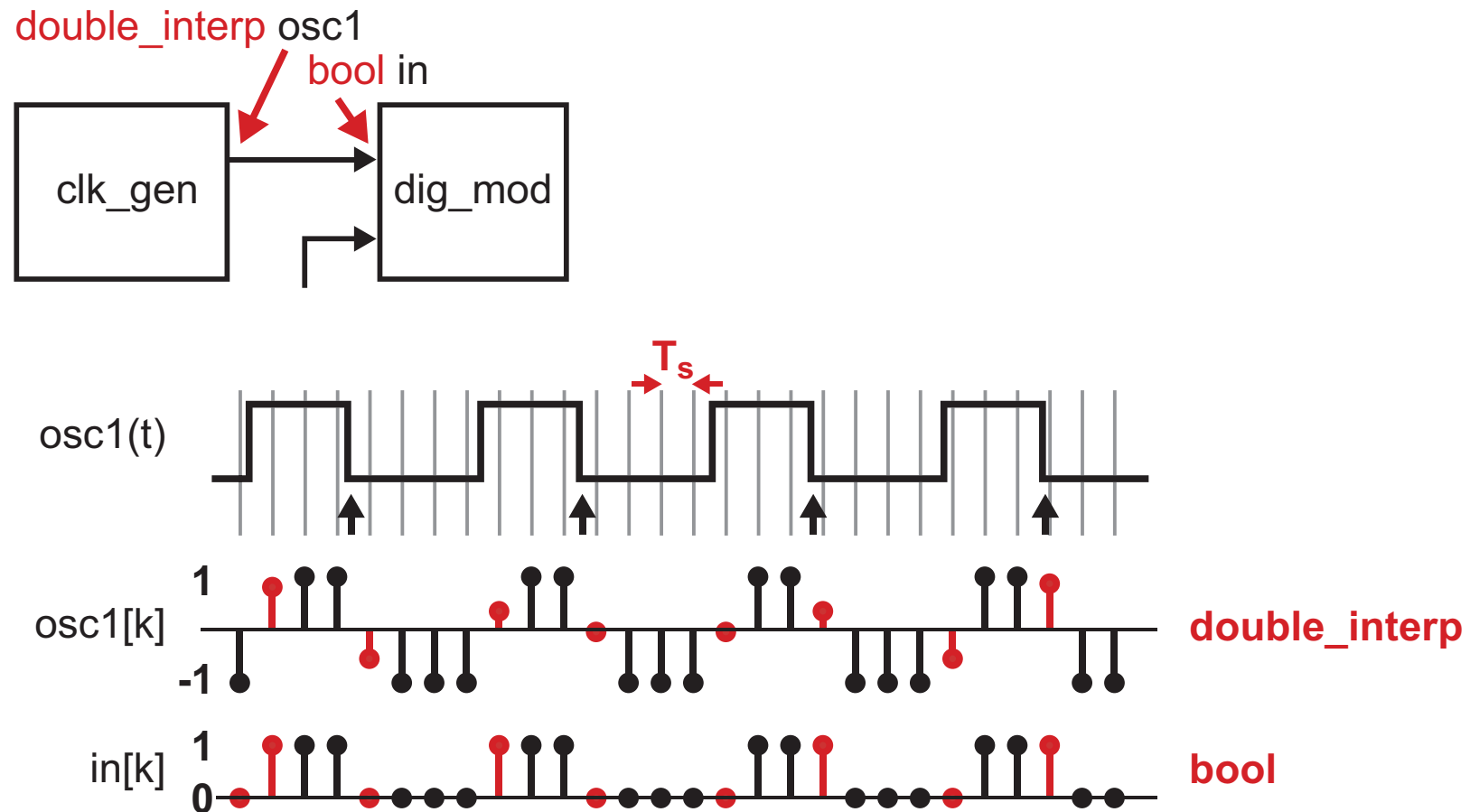Feeding Bool Input with Double_Interp Signal




- **Conversion module automatically inserted**
 - -1,1 signaling converted to 0,1 signaling
 - High resolution edge timing information is lost

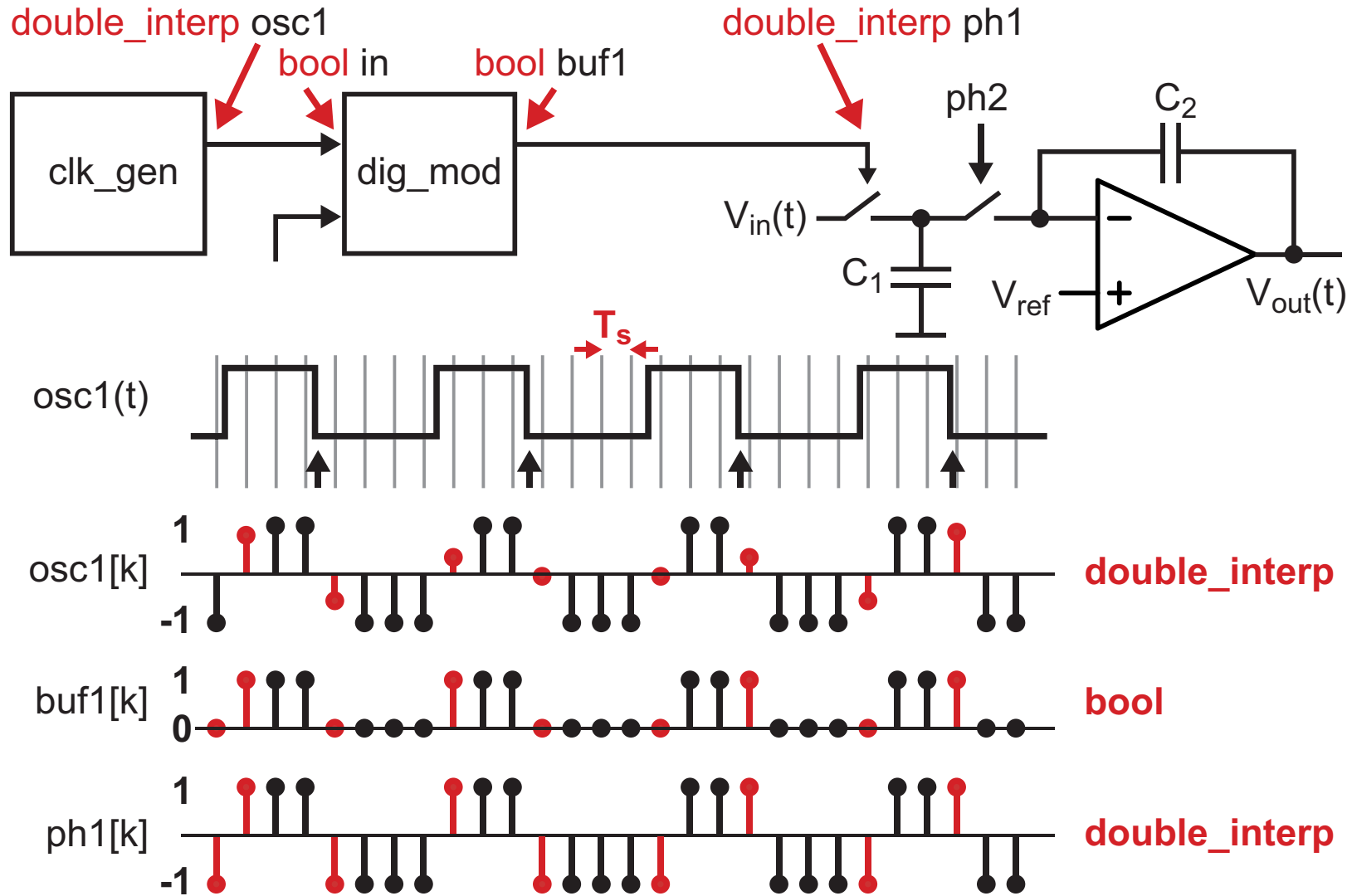Feeding Double_Interp Input with Bool Signal



- Automatic translation of 0,1 signaling to -1,1 signaling
 - Loss of timing information causes quantization noise!

Restoring Fine Timing Information

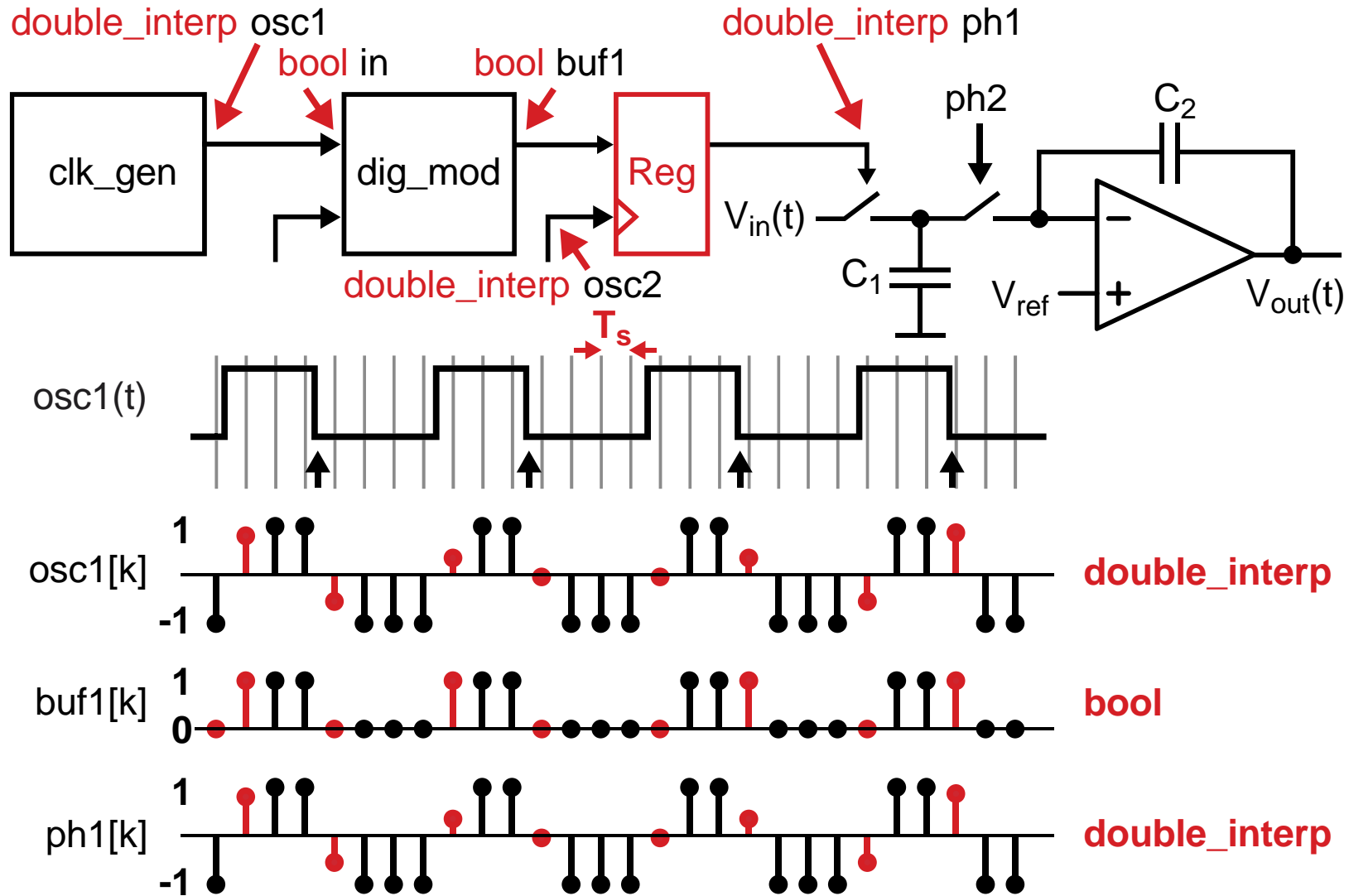

- Use `dff` or `reg_double_retime` (Library: `CppSimModules`)
 - Above figure is simplified – ignores some additional delays

Supported Electrical Elements in CppSim

resistor




capacitor




inductor




electrical_transformer

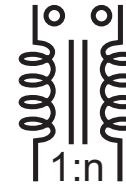


mutual_inductors

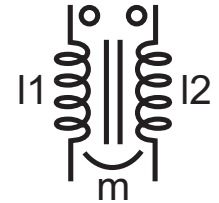


VCCS

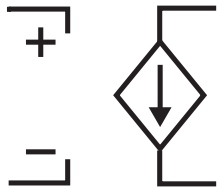


CCCS

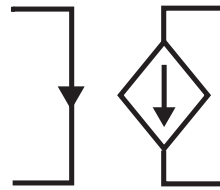


VCVS

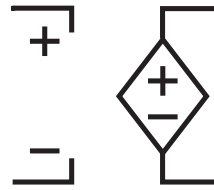

CCVS

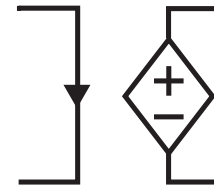

ccvs_single_out

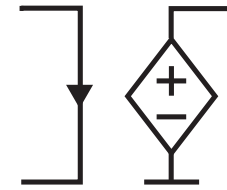

electrical_diode



electrical_switch



dc_voltage




dc_current




dc_voltage_with_noise




dc_voltage_with_noise_sq

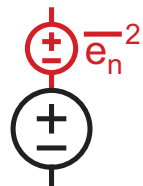


dc_current_with_noise

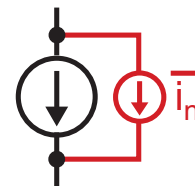

dc_current_with_noise_sq

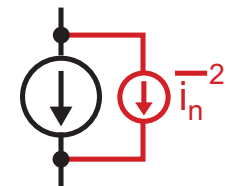

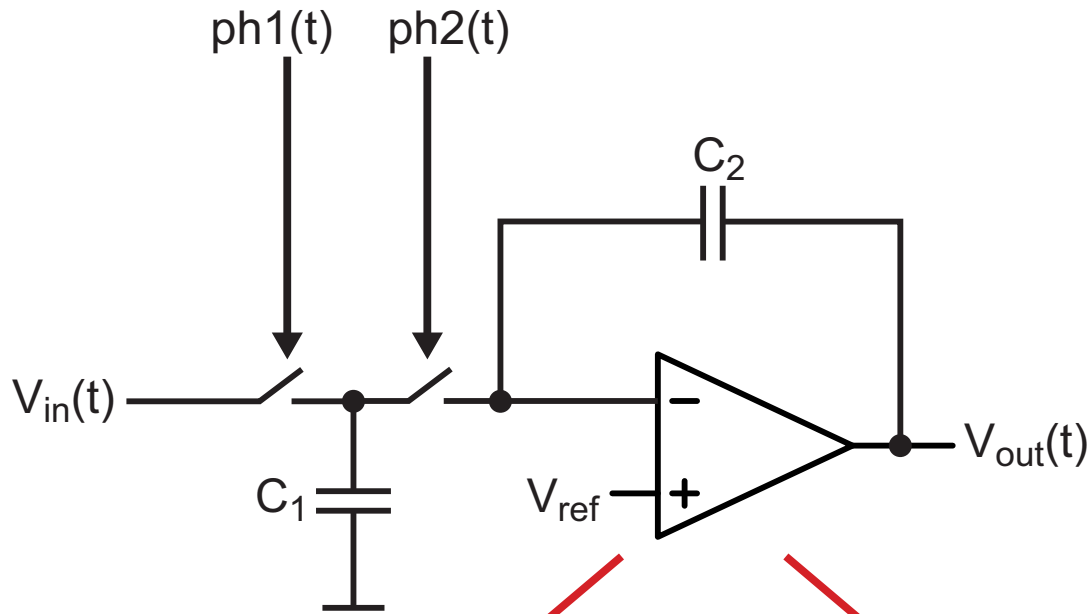
CppSim Code Versus Electrical Element Modules



code:


```
Filter filt1("K", "1+1/wo*s", ...)
      ⋮
vout = filt1(vinp-vinm)
```

electrical_element:

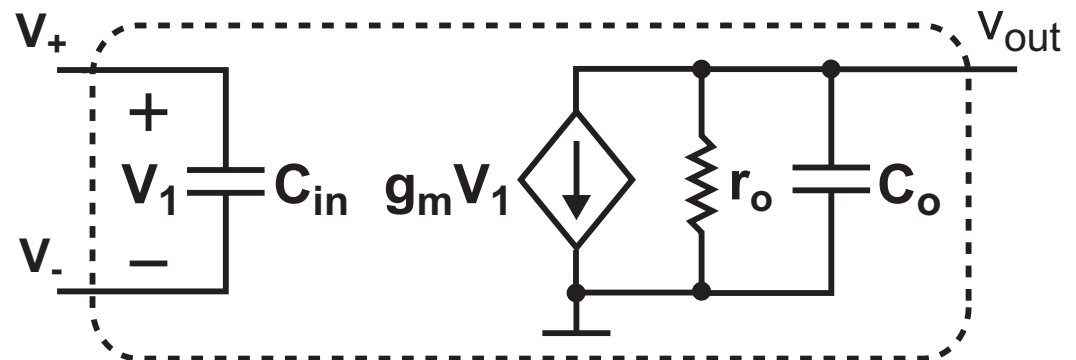


- Which approach is best for circuit blocks such as opamps?

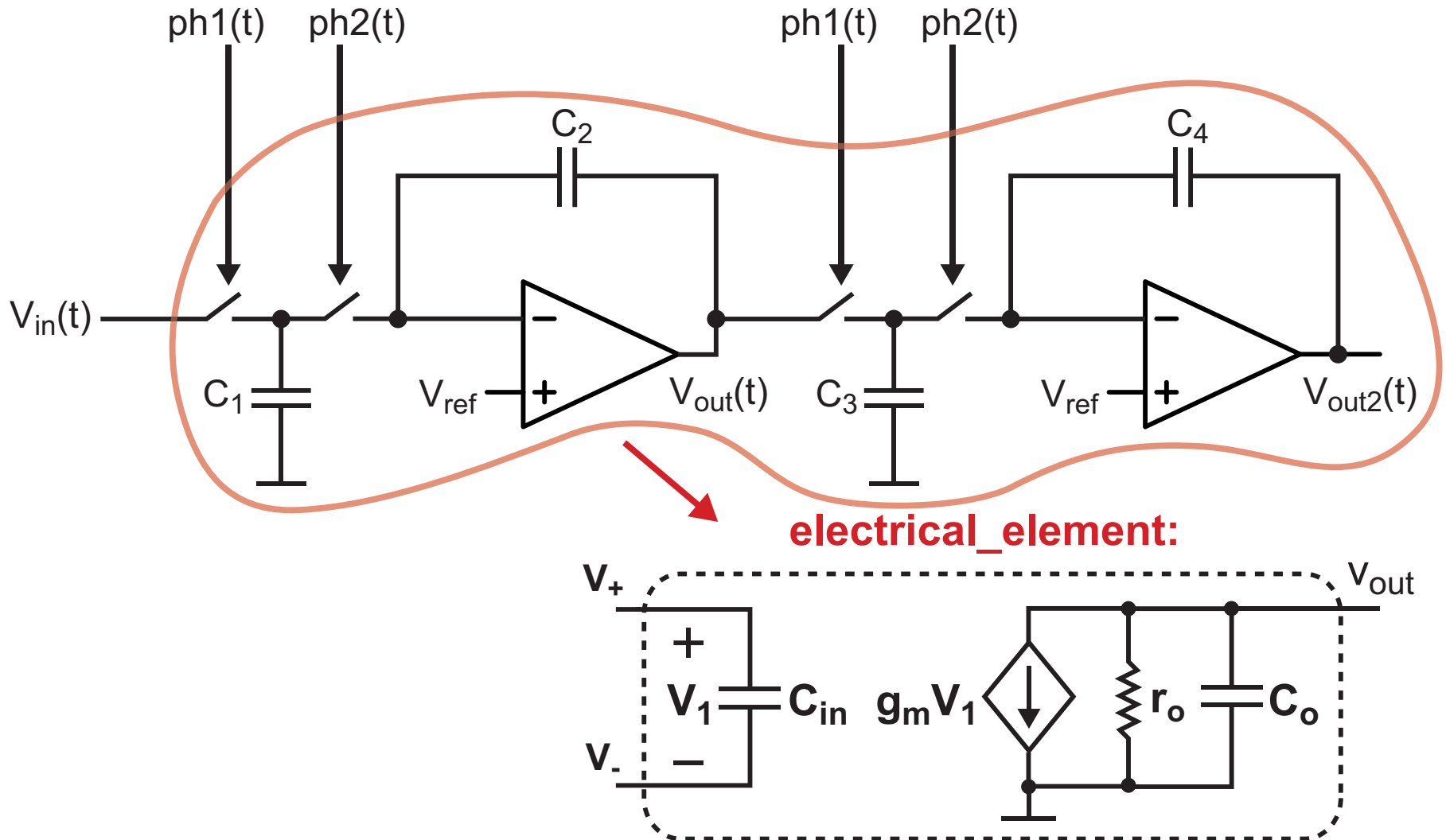Complexity Issue with Electrical Element Modules



- State-space calculations increase as (number of nodes)²
 - Large networks dramatically slow down simulation speed

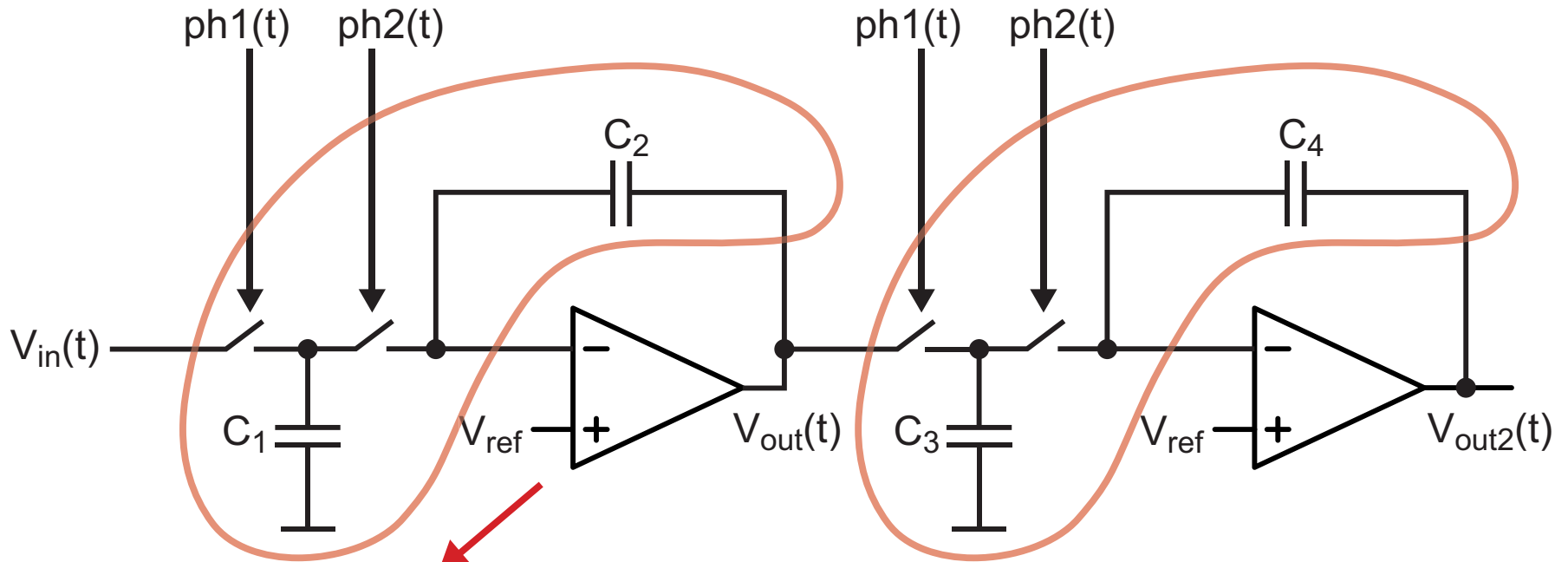Code Modules Allow De-Coupling Between Networks



code:

Filter filt1("K", "1+1/wo*s", ...)


⋮

vout = filt1(vinp-vinm)

- Code modules are not sensitive to loading
 - Allows CppSim to automatically separate into sub-networks


Code modules preferred to achieve fast simulation speed

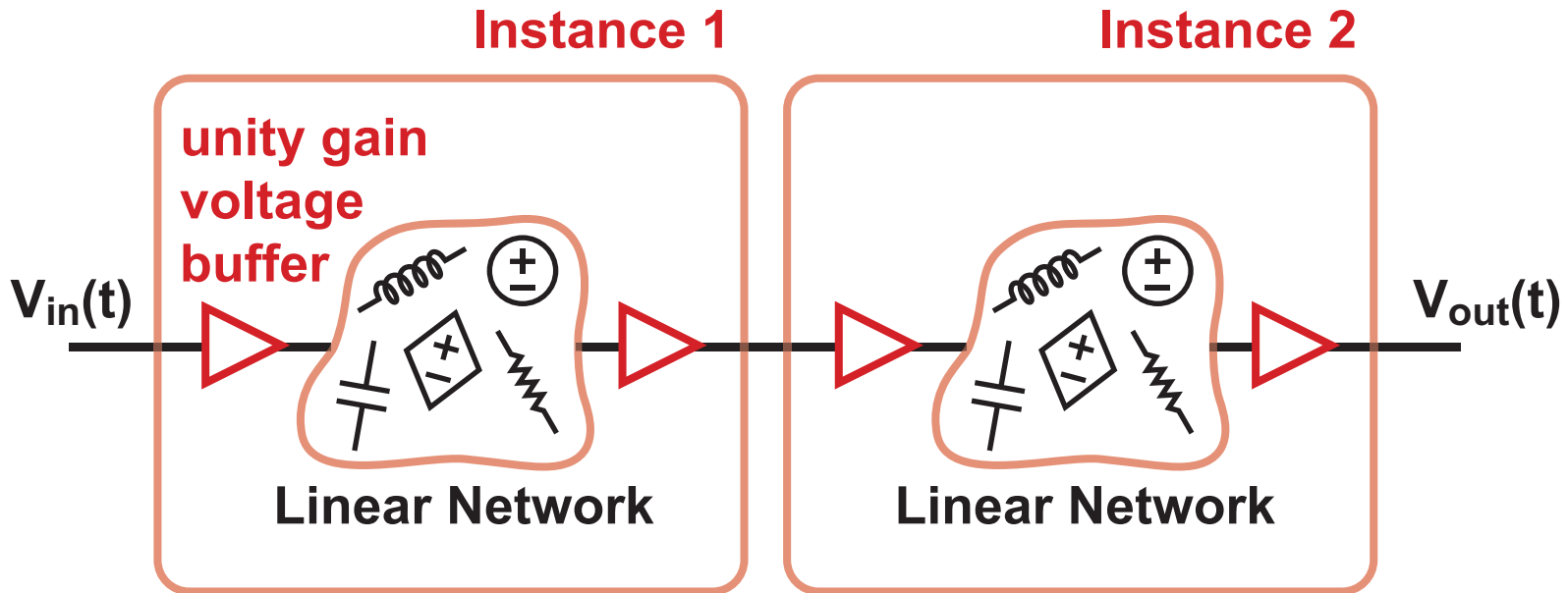Impact of Hierarchy on Electrical Element Networks




- CppSim implicitly inserts unity gain voltage buffers at all inputs and outputs of instances
 - Allows hierarchical simulation structure of overall system to be retained
 - De-couples networks at instance level to discourage creation of large state-space models

Example: A Second Order RC Network

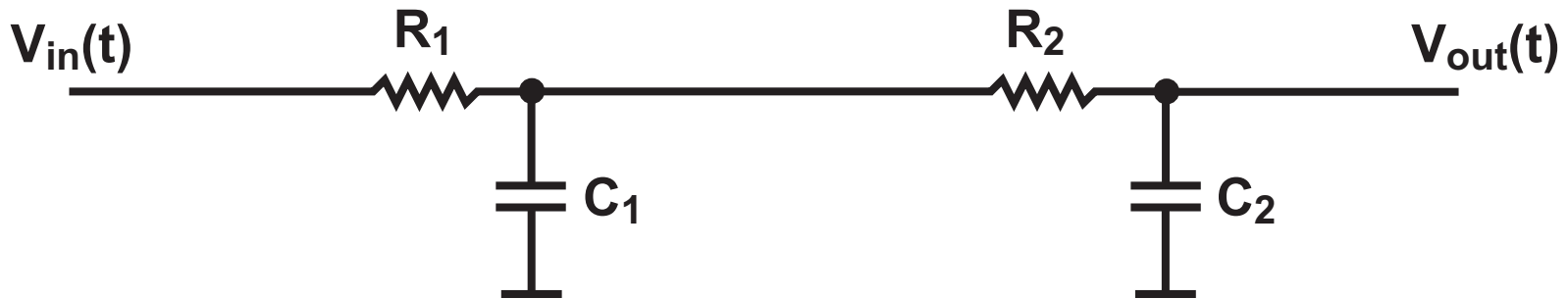


- Resulting transfer function is **NOT** simply the cascade of two identical RC filters
 - Actual pole locations are influenced by mutual coupling of the two first-order RC networks

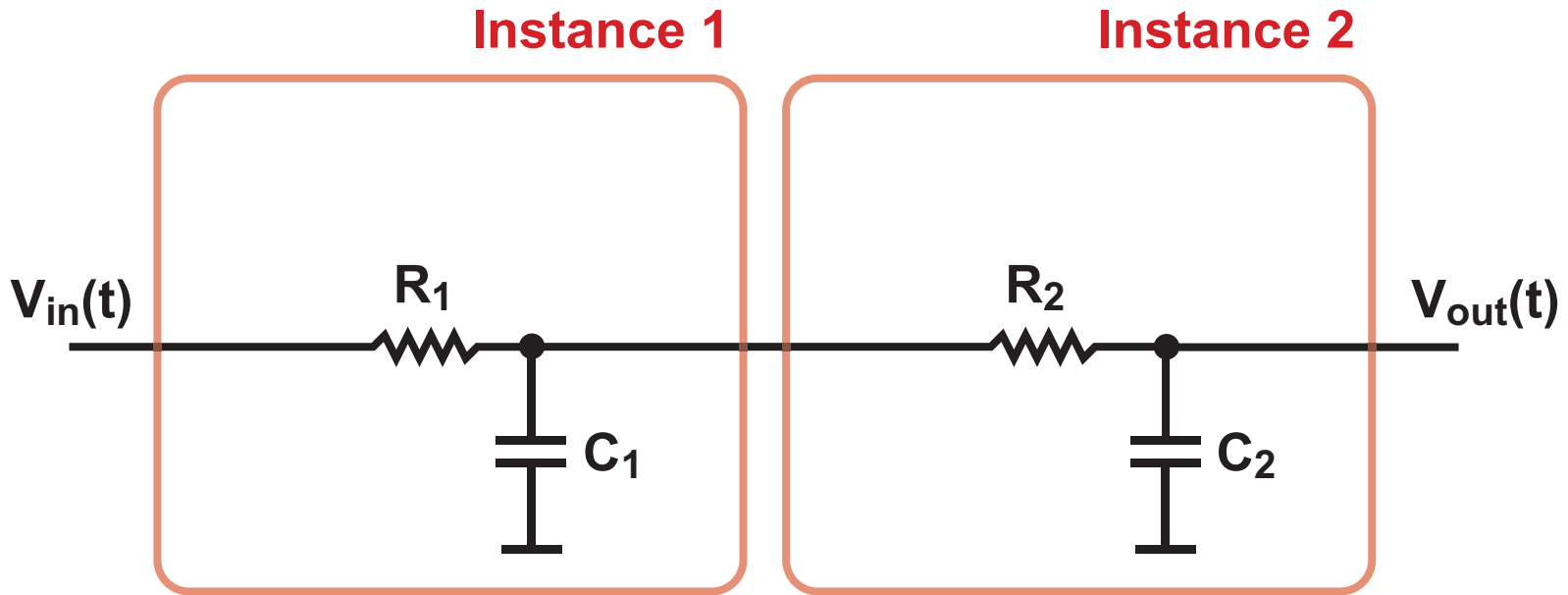Cascade of First Order RC Networks as Instances



- This would appear to be the same as cascading the RC networks at the same level of hierarchy...

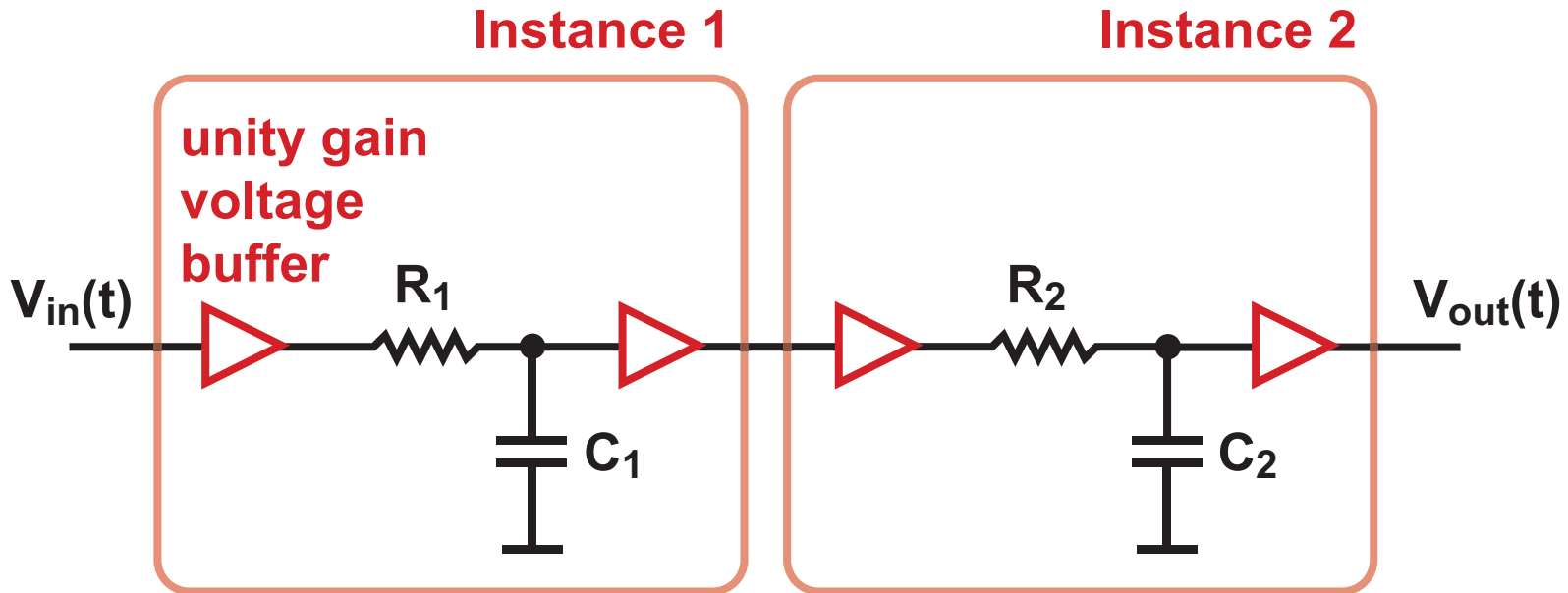
Recall Unity Gain Voltage Buffer Insertion



- CppSim implicitly adds unity gain voltage buffers
 - Resulting transfer function is actually the cascade of two identical RC filters



How do you achieve network coupling with hierarchy?

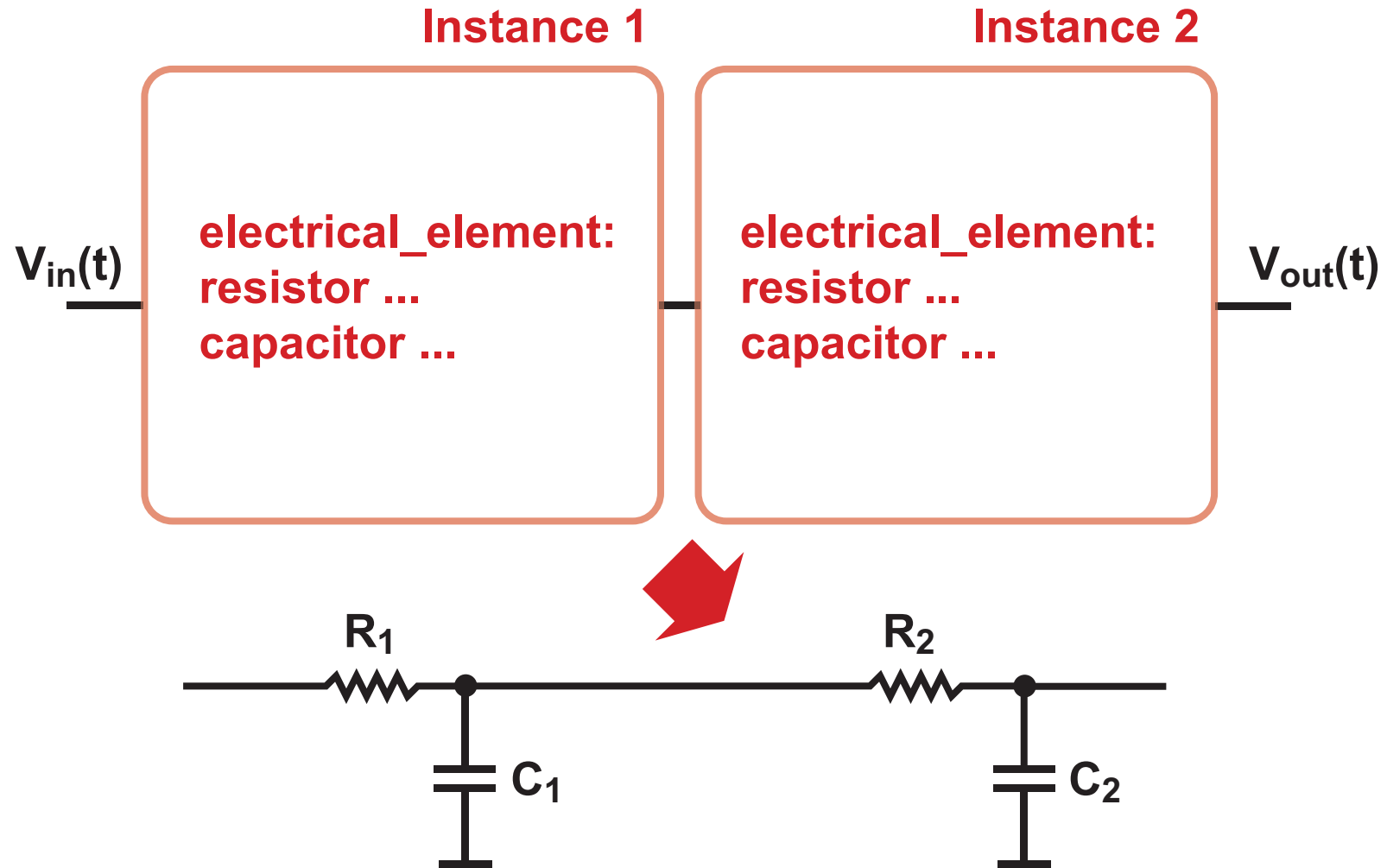Electrical Element Modules Form Coupled Networks



CppSim allows one level of hierarchy for coupled networks

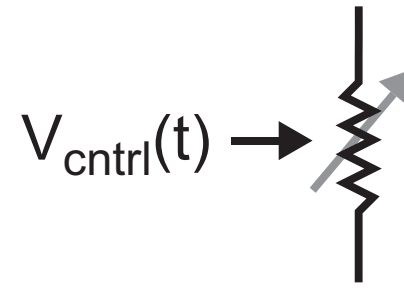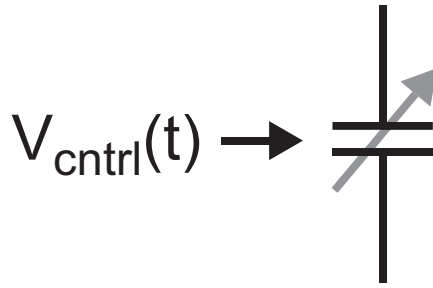Voltage-Controlled Capacitance and Resistance



- **Electrical elements are limited to linear components**
 - **Combine CppSim modules with electrical elements to create nonlinear circuits**
 - Key technique: use CppSim module to perturb the behavior of the linear electrical element based on the voltage across its terminals and the input control voltage
- **Examples are provided of voltage-controlled capacitance and resistance in CppSim (Windows/Mac)**
 - **Library: Electrical_Examples**
 - Voltage-controlled capacitance: test_varcap_electrical
 - Voltage-controlled resistance: test_var_res_electrical

Summary of Analog Modeling in CppSim

CppSim Code Modules

- Require unilateral flow but allow arbitrary analog functions including nonlinearity, filtering, hysteresis, etc.

Electrical Element Modules

- Enable straightforward modeling of linear networks with switches (and, to a more limited extent, diodes)
 - User simply creates schematic level representation
 - State-space model of network automatically created
- Fast speed retained by keeping network sizes small
 - De-coupled networks are automatically separated
 - Instances are decoupled unless they are electrical elements
- High accuracy retained for time-based circuits
 - Constant time step allows straightforward FFT analysis
 - Double_interp protocol enforced for electrical switches

CppSim versus VppSim

■ CppSim

- **C++ is the simulation engine**
 - Verilog code translated into C++ classes using Verilator
- **Best option when system simulation focuses on analog performance with digital support**

■ VppSim


- **Verilog is the simulation engine**
 - C++ blocks accessed through the Verilog PLI
- **Best option when system simulation focuses on digital verification with C++ stimulus**

Constant time step approach allows seamless connection between C++ and Verilog models

VppSim Example: Utilize CppSim Module in Verilog

CppSim module
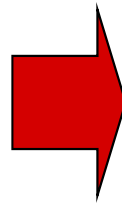
```
module: leadlagfilter
parameters: double fz, double fp,
            double gain
inputs: double in
outputs: double out
static_variables:
classes: Filter filt("1+1/(2*pi*fz)s",
                    "C3*s + C3/(2*pi*fp)*s^2",
                    "C3,fz,fp,Ts",1/gain,fz,fp,Ts);
init:
code:
filt.inp(in);
out = filt.out;
```



Resulting Verilog module for VppSim

```
////// Auto-generated from CppSim module //////
module leadlagfilter(in, out);
    parameter fz = 0.00000000e+00;
    parameter fp = 0.00000000e+00;
    parameter gain = 0.00000000e+00;
    input in;
    output out;

    wreal in;
    real in_rv;
    wreal out;
    real out_rv;


    assign out = out_rv;

    initial begin
        assign in_rv = in;
    end


    always begin
        #1
        $leadlagfilter_cpp(in_rv,out_rv,fz,fp,gain);
    end
endmodule
```

Digital Modeling in CppSim

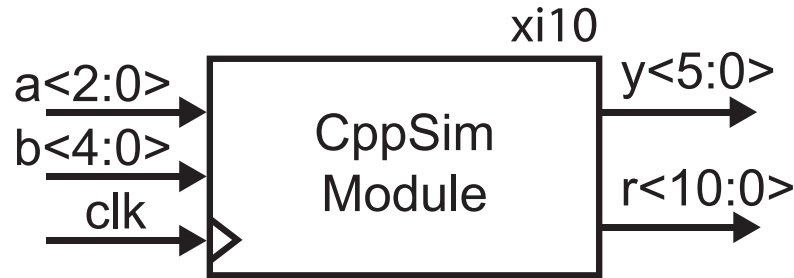Code Modules: CppSim or Synthesizable Verilog



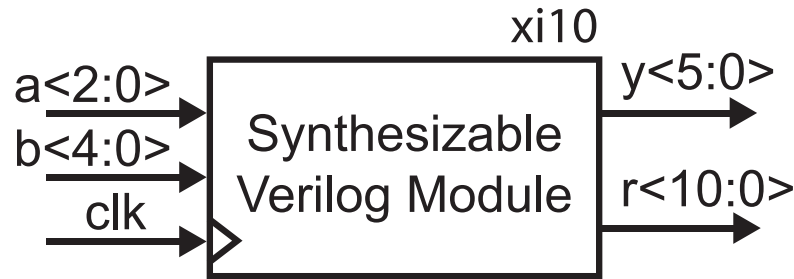
```
module: dig_mod
inputs:
bool a[2:0], bool b[4:0], bool clk
outputs:
bool y[5:0], bool r[10:0]
⋮
```



```
module dig_mod(a, b, clk, y, r);
input [2:0] a;
input [4:0] b;
input clk;
output [5:0] y;
output [10:0] r;
⋮
```

- **CppSim modules utilize bool signals**
 - Correspond to integer vectors whose elements are 0 or 1
- **Verilog modules must be synthesizable in CppSim**
 - Note: full support of Verilog in VppSim

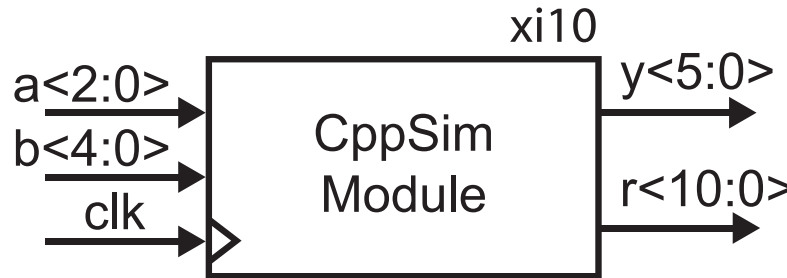Getting and Setting Boolean Signal Values (CppSim)




```
module: dig_mod
inputs:
bool a[2:0], bool b[4:0], bool clk
outputs:
bool y[5:0], bool r[10:0]
⋮
```

```
a_dec = a.get_decimal_value(); // full bit range (a[2:0])
b_dec = b.get_decimal_value(3,1); // limited bit range (b[3:1])
b_bit1 = b.get_elem(1); // get b[1]
⋮
y.set_decimal_value(15); // full bit range (y[5:0] = 15)
r.set_decimal_value(21,7,2); // limited bit range (r[7:2] = 21)
r.set_elem(8,1); // set r[8] = 1
```

- **Bool signals: integer vectors with element values of 0 or 1**
 - Support functions such as `get_elem()`, `set_elem()`, etc.
 - For convenience: `get_decimal_value()`, `set_decimal_value()`
 - Restricted to 32-bit values

Implementing Clock Edge Based Processing

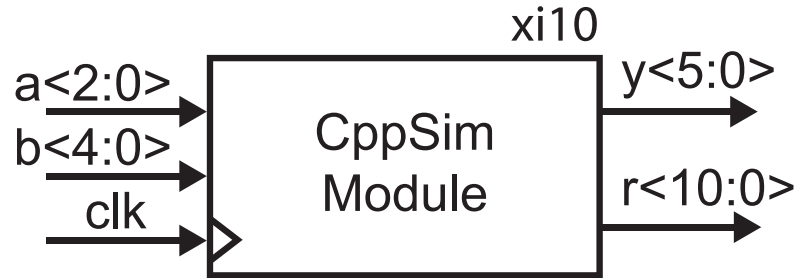

```
module: dig_mod
inputs:
bool a[2:0], bool b[4:0], bool clk
outputs:
bool y[5:0], bool r[10:0]
⋮
```

```
EdgeDetect pos_clk_edge()
EdgeDetect neg_clk_edge()
```

```
timing_sensitivity: posedge clk
```

```
code:
if (pos_clk_edge.inp(clk))
{
    ⋮
}
if (neg_clk_edge.inp(-clk))
{
    ⋮
}
```

```
code:
⋮
```

- **timing_sensitivity:** clk must be of type **bool**
- **EdgeDetect:** clk must be of type **double_interp**

EdgeDetect() versus timing_sensitivity: for VppSim

EdgeDetect (simplified)

```
///// Auto-generated from CppSim module /////  
module dig_mod(a,b,clk,y,r);
```

```
    always begin  
        #1  
        $dig_mod_cpp(a,b,clk,y,r);  
    end  
endmodule
```

- **PLI routine is called every time step**
 - Dramatically slows down VppSim!

timing_sensitivity:


```
///// Auto-generated from CppSim module /////  
module dig_mod(a,b,clk,y,r);
```

```
    always@(posedge clk) begin  
        $dig_mod_cpp(a,b,clk,y,r);  
    end  
endmodule
```

- **PLI routine is only called on positive clk edges**
 - Much less impact on simulation speed

Use **timing_sensitivity**: unless you need to perform computation during every time step
(Note: no penalty for **EdgeDetect** method in CppSim)

Buses, Bundles, and Iterated Instances

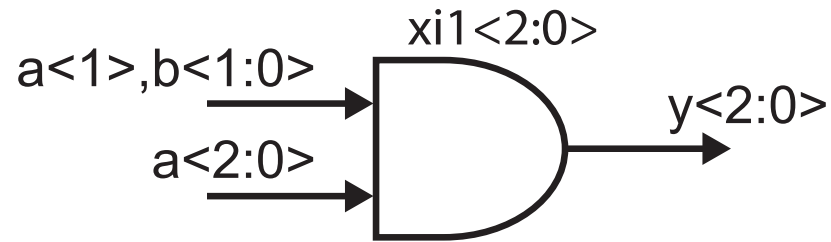

- **Basic conventions supported**
 - Iterated instance: $xi1<2:0>$
 - Bus: $a<2:0>$
 - Bundle: $a<1>, b<1:0>$
- **Key rules for bused signals:**
 - **Code modules: buses only valid for type `bool`**
 - Exception for `electrical_element` modules:
 - Declare as `bool`, but actual type becomes `double`
 - **Schematic signals: buses can be any type**

VppSim Example: Using Buses in CppSim Module

CppSim module

```
module: queue2
parameters: int bit_width
inputs:    double_interp clk,
           double rst_n,
           bool in[2047:0],
           int enqueue,
           bool dequeue[31:0]
outputs:  bool out[2047:0],
           bool not_empty[31:0],
           int not_full
```



Resulting Verilog module for VppSim

```
////////// Auto-generated from CppSim module //////////
module queue2(clk, rst_n, in, enqueue,
              dequeue, out, not_empty,
              not_full);

    parameter bit_width = 0;
    input clk;
    input rst_n;
    input [2047:0] in;
    input [31:0] enqueue;
    input [31:0] dequeue;
    output [2047:0] out;
    output [31:0] not_empty;
    output [31:0] not_full;


    wreal clk;
    real clk_rv;
    wreal rst_n;
    real rst_n_rv;
```



Summary of Digital Modeling


- Verilog or CppSim code modules are supported
 - CppSim simulator: Verilog must be synthesizable code
 - VppSim simulator: Verilog is fully supported
- Key constructs for CppSim modules:
 - **bool** signal type allows bus notation
 - **timing_sensitivity**: advantageous for VppSim simulator
- Buses, bundles, and iterated instances supported
- Care should be taken to avoid introducing timing quantization noise when passing digital signals back to analog
 - Conversion of **double_interp** signals to type **bool** leads to loss of high resolution timing information of edges

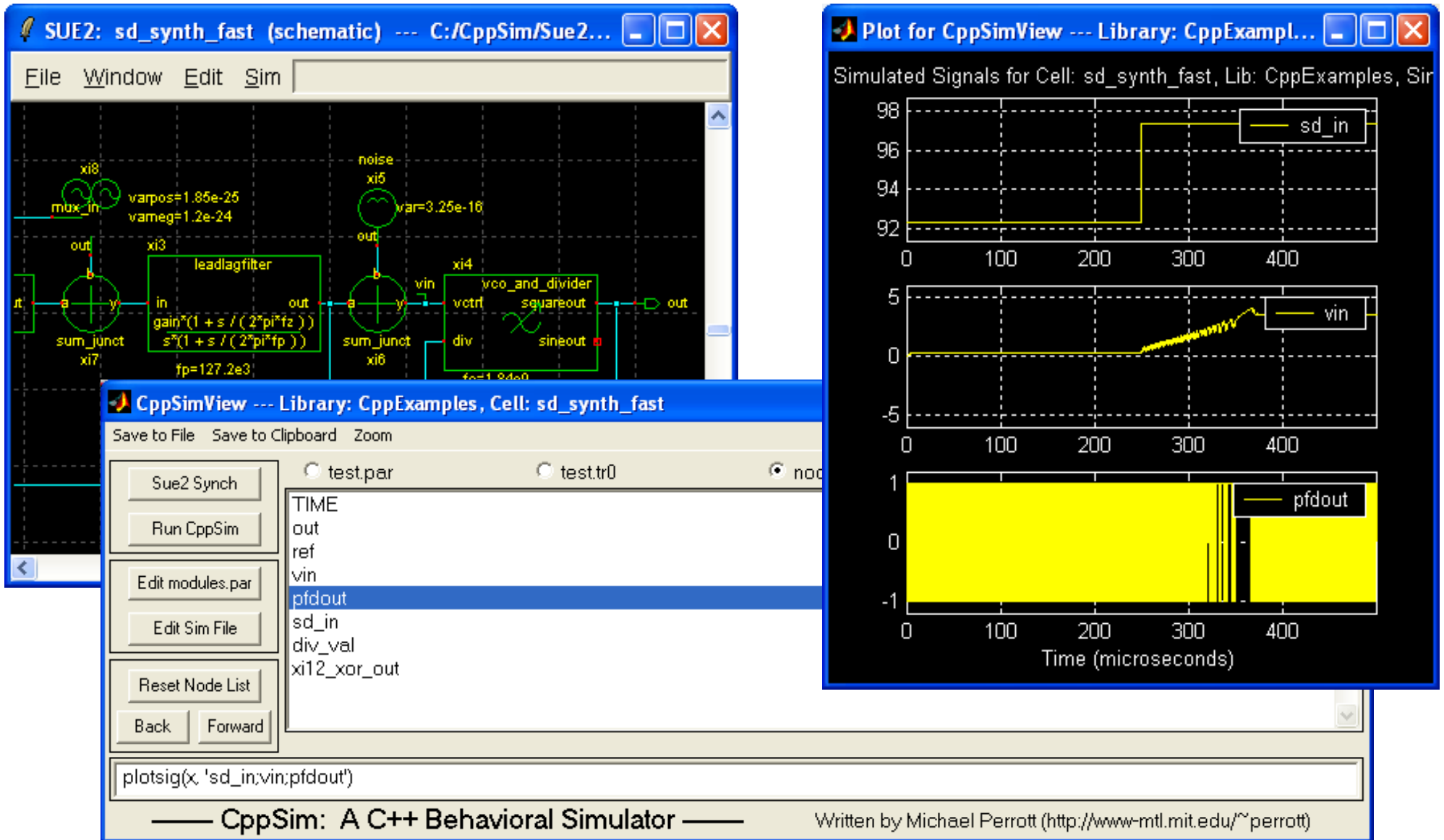Screenshot of CppSim/VppSim (Windows Version)



Readily Interfaces with Matlab and GTKWave

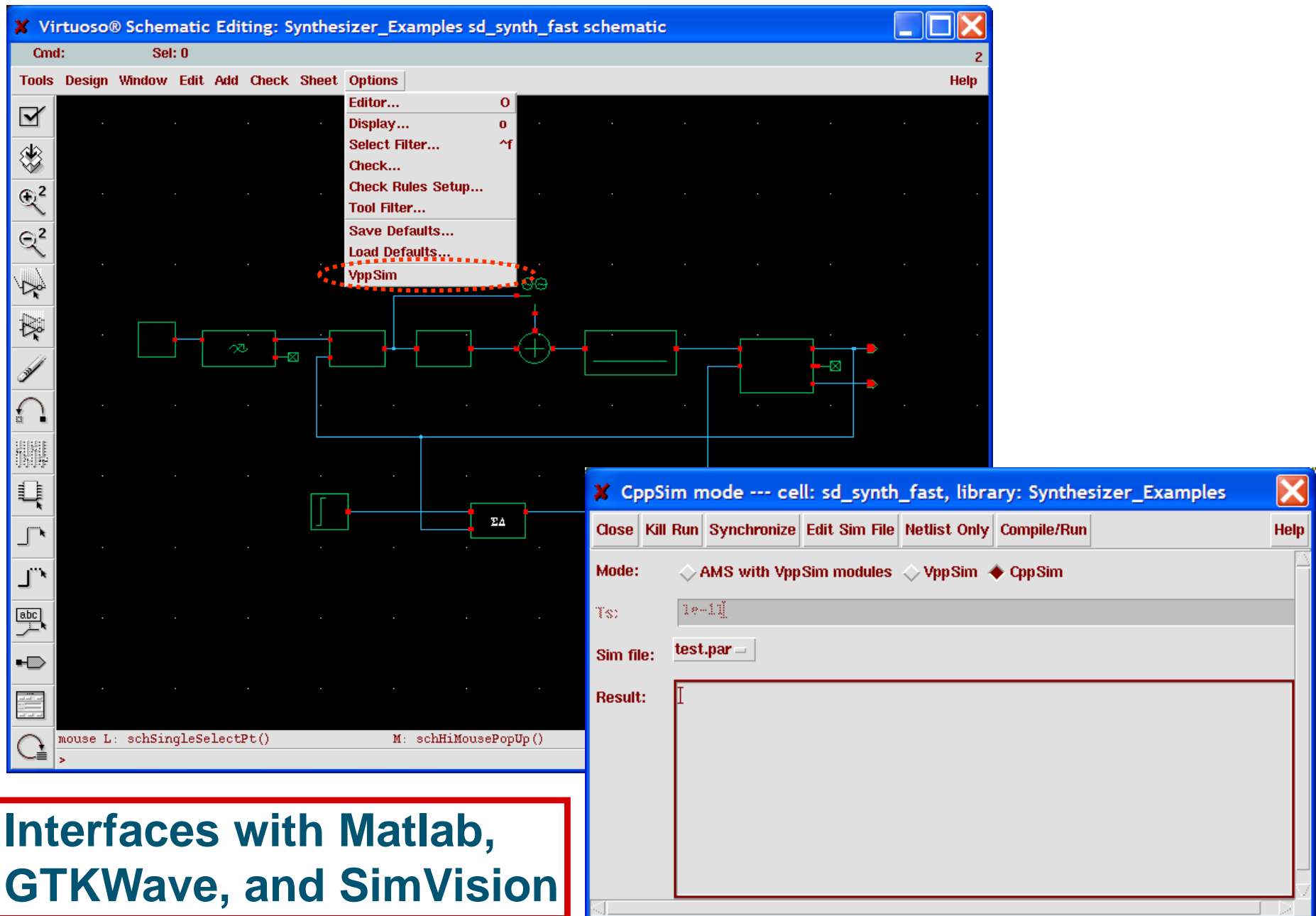Screenshot of CppSim/VppSim (Cadence Version)



Free Download at www.cppsim.com



The screenshot shows a web browser window with the address bar displaying www.cppsim.com. The website features a navigation menu with links for Home, Download, About, Manuals, Tutorials, Publications, and Lectures. A central banner with a blue background and glowing circuit lines contains the text: "Discover a faster and easier way to perform system level simulation of complex mixed-signal circuits." Below the banner are six circular icons representing the site's features: Download, About, Manuals, Tutorials, Publications, and Lectures. A testimonial box on the left contains a quote about the challenges of timing simulation. The main content area highlights that CppSim automatically generates, compiles, and runs C++ code based on schematic designs, and lists three key features: Graphical Interface, Analog modules, and Digital modules.

CppSim System Simulator

Home Download About Manuals Tutorials Publications Lectures

Discover a faster and easier way to perform system level simulation of complex mixed-signal circuits.

Download About Manuals Tutorials Publications Lectures

"Designing precision timing circuits that exhibit grossly non-linear behavior requires performing accurate simulations in the time domain. Such simulations take prohibitively long, even in commercial behavioral simulators, which have often limited our ability to evaluate new PLL, CDR, and ADC architectures in the past. CppSim and its Cadence compatibility have filled this void and have been instrumental in the design of

CppSim automatically generates, compiles, and runs C++ code corresponding to the schematic design that you create.

- Graphical Interface:** Systems are specified and simulated within a schematic editor, Sue2, and results are viewed using a waveform viewer (CppSimView or GTKWave).
- Analog modules:** A simple text template for each module is filled in by the user which can make use of a rich set of C++ classes to represent common functions such as filtering, noise, etc.
- Digital modules:** CppSim utilizes Verilator to automatically create C++ code corresponding to your Verilog modules, and seamlessly integrates this code into your system simulation.

Many Tutorials Available for CppSim/VppSim


- **Switched Capacitor 2nd Order Delta-Sigma ADC**
- **Phase Locked Loops (Analog and Digital)**
- **VCO-based ADCs**
- **GMSK modulator**
- **Decision Feedback Equalization**
- **Optical-Electrical Downversion and Digitization**
- **OFDM Transceiver**

 **See <http://www.cppsim.com>**

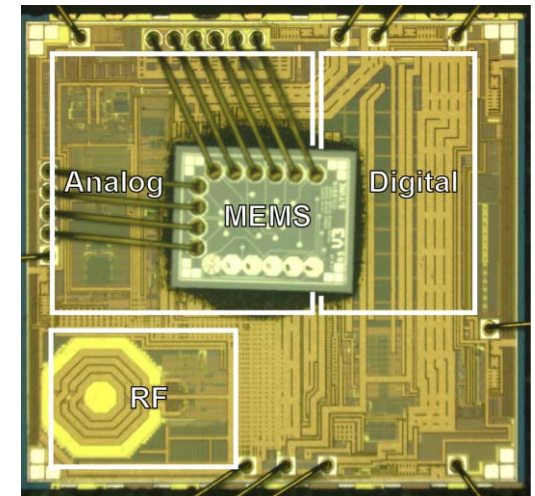Example Benchmarks for a Full Chip Simulation

Tabulated simulation times for a MEMS-based oscillator:

- **SPICE-level** model
 - Checking of floating gate, over-voltage, startup of bandgap and regulators, etc.
 - Spectre Turbo: 2 microseconds/day
 - BDA: **8 microseconds/day**
- **Architectural** model using CppSim
 - Examination of noise and analog dynamics
 - **2.8 milliseconds/hour**
- **Verification** model using VppSim
 - Validation of digital functionality in the context of analog control and hybrid digital/analog systems
 - **7 milliseconds/minute**



Conclusion

- **CppSim is designed for high productivity and versatility**
 - **Easy to create your own code blocks**
 - Use existing modules to see examples, but don't limit yourself to what is available
 - **Allows very detailed modeling of complex circuits**
 - You are not confined to an overly simplified model
 - **Invites a scripted approach to running simulations**
 - Excellent integration with Matlab/Octave and Python
 - **Runs in Windows, Mac OS X, or within Cadence**
 - Has been used to simulate entire ICs in Cadence
- **Extensive 14 year track record of enabling new circuit architectures with first chip success**