


***Short Course On
Phase-Locked Loops and Their Applications
Day 2, PM Lecture***

***Basic Building Blocks (Part II)
High Speed Frequency Dividers, Phase Detectors,
Charge Pumps, and Loop Filter Design***

**Michael Perrott
August 12, 2008**

**Copyright © 2008 by Michael H. Perrott
All rights reserved**

Fractional-N Frequency Synthesis

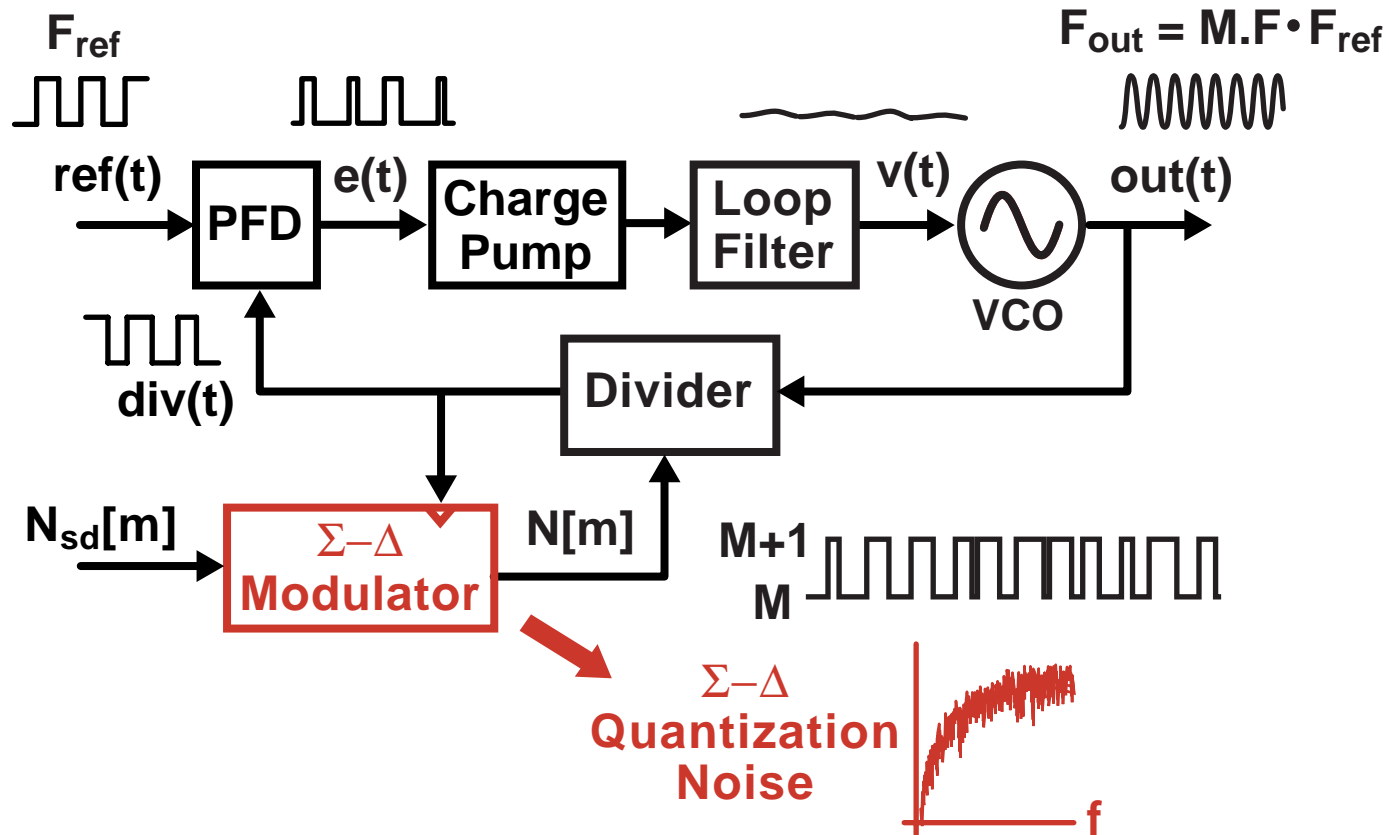

■ Challenging building blocks


- VCO
- Divider
- Charge Pump (and PFD)

Outline of Talk

- **High speed frequency dividers**
 - **Background of key digital building blocks**
- **PFD and Charge Pumps**
- **Loop filter design**
 - **Closed loop PLL design using CAD**


Digital Background for Dividers

Edge-triggered Registers

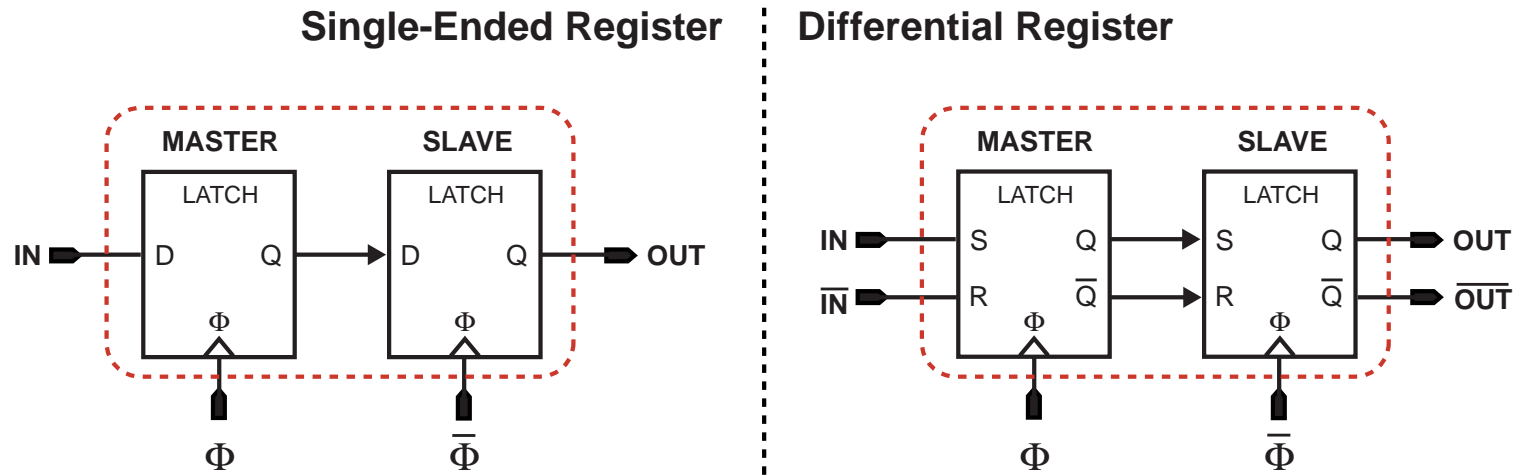


- Achieved by cascading two latches that are transparent out of phase from one another
- Two general classes of latches
 - Static – employ positive feedback
 - Robust
 - Dynamic – store charge on parasitic capacitance
 - Smaller, lower power in most cases
 - Negative: must be refreshed (due to leakage currents)

Static Latches

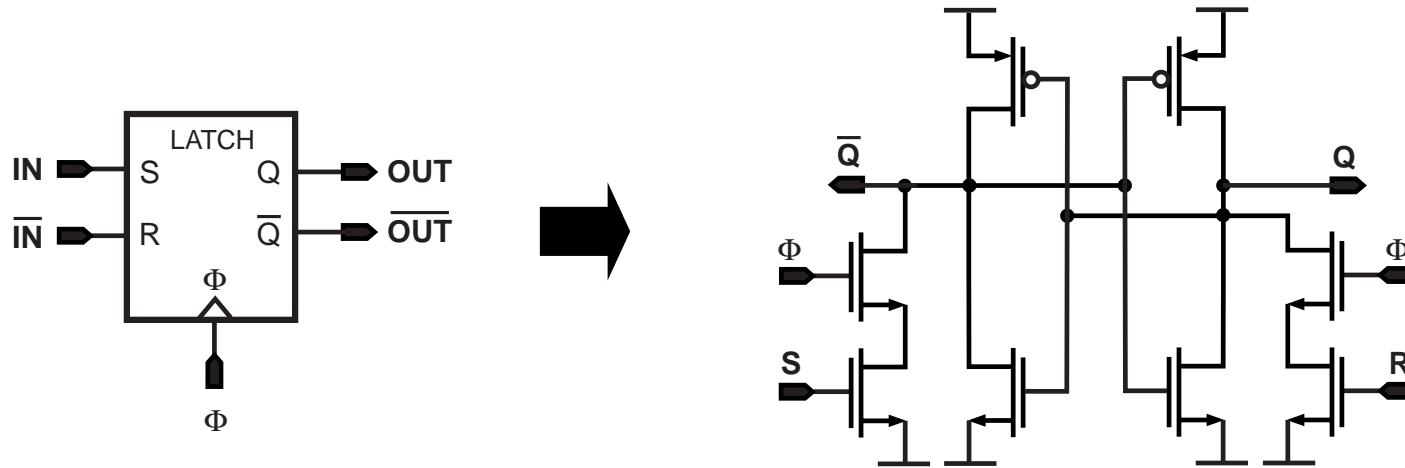


- **Classical case employs cross-coupled NAND/NOR gates to achieve positive feedback**
- **Above example uses cross-coupled inverters for positive feedback**
 - Set, reset, and clock transistors designed to have enough drive to overpower cross-coupled inverters
 - Relatively small number of transistors
 - Robust

Dynamic Latches

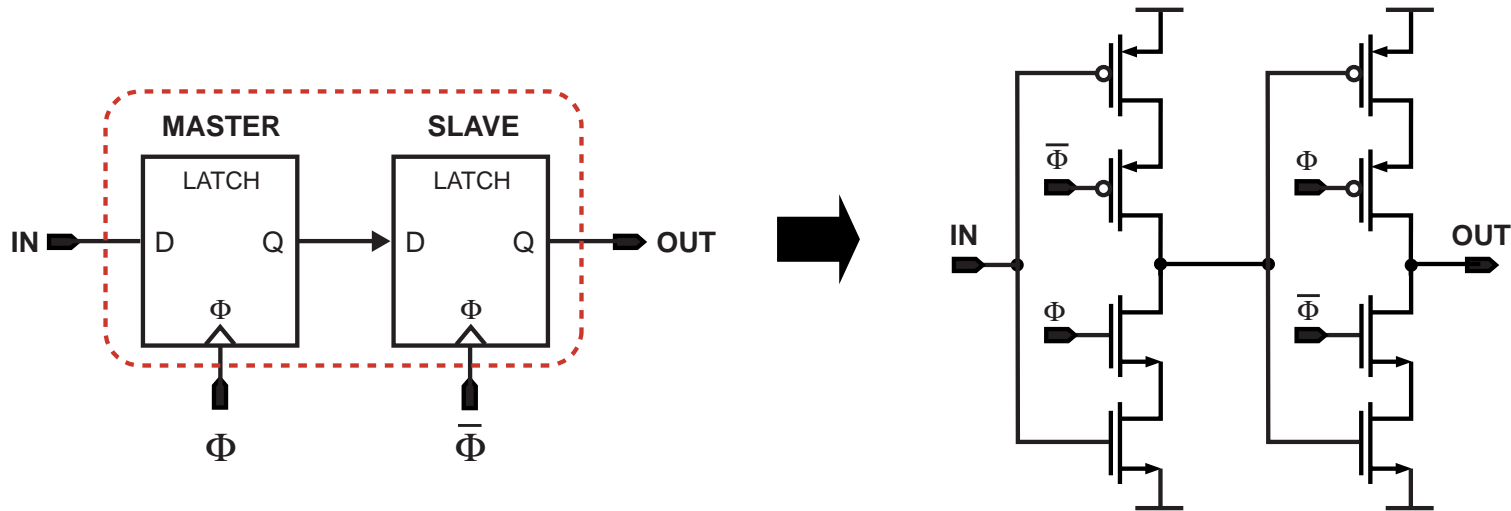

- **Leverage CMOS technology**
 - High quality switches with small leakage available
 - Can switch in and store charge on parasitic capacitances quite reliably
- **Achieves faster speed than full swing logic with fewer transistors**
- **Issues: higher sensitivity to noise, minimum refresh rate required due to charge leakage**


True Single Phase Clocked (TSPC) Latches

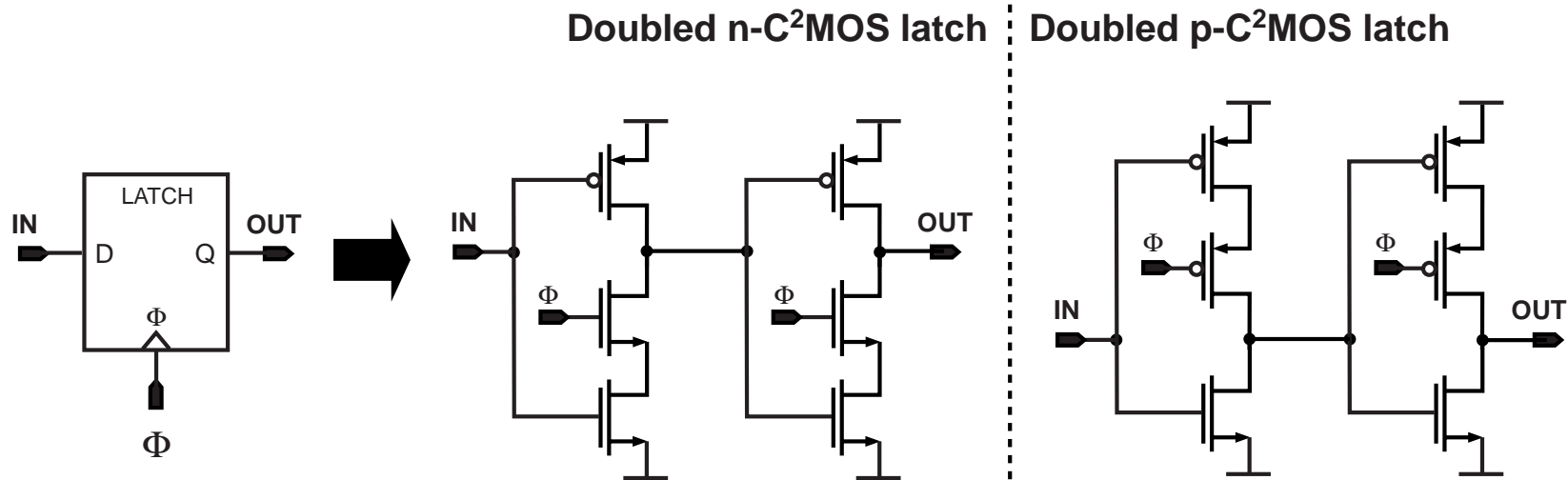


- **Allow register implementations with only one clock!**
 - Latches made transparent at different portions of clock cycle by using appropriate latch “flavor” – n or p
 - n latches are transparent only when Φ is 1
 - p latches are transparent only when Φ is 0
- **Benefits: simplified clock distribution, high speed**

Example TSPC Registers

- Positive edge-triggered version

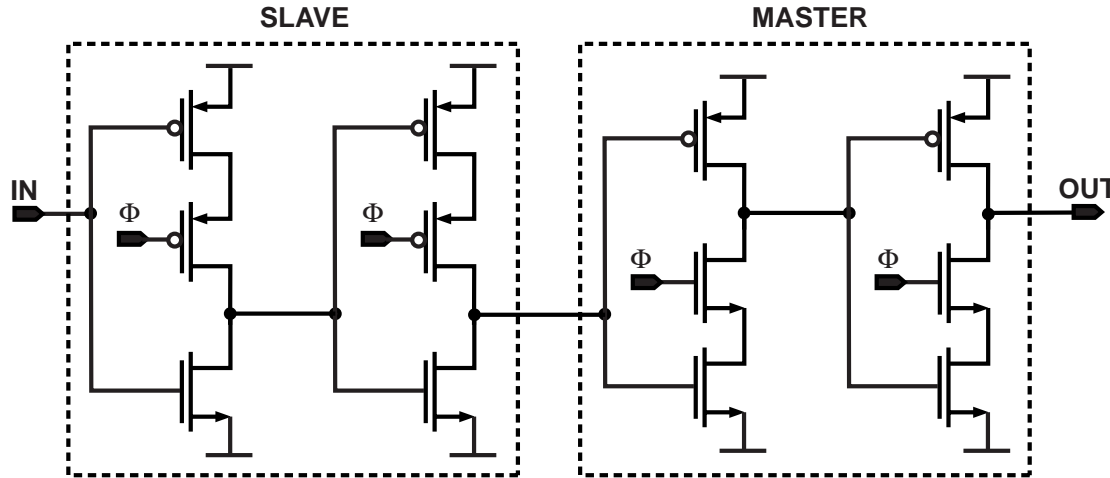


- Negative edge-triggered version

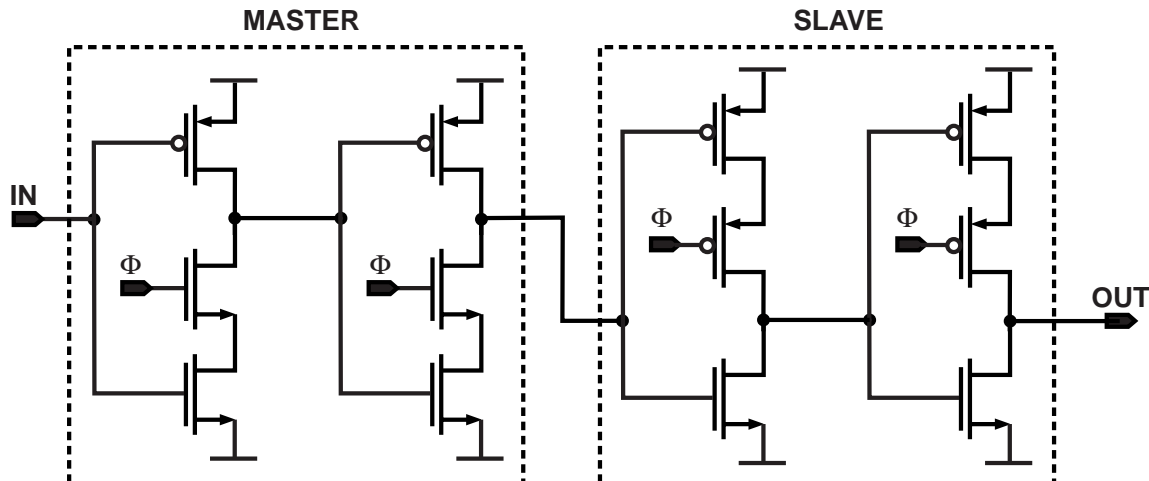


A Simplified Approach to TSPC Registers

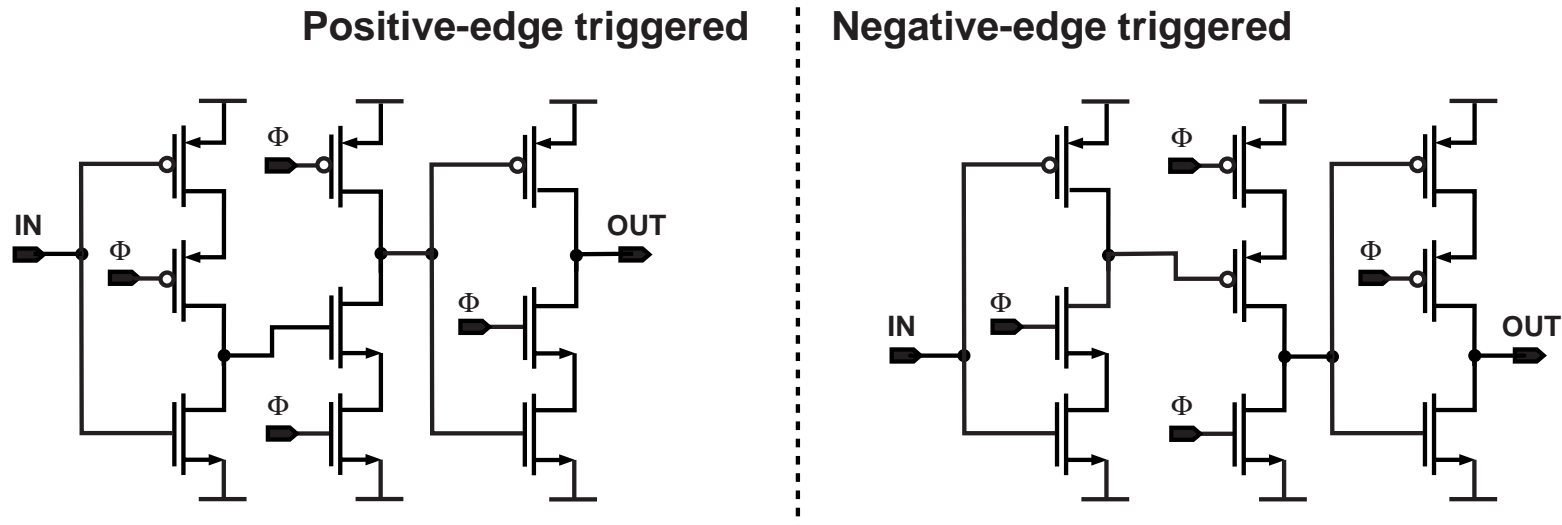- Clever implementation of TSPC approach can be achieved with reduced transistor count




- For more info on TSPC approach, see
 - J. Yuan and C. Svensson, “New Single-Clock CMOS Latches and Flipflops with Improved Speed and Power Savings”, JSSC, Jan 1997, pp 62-69

Embedding of Logic within Latches

 

- We can often increase the speed of a logic function fed into a latch through embedding
 - Latch slowed down by extra transistors, but logic/latch combination is faster than direct cascade of the functions
- Method can be applied to both static and dynamic approaches
 - Dynamic approach shown above

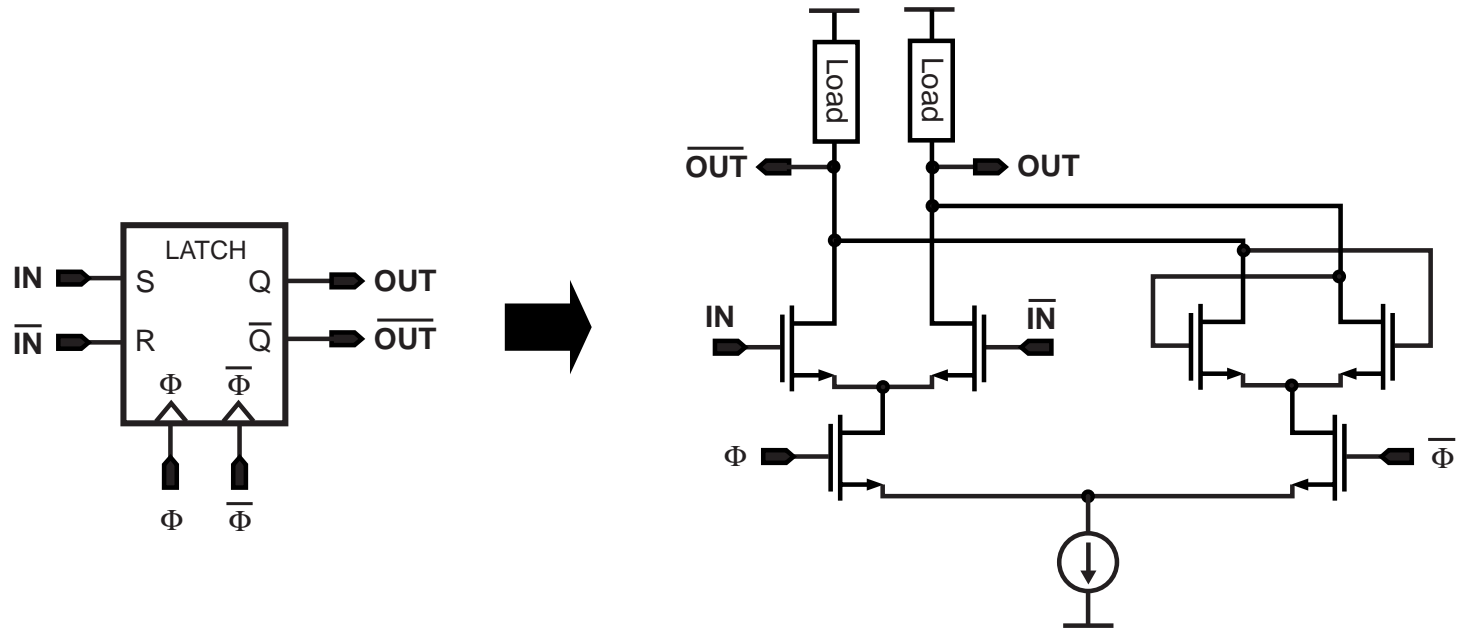
Highest Speed Achieved with Differential CML Latch



- **Employs positive feedback for memory**
 - Realized with cross-coupled NMOS differential pair
- **Method of operation**
 - Follow mode: current directed through differential amplifier that passes input signal
 - Hold mode: current shifted to cross-coupled pair


High Speed Frequency Dividers

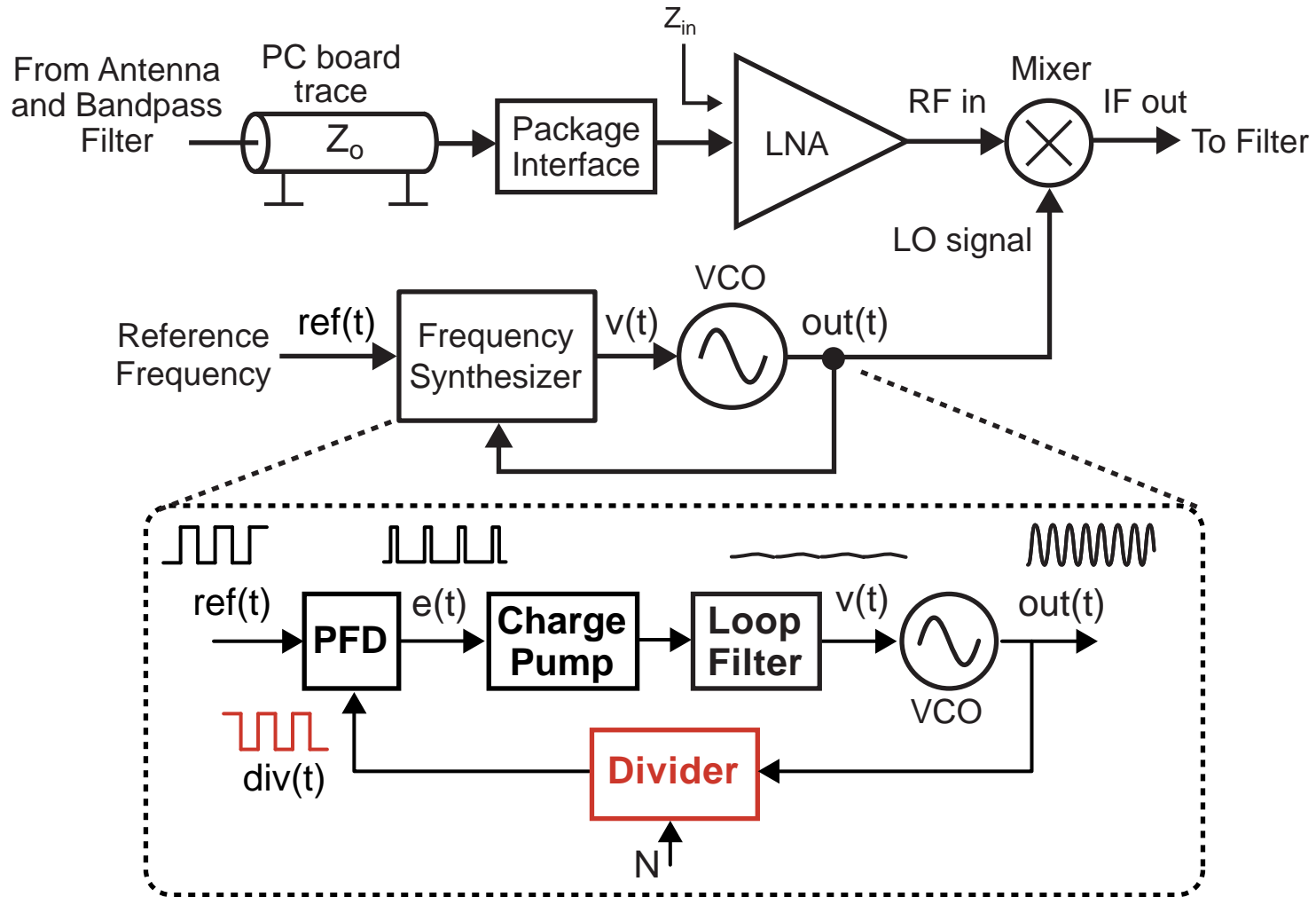High Speed Frequency Dividers in Wireless Systems





- Design Issues: high speed, low power

Divide-by-2 Circuit (Johnson Counter)

 

- Achieves frequency division by clocking two latches (i.e., a register) in negative feedback
- Latches may be implemented in various ways according to speed/power requirements

Divide-by-2 Using a TSPC register

  




■ Advantages

- Reasonably fast, compact size
- No static power dissipation, differential clock not required

■ Disadvantages


- Slowed down by stacked PMOS, signals goes through three gates per cycle
- Requires full swing input clock signal

Divide-by-2 Using Razavi's Topology

   

- Faster topology than TSPC approach
- See B. Razavi et. al., “Design of High Speed, Low Power Frequency Dividers and Phase-Locked Loops in Deep Submicron CMOS”, JSSC, Feb 1995, pp 101-109

 Explanation of Razavi Divider Operation (Part 1)




■ Left latch:

- Clock drives current from PMOS devices of a given latch onto the NMOS cross-coupled pair
- Latch output voltage rises asymmetrically according to voltage setting on gates of outside NMOS devices

■ Right latch:

- Outside NMOS devices discharge the latch output voltage as the left latch output voltage rises

 Explanation of Razavi Divider Operation (Part 2)




■ Right latch:

- Clock drives current from PMOS devices of a given latch onto the NMOS cross-coupled pair
- Latch output voltage rises asymmetrically according to voltage setting on gates of outside NMOS devices

■ Left latch:



- Outside NMOS devices discharge the latch output voltage as the left latch output voltage rises

 Explanation of Razavi Divider Operation (Part 3)



- **Process starts over again with current being driven into left latch**
 - Voltage polarity at the output of the latch has now flipped

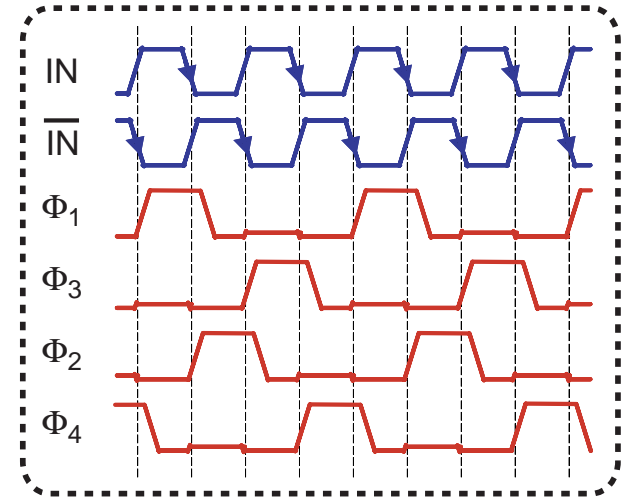 Advantages and Disadvantages of Razavi Topology




Advantages

- Fast – no stacked PMOS, signal goes through only two gates per cycle

Disadvantages


- Static power
- Full swing, differential input clock signal required
- Note: quarter period duty cycle can be turned into fifty percent duty cycle with OR gates after the divider
 - See my thesis at <http://www-mtl.mit.edu/~perrott>

Divide-by-2 Using Wang Topology

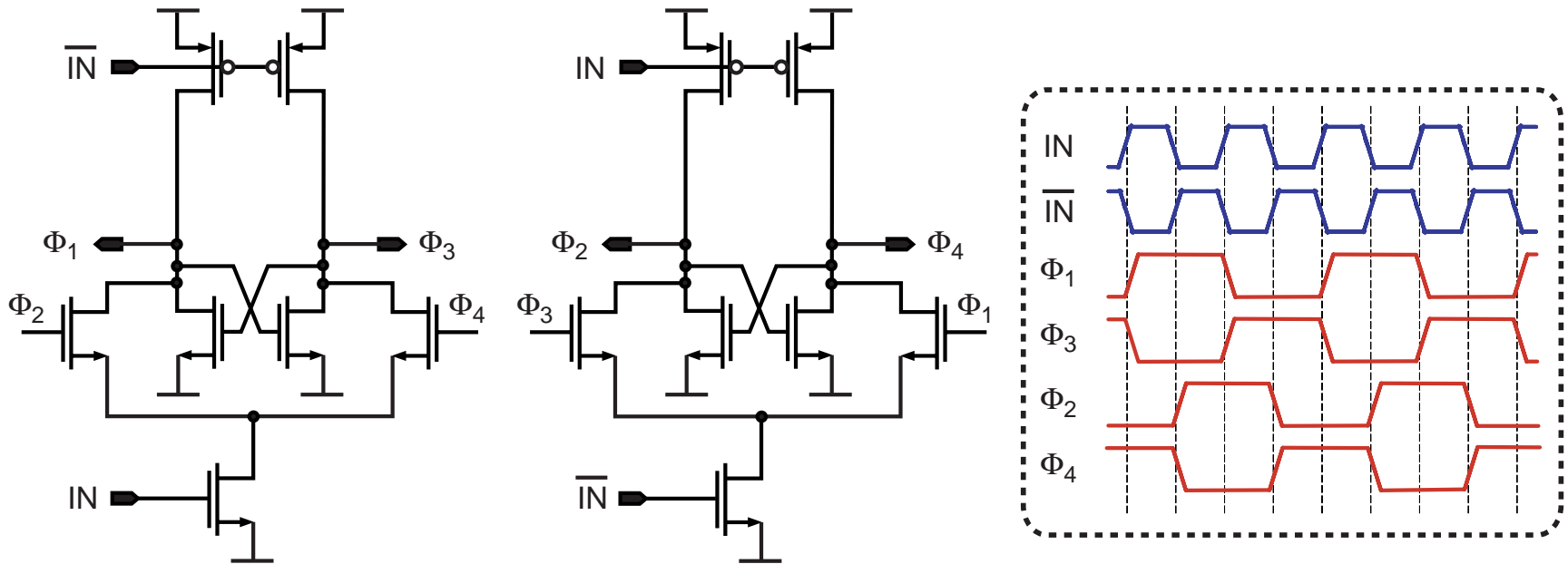

- **Claims to be faster than Razavi topology**
 - Chief difference is addition of NMOS clock devices and different scaling of upper PMOS devices
- **See HongMo Wang, “A 1.8 V 3 mW 16.8 GHz Frequency Divider in 0.25 μ m CMOS”, ISSCC 2000, pp 196-197**

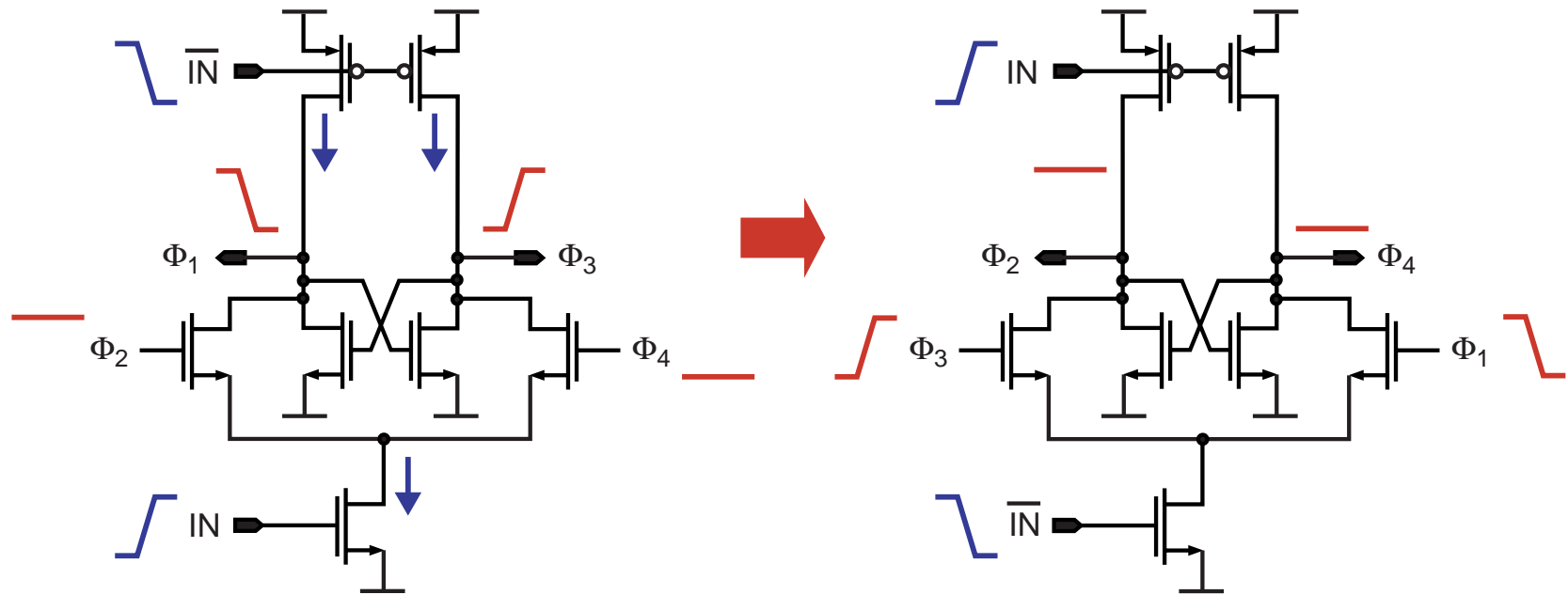Explanation of Wang Topology Operation (Part 1)




- **Left latch**

- Current driven into latch and output voltage responds similar to Razavi architecture

- **Right latch**


- Different than Razavi architecture in that latch output voltage is *not* discharged due to presence of extra NMOS

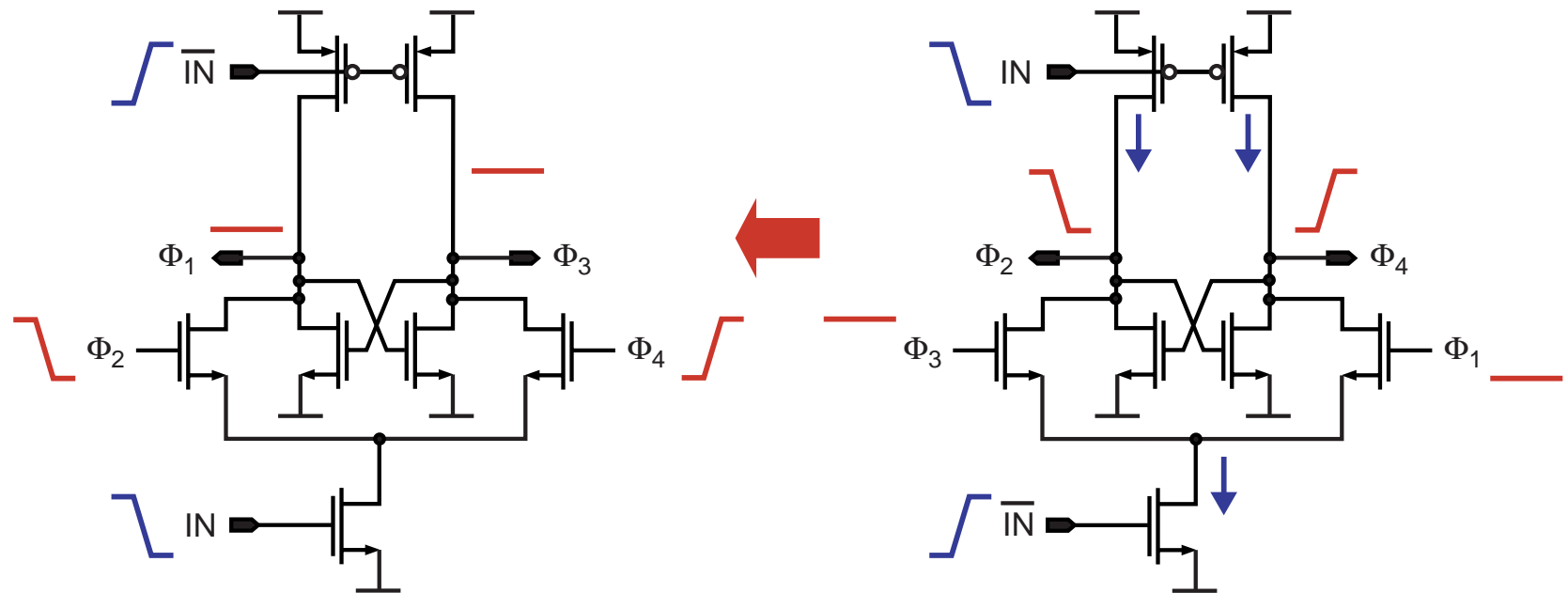Explanation of Wang Topology Operation (Part 2)



- Same process repeats on the right side
 - The left side maintains its voltages due to presence of NMOS device

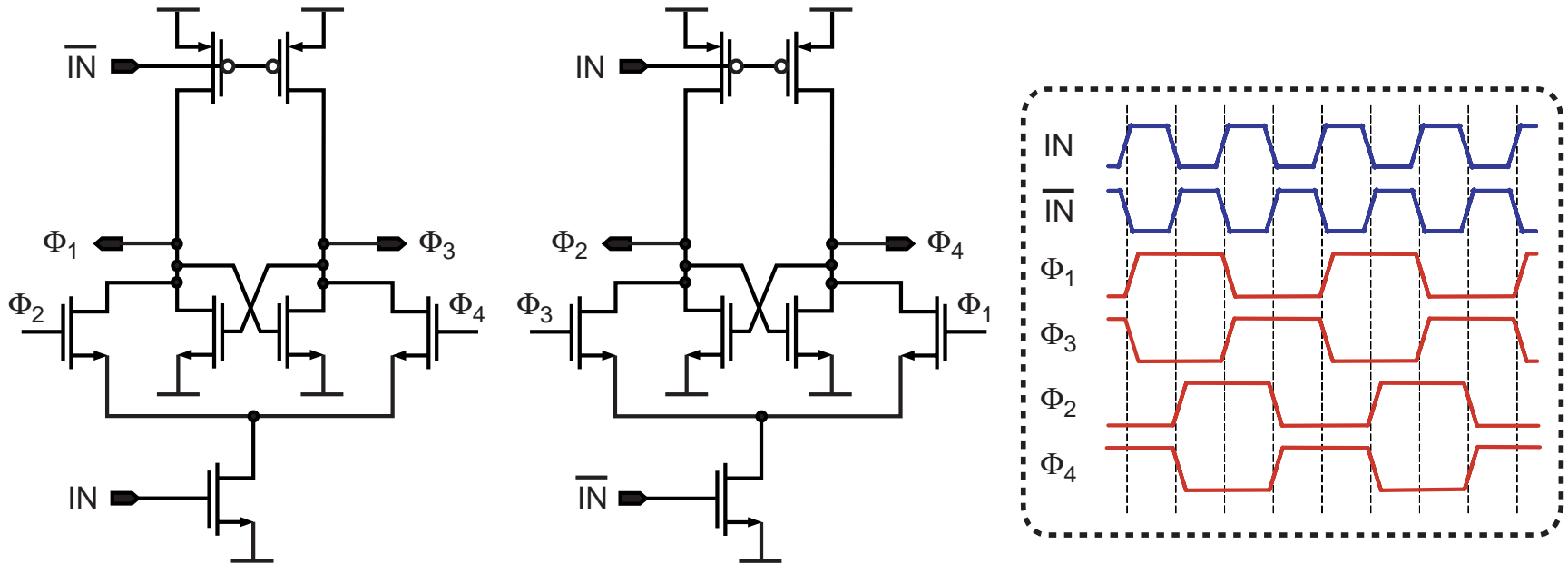Advantages and Disadvantages of Wang Topology




■ Advantages

- Fast – no stacked PMOS, signal goes through only two gates per cycle

■ Disadvantages


- Static power
- Full swing, differential input clock signal required

Divide-by-2 Using CML Latches

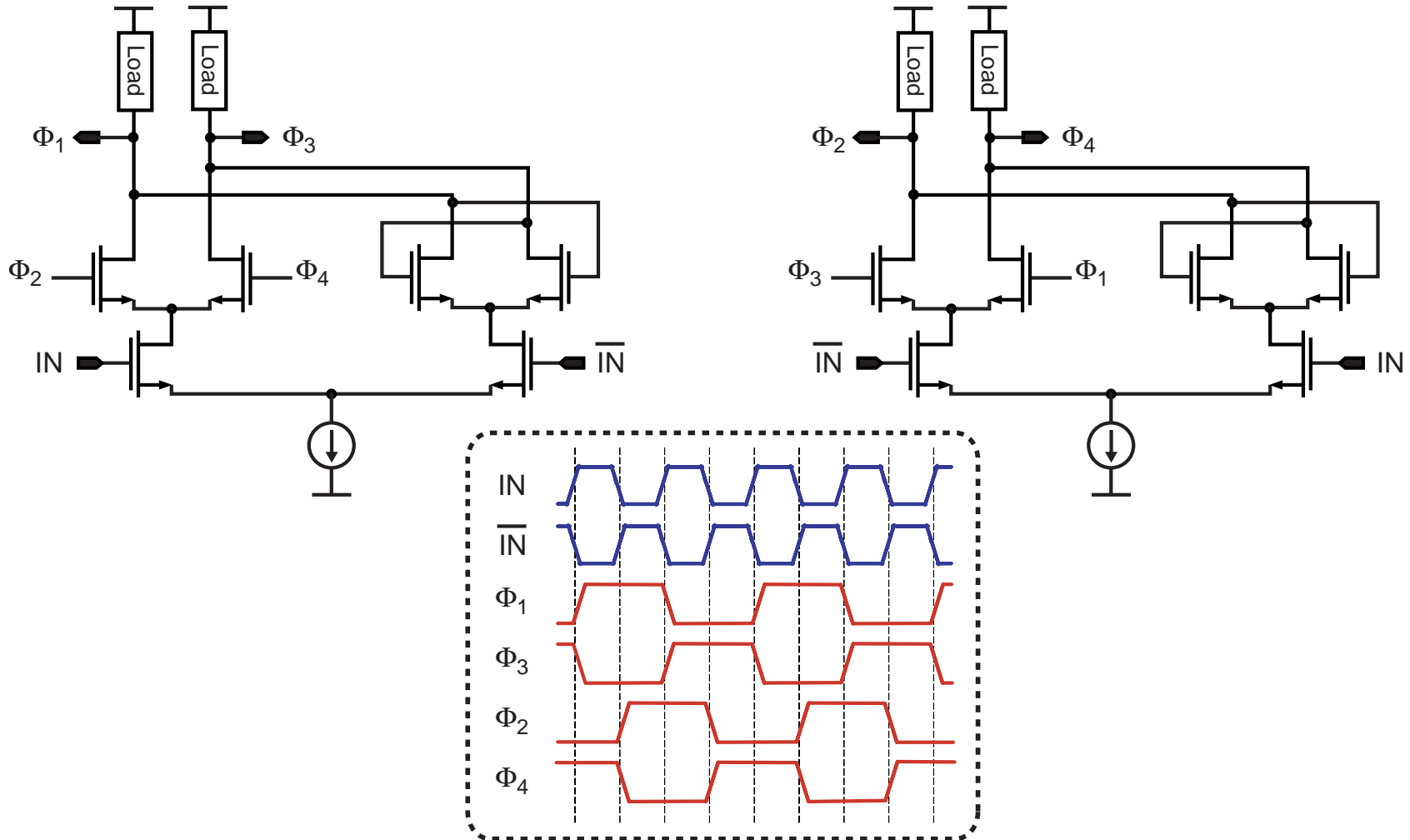

- Fastest structure uses resistors for load

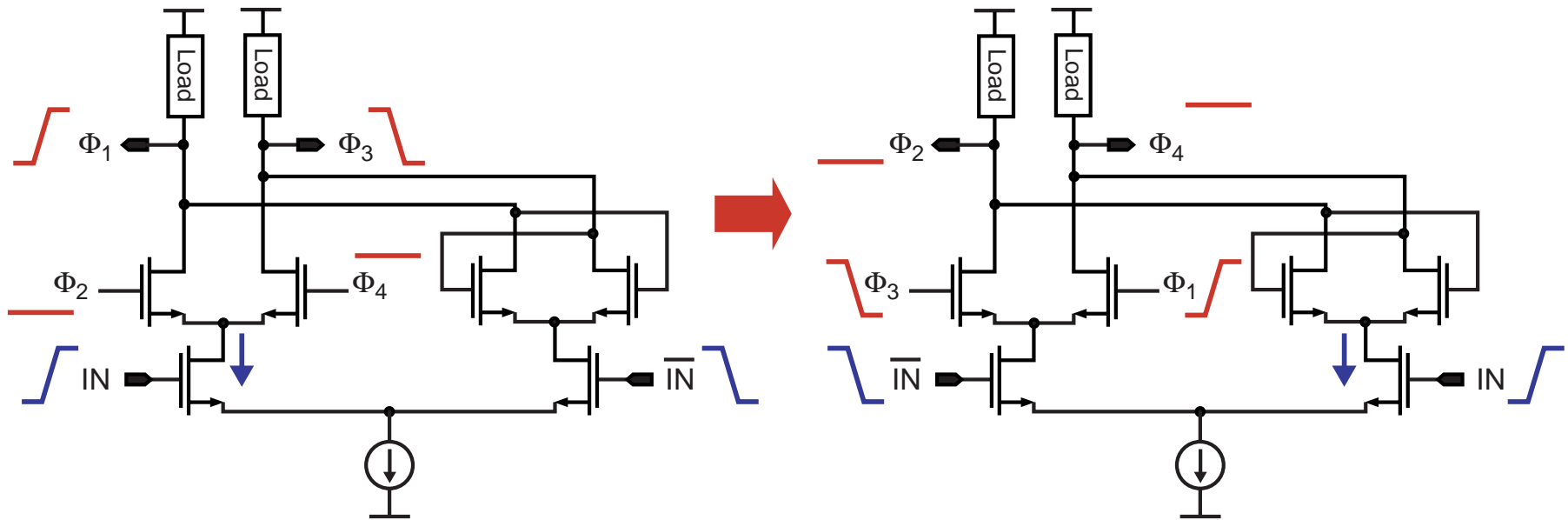Explanation of CML Topology Operation (Part 1)




■ Left latch

- Current directed into differential amp portion of latch
 - Latch output follows input from right latch

■ Right latch

- Current directed into cross-coupled pair portion of latch
 - Latch output is held

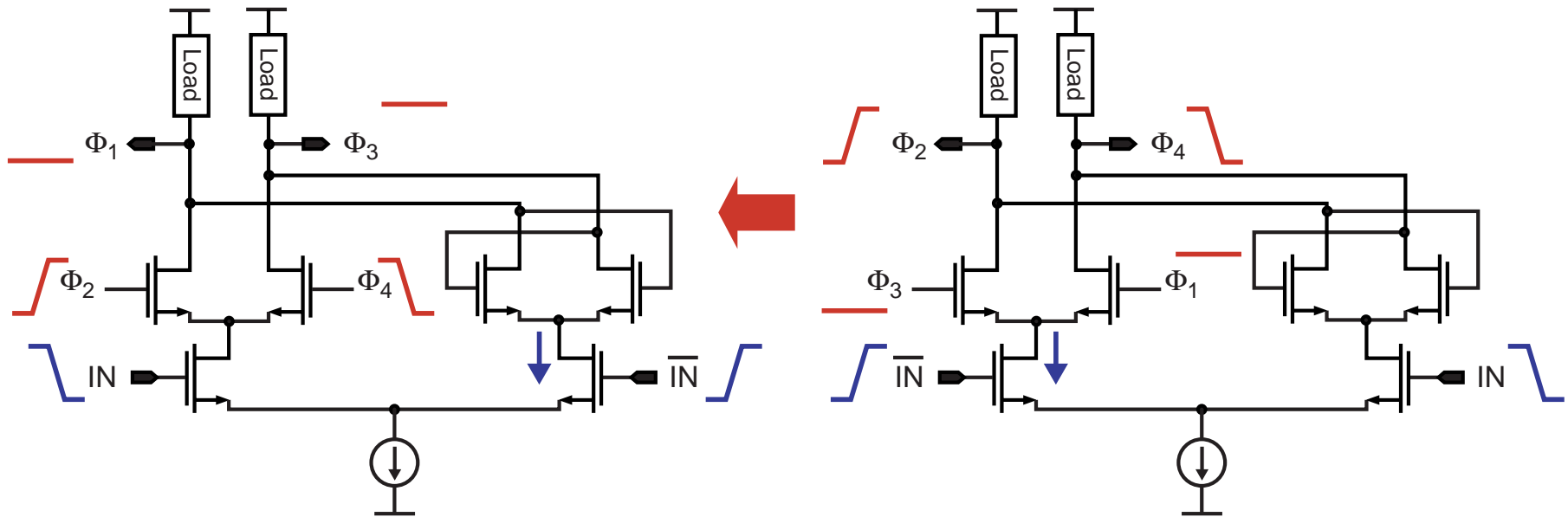Explanation of CML Topology Operation (Part 2)




- **Left latch**

- **Current is directed into cross-coupled pair**
 - Latch output voltage retained

- **Right latch**

- **Current is directed into differential amp**
 - Latch output voltage follows input from left latch

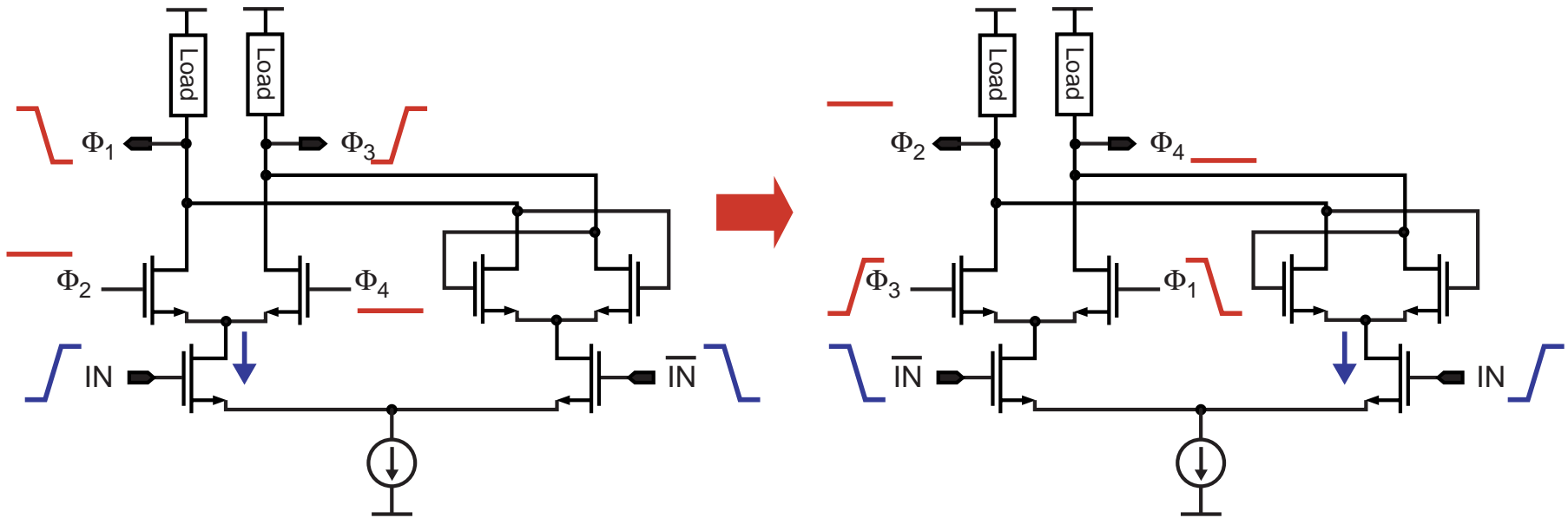Explanation of CML Topology Operation (Part 3)



- Same process repeats on left side
 - Voltage polarity is now flipped

Advantages and Disadvantages of CML Topology

■ **Advantages**


- **Very fast – no PMOS at all, signal goes through only two gates per cycle**
- **Smaller input swing for input clock than previous approaches**
 - **Allows signal transitioning at higher frequencies**

■ **Disadvantages**

- **Static power**
- **Differential signals required**
- **Large area compared to previous approaches**
- **Biasing sources required**


- **Note: additional speedup can be obtained by using inductor peaking (i.e., place inductor in load)**

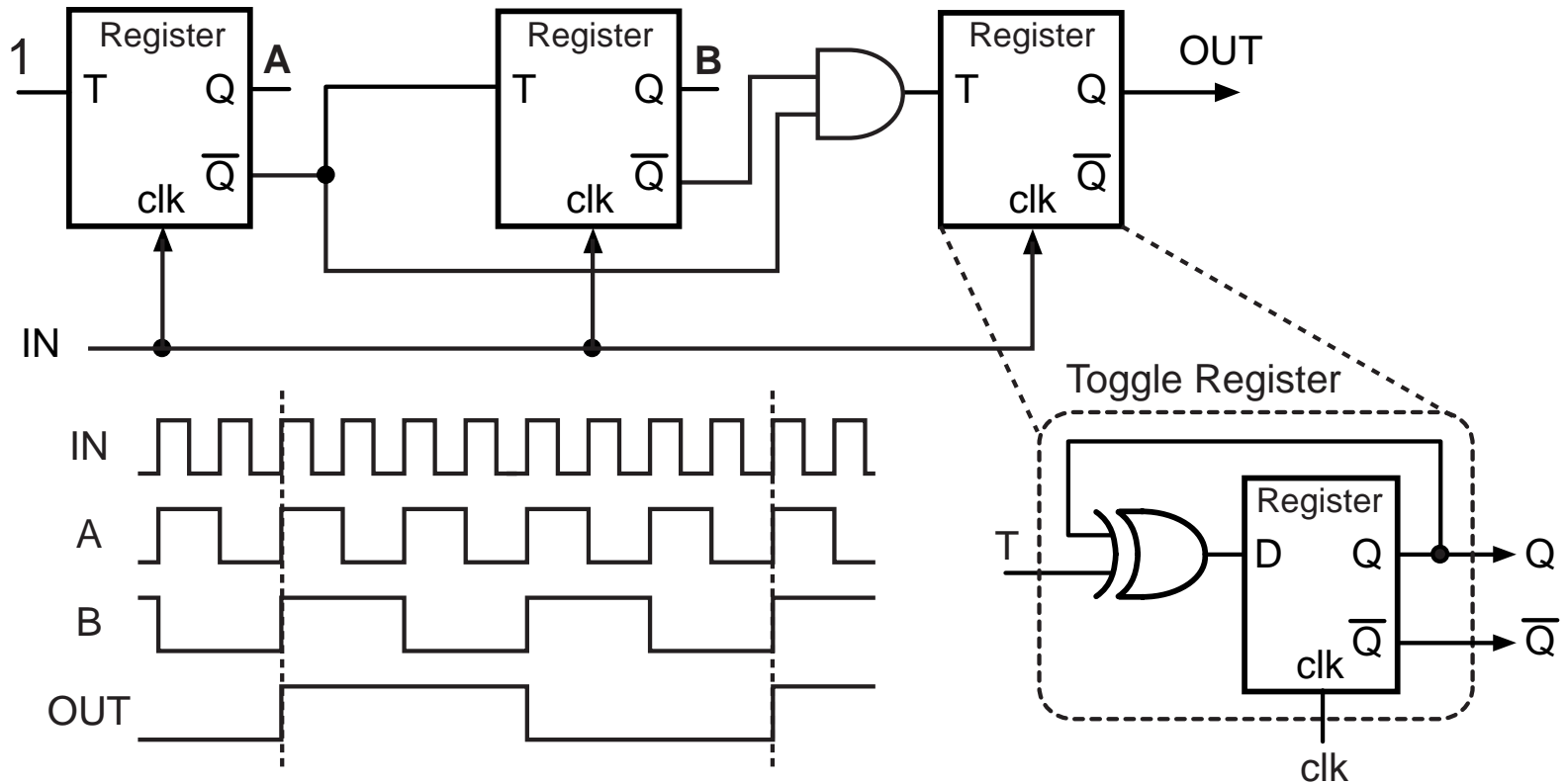Creating Higher Divide Values (Synchronous Approach)




- **Cascades toggle registers and logic to perform division**
 - Advantage: low jitter (explained shortly)
 - Problems: high power (all registers run at high frequency), high loading on clock (IN signal drives *all* registers)

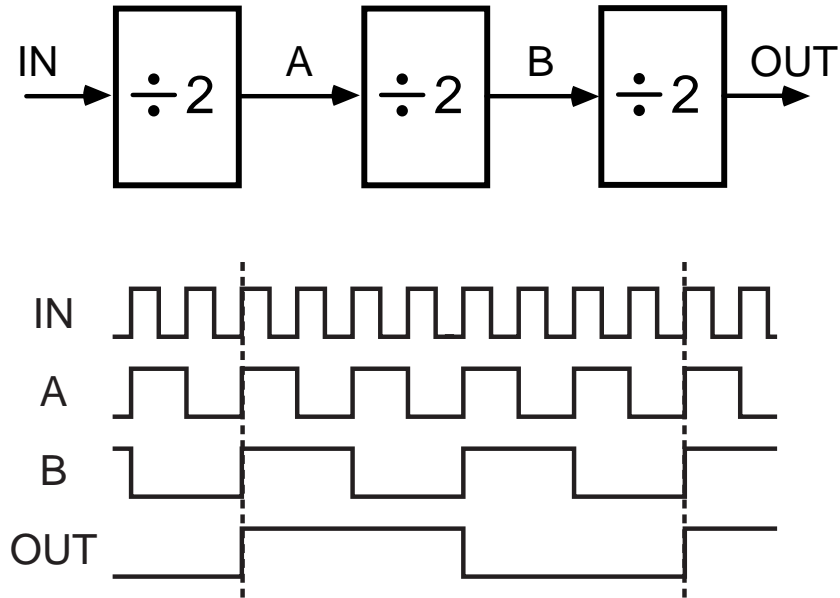Creating Higher Divide Values (Asynchronous Approach)




- Higher division achieved by simply cascading divide-by-2 stages
- Advantages over synchronous approach
 - Lower power: each stage runs at a lower frequency, allowing power to be correspondingly reduced
 - Less loading of input: IN signal only drives first stage
- Disadvantage: jitter is larger

Jitter in Asynchronous Designs

 


- Each logic stage adds jitter to its output
 - Jitter accumulates as it passes through more and more gates

Jitter in Synchronous Designs

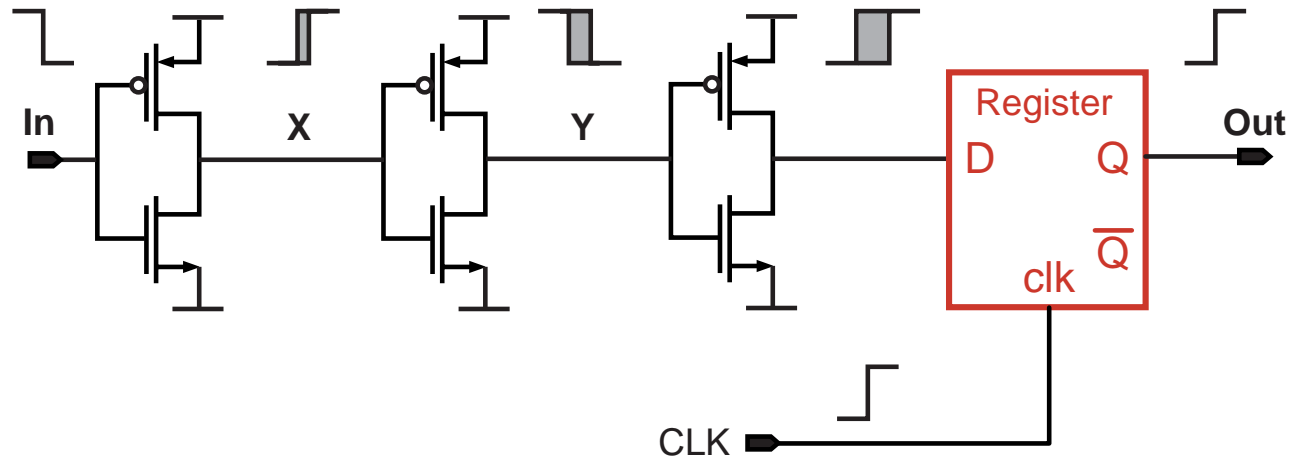


- **Transition time of register output is set by the clock, not the incoming data input**
 - Synchronous circuits have jitter performance corresponding to their clock
 - Jitter does not accumulate as signal travels through synchronous stages

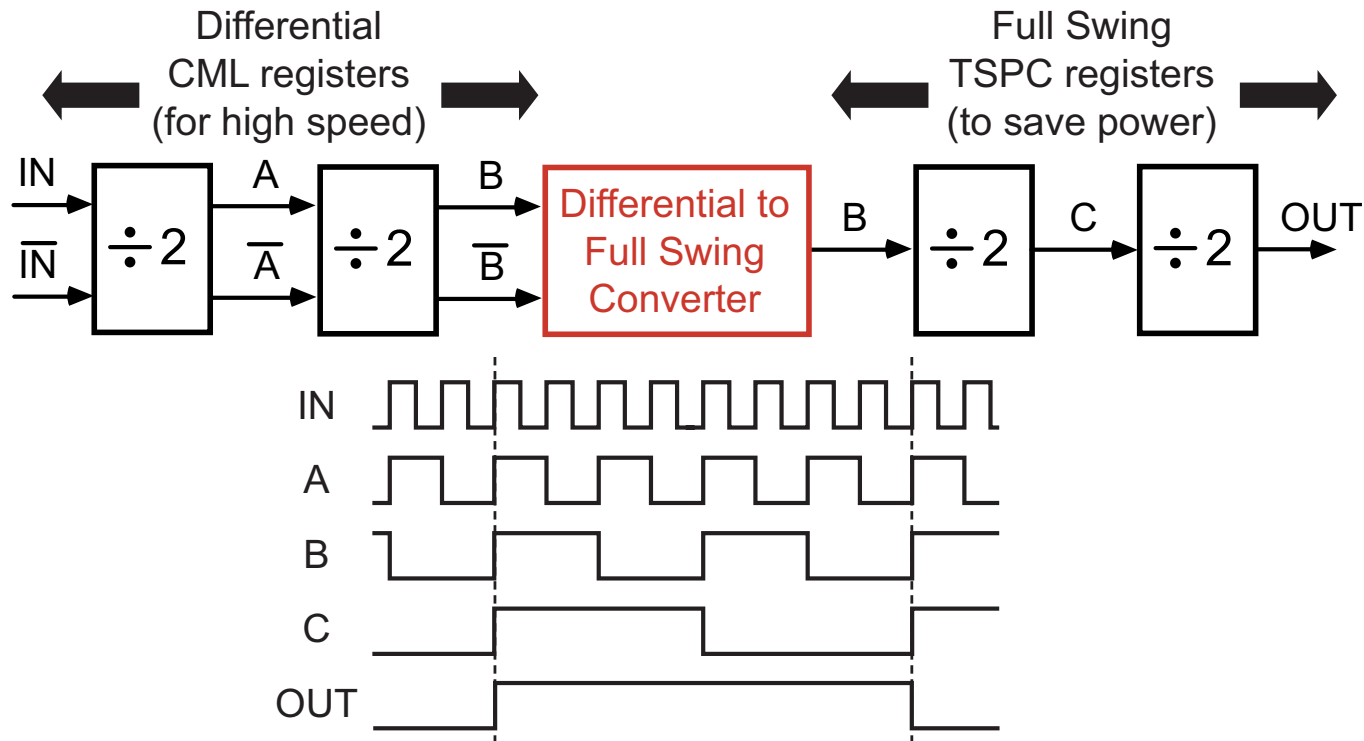High Speed, Low Power Asynchronous Dividers




- **Highest speed achieved with differential CML registers**
 - Static power consumption not an issue for high speed sections, but wasteful in low speed sections
- **Lower power achieved by using full swing logic for low speed sections**

Differential to Full Swing Converter

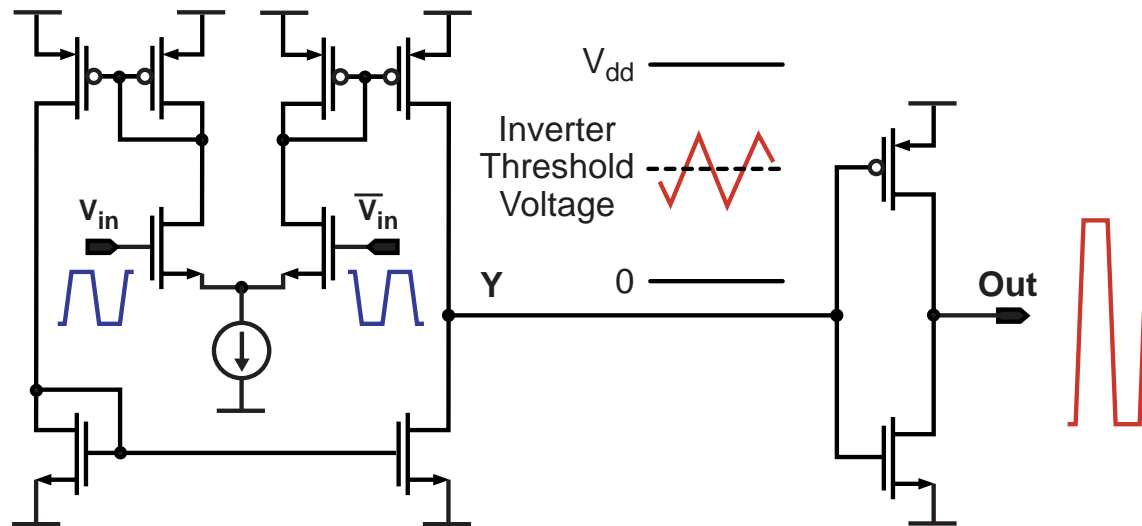


- Use an opamp style circuit to translate differential input voltage to a single-ended output
- Use an inverter to amplify the single-ended output to full swing level

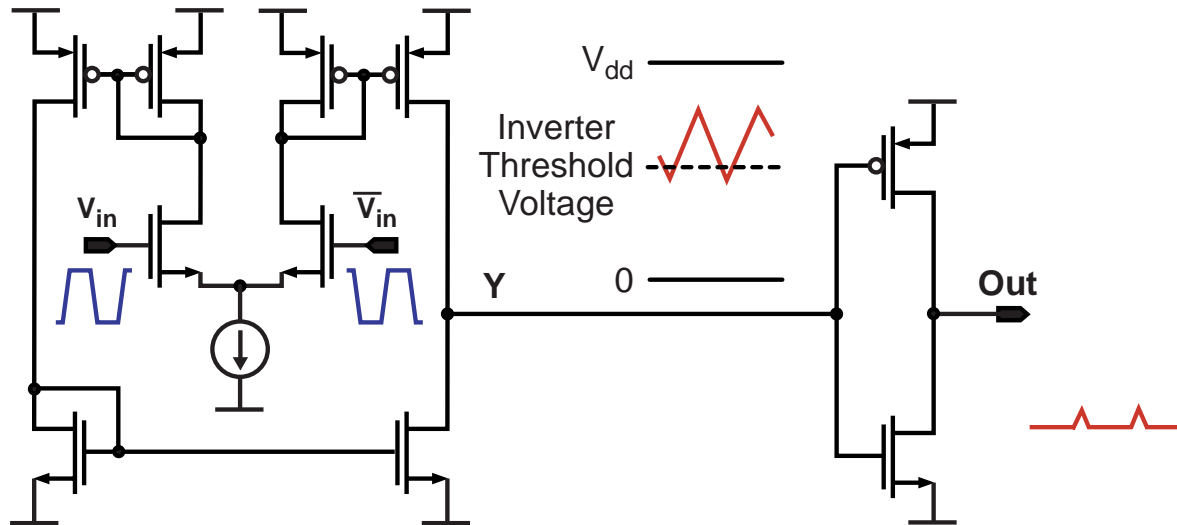Issue: Architecture Very Sensitive to DC Offset




- Opamp style circuit has very high DC gain from V_{in} to node Y
- DC offset will cause signal to rise above or fall below inverter threshold
 - Output signal rails rather than pulsing

Use Resistor Feedback to Reduce DC Gain

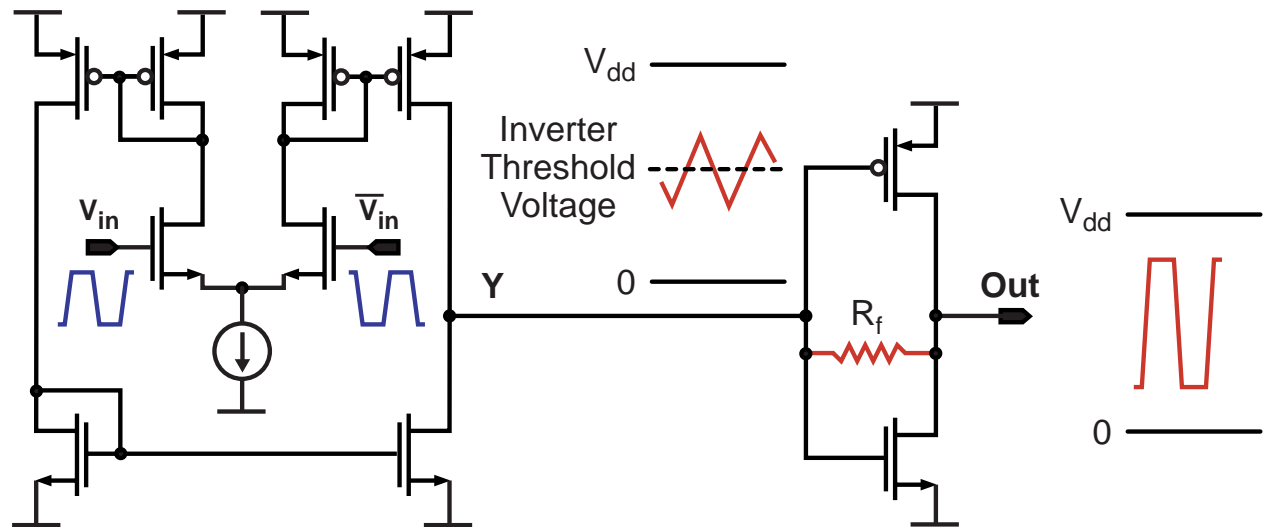


- **Idea: create transresistance amplifier rather than voltage amplifier out of inverter by using feedback resistor**
 - Presents a low impedance to node Y
 - Current from opamp style circuit is shunted through resistor
 - DC offset at input shifts output waveform slightly, but not node Y (to first order)
- **Circuit is robust against DC offset!**

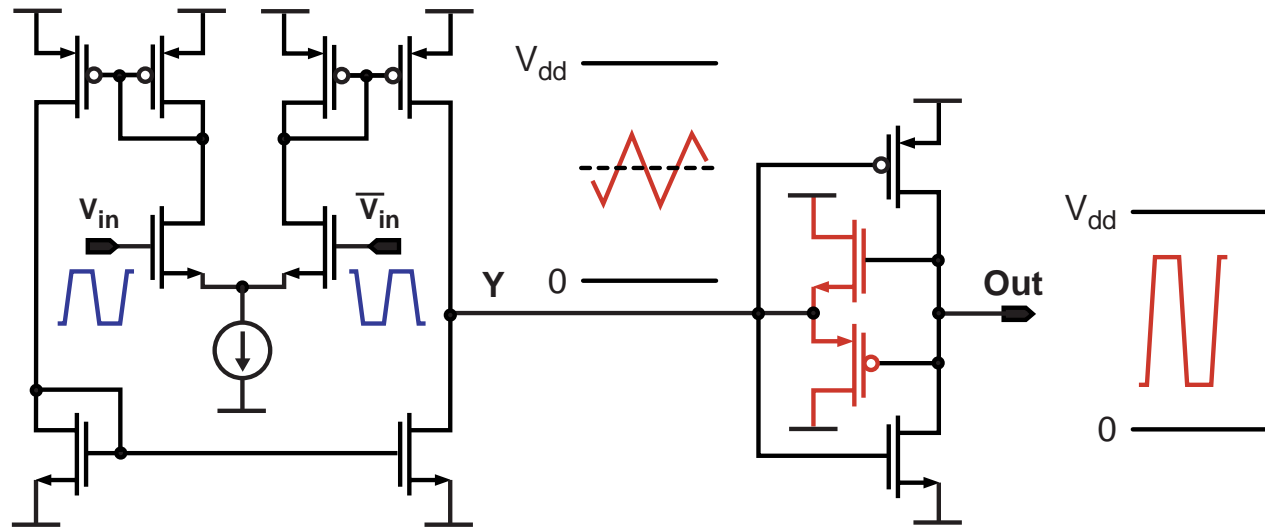Alternate Implementation of Inverter Feedback




- **Nonlinear feedback using MOS devices can be used in place of resistor**
 - Smaller area than resistor implementation
- **Analysis done by examining impact of feedback when output is high or low**

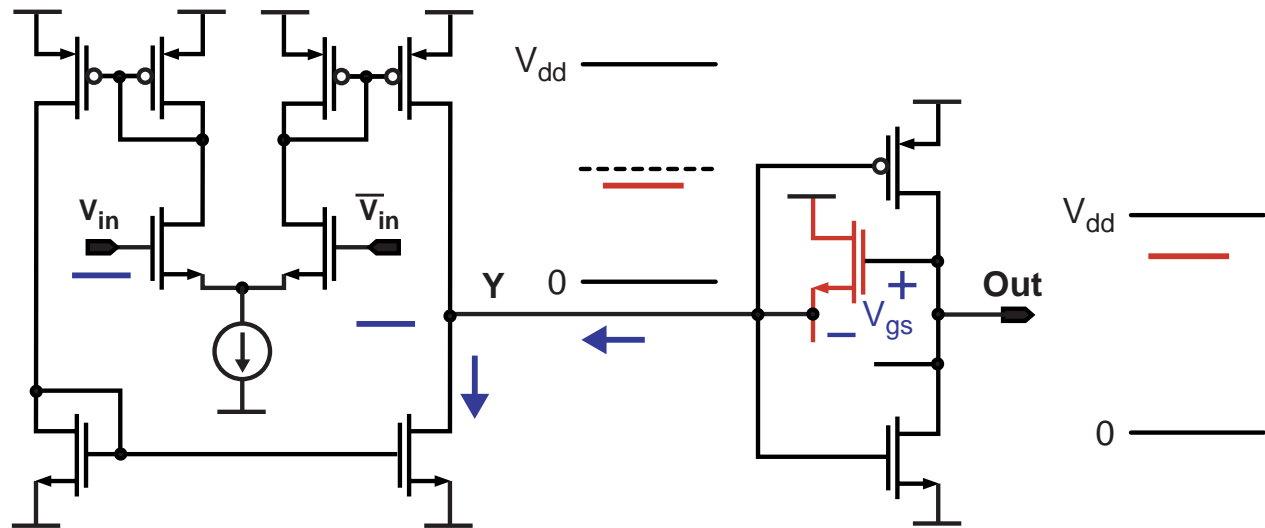Impact of Nonlinear Feedback When Output is High




- Corresponds to case where current flows into node Y
 - NMOS device acts like source follower
 - PMOS device is shut off
- Output is approximately set to V_{gs} of NMOS feedback device away from inverter threshold voltage
 - Inverter input is set to a value that yields that output voltage
 - High DC gain of inverter insures it is close to inverter threshold

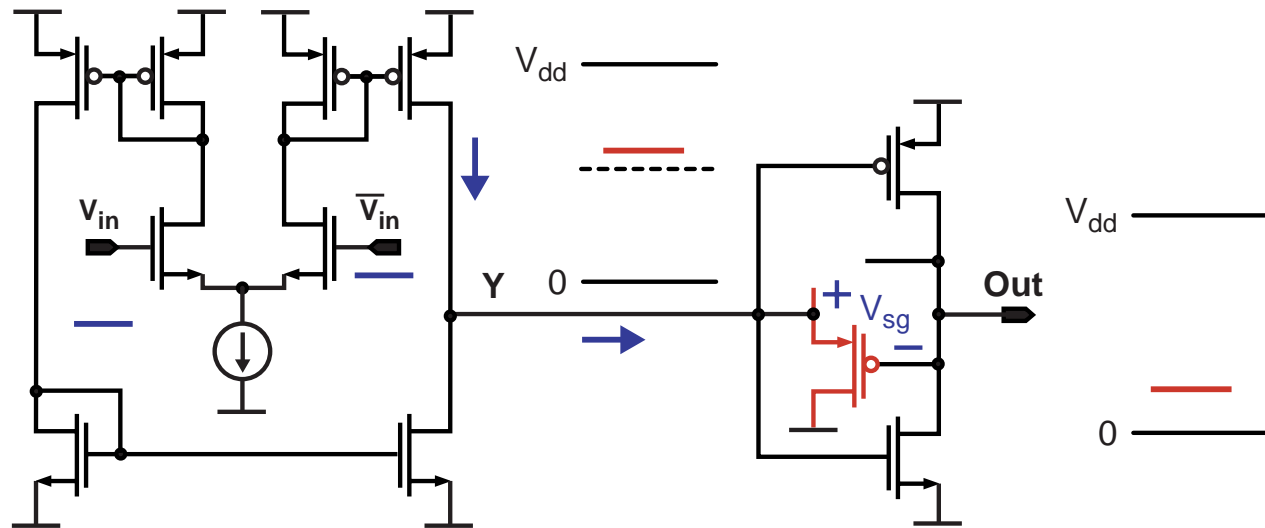Impact of Nonlinear Feedback When Output is Low




- **Corresponds to case where current flows out of node Y**
 - NMOS device is shut off
 - PMOS device acts like source follower
- **Output is approximately set to V_{gs} of PMOS feedback device away from inverter threshold voltage**
 - Inverter input is set to a value that yields that output voltage
 - High DC gain of inverter insures it is close to inverter threshold

Variable Frequency Division

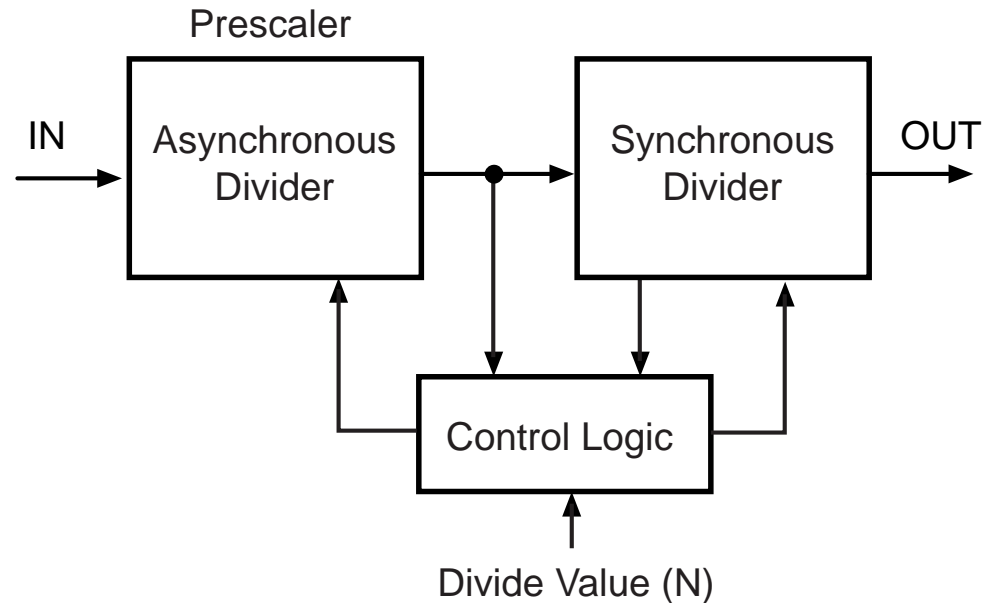


- **Classical design partitions variable divider into two sections**
 - **Asynchronous section (called a prescaler) is fast**
 - Often supports a limited range of divide values
 - **Synchronous section has no jitter accumulation and a wide range of divide values**
 - **Control logic coordinates sections to produce a wide range of divide values**

Dual Modulus Prescalers

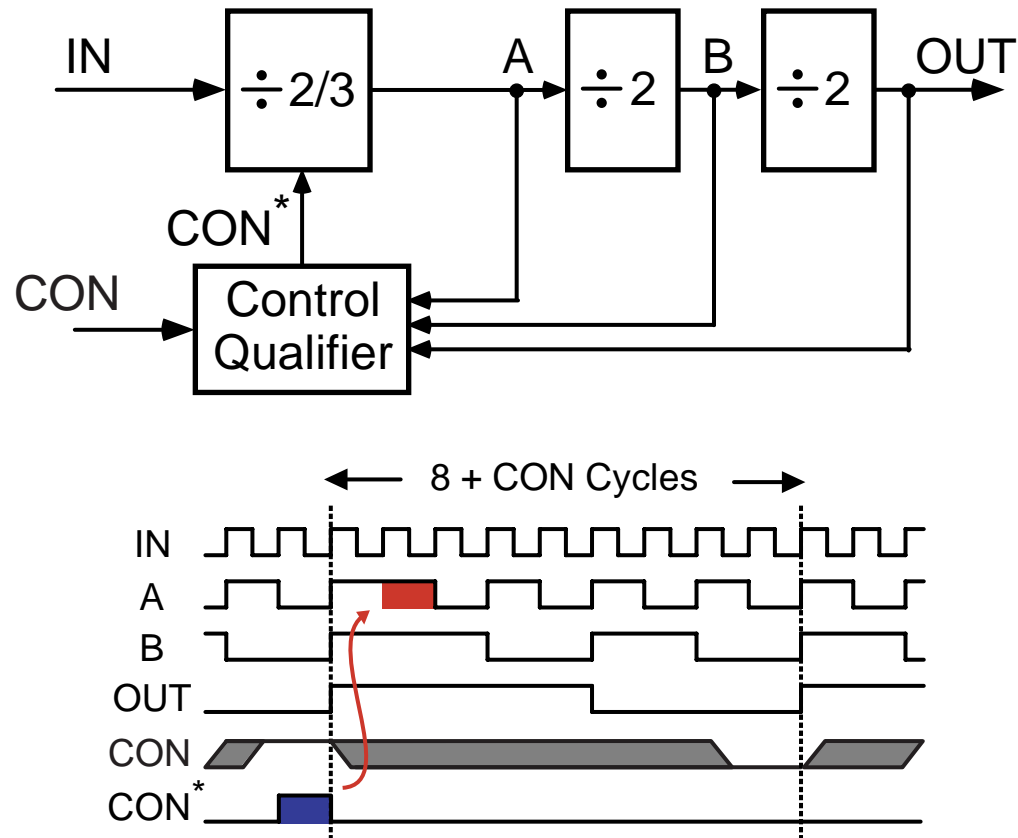


- **Dual modulus design supports two divide values**
 - In this case, divide-by-8 or 9 according to **CON** signal
- **One cycle resolution achieved with front-end “2/3” divider**

 Control Qualifier Design (Classical Approach)




- **Must align CON signal to first “2/3” divider stage**
 - CON signal is based on logic clocked by divider output
 - There will be skew between “2/3” divider timing and CON
- **Classical approach cleverly utilizes outputs from each section to “gate” the CON signal to “2/3” divider**

Multi-Modulus Prescalers

 


- Cascaded 2/3 sections achieves a range of 2^n to $2^{n+1}-1$
 - Above example is 8/ ... /15 divider
- Asynchronous design allows high speed and low power operation to be achieved
 - Only negative is jitter accumulation

A More Modular Design

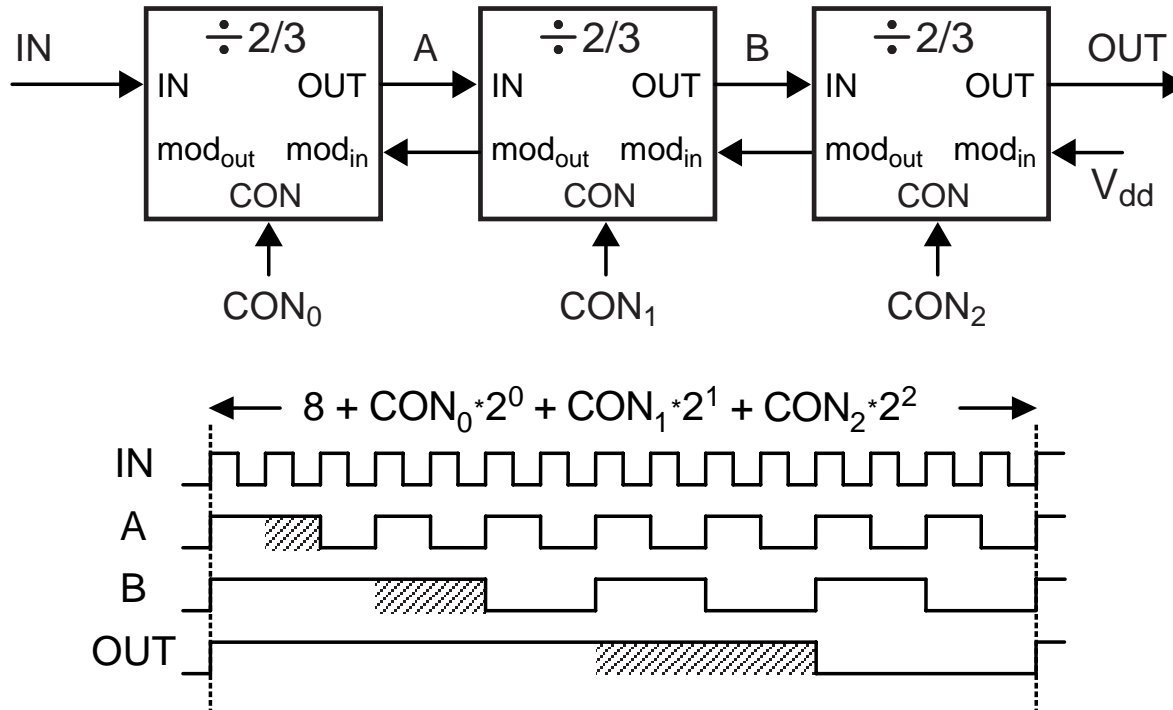


- Perform control qualification by synchronizing within each stage before passing to previous one
 - Compare to previous slide in which all outputs required for qualification of first 2/3 stage
- See Vaucher et. al., “A Family of Low-Power Truly Modular Programmable Dividers ...”, JSSC, July 2000

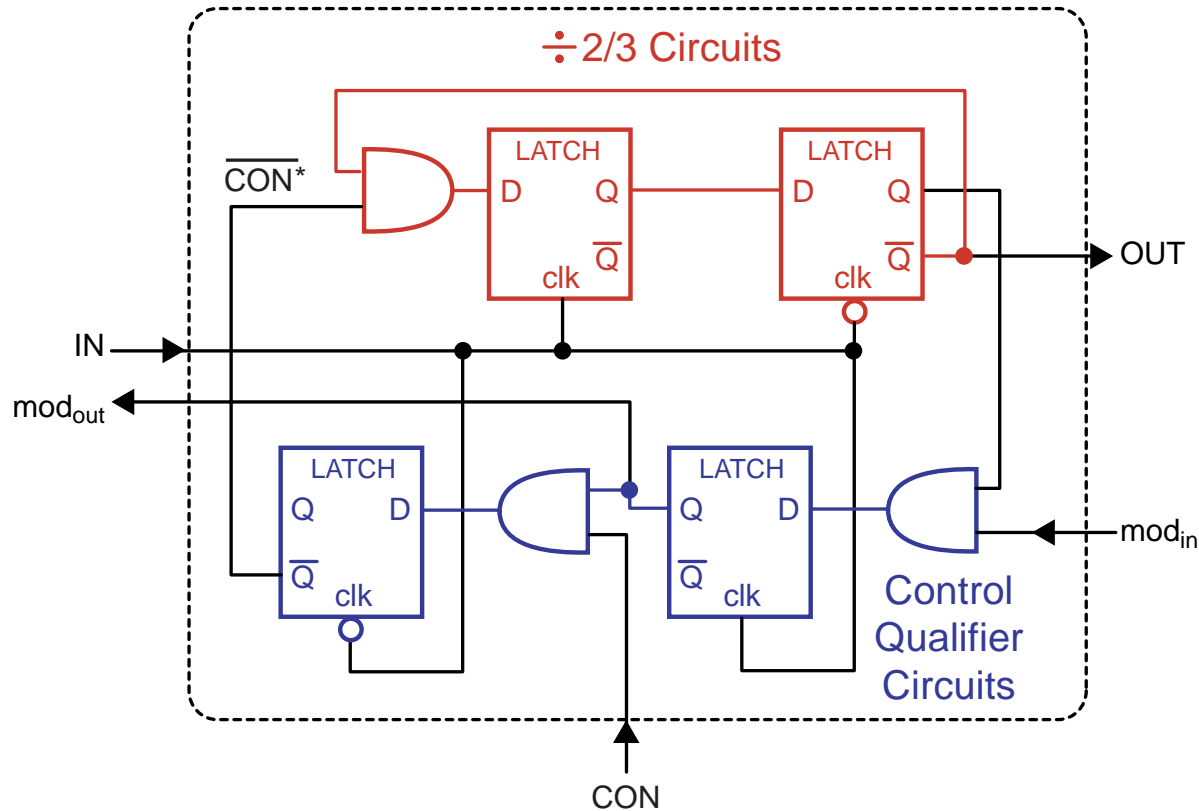Implementation of 2/3 Sections in Modular Approach



- Approach has similar complexity to classical design
 - Consists of two registers with accompanying logic gates
- Cleverly utilizes “gating” register to pass synchronized control qualifying signal to the previous stage

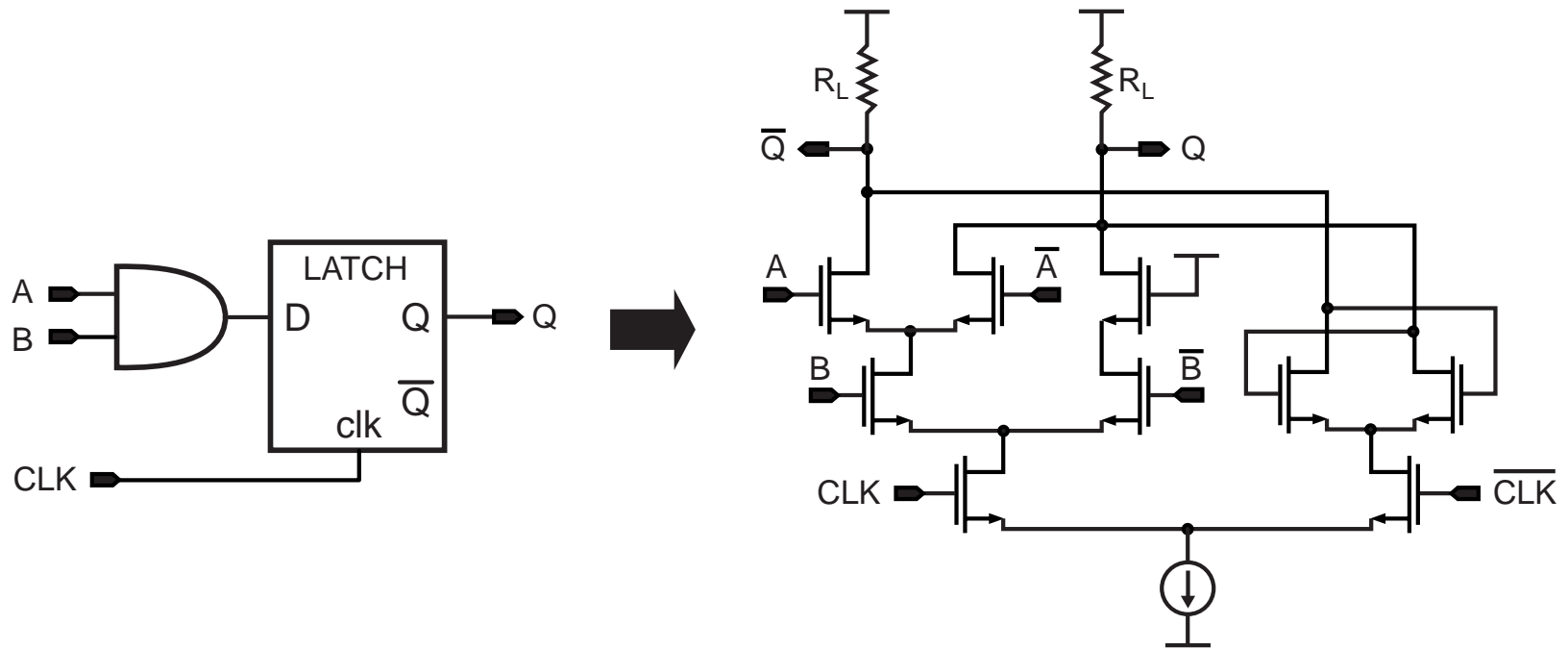
Implementation of Latch and And Gate in 2/3 Section



- **Combine AND gate and latch for faster speed and lower power dissipation**
- **Note that all primitives in 2/3 Section on previous slide consist of this combination or just a straight latch**

Can We Go Even Faster?


Speed Limitations of Divide-by-2 Circuit

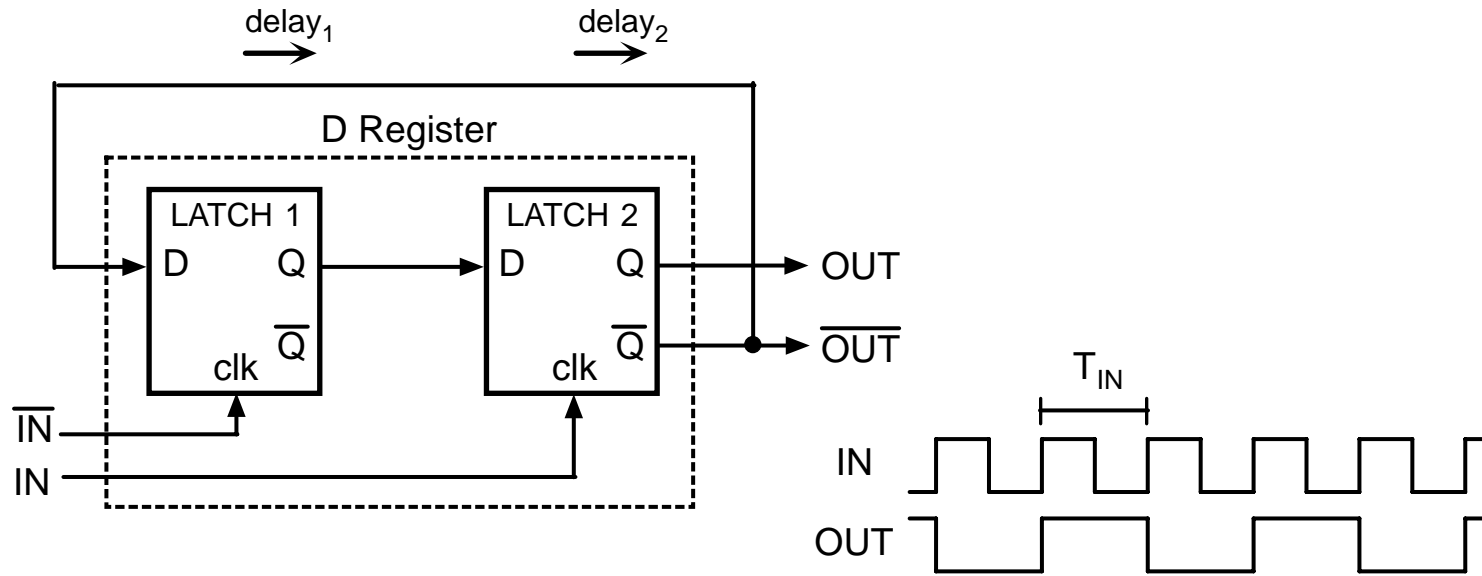

- **Maximum speed limited only by propagation delay ($delay_1$, $delay_2$) of latches and setup time of latches (T_s)**

$$\frac{T_{IN}}{2} > delay_1 + T_s, \quad \frac{T_{IN}}{2} > delay_2 + T_s$$

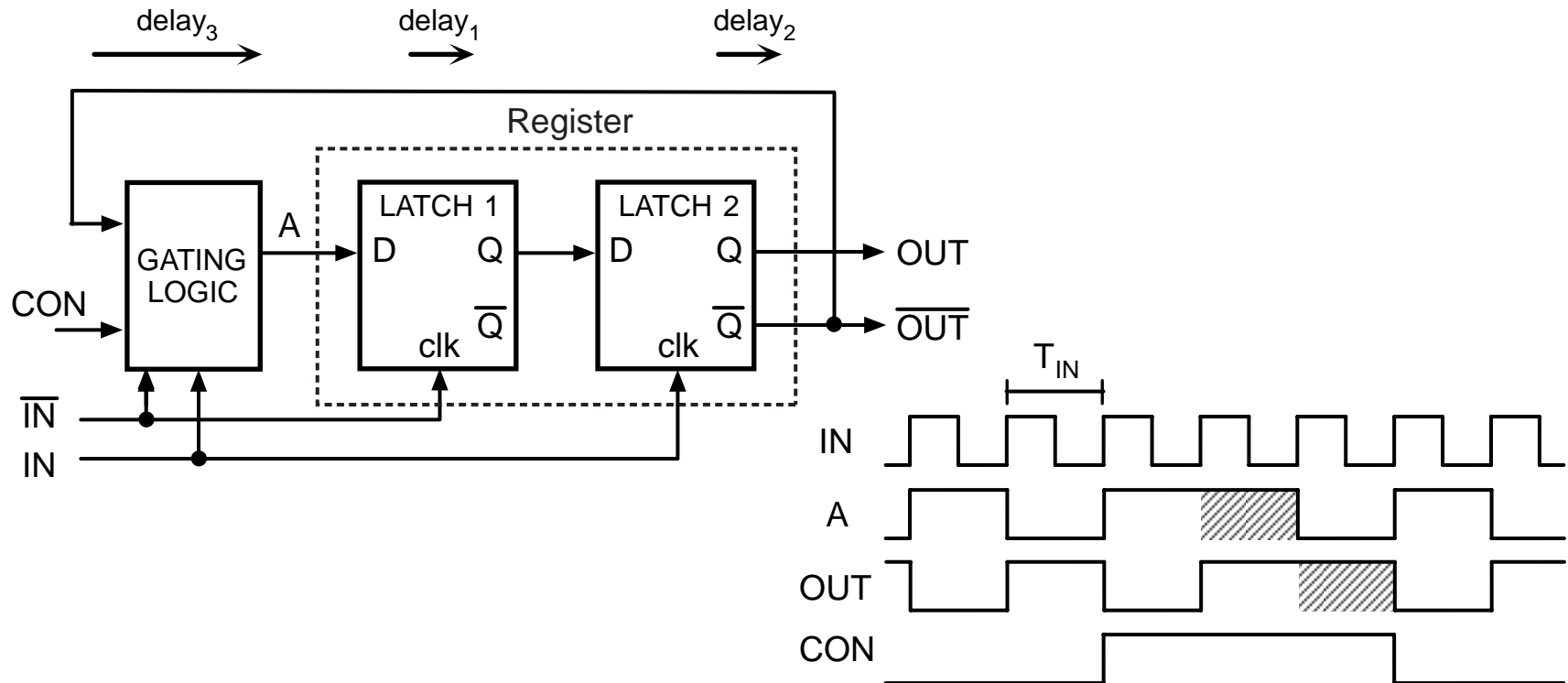Speed Limitations of Gated Divide-by-2/3 Circuit




- Maximum speed limited by latch *plus* gating logic

$$\frac{T_{IN}}{2} > delay_2 + delay_3 + T_s$$

- Gated divide-by-2/3 *fundamentally* slower than divide-by-2

Divide-by-2/3 Using Phase Shifting

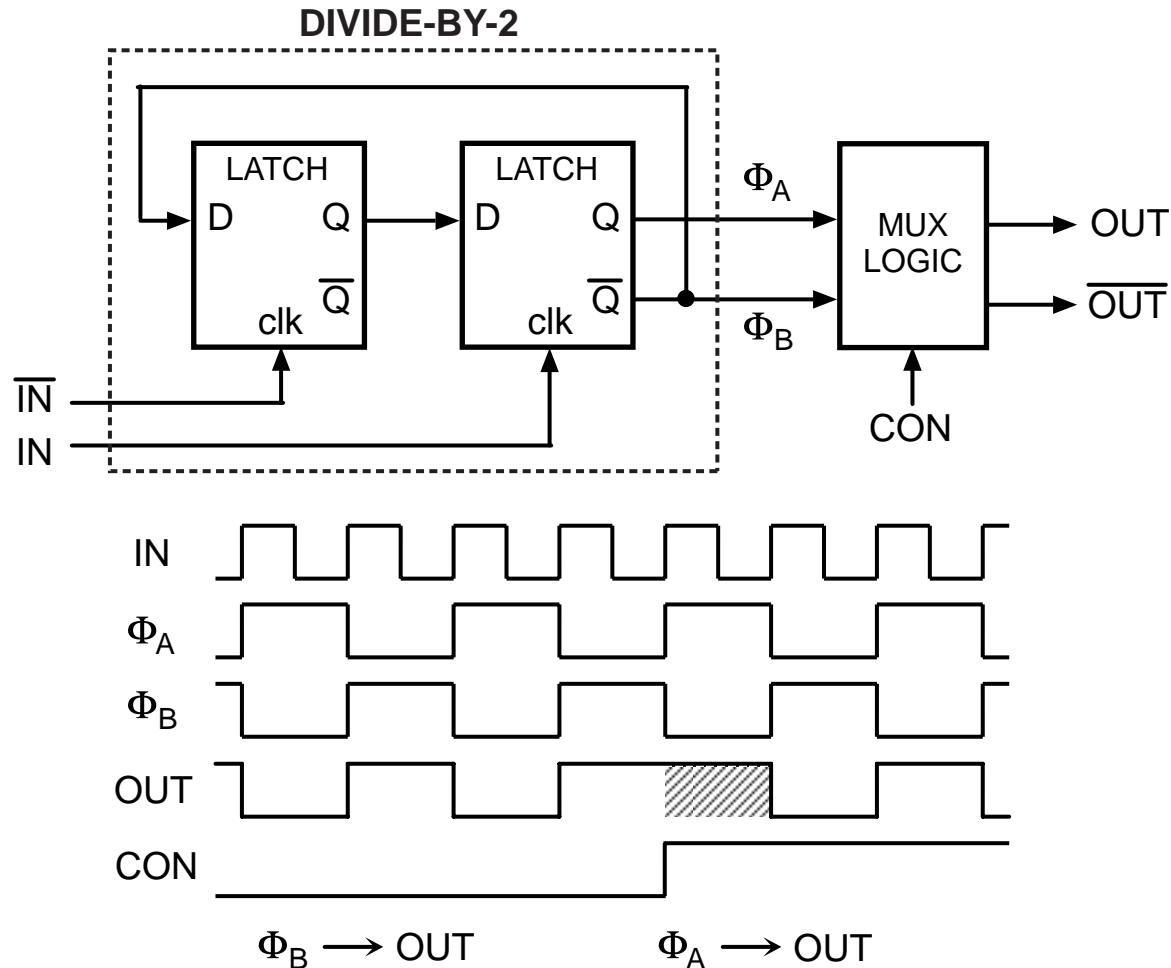


- Achieves speed of divide-by-2 circuits!
 - MUX logic runs at half the input clock speed

Implementation Challenges to Phase Shifting

- **Avoiding glitches**
 - **By assumption of sine wave characteristics**
 - Craninckx et. al., “A 1.75 GHz/3 V Dual-Modulus Divide-by-128/129 Prescaler ...”, JSSC, July 1996
 - **By make-before-break switching**
 - My thesis: <http://www-mtl.mit.edu/~perrott/>
 - **Through re-timed multiplexor**
 - Krishnapura et. al, “A 5.3 GHz Programmable Divider for HiPerLan in 0.25 μ m CMOS”, JSSC, July 2000


- **Avoiding jitter due to mismatch in phases**
 - **Through calibration**
 - Park et. al., “A 1.8-GHz Self-Calibrated Phase-Locked Loop with Precise I/Q Matching”, JSSC, May 2001

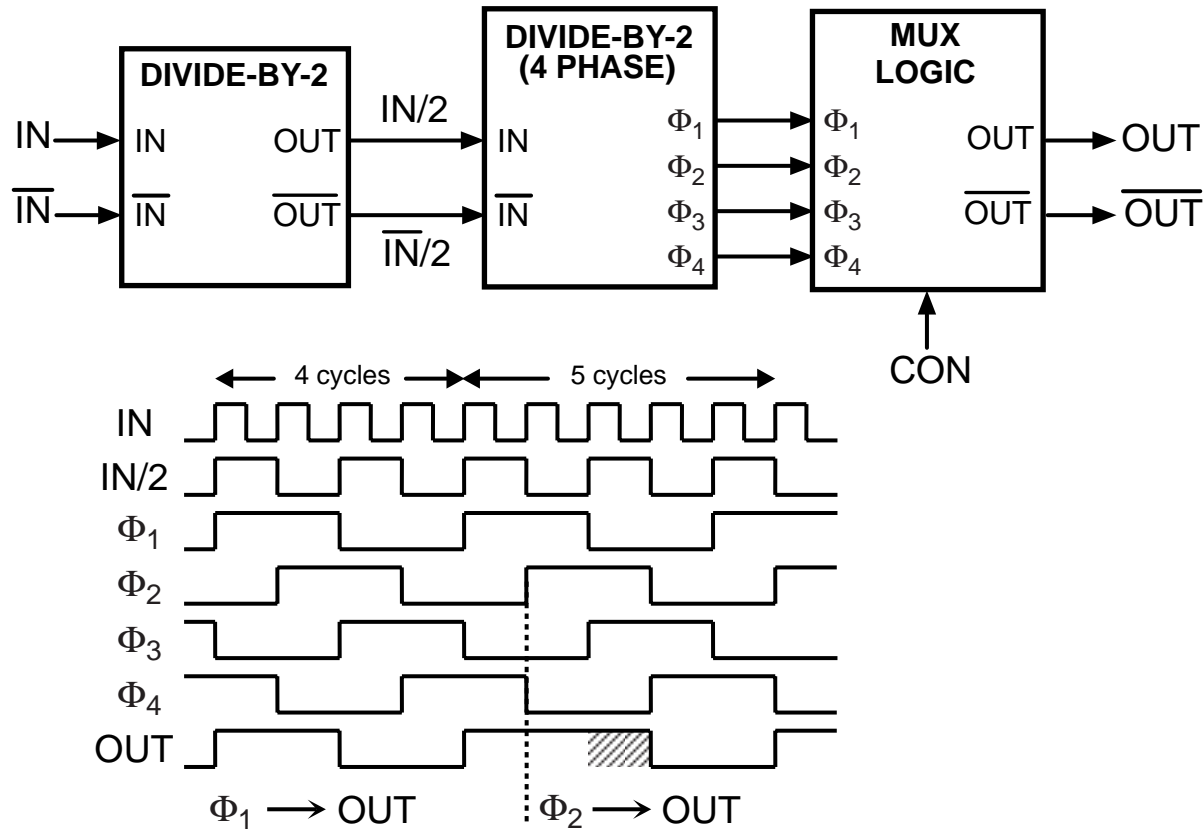Further Reduction of MUX Operating Frequency




- **Leverage the fact that divide-by-2 circuit has 4 phases**
 - Create divide-by-4/5 by cascading *two* divide-by-2 circuits
 - Note that single cycle pulse swallowing still achieved
 - **Mux operates at one fourth the input frequency!**

 Impact of Divide-by-4/5 in Multi-Modulus Prescaler




- Issue – gaps are created in divide value range
 - Divide-by-4/5 lowers swallowing resolution of following stage

Method to “Fill In” Divide Value Range

 

- Allow divide-by-4/5 to swallow more than one input cycle per OUT period
 - Divide-by-4/5 changed to Divide-by-4/5/6/7
- Note: at least two divide-by-2/3 sections must follow

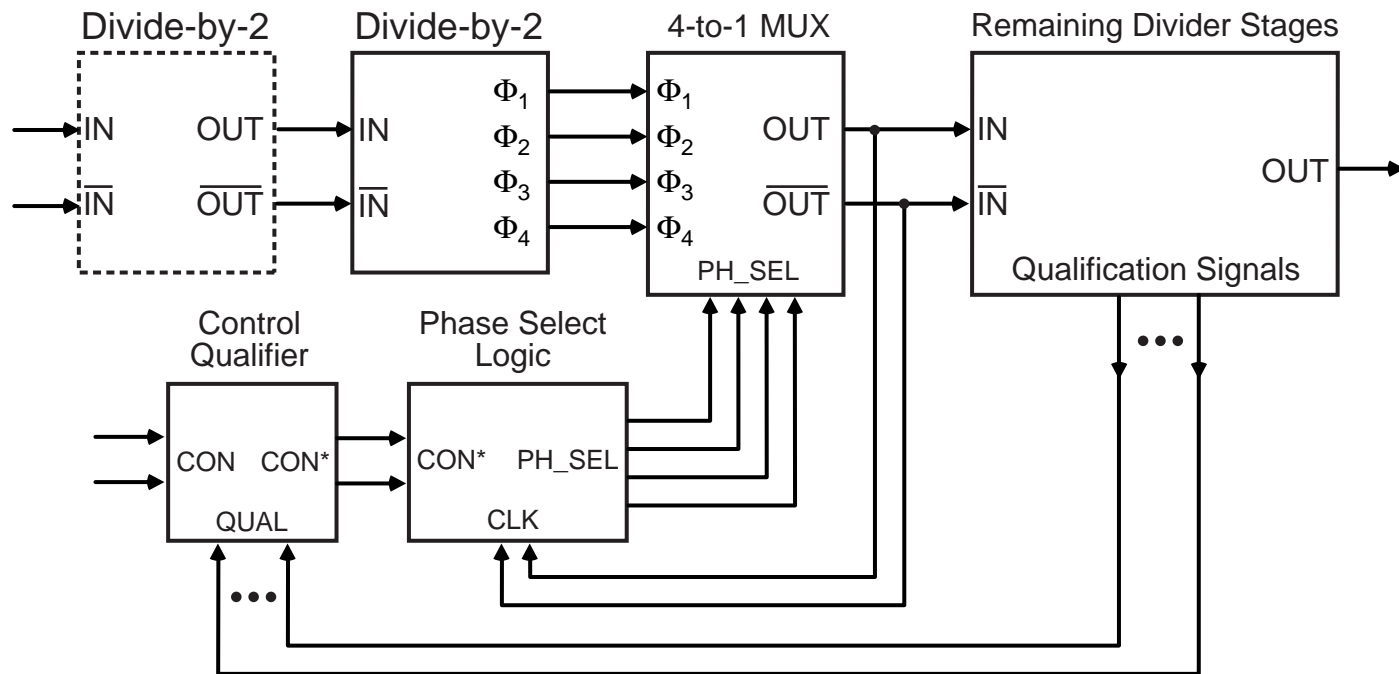
Example Architecture for a Phase-Shifted Divider



- Phase shifting in first divide-by-4/5/6/7 stage to achieve high speed
- Remaining stages correspond to gated divide-by-2/3 cells
- For details, see my thesis
 - <http://www-mtl.mit.edu/~perrott/>


PFD/Charge Pump

Analog Phase Comparison Path

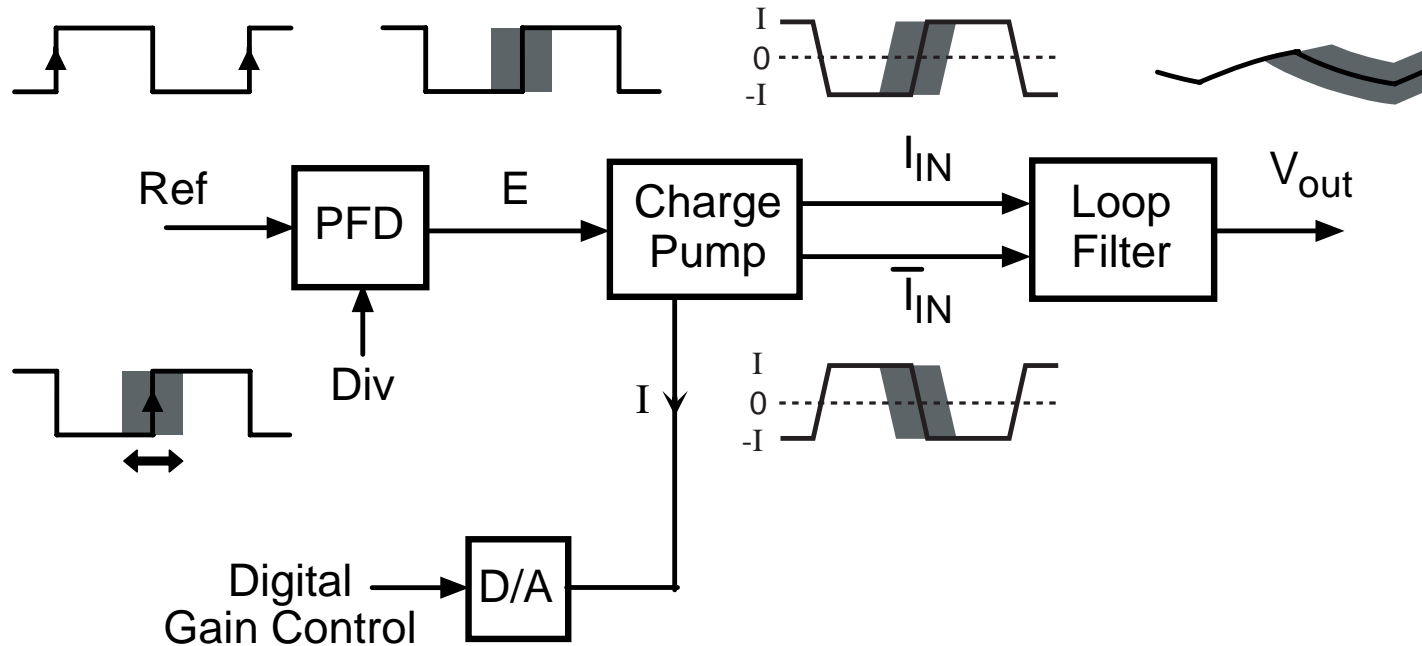


- Performs measurement of Ref and Div phase difference
- Sets PLL bandwidth and determines PLL stability
 - Note: Digital control of charge pump current allows tuning
- Key performance issues
 - Linearity, noise, power, area

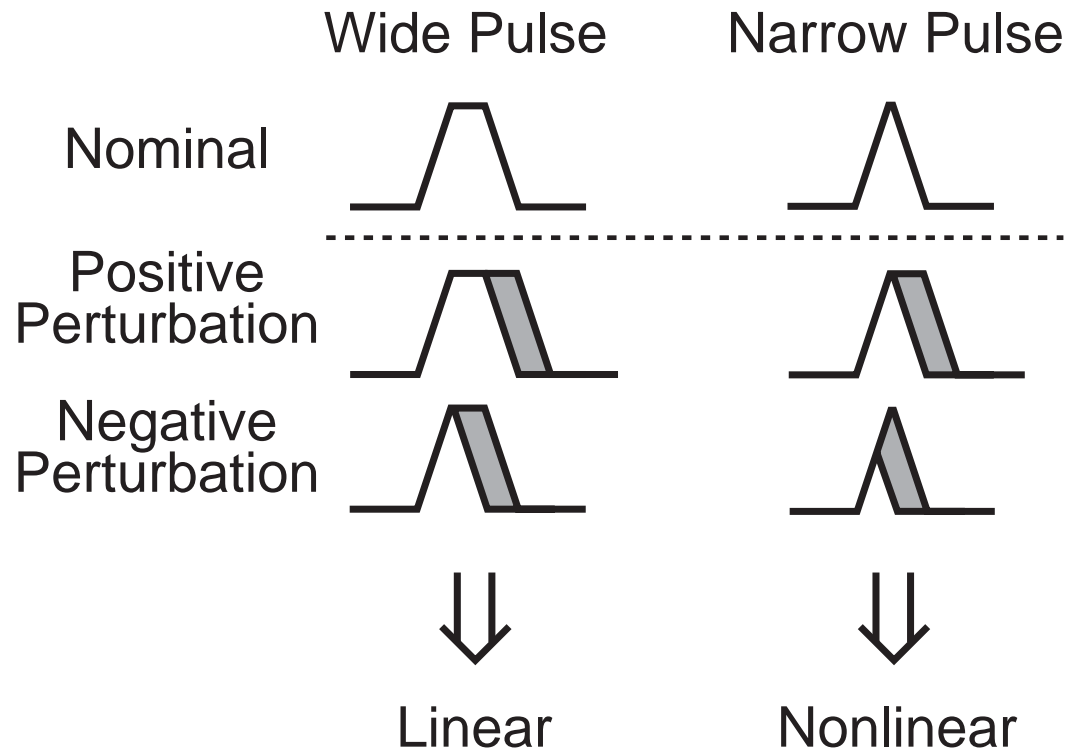Achieving Linear Operation of PFD/Charge Pump




- **Key issue: pulses need to fully settle to avoid nonlinearity in PFD/charge pump**
 - Impact of nonlinearity is noise folding/spurs
 - Runt pulses cause “dead zone” in PFD characteristic

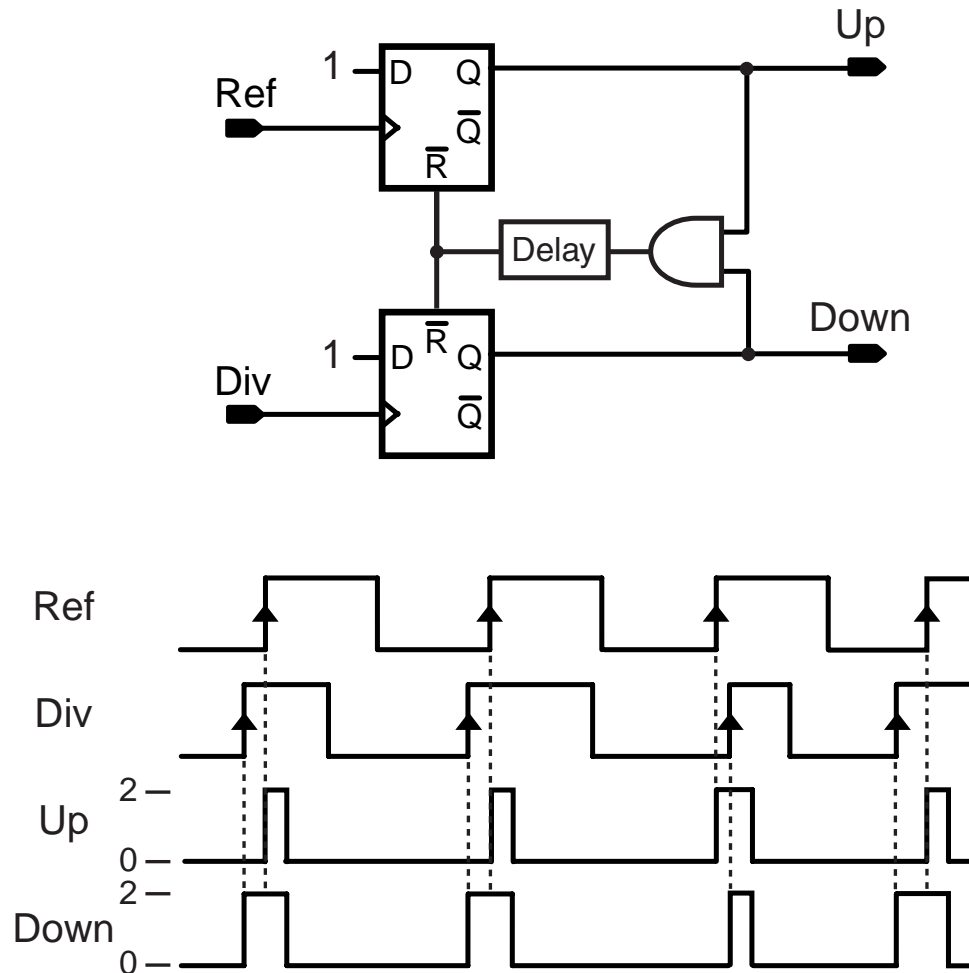Add Delay in Reset Path to Prevent Dead Zone




- **Minimum pulse width set by length of delay**
 - **Avoids incomplete settling at the expense of higher noise**

Simple View of Charge Pump

 



- Current sources implemented by current mirror circuits
 - Variation puts switches at supply/gnd rails
- Key issue: hard to achieve precise matching of up and down currents

Practical Charge Pump Characteristic

 

- Gain slope changes due to up/down current mismatch
 - Causes nonlinearity in phase comparison operation
- Offset in phase due to timing mismatch between Up and Down PFD paths


Offset PFD for High Linearity

 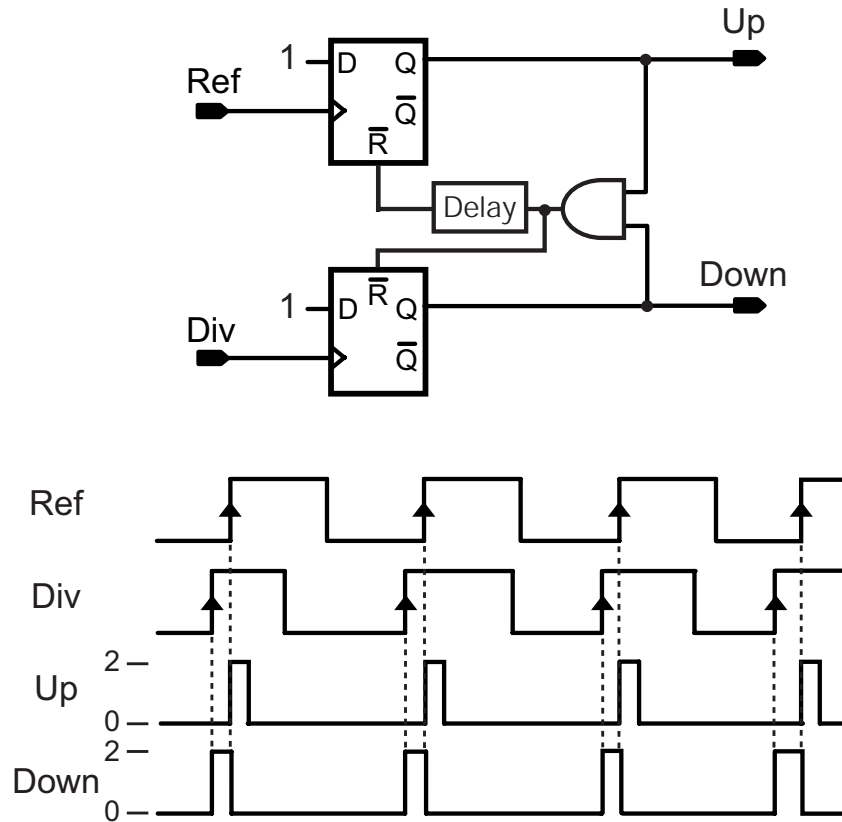


- **Change delay path such that Up pulse is always constant and follows Down pulse**
 - Only Down pulse varies in width
- **Confines phase variation to one side of PFD characteristic**

Single-Ended Versus Differential Charge Pumps

Single-Ended

 

Differential

 

- **Stray capacitance causes increased transient times for charge pump**
 - Increases the minimum required on-time of PFD pulses
- **Differential structure substantially reduces impact of stray capacitance**
 - Reduces voltage variation on cap due to switching action


Loop Filter Design

Outline


- **Closed-Loop Design of Frequency Synthesizers**
 - **Introduction**
 - **Background on Classical Open Loop Design Approach**
 - **Closed Loop Design Approach**
 - **Example and Verification**
 - **Conclusion**

$\Sigma\text{-}\Delta$ Fractional-N Frequency Synthesizer

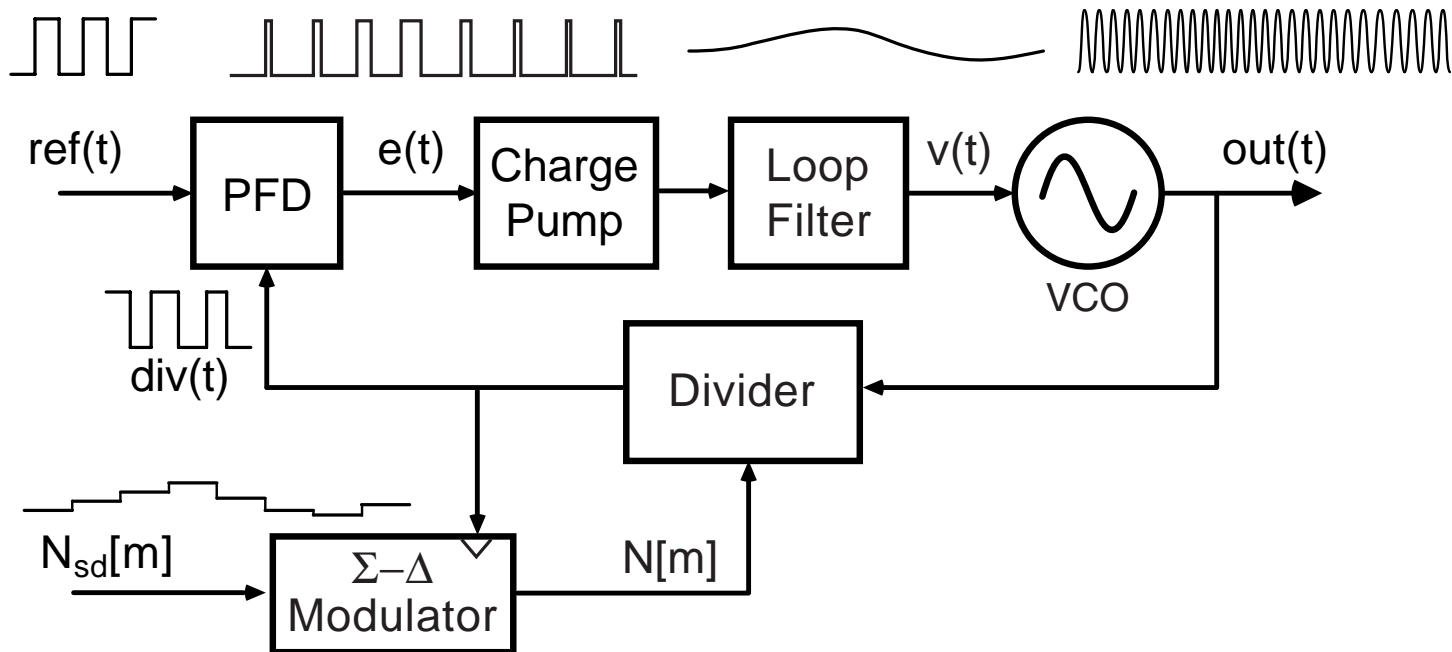- Focus on this architecture since it is essentially a “super set” of other synthesizers, including integer-N and fractional-N
 - If we can design and simulate this structure, we can also do so for classical integer-N designs



Frequency-domain Model

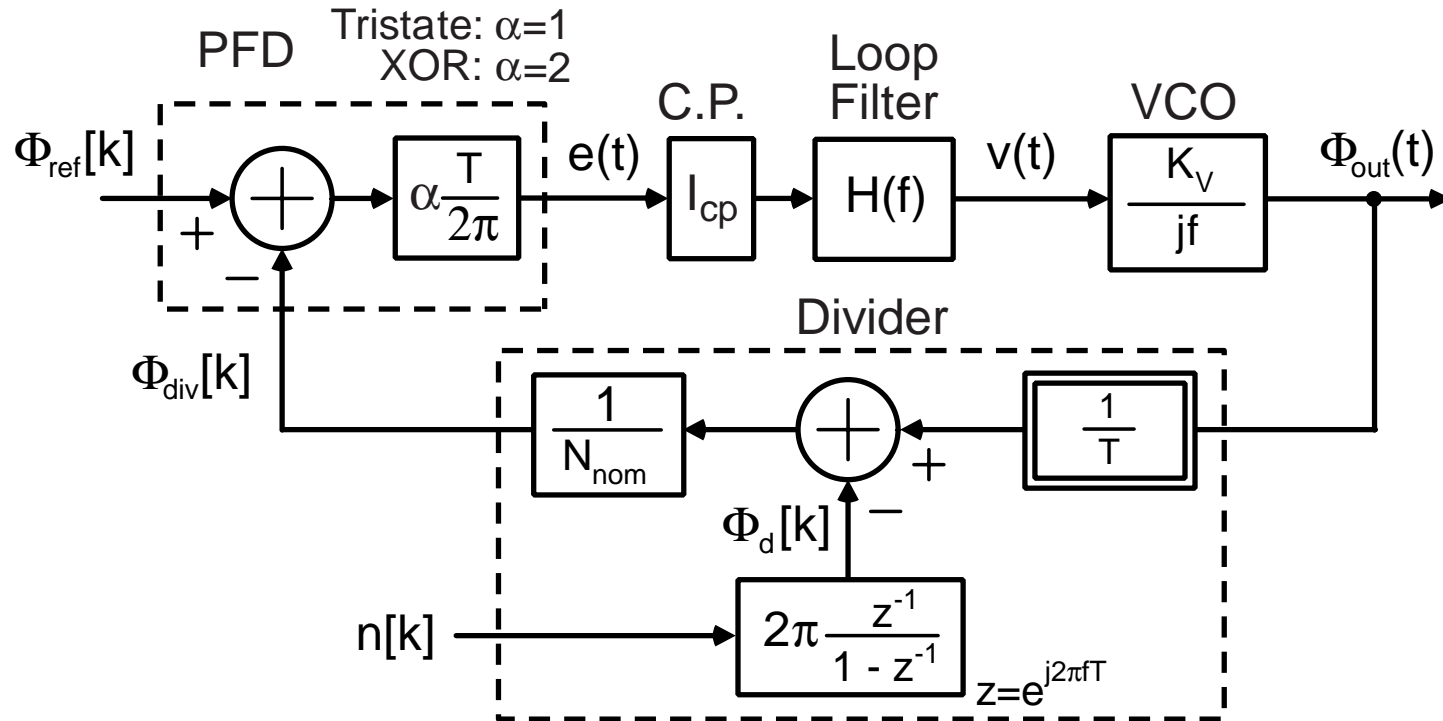

See Perrott et. al. *JSSC*,
Aug. 2002 for details

- Closed loop dynamics parameterized by

$$G(f) = \frac{A(f)}{1 + A(f)}$$


where $A(f) = \frac{\alpha I_{cp} H(f) K_V}{N_{nom} 2\pi j f}$

Review of Classical Design Approach



Given the desired closed-loop bandwidth, order, and system type:

- 1. Choose an appropriate topology for $H(f)$**
 - **Depends on order, type**
- 2. Choose pole/zero values for $H(f)$ as appropriate for the required bandwidth**
- 3. Adjust the open-loop gain to achieve the required bandwidth while maintaining stability**
 - **Plot gain and phase bode plots of $A(f)$**
 - **Use phase (or gain) margin criterion to infer stability**

 Example: First Order, Type I with Parasitic Poles



  First Order, Type I: Frequency and Step Responses



Limitations of Open Loop Design Approach


- **Constrained for applications which require precise filter response**
- **Complicated once parasitic poles are taken into account**
- **Poor control over filter shape**
- **Inadequate for systems with third order rolloff**
 - **Phase margin criterion based on second order systems**



**Closed loop design approach:
Directly design $G(f)$ by specifying dominant pole and zero locations on the s-plane (pole-zero diagram)**

Closed Loop Design Approach: Overview

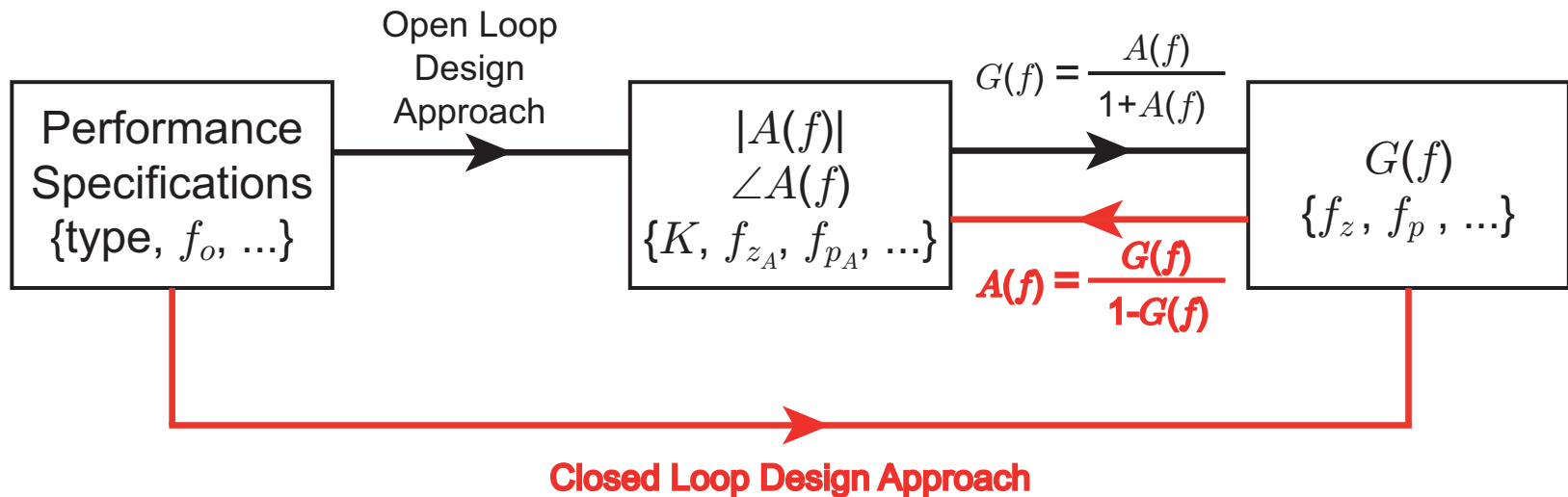- **G(f) completely describes the closed loop dynamics**
 - Design of this function is the ultimate goal




- Instead of indirectly designing **G(f)** using plots of **A(f)**, solve for **G(f)** directly as a function of specification parameters
- Solve for **A(f)** that will achieve desired **G(f)**
- Account for the impact of parasitic poles/zeros

Closed Loop Design Approach: Implementation

- **Download PLL Design Assistant Software**
 - **Part of CppSim package at <http://www.cppsim.com>**
- **Read accompanying manual**
- **Algorithm described by C.Y. Lau et. al. in “Fractional-N Frequency Synthesizer Design at the Transfer Function Level Using a Direct Closed Loop Realization Algorithm”, Design Automation Conference, 2003**

 
Definition of Bandwidth, Order, and Shape for $G(f)$



- **Bandwidth – f_0**
 - Defined in asymptotic manner as shown
- **Order – n**
 - Defined according to the rolloff characteristic of $G(f)$
- **Shape**
 - Defined according to standard filter design methodologies
 - Butterworth, Bessel, Chebyshev, etc.

Definition of Type

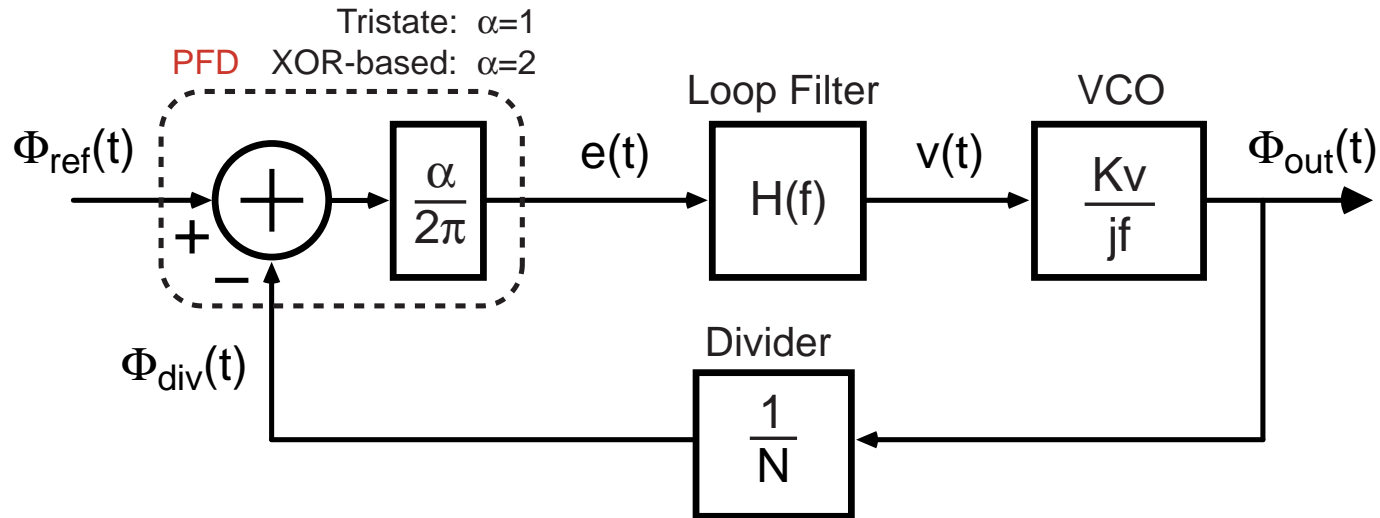- **Type I: one integrator in PLL open loop transfer function**
 - VCO adds on integrator
 - Loop filter, $H(f)$, has no integrators
- **Type II: two integrators in PLL open loop transfer function**
 - Loop filter, $H(f)$, has one integrator



Loop Filter Transfer Function Vs Type and Order of G(f)

H(s) Topology For Different Type and Orders of G(f)

	Type I	Type II
Order 1	K_{LP}	$K_{LP} \frac{1+s/w_z}{s}$
Order 2	$\frac{K_{LP}}{1+s/w_p}$	$K_{LP} \frac{1+s/w_z}{s(1+s/w_p)}$
Order 3	$\frac{K_{LP}}{1+s/(w_p Q_p)+(s/w_p)^2}$	$\frac{K_{LP}(1+s/w_z)}{s(1+s/(w_p Q_p)+(s/w_p)^2)}$


where $K_{LP} = K \frac{N_{nom}}{K_v I_{cp} \alpha}$

Calculated from software

- **Practical PLL implementations limited to above**
 - Prohibitive analog complexity for higher order, type
- **Open loop gain, K, will be calculated by algorithm**
 - Loop filter gain related to open loop gain as shown above


Passive Topologies to Realize a Second Order PLL

Type I, Order 2

 

$$\frac{V_{out}}{I_{in}} = \frac{R_1}{1+sR_1C_1}$$

Type II, Order 2

 


$$\frac{V_{out}}{I_{in}} = \frac{1}{s(C_1+C_2)} \frac{1+sR_1C_2}{1+sR_1C_{||}}$$

- **DAC is used for Type I implementation to coarsely tune VCO**
 - Allows full range of VCO to be achieved


Passive Topologies to Realize a Third Order PLL

Type I, Order 3

 

$$\frac{V_{out}}{I_{in}} = \frac{R_1}{1+sR_1C_1+s^2L_1C_1}$$

Type II, Order 3

 


$$\frac{V_{out}}{I_{in}} = \frac{1}{s(C_1+C_2)} \frac{1+sR_1C_2}{1+sR_1C_{||}+s^2L_1C_{||}}$$

where $C_{||} = C_1C_2/(C_1+C_2)$

- Inductor is necessary to create a complex pole pair
 - Must be implemented off-chip due to its large value

 Problem with Passive Loop Filter Implementations


- Large voltage swing required at charge pump output
 - Must support full range of VCO input
- Non-ideal behavior of inductors (for third order $G(f)$ implementations)
 - Hard to realize large inductor values
 - Self resonance of inductor reduces high frequency attenuation




Alternative: active loop filter implementation

Guidelines for Active Loop Filter Design

 - Use topologies with unity gain feedback in the opamp
 - Minimizes influence of opamp noise



 
- Perform level shifting in feedback of opamp
 - Fixes voltage at charge pump output



- Prevent fast edges from directly reaching opamp inputs
 - Will otherwise cause opamp to be driven into nonlinear region of operation


Active Topologies To Realize a Second Order PLL

Type I, Order 2

 

$$\frac{V_{out}}{I_{in}} = \frac{R_1}{1+sR_1C_1}$$

Type II, Order 2

 


$$\frac{V_{out}}{I_{in}} = \frac{1+sR_1(C_1+C_2+C_3)}{sC_2(1+sR_1C_1)}$$

- Follows guidelines from previous slide
- Charge pump output is terminated directly with a high Q capacitor
 - Smooths fast edges from charge pump before they reach the opamp input(s)


Active Topologies To Realize a Third Order PLL

Type I, Order 3

 

$$\frac{V_{out}}{I_{in}} = \frac{-R_2}{1+s(R_1+R_2)C_2+s^2R_1R_2C_1C_2}$$

Type II, Order 3

 

$$\frac{V_{out}}{I_{in}} = \frac{-1}{s(C_1+C_2)} \frac{1+sR_2C_3}{1+sC_{||}(R_1(1+C_1/C_3)+R_2)+s^2R_1R_2C_1C_{||}}$$

where $C_{||} = C_2C_3/(C_2+C_3)$

- Follows active implementation guidelines from a few slides ago

Example Design

- Type II, 3rd order, Butterworth, $f_o = 300\text{kHz}$, $f_z/f_o = 0.125$
 - No parasitic poles
- Required loop filter transfer function can be found from table:

$$\Rightarrow H(s) = \frac{K_{LF} \left(1 + \frac{s}{w_z}\right)}{s \left(1 + \frac{s}{w_p Q_p} + \left(\frac{s}{w_p}\right)^2\right)} \quad \text{where}$$



$$K_{LF} = \frac{N_{nom} K}{\alpha I_{cp} K_v}$$

Use PLL Design Assistant to Calculate Parameters

$$H(s) = \frac{K_{LF} \left(1 + \frac{s}{w_z}\right)}{s \left(1 + \frac{s}{w_p Q_p} + \left(\frac{s}{w_p}\right)^2\right)} \quad \text{where} \quad K_{LF} = \frac{N_{nom} K}{\alpha I_{cp} K_v}$$

Dynamic Parameters		Noise Parameters	
fo: <input type="text" value="300e3"/> Hz	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>	ref. freq: <input type="text"/> Hz	
order: <input type="radio"/> 1 <input type="radio"/> 2 <input checked="" type="radio"/> 3	paris. Q: <input type="text"/> <input type="button" value="On"/>	out freq.: <input type="text"/> Hz	
shape: <input checked="" type="radio"/> Butter <input type="radio"/> Bessel	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>	Detector: <input type="text"/> dBc/Hz <input type="button" value="On"/>	
<input type="radio"/> Cheby1 <input type="radio"/> Cheby2 <input type="radio"/> Elliptical	paris. Q: <input type="text"/> <input type="button" value="On"/>	VCO: <input type="text"/> dBc/Hz <input type="button" value="On"/>	
ripple: <input type="text"/> dB	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>	freq. offset: <input type="text"/> Hz	
type: <input type="radio"/> 1 <input checked="" type="radio"/> 2	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>	S-D: <input type="radio"/> 1 <input type="radio"/> 2 <input type="button" value="On"/> <input type="text"/> <input type="button" value="On"/>	
fz/fo: <input type="text" value="0.125"/> Hz	paris. zero: <input type="text"/> Hz <input type="button" value="On"/>	<input type="radio"/> 3 <input type="radio"/> 4 <input type="radio"/> 5	
	paris. zero: <input type="text"/> Hz <input type="button" value="On"/>		
Resulting Open Loop Parameters		Resulting Plots and Jitter	
K: <input type="text" value="2.538e+011"/> alter: <input type="text"/> <input type="button" value="On"/>		<input checked="" type="radio"/> Pole/Zero Diagram <input type="radio"/> Transfer Function	
fp: <input type="text" value="4.583e+005"/> Hz alter: <input type="text"/> <input type="button" value="On"/>		<input type="radio"/> Step Response <input type="radio"/> Noise Plot	
fz: <input type="text" value="3.750e+004"/> Hz alter: <input type="text"/> <input type="button" value="On"/>		Xmin? <input type="text"/> Xmax? <input type="text"/> Ymin? <input type="text"/> Ymax? <input type="text"/>	
Qp: <input type="text" value="7.050e-001"/> alter: <input type="text"/> <input type="button" value="On"/>		rms jitter: <input type="text"/>	
PLL Design Assistant		Written by Michael Perrott (http://www-mtl.mit.edu/~perrott)	

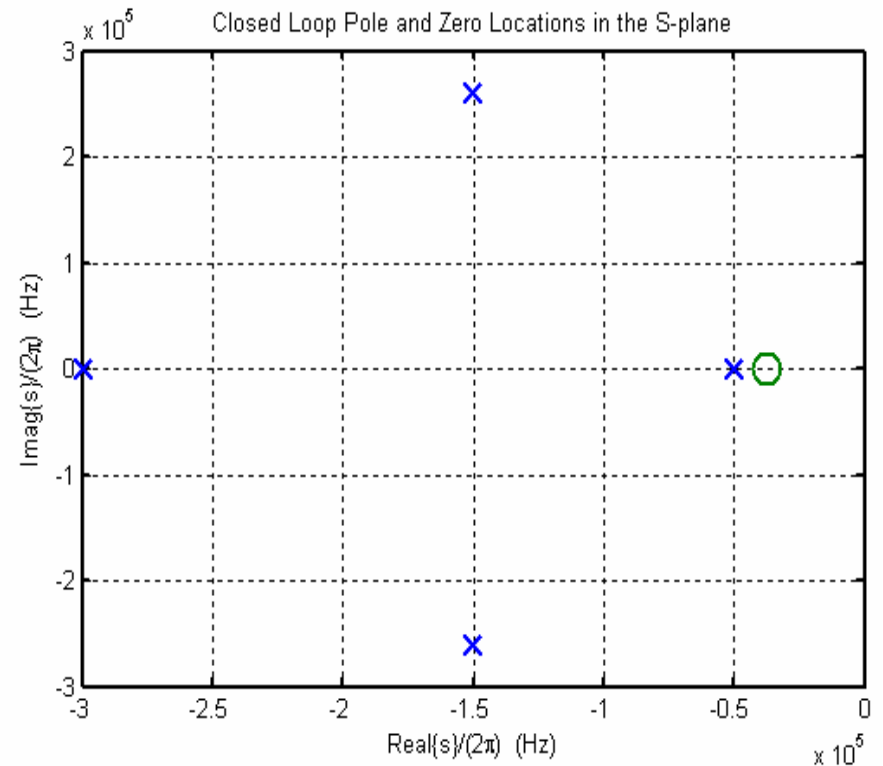 Resulting Step Response and Pole/Zero Diagram




Impact of Open Loop Parameter Variations

Dynamic Parameters		Noise Parameters	
fo: <input type="text" value="300e3"/> Hz	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>	ref. freq: <input type="text"/> Hz	out freq.: <input type="text"/> Hz
order: <input type="radio"/> 1 <input type="radio"/> 2 <input checked="" type="radio"/> 3	paris. Q: <input type="text"/> <input type="button" value="On"/>	Detector: <input type="text"/> dBc/Hz <input type="button" value="On"/>	VCO: <input type="text"/> dBc/Hz <input type="button" value="On"/>
shape: <input checked="" type="radio"/> Butter <input type="radio"/> Bessel	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>	freq. offset: <input type="text"/> Hz	S-D: <input type="radio"/> 1 <input type="radio"/> 2 <input type="button" value="On"/> <input type="text"/> <input type="button" value="On"/>
<input type="radio"/> Cheby1 <input type="radio"/> Cheby2 <input type="radio"/> Elliptical	paris. Q: <input type="text"/> <input type="button" value="On"/>		
ripple: <input type="text"/> dB	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>		
type: <input type="radio"/> 1 <input checked="" type="radio"/> 2	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>		
fz/fo: <input type="text" value="0.125"/> Hz	paris. zero: <input type="text"/> Hz <input type="button" value="On"/>		
	paris. zero: <input type="text"/> Hz <input type="button" value="On"/>		
Resulting Open Loop Parameters		Resulting Plots and Jitter	
K: <input type="text" value="2.538e+011"/>	alter: <input type="text" value="-0.2:0.2:0.2"/> <input type="button" value="On"/>	<input type="radio"/> Pole/Zero Diagram	<input type="radio"/> Transfer Function
fp: <input type="text" value="4.583e+005"/> Hz	alter: <input type="text" value="-0.2:0.2:0.2"/> <input type="button" value="On"/>	<input checked="" type="radio"/> Step Response	<input type="radio"/> Noise Plot
fz: <input type="text" value="3.750e+004"/> Hz	alter: <input type="text"/> <input type="button" value="On"/>	Xmin? <input type="text"/>	Xmax? <input type="text"/>
Qp: <input type="text" value="7.050e-001"/>	alter: <input type="text"/> <input type="button" value="On"/>	Ymin? <input type="text"/>	Ymax? <input type="text"/>
<input type="button" value="Apply"/>		rms jitter: <input type="text"/>	
PLL Design Assistant		Written by Michael Perrott (http://www-mtl.mit.edu/~perrott)	

- Open loop parameter variations can be directly entered into tool

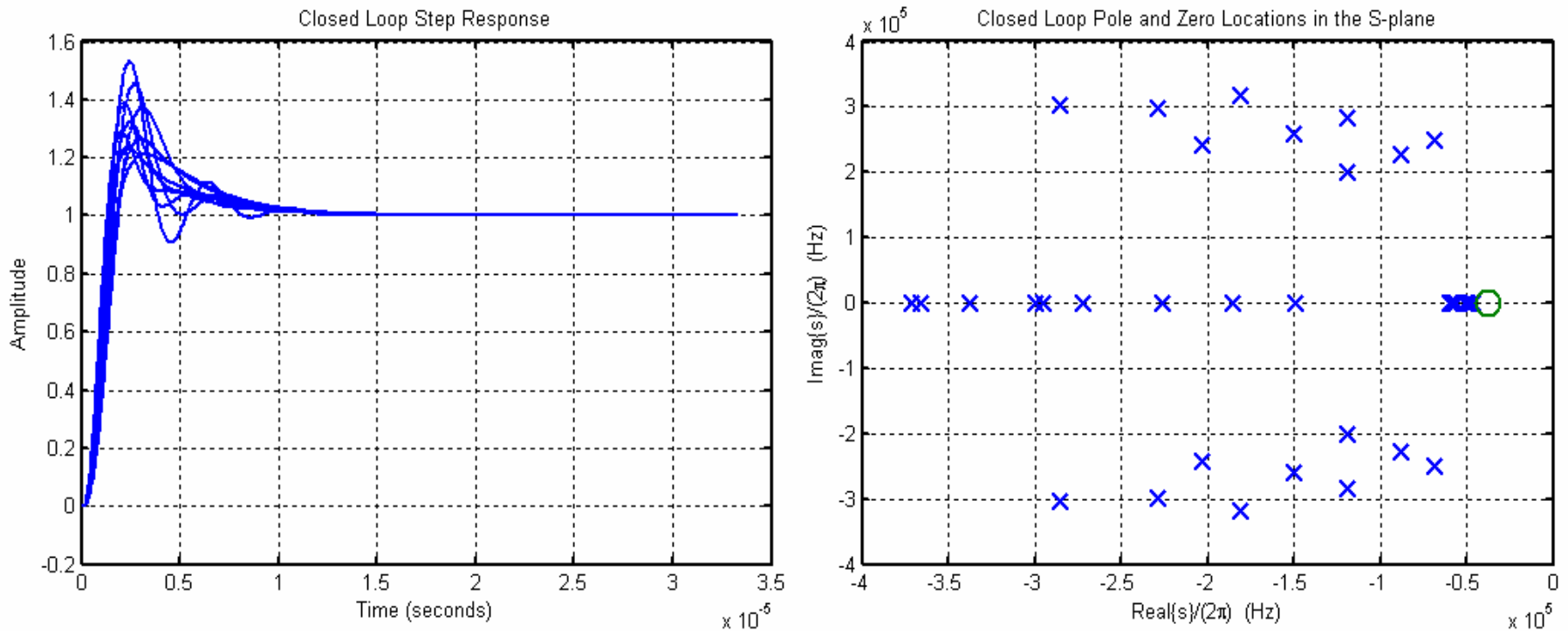Resulting Step Responses and Pole/Zero Diagrams



- Impact of variations on the loop dynamics can be visualized instantly and taken into account at early stage of design

Design with Parasitic Pole

- Include a parasitic pole at nominal value $f_{p1} = 1.2\text{MHz}$

$$H(s) = \frac{K_{LF} \left(1 + \frac{s}{w_z}\right)}{s \left(1 + \frac{s}{w_p Q_p} + \left(\frac{s}{w_p}\right)^2\right) \left(1 + \frac{s}{w_{p1}}\right)}$$

Dynamic Parameters		Noise Parameters	
fo: <input type="text" value="300e3"/> Hz	paris. pole: <input type="text" value="1.2e6"/> Hz <input type="checkbox"/>	ref. freq: <input type="text" value="Value?"/> Hz	
order: <input type="radio"/> 1 <input type="radio"/> 2 <input checked="" type="radio"/> 3	paris. Q: <input type="text"/> <input type="checkbox"/>	out freq: <input type="text" value="Value?"/> Hz	
shape: <input checked="" type="radio"/> Butter <input type="radio"/> Bessel	paris. pole: <input type="text"/> Hz <input type="checkbox"/>	Detector: <input type="text"/> dBc/Hz <input type="checkbox"/>	
<input type="radio"/> Cheby1 <input type="radio"/> Cheby2 <input type="radio"/> Elliptical	paris. Q: <input type="text"/> <input type="checkbox"/>	VCO: <input type="text"/> dBc/Hz <input type="checkbox"/>	
ripple: <input type="text"/> dB	paris. pole: <input type="text"/> Hz <input type="checkbox"/>	freq. offset: <input type="text"/> Hz	
type: <input type="radio"/> 1 <input checked="" type="radio"/> 2	paris. pole: <input type="text"/> Hz <input type="checkbox"/>	S-D: <input type="radio"/> 1 <input type="radio"/> 2 <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/> <input type="checkbox"/>	
fz/fo: <input type="text" value="1/8"/> Hz	paris. pole: <input type="text"/> Hz <input type="checkbox"/>		
	paris. zero: <input type="text"/> Hz <input type="checkbox"/>		
	paris. zero: <input type="text"/> Hz <input type="checkbox"/>		
Resulting Open-Loop Parameters		Resulting Plots and Jitter	
K: <input type="text" value="2.294e+011"/>	alter: <input type="text"/> <input type="checkbox"/>	<input checked="" type="radio"/> Pole/Zero Diagram	<input type="radio"/> Transfer Function
fp: <input type="text" value="4.841e+005"/> Hz	alter: <input type="text"/> <input type="checkbox"/>	<input type="radio"/> Step Response	<input type="radio"/> Noise Plot
fz: <input type="text" value="3.750e+004"/> Hz	alter: <input type="text"/> <input type="checkbox"/>	Xmin? <input type="text"/>	Xmax? <input type="text"/>
Qp: <input type="text" value="7.931e-001"/>	alter: <input type="text"/> <input type="checkbox"/>	Ymin? <input type="text"/>	Ymax? <input type="text"/>
<input type="button" value="Apply"/>		rms jitter: <input type="text"/>	
PLL Design Assistant		Written by Michael Perrott (http://www-mtl.mit.edu/~perrott)	

⇒ K , f_p and Q_p are adjusted to obtain the same dominant pole locations


Noise Estimation

- Phase noise plots can be easily obtained
 - Jitter calculated by integrating over frequency range


Dynamic Parameters		Noise Parameters	
fo: <input type="text" value="300e3"/> Hz	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>	ref. freq: <input type="text" value="20e6"/> Hz	<input type="button" value="On"/>
order: <input type="radio"/> 1 <input type="radio"/> 2 <input checked="" type="radio"/> 3	paris. Q: <input type="text"/> <input type="button" value="On"/>	out freq.: <input type="text" value="1.84e9"/> Hz	<input type="button" value="On"/>
shape: <input checked="" type="radio"/> Butter <input type="radio"/> Bessel	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>	Detector: <input type="text" value="-75.9"/> dBc/Hz <input type="button" value="On"/>	<input type="button" value="On"/>
<input type="radio"/> Cheby1 <input type="radio"/> Cheby2 <input type="radio"/> Elliptical	paris. Q: <input type="text"/> <input type="button" value="On"/>	VCO: <input type="text" value="-139.3"/> dBc/Hz <input type="button" value="On"/>	<input type="button" value="On"/>
ripple: <input type="text"/> dB	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>	freq. offset: <input type="text" value="5e6"/> Hz	<input type="button" value="On"/>
type: <input type="radio"/> 1 <input checked="" type="radio"/> 2	paris. pole: <input type="text"/> Hz <input type="button" value="On"/>	S-D: <input type="radio"/> 1 <input type="radio"/> 2 <input type="button" value="On"/>	<input type="button" value="On"/>
fz/fo: <input type="text" value="0.125"/> Hz	paris. zero: <input type="text"/> Hz <input type="button" value="On"/>	<input checked="" type="radio"/> 3 <input type="radio"/> 4 <input type="radio"/> 5	<input type="button" value="On"/>
Resulting Open Loop Parameters		Resulting Plots and Jitter	
K: <input type="text" value="2.538e+011"/> alter: <input type="text"/> <input type="button" value="On"/>	<input type="button" value="Apply"/>	<input type="radio"/> Pole/Zero Diagram	<input type="radio"/> Transfer Function
fp: <input type="text" value="4.583e+005"/> Hz alter: <input type="text"/> <input type="button" value="On"/>		<input type="radio"/> Step Response	<input checked="" type="radio"/> Noise Plot
fz: <input type="text" value="3.750e+004"/> Hz alter: <input type="text"/> <input type="button" value="On"/>		<input type="text" value="1e4"/> <input type="text" value="1e8"/> <input type="text" value="-180"/> <input type="text" value="-60"/>	
Qp: <input type="text" value="7.050e-001"/> alter: <input type="text"/> <input type="button" value="On"/>		rms jitter: <input type="text" value="13.791 ps"/>	
PLL Design Assistant		Written by Michael Perrott (http://www-ml.mit.edu/~perrott)	

Calculated Versus Simulated Phase Noise Spectrum

Without parasitic pole:

 


RMS jitter = 13.791ps

 


Calculated Versus Simulated Phase Noise Spectrum


With parasitic pole at 1.2 MHz:

 

RMS jitter = 14.057ps

 

 Noise under Open Loop Parameter Variations



RMS jitter = 11.678ps (min), 18.211ps (max)

- Impact of open loop parameter variations on phase noise and jitter can be visualized immediately

Conclusion

- **CAD-based closed loop design approach facilitates:**
 - **Accurate control of closed loop dynamics**
 - Bandwidth, Order, Shape, Type
 - **Straightforward design of higher order PLL's**
 - **Direct assessment of impact of parasitic poles/zeros**
- **Techniques implemented in a GUI-based CAD tool**

- **Beginners can quickly come up to speed in designing PLL's**
- **Experienced designers can quickly evaluate the performance of different PLL configurations**